

4-1. Simplify the following expressions using Boolean algebra.

(a)  $x = ABC + \bar{A}C$

$$= C (AB + \bar{A})$$

$$= C (\bar{A} + B)$$

Recall:  $x + \bar{x}y = x + y$

$$x = \underline{\bar{A}C + BC} \quad (\text{SOP form})$$

4-1

(b)  $y = (Q + R)(\bar{Q} + \bar{R})$

$$= \underbrace{Q\bar{Q}}_0 + Q\bar{R} + R\bar{Q} + \underbrace{R\bar{R}}_0$$

$$y = \underline{Q\bar{R} + \bar{Q}R}$$

4-1

$$(c) w = \overline{A}BC + A\overline{B}C + \overline{A}$$

$$= AC(\underbrace{B + \overline{B}}_1) + \overline{A}$$

$$= \underbrace{AC + \overline{A}}$$

$$= \underline{\underline{\overline{A} + C}}$$

Recall:  $x + \overline{x}y = x + y$

4-1

$$(d) q = \overline{RST}(R + S + T)$$

$$= (\overline{R} + \overline{S} + \overline{T})(\overline{R} \cdot \overline{S} \cdot \overline{T})$$

$$= (\overline{R} + \overline{S} + \overline{T}) \overline{R} \overline{S} \overline{T}$$

$$= \underbrace{\overline{R}}_R \overline{R} \overline{S} \overline{T} + \overline{S} \underbrace{\overline{R}}_S \overline{S} \overline{T} + \overline{T} \overline{R} \underbrace{\overline{S}}_T \overline{T}$$

$$= \overline{R} \overline{S} \overline{T} + \overline{R} \overline{S} \overline{T} + \overline{R} \overline{S} \overline{T}$$

$$= \underline{\underline{\overline{R} \overline{S} \overline{T}}}$$

Recall:  $a \cdot a = a$

Recall:  $a + a + a = a$

4-1 Hint: Try to get something like:  $a + \bar{a}$  (which = 1)

$$(e) x = \underbrace{\bar{A}\bar{B}\bar{C}}_{(1)} + \underbrace{\bar{A}BC}_{(2)} + \underbrace{ABC}_{(1)} + \underbrace{A\bar{B}\bar{C}}_{(1)} + \underbrace{A\bar{B}C}_{(2)}$$

$$= \underbrace{(\bar{A}+A)}_1 \bar{B}\bar{C} + \underbrace{(\bar{A}+A)}_1 BC + A\bar{B}C$$

$$= \bar{B}\bar{C} + BC + A\bar{B}C$$

Alt.  
ans

$$\begin{aligned} & BC + \bar{B}(\bar{C} + AC) \\ &= BC + \bar{B}(\bar{C} + A) \\ &= \underline{BC + \bar{B}\bar{C} + A\bar{B}} \end{aligned}$$

$$= \bar{B}\bar{C} + C(\underbrace{B + A\bar{B}}_{\downarrow})$$

$$= \bar{B}\bar{C} + C(\underbrace{B + A}_{\downarrow})$$

Recall:  $x + \bar{x}y = x + y$

$$= \underline{\underline{\bar{B}\bar{C} + BC + AC}}$$

4-1

$$(f) z = \underbrace{(B + \bar{C})(\bar{B} + C)}_{\downarrow} + \underbrace{\bar{A} + B + \bar{C}}_{\downarrow}$$

$$= (\underbrace{B\bar{B}}_0 + BC + \bar{C}\bar{B} + \underbrace{\bar{C}C}_0) + (\bar{A} \cdot \bar{B} \cdot \bar{C})$$

$$= BC + \bar{B}\bar{C} + A\bar{B}C$$

Alt.  
ans.

$$= BC + \bar{B}(\bar{C} + AC)$$

$$= BC + \bar{B}(\bar{C} + A)$$

$$= \underline{\underline{BC + \bar{B}\bar{C} + A\bar{B}}}$$

$$\begin{aligned} & C(\underbrace{B + A\bar{B}}_{\downarrow}) + \bar{B}\bar{C} \\ &= C(\underbrace{B + A}_{\downarrow}) + \bar{B}\bar{C} \\ &= \underline{\underline{BC + AC + \bar{B}\bar{C}}} \end{aligned}$$

4-1

$$(g) y = \overline{(C + D)} + \overline{A}C\overline{D} + A\overline{B}\overline{C} + \overline{A}\overline{B}CD + A\overline{C}\overline{D}$$

$$= \overline{C} \cdot \overline{D} + \overline{A}\overline{C}\overline{D} + A\overline{B}\overline{C} + \overline{A}\overline{B}CD + A\overline{C}\overline{D}$$

$$= \overline{C}\overline{D} + \overline{C}\overline{D}(\underbrace{\overline{A} + A}_1) + A\overline{B}\overline{C} + \overline{A}\overline{B}CD$$

$$= (\underbrace{\overline{C} + C}_1)\overline{D} + A\overline{B}\overline{C} + \overline{A}\overline{B}CD$$

$$= \overline{D} + \overline{A}\overline{B}CD + A\overline{B}\overline{C}$$

$$= \overline{D} + \overline{A}\overline{B}C + A\overline{B}\overline{C}$$

Recall:  $x + \overline{x}y = x + y$

4-1

$$(h) x = AB(\overline{C}D) + \overline{A}BD + \overline{B}\overline{C}\overline{D}$$

$$= AB(\overline{C} + D) + \overline{A}BD + \overline{B}\overline{C}\overline{D}$$

$$= AB(C + D) + \overline{A}BD + \overline{B}\overline{C}\overline{D}$$

$$= \underline{ABC + AB\overline{D} + \overline{A}BD + \overline{B}\overline{C}\overline{D}}$$

✓44. Design the logic circuit corresponding to the truth table shown in Table 4-9.

**Step 1:** Truth-Table (already given in this problem)

| A | B | C | x |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

**Step 2:**

Write down the product terms which output = 1.

**Step 3:** Add the above terms to form the SOP expression:

$$x = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC$$

000    010    011    100    111

**Step 4:** Simplify the above SOP expression: (either using algebra or K-map)


$$\begin{aligned}
 x &= \underbrace{\bar{A}\bar{B}\bar{C}}_{(1)} + \underbrace{\bar{A}B\bar{C}}_{(2)} + \underbrace{\bar{A}BC}_{(2)} + \underbrace{A\bar{B}\bar{C}}_{(2)} + \underbrace{ABC}_{(2)} \\
 &= \underbrace{\bar{A}\bar{C}(\bar{B}+B)}_{(1)} + \underbrace{BC(\bar{A}+A)}_{(2)} + A\bar{B}\bar{C} \\
 &= \bar{A}\bar{C} + BC + A\bar{B}\bar{C}
 \end{aligned}$$

$$= \bar{C}(\bar{A} + A\bar{B}) + BC$$

$$= \bar{C}(\bar{A} + \bar{B}) + BC$$


$$x = \bar{A}\bar{C} + \bar{B}\bar{C} + BC$$

**Step 5:** Circuit

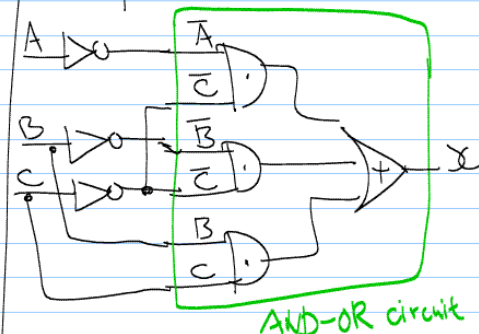


Alt: Simplify with K-map
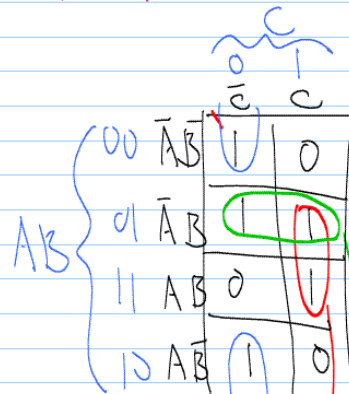
$$X = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC$$



$$X = \bar{B}\bar{C} + BC + \bar{A}B$$

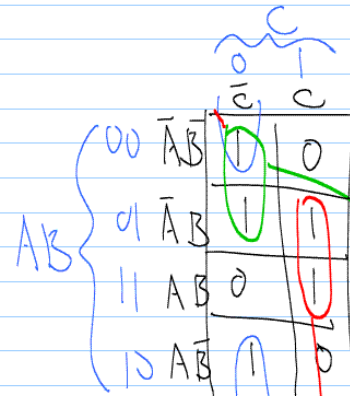

$$X = \bar{B}\bar{C} + BC + \bar{A}\bar{C}$$

Both are correct


→ 4-8. Figure 4-63 shows a diagram for an automobile alarm circuit used to detect certain undesirable conditions. The three switches are used to indicate the status of the door by the driver's seat, the ignition, and the headlights, respectively. Design the logic circuit with these three switches as inputs so that the alarm will be activated whenever **either** of the following conditions exists:

- OR {
- ① The headlights are on **while** the ignition is off.
  - ② The door is open **while** the ignition is on.
- ie AND

From logic reasoning:

$$\text{Alarm} = \bar{L} \cdot \bar{I} + D \cdot I$$

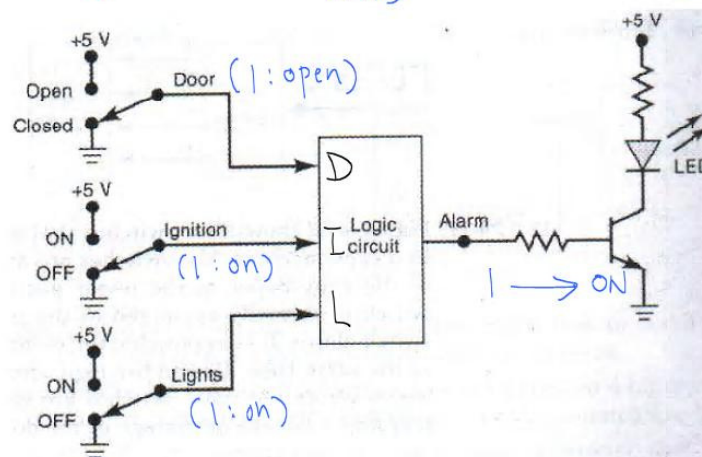Let's compare with the truth-table method.



(on when Alarm = 1)

## Step 1: Truth-table


| D | I | L | Alarm |
|---|---|---|-------|
| 0 | 0 | 0 | 0     |
| 0 | 0 | 1 | 1     |
| 0 | 1 | 0 | 0     |
| 0 | 1 | 1 | 0     |
| 1 | 0 | 0 | 0     |
| 1 | 0 | 1 | 1     |
| 1 | 1 | 0 | 1     |
| 1 | 1 | 1 | 1     |

Step 2

Light on, Ignition off

Door open, Ignition On

## Step 5: Circuit

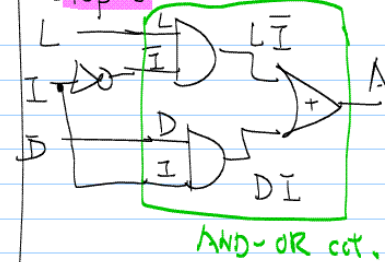

Step 3 (SOP):  $A = \bar{D}\bar{I}L + \bar{D}I\bar{L} + D\bar{I}\bar{L} + DIL$

Step 4 (Simplify):  $= (\bar{D} + D)\bar{I}L + D\bar{I}(\bar{L} + L)$


$$A = \bar{I}L + DI$$

→ 4-9. Implement the circuit of Problem 4-4 using all NAND gates.

| A | B | C | x |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

From 4-4:

AND-OR circuit

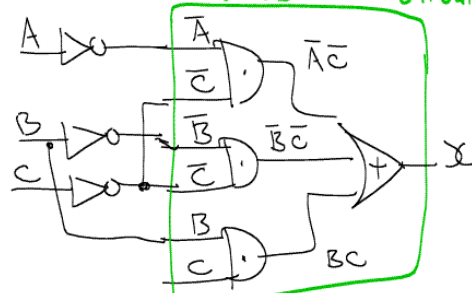


Recall:


is same as

Recall:

can cancel,  
they have no  
net effect

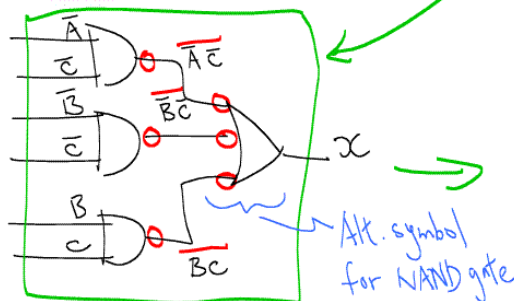


All NAND ckt.

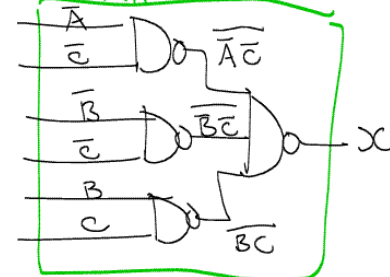




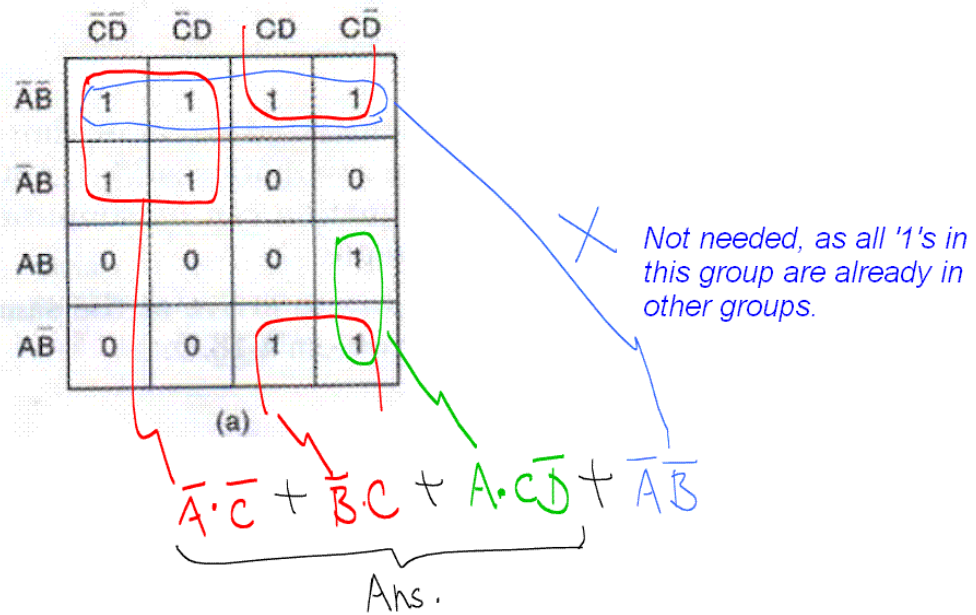3 → 4-11. Determine the minimum expression for each K map in Figure 4-64. Pay particular attention to step 5 for the map in (a).



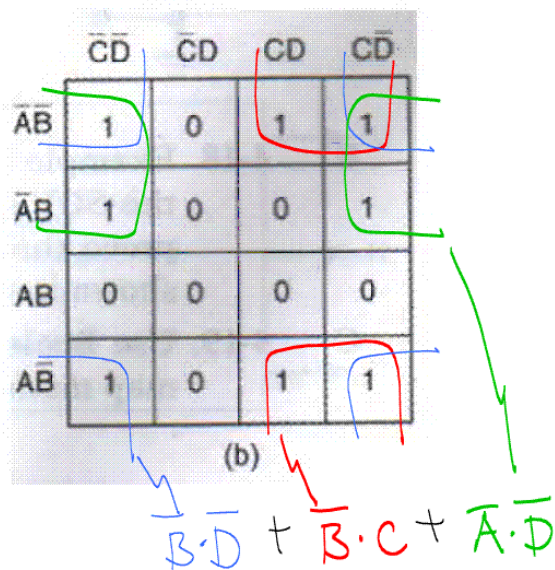→ 4-11. Determine the minimum expression for





4-11. Determine the minimum expression for


|                  | $\bar{C}$ | $C$ |
|------------------|-----------|-----|
| $\bar{A}\bar{B}$ | 0         | 1   |
| $\bar{A}B$       | 0         | 0   |
| $AB$             | 1         | 0   |
| $A\bar{B}$       | 1         | X   |

(c)

Don't care

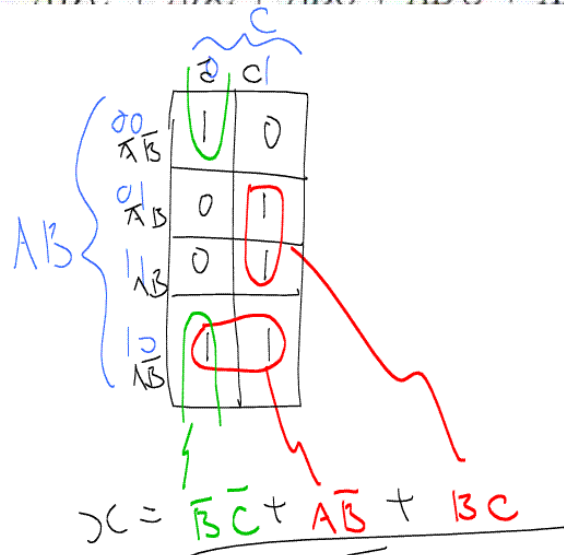4-12. Simplify the expression in Problem 4-1(e) using a K map.


$$(c) \quad x = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + A\overline{B}C + A\overline{B}C$$



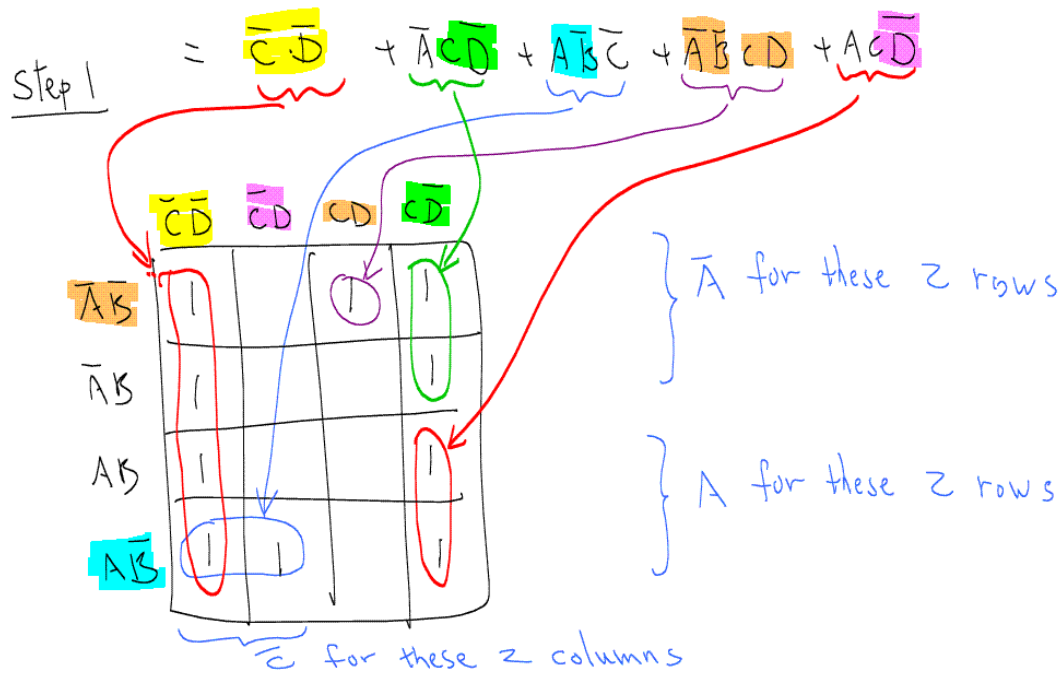4-13. Simplify the expression in Problem 4-1(g) using a K map.

(Have to change to SOP form first)

$$(g) y = (C + D) + \bar{A}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C\bar{D} + A\bar{C}\bar{D}$$



Step 2

Re-group the '1's:

