

NOTE: 1) Solutions which are to be reproduced are to be typed or hand-written in **black ball point or black ink.**
2) All solutions for the same subject should be stapled together, with the sheet no. indicated in running order on the top right hand corner.

NOT TO BE GIVEN TO
STUDENT

NO	SOLUTION	Marks	Total Marks								
B1.											
	1 0 2 1 ₁₀										
(a)											
	512 256 128 64 32 16 8 4 2 1	5									
	1 1 1 1 1 1 1 1 0 1										
	1 7 7 5 ₈										
(b)		5									
	0001 1001 0110 0011 _{BCD}										
	1 9 6 3 ₁₀										
(c)		5									
	<table border="1"> <tr> <td>E</td><td>C</td><td>A</td><td>D</td></tr> <tr> <td>1110</td><td>1100</td><td>1010</td><td>1101₂</td></tr> </table>	E	C	A	D	1110	1100	1010	1101 ₂		
E	C	A	D								
1110	1100	1010	1101 ₂								
			15								


NOTE: 1) Solutions which are to be reproduced are to be typed or hand written in **black ball point or black ink**.
 2) All solutions for the same subject should be stapled together, with the sheet no. indicated in running order on the top right hand corner.

**NOT TO BE GIVEN TO
STUDENT**

SINGAPORE POLYTECHNIC

NOTE: 1) Solutions which are to be reproduced are to be typed or hand written in **black ball point or black ink.**
2) All solutions for the same subject should be stapled together, with the sheet no. indicated in running order on the top right hand corner.

NOT TO BE GIVEN TO
STUDENT

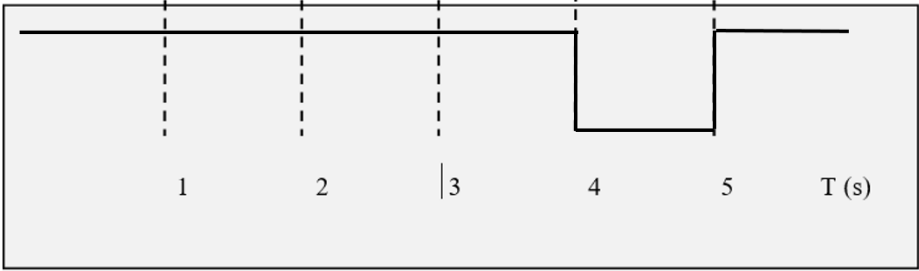NO	SOLUTION	Marks	Total Marks
B3			
(a)	$\overline{\overline{\overline{ABC}}} + \overline{B}$ $= \overline{\overline{AB}} + \overline{C} + \overline{B}$ $= \overline{AB} + \overline{C} + \overline{B}$ $= \overline{A} + \overline{B} + \overline{C}$	5	
(b)		10	

NOTE:

- 1) Solutions which are to be reproduced are to be typed or hand written in **black ball point or black ink**.
 2) All solutions for the same subject should be stapled together, with the sheet no. indicated in running order on the top right hand corner.

**NOT TO BE GIVEN TO
STUDENT**

NO	SOLUTION	Marks	Total Marks
B4			
		2	
(a)	7474		
(b)			
	74C74	2	
	MOD=f _{clock} /f _{max}		
(c)			
	=128khz/1khz	5	
	=128		
	1000/128 has remainder 104		
(d)			
	104+4		
		6	
	The count is 108		
			15

NOTE: 1) Solutions which are to be reproduced are to be typed or hand written in **black ball point or black ink**.
 2) All solutions for the same subject should be stapled together, with the sheet no. indicated in running order on the top right hand corner.

**NOT TO BE GIVEN TO
STUDENT**

NO	SOLUTION	Marks	Total Marks																																																																																										
C1																																																																																													
(a)	<table><tr><th colspan="4">Input</th><th>Output</th></tr><tr><th>D</th><th>C</th><th>B</th><th>A</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td><td>X</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td><td>X</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td><td>X</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td><td>X</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>X</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td><td>X</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td><td>X</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>X</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td><td>X</td></tr></table>	Input				Output	D	C	B	A	Z	0	0	0	0	X	0	0	0	1	1	0	0	1	0	0	0	0	1	1	0	0	1	0	0	1	0	1	0	1	X	0	1	1	0	X	0	1	1	1	1	1	0	0	0	0	1	0	0	1	1	1	0	1	0	X	1	0	1	1	X	1	1	0	0	X	1	1	0	1	X	1	1	1	0	X	1	1	1	1	X	7	
Input				Output																																																																																									
D	C	B	A	Z																																																																																									
0	0	0	0	X																																																																																									
0	0	0	1	1																																																																																									
0	0	1	0	0																																																																																									
0	0	1	1	0																																																																																									
0	1	0	0	1																																																																																									
0	1	0	1	X																																																																																									
0	1	1	0	X																																																																																									
0	1	1	1	1																																																																																									
1	0	0	0	0																																																																																									
1	0	0	1	1																																																																																									
1	0	1	0	X																																																																																									
1	0	1	1	X																																																																																									
1	1	0	0	X																																																																																									
1	1	0	1	X																																																																																									
1	1	1	0	X																																																																																									
1	1	1	1	X																																																																																									

NOTE: 1) Solutions which are to be reproduced are to be typed or hand written in **black ball point or black ink**.
 2) All solutions for the same subject should be stapled together, with the sheet no. indicated in running order on the top right hand corner.

**NOT TO BE GIVEN TO
STUDENT**

NO	SOLUTION	Marks	Total Marks
(b)	<p>Correct K-map - 3 marks</p> <p>Correct simplified logic expression - 2 marks</p> $F = C + \overline{B}A$	5	
(c)	$F = \overline{\overline{C + \overline{B}A}}$ $= \overline{C + \overline{B}A}$ $= \overline{C} + \overline{\overline{B}A}$ $= \overline{C} + B + A$	3	

NOTE: 1) Solutions which are to be reproduced are to be typed or hand written in **black ball point or black ink**.
 2) All solutions for the same subject should be stapled together, with the sheet no. indicated in running order on the top right hand corner.

NOT TO BE GIVEN TO
STUDENT

NOTE: 1) Solutions which are to be reproduced are to be typed or hand written in **black ball point or black ink.**
2) All solutions for the same subject should be stapled together, with the sheet no. indicated in running order on the top right hand corner.

NOT TO BE GIVEN TO
STUDENT