
 


# Chapter 3 - Synchronous Sequential Logic System

## Sequential Logic Circuit:


- Outputs depend on current state & inputs.
- Also known as **Finite State Machine (FSM)**.
- **Synchronous** sequential logic circuit:
  - Changes states **only at PGT/NGT** of clock signal.
  - Contains synchronised flip-flops for keeping track of its states.  
(Driven by a common clock)
  - Simple examples: synchronous counter, shift register etc.
  - Great majority of sequential logic circuits are synchronous.
- **Asynchronous** sequential logic circuit: (Not covered in this module.)
  - No clock signal, **output feedback to input**.
  - A simple example: NAND gate latch.

State Transition Diagram

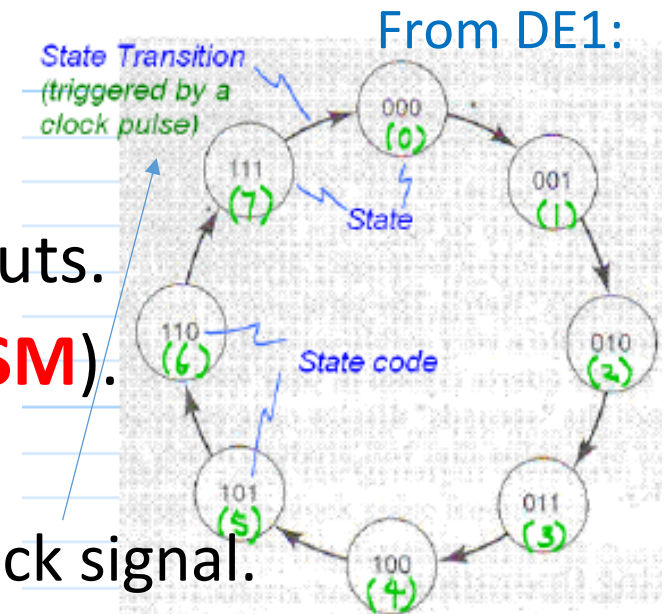

**Figure 1 (Notes 3-1)**
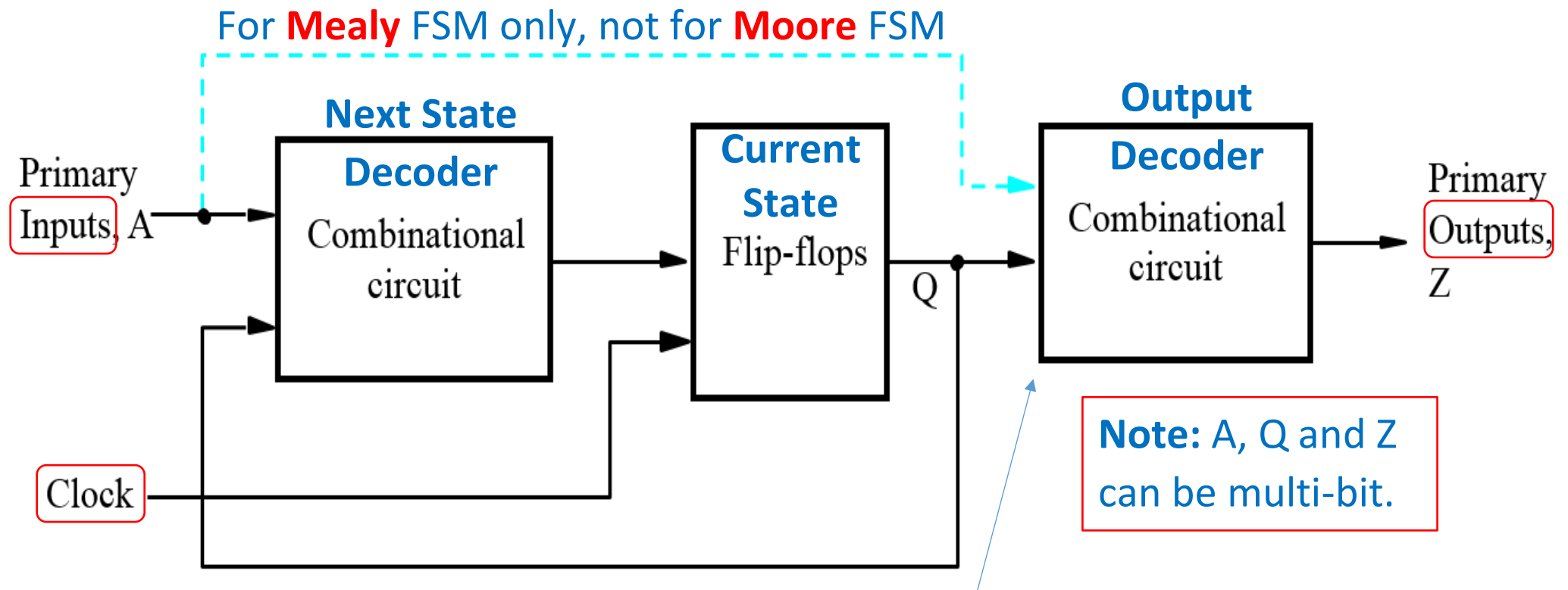
## **General block diagram of a synchronous sequential circuit**



**Moore** type FSM – outputs depend on current state only.


**Mealy** type FSM – outputs depend on current state as well as inputs.

## Example (Notes 3-2)

### Automatic vehicle speed controller:

- Input  $w=1$ : indicates over-speed.
- Output  $z=1$ : apply brake.
- Apply brake ( $z=1$ ) if there are 2 consecutive measurements of over-speed ( $w=1$ ).

#### 2.1 - State Diagram: (Notes 3-3)

 


## Example 1 (Notes 3-4)


Draw the state diagram for a FSM with the following specifications:

1. The circuit has one input,  $w$ , and one output,  $z$ .
2. All changes occur on positive edges of the clock signal.
3. Output  $z=1$  if the input sequence for  $w$  is 101 for any three consecutive clock cycles. Otherwise,  $z=0$ .

**Solution:**

 


## 2.2 State Table (Notes 3-5)

 

**Fig 3.4 State table** (for the State Diagram in Fig 3.3)

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

## Example 2 (Notes 3-5)

 


State table for the  
State Diagram in Ex 1:

Present state	Next state		Output z
	w=0	w=1	
A	A	B	0
B	C	B	0
C	A	D	0
D	C	B	1
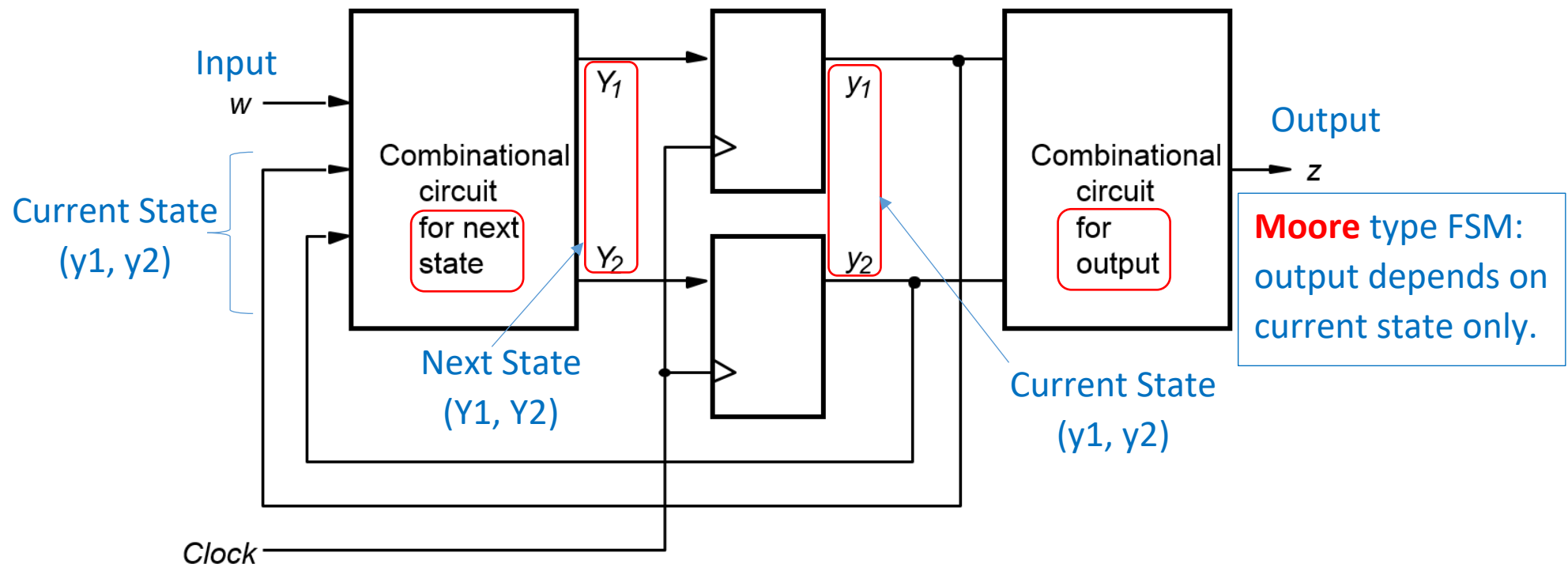
## 2.3 State Assignment (Notes 3-6)

- Assign a unique N-bit binary number for each state.
- Each bit (state variable) is stored at the Q output of a flip-flop.
- **Binary state assignment** is simple but not most efficient.
- Proper state assignment leading to simpler circuit will be covered in Section 7 (Notes 3-24).



# Example:

Fig 3.3 State Diagram

 


Fig 3.6 State-assigned table

Present state	Next state		Output  z
	w = 0	w = 1	
	$y_2 y_1$	$Y_2 Y_1$	
A	00	00	0
B	01	10	0
C	10	10	1
	11	dd	d

Present state	Next state		Output  z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	C	1

Fig 3.4 State table

Assign any 3 binary numbers to the 3 states (A, B, C).


Assign “don’t care” (x or d) to the unused state for “next state” and “output” in order to simplify their circuits.



## 2.4 Excitation Table (Notes 3-7)

Excitation table is basically the truth table of the **next state circuit** and **output circuit**:

	Present state $Q_2 Q_1$ $y_2 y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$D_2 D_1$ $Y_2 Y_1$	$D_2 D_1$ $Y_2 Y_1$	
A	00	<b>A</b> 00	<b>B</b> 01	0
B	01	<b>A</b> 00	<b>C</b> 10	0
C	10	<b>A</b> 00	<b>C</b> 10	1
	11	$d\bar{d}$	$d\bar{d}$	$d$

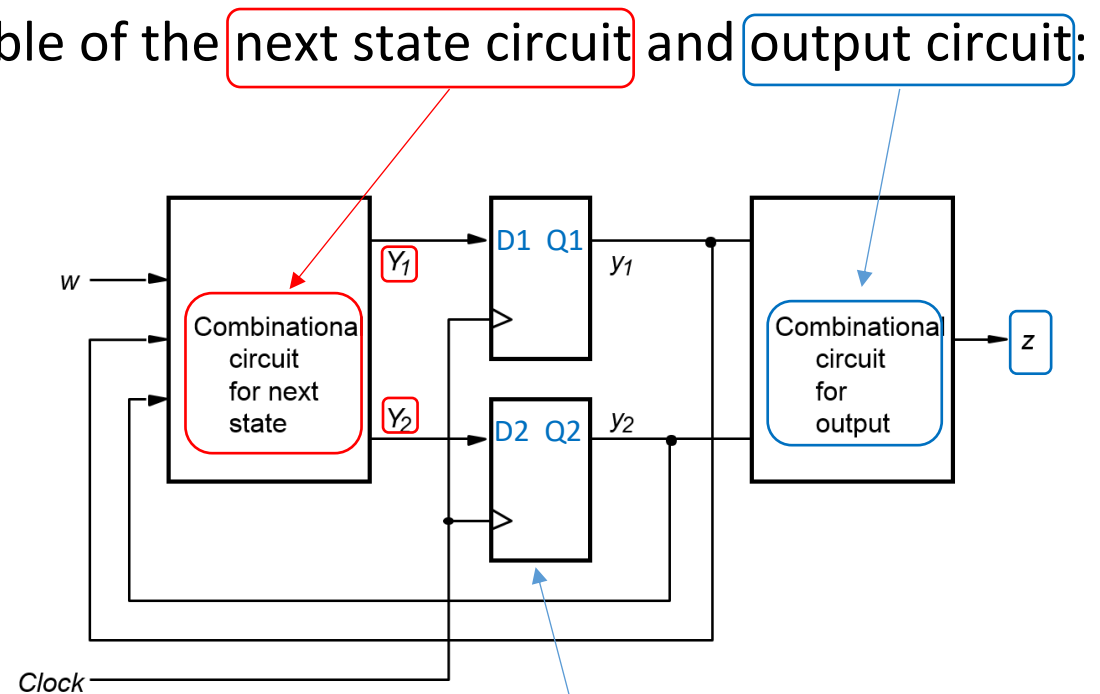

Implementing with D flip-flops.

$y_2 \backslash y_1$	0	1
0	0	0
1	1	d

$$z = y_2$$

$w \backslash y_2 y_1$	00	01	11	10
0	0	0	d	0
1	1	0	d	0

$$Y_1 = D_1 = w\bar{y}_1\bar{y}_2$$

$w \backslash y_2 y_1$	00	01	11	10
0	0	0	d	0
1	0	1	d	1

$$Y_2 = D_2 = wy_1 + wy_2$$


$$= w(y_1 + y_2)$$

3 gates

2 gates

## “11” sequence detector implemented using D-type flip-flops:

\_\_\_\_\_

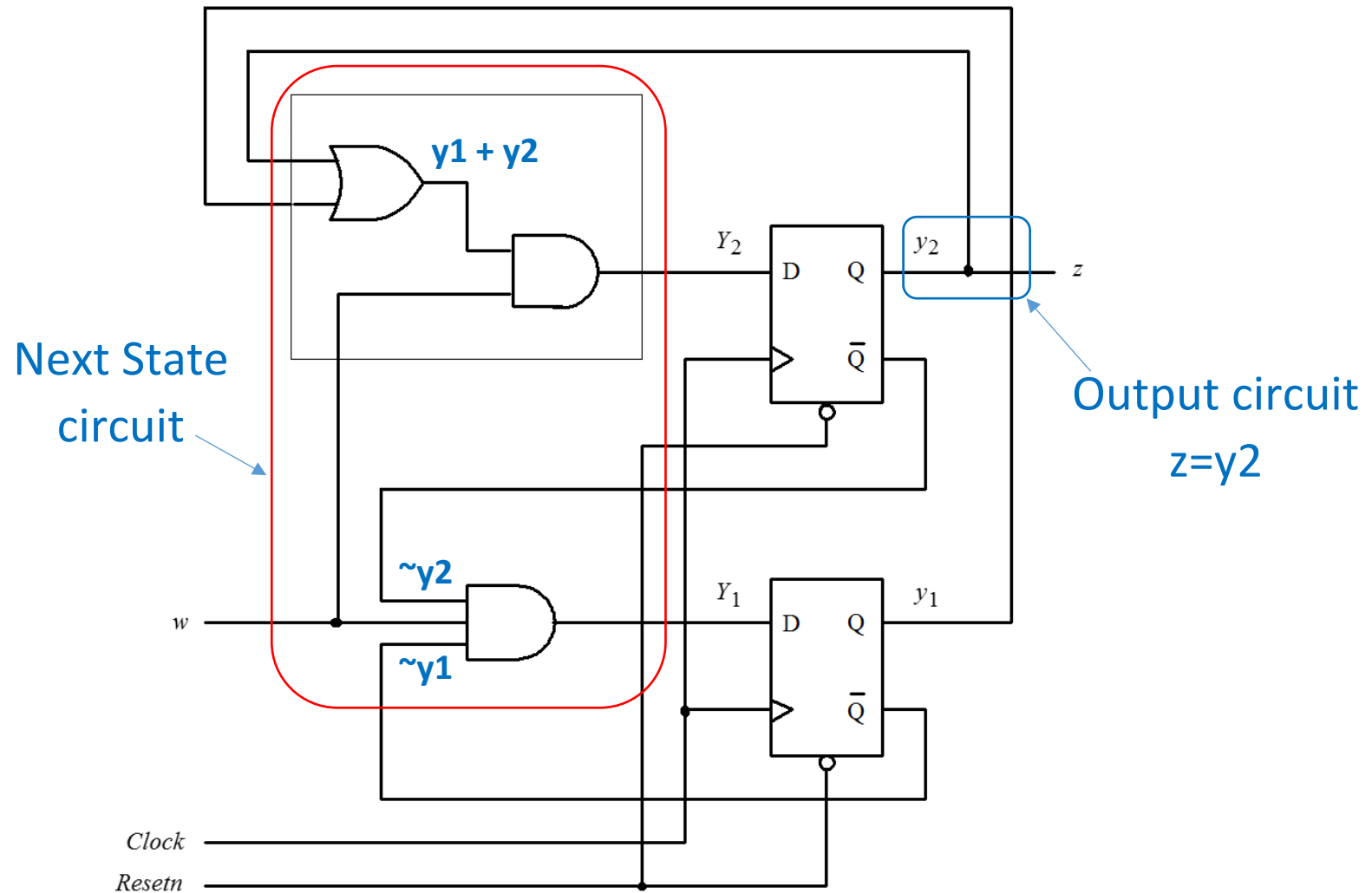

While it is easier to design with D flip-flops, using J-K flip-flops often results in simpler logic for the “next state” decoder.

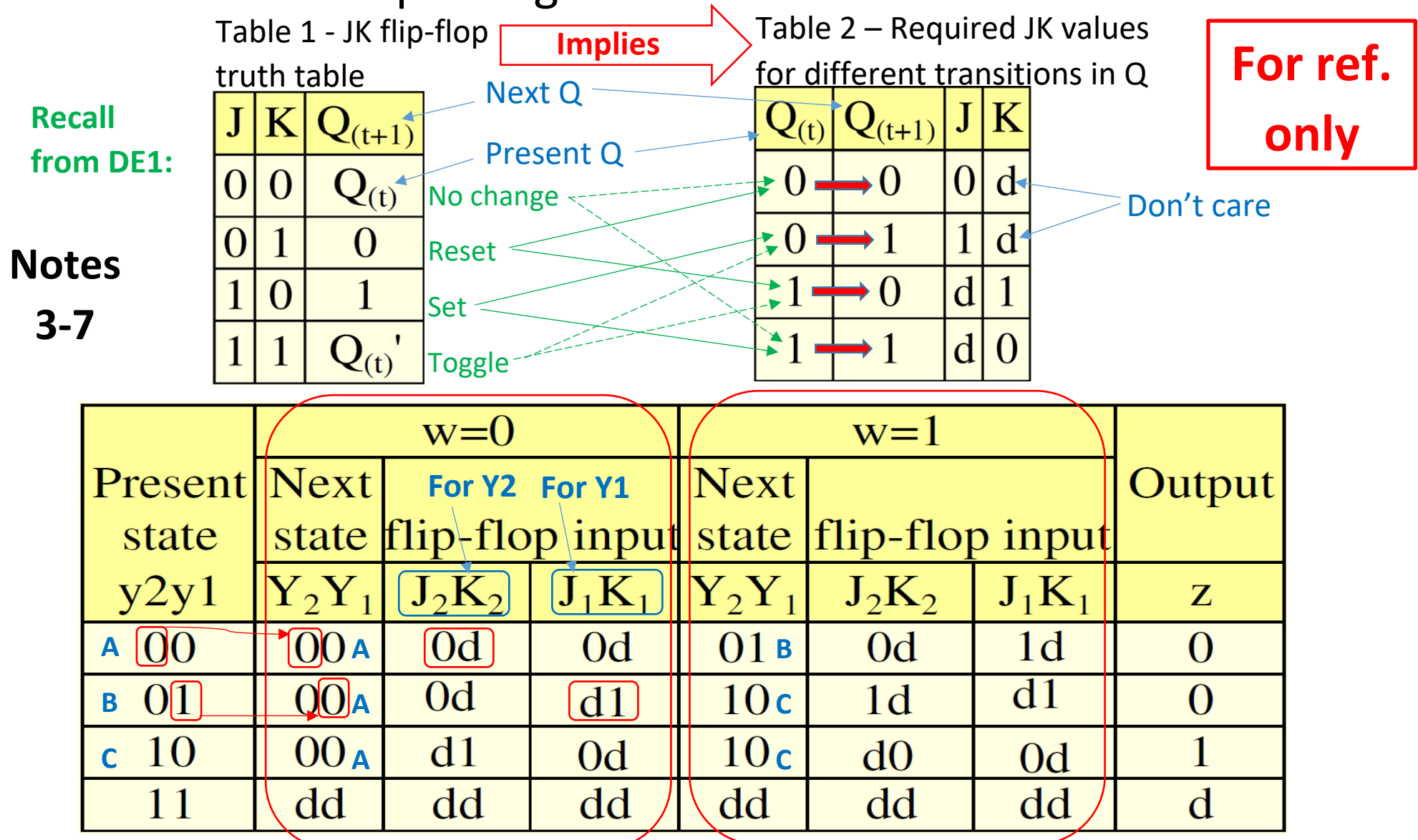


Figure 7. Excitation table for JK flip-flops. (Notes 3-7)

Some may prefer to present the above excitation table in the traditional truth table form:

**For ref.  
only**

Present State			Primary Input	Next State			For $y_2 \rightarrow Y_2$		For $y_1 \rightarrow Y_1$		Primary Output
	y2	y1	w		Y2	Y1	J2	K2	J1	K1	Z
A	0	0	0	A	0	0	0	X	0	X	0
A	0	0	1	B	0	1	0	X	1	X	0
B	0	1	0	A	0	0	0	X	X	1	0
B	0	1	1	C	1	0	1	X	X	1	0
C	1	0	0	A	0	0	X	1	0	X	1
C	1	0	1	C	1	0	X	0	0	X	1
	1	1	0		X	X	X	X	X	X	X
	1	1	1		X	X	X	X	X	X	X

$y_2 \rightarrow Y_2$  in red

$y_1 \rightarrow Y_1$  in blue

Transition

$Q_{(t)}$	$Q_{(t+1)}$	J	K
0	→ 0	0	d
0	→ 1	1	d
1	→ 0	d	1
1	→ 1	d	0

Inputs to the  
**next state**  
circuit.

The required  
**next state.**

# Notes 3-9

**For ref. only**

**Figure 10** - K-map for J2, K2, J1 and K1

		$y_2 y_1$			
		00	01	11	10
$w$	0	0	0	d	d
	1	0	1	d	d

$$J_2 = wy_1$$

		$y_2 y_1$			
		00	01	11	10
$w$	0	d	d	d	1
	1	d	d	d	0

$$K_2 = \overline{w}$$

		$y_2 y_1$			
		00	01	11	10
$w$	0	0	d	d	0
	1	1	d	d	0


$$J_1 = w\overline{y_2}$$

		$y_2 y_1$			
		00	01	11	10
$w$	0	d	1	d	d
	1	d	1	d	d


$$K_1 = 1$$

**Figure 11** - "11" sequence detector implemented using JK flip-flops

Next State  
circuit

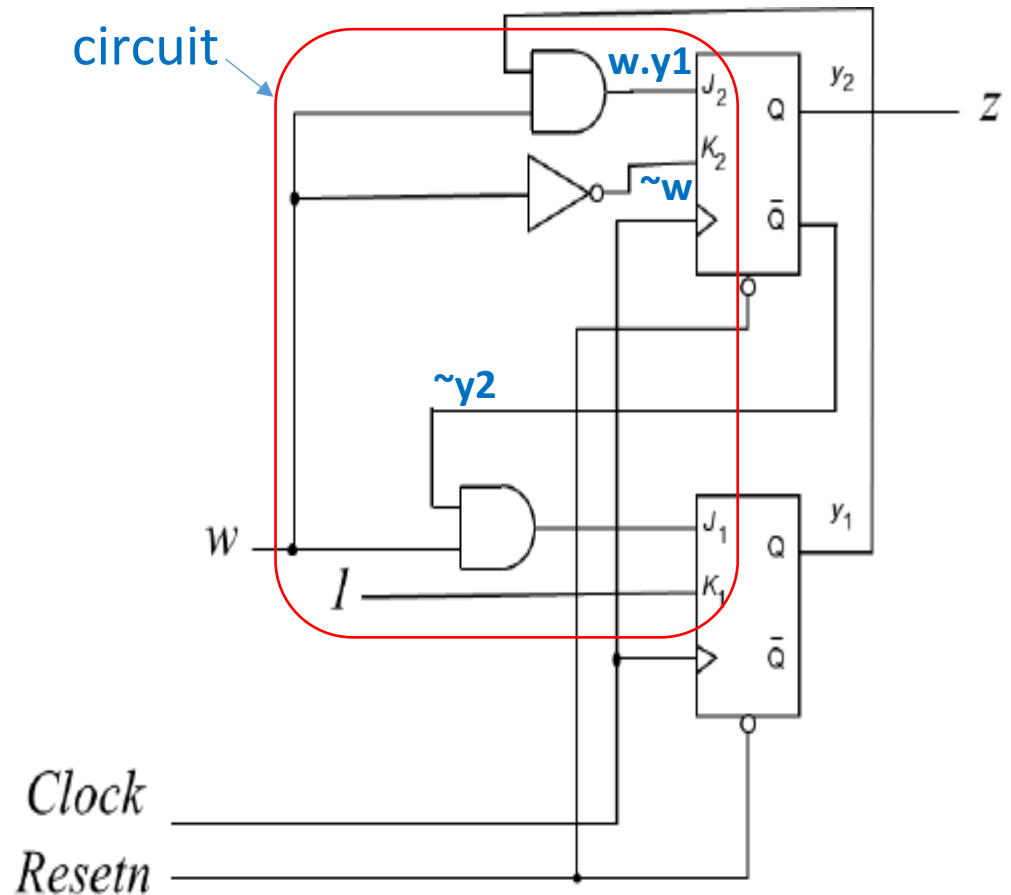


**Figure 12** - Timing diagram of “11” sequence detector (Notes 3-10)

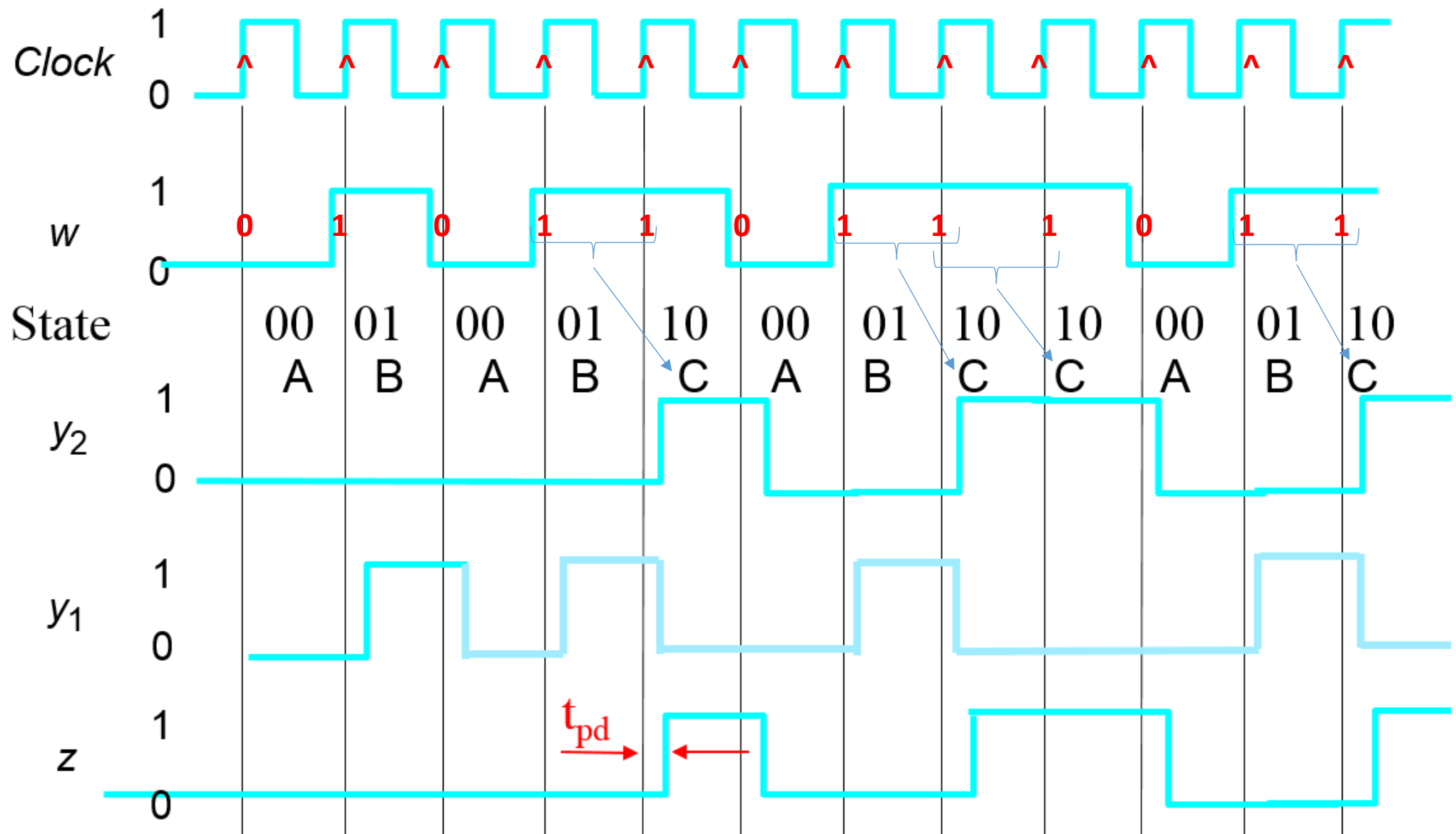 

### Example 3 (Notes 3-10)

Derive the state-assigned table for the FSM in Example 1 and hence draw the schematic diagram of the FSM using D-type flip-flops.



Present state $Q_2 Q_1$ $Y_2 Y_1$	Next state, $Y_2 Y_1$		Output $Z$
	$w=0$ $D_2 D_1$	$w=1$ $D_2 D_1$	
<b>A</b> 00	<b>A</b> 00	<b>B</b> 01	0
<b>B</b> 01	<b>C</b> 10	<b>B</b> 01	0
<b>C</b> 10	<b>A</b> 00	<b>D</b> 11	0
<b>D</b> 11	<b>C</b> 10	<b>B</b> 01	1

**Solution:**

$$Z = y_2 y_1$$

$$D_2 = Y_2 = w' y_1 + w y_2 y_1$$

$$D_1 = Y_1 = w$$

$D_2$		$w$	
		0	1
$y_2 y_1$	00	0	0
	01	1	0
	11	1	0
	10	0	1


$D_1$		$w$	
		0	1
$y_2 y_1$	00	0	1
	01	0	1
	11	0	1
	10	0	1

## Schematic diagram of the FSM using D-type flip-flops:

$$z = y_2 y_1$$

$$D_2 = Y_2 = w' y_1 + w y_2 y_1$$

$$D_1 = Y_1 = w$$

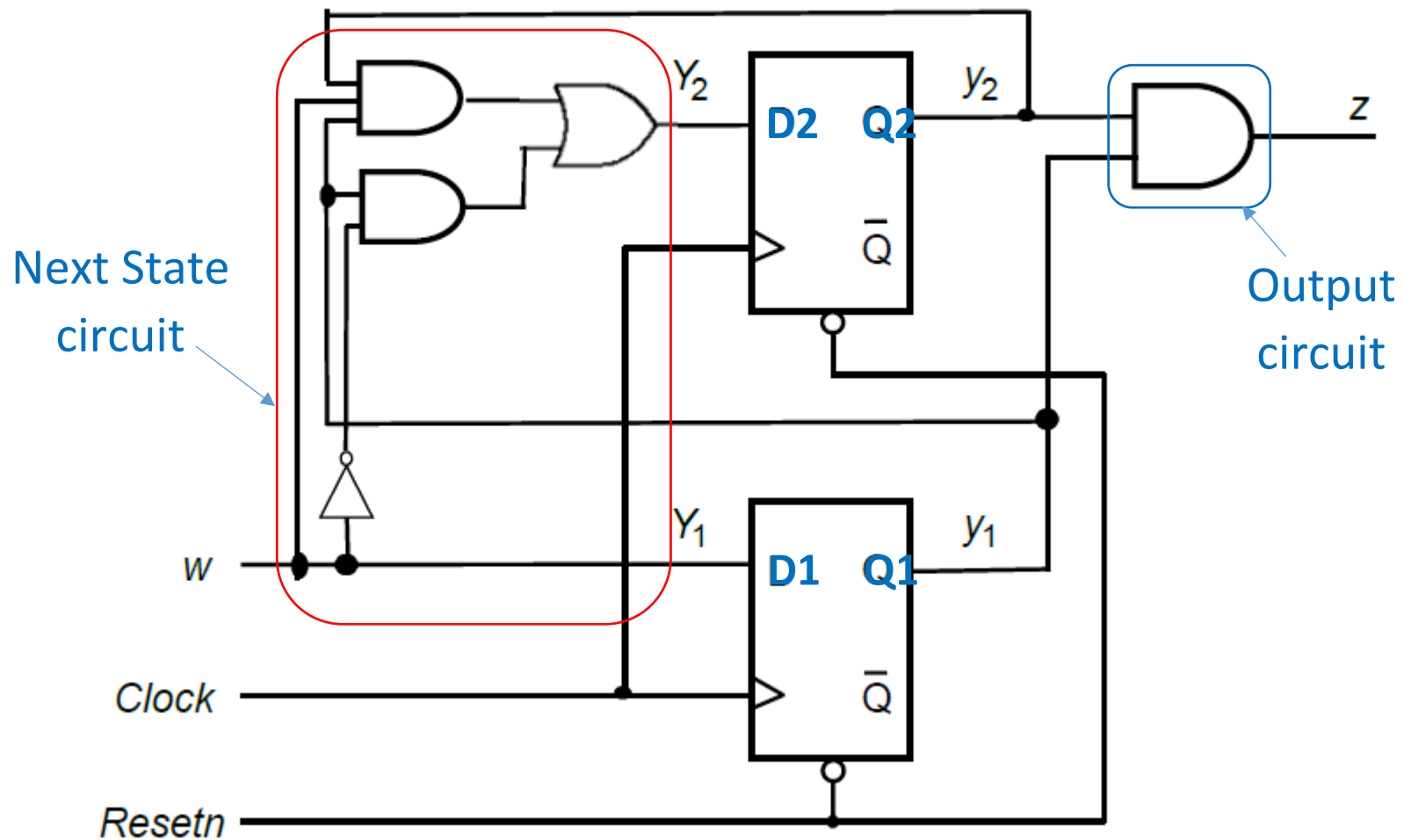



## **2.6 Summary of FSM design procedure (Notes 3-11)**

1. Obtain the specification of the desired FSM.
2. Draw the state diagram.
3. Derive the state table.
4. Assign state code.
5. Derive the state-assigned table and/or excitation table.
6. Derive the output & flip-flop input equations.
7. Implement the circuit from the equations derived.