

Circuit Analysis

Voltage and Current Sources




Objective

- & Understand the characteristics of voltage and current sources
- & Understand the principle of source conversion
- & Operate voltage sources and current sources in series and parallel combination and find equivalent circuit.




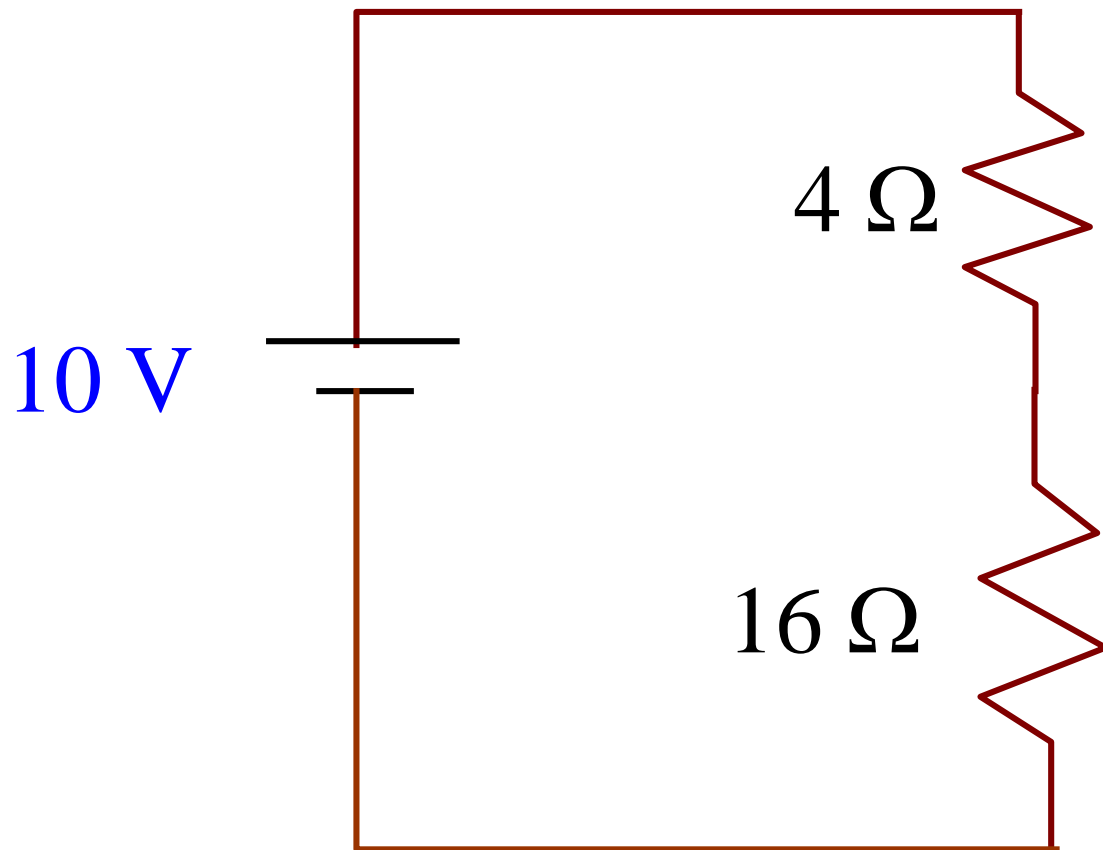The use of arrow to represent potential difference






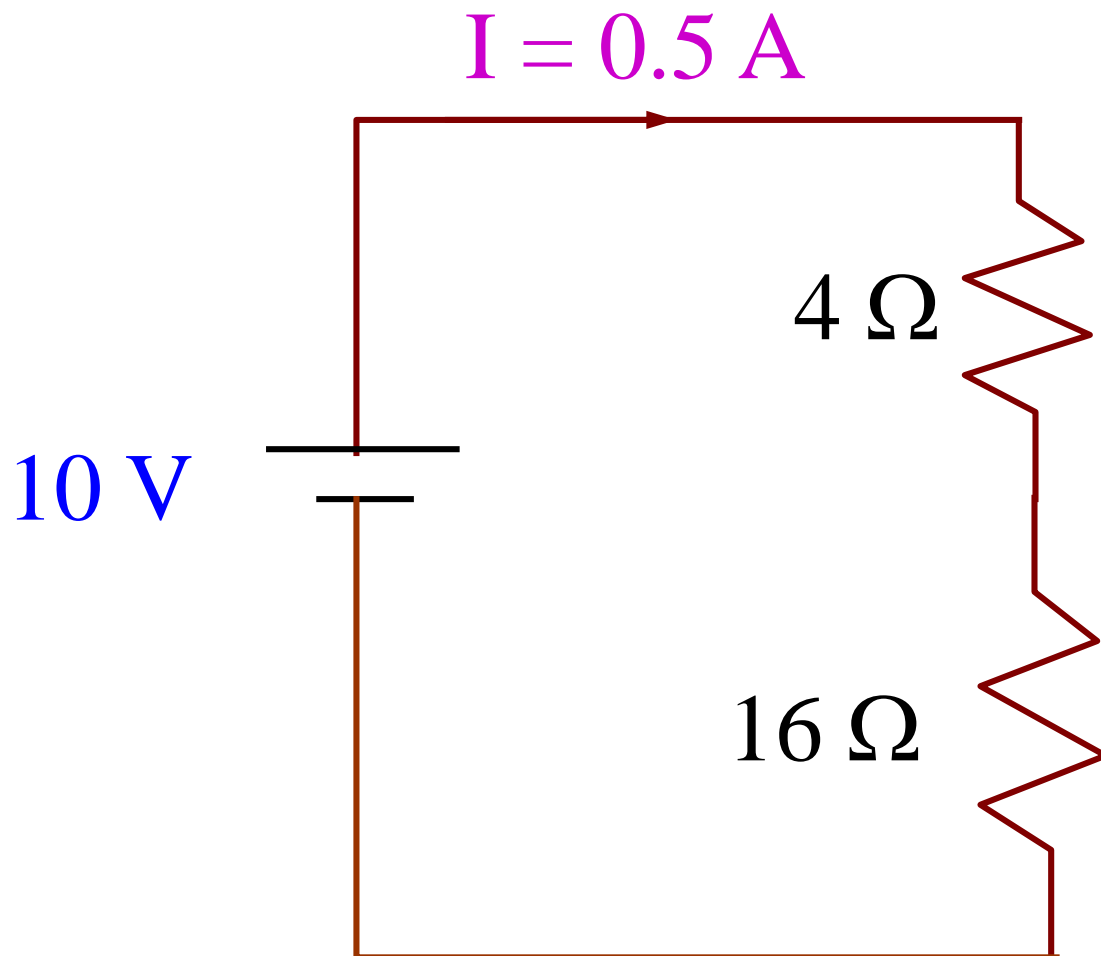
The use of arrow to represent potential difference






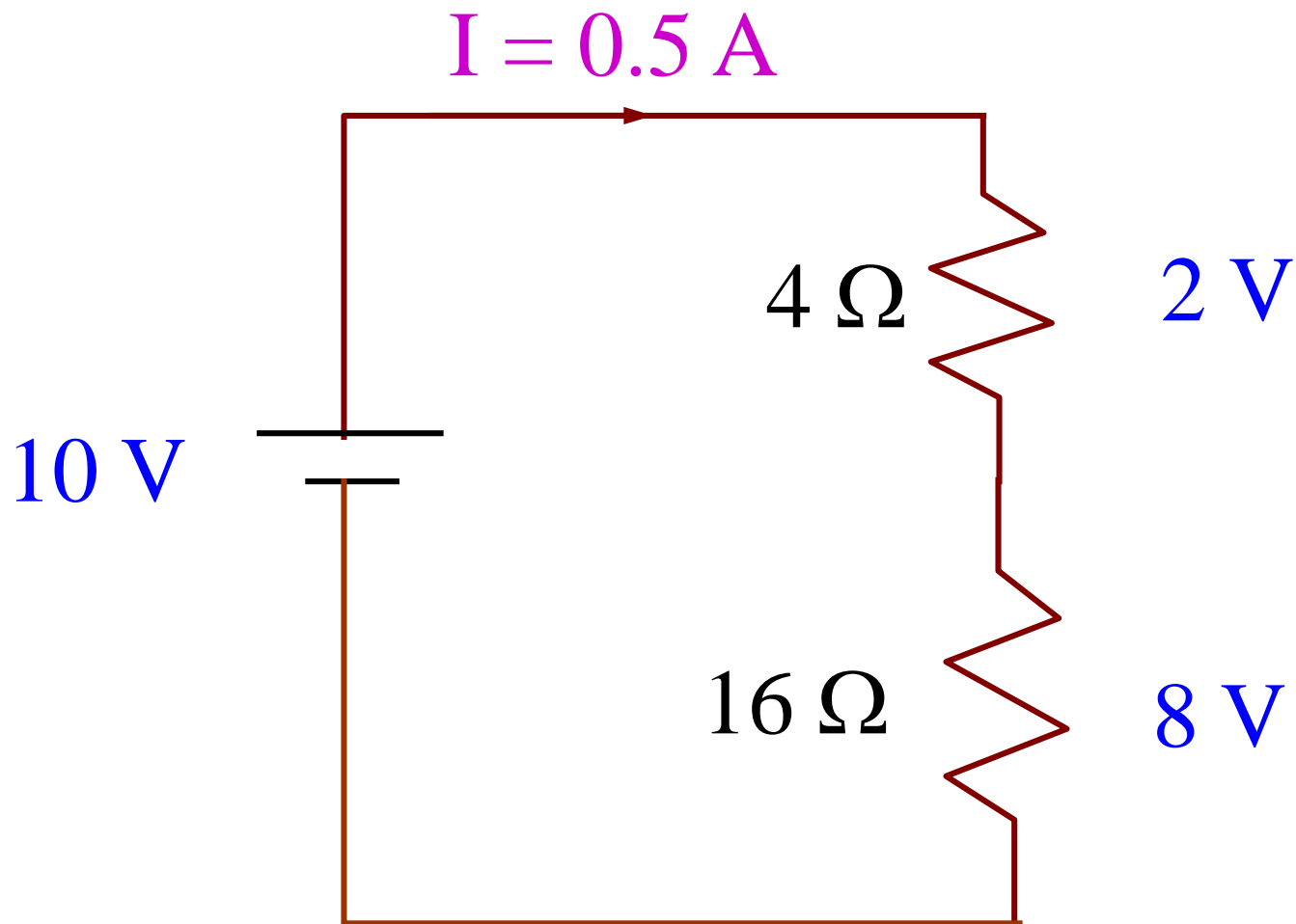
The use of arrow to represent potential difference




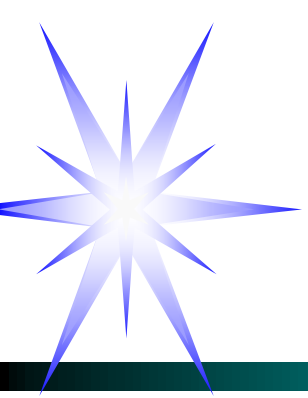


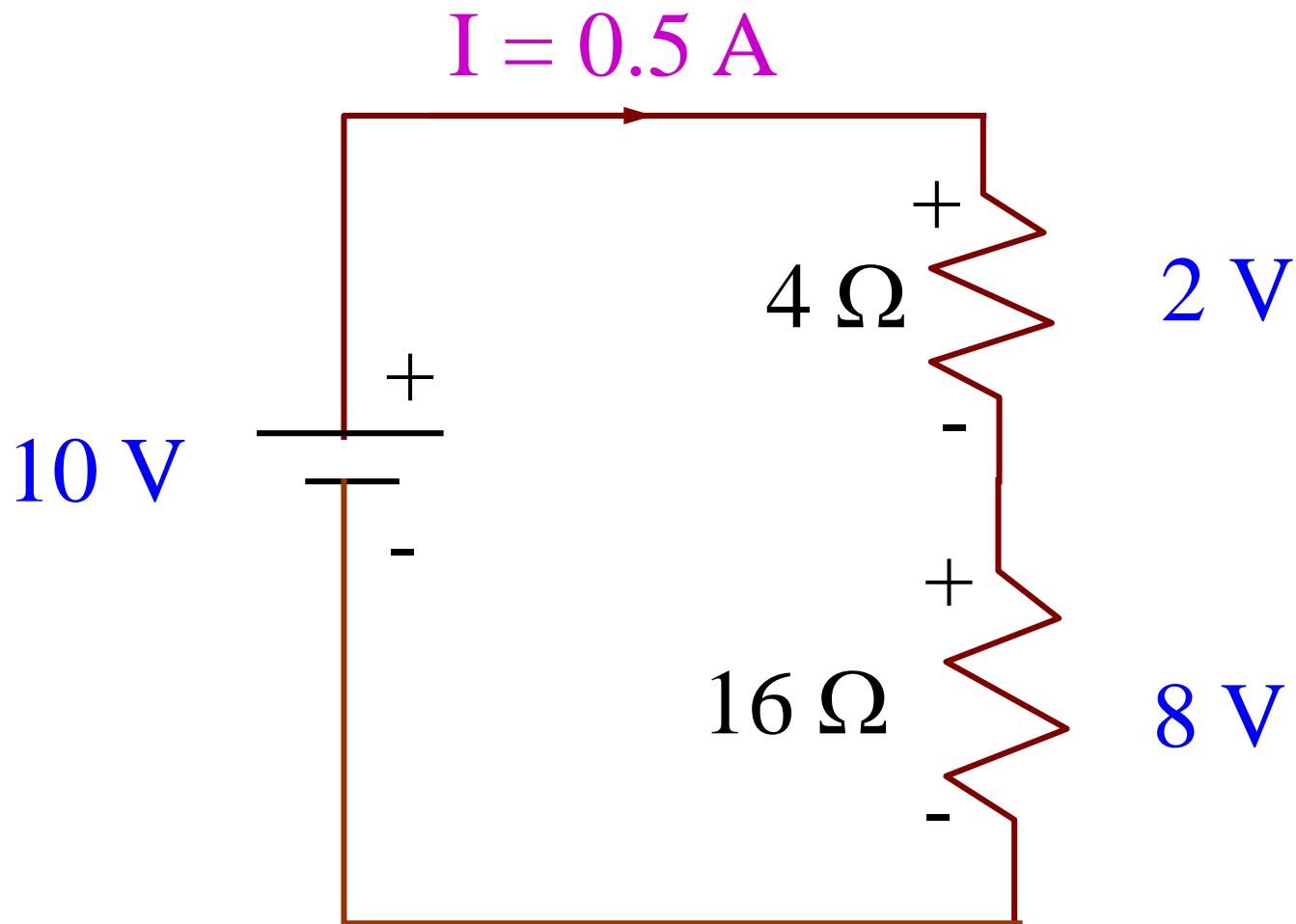
The use of arrow to represent potential difference



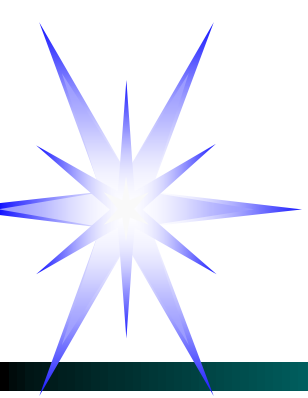


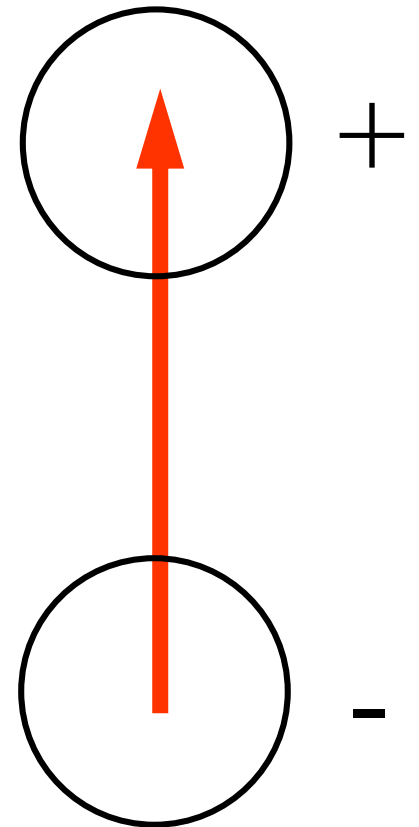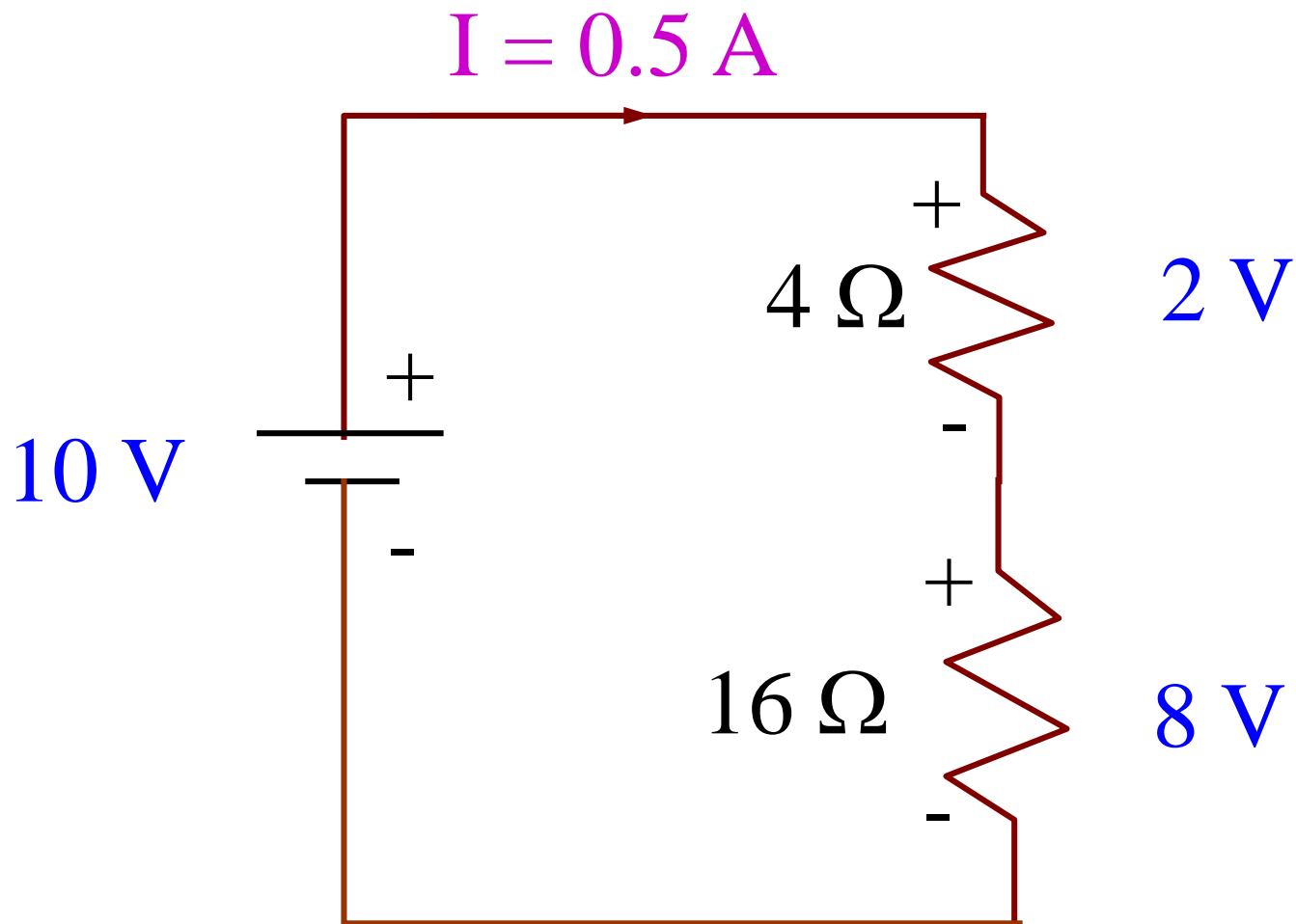The use of arrow to represent potential difference



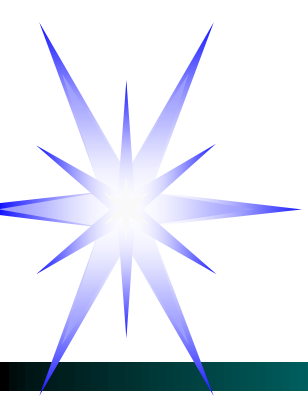


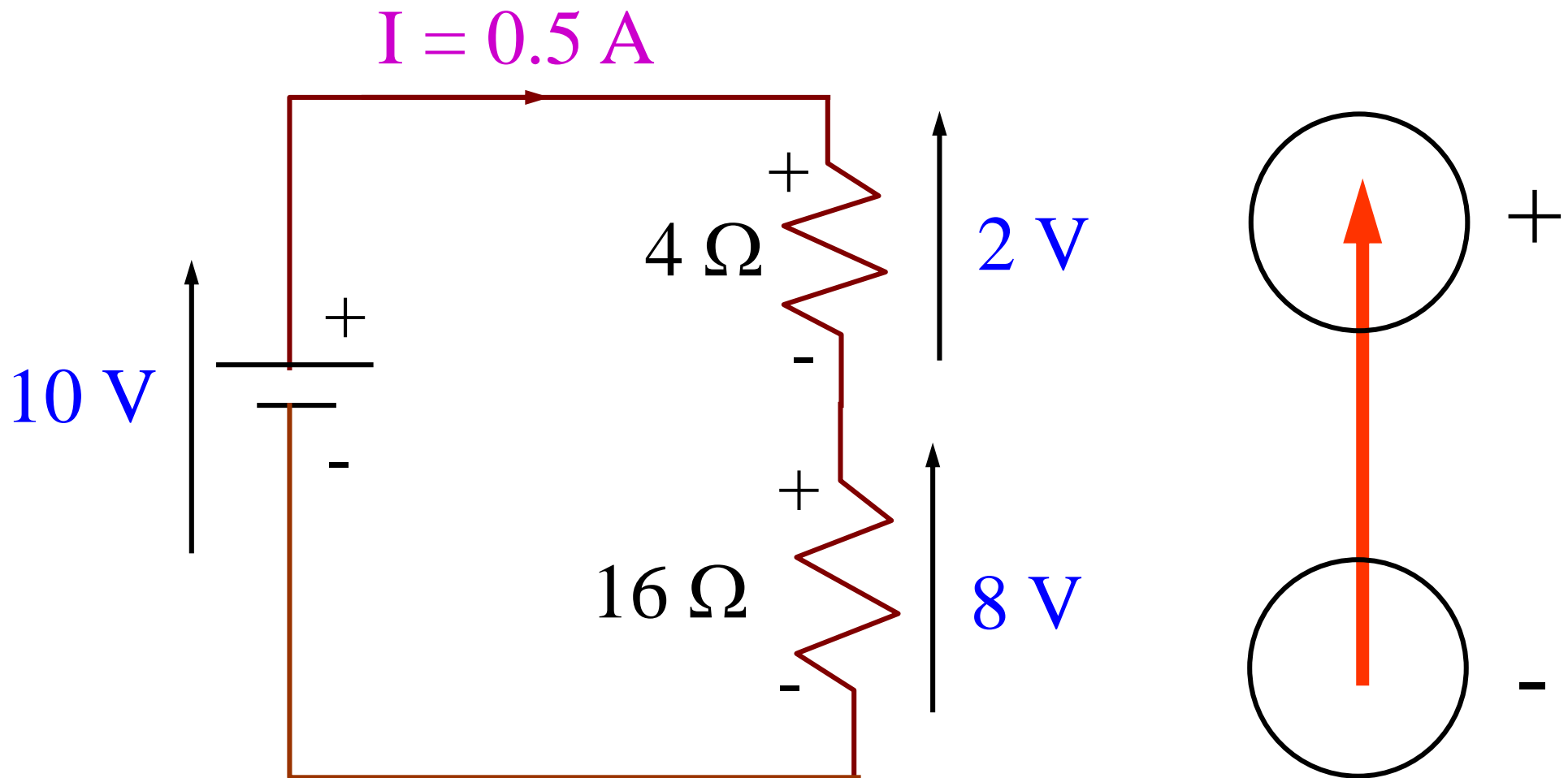
The use of arrow to represent potential difference






Constant Voltage Source

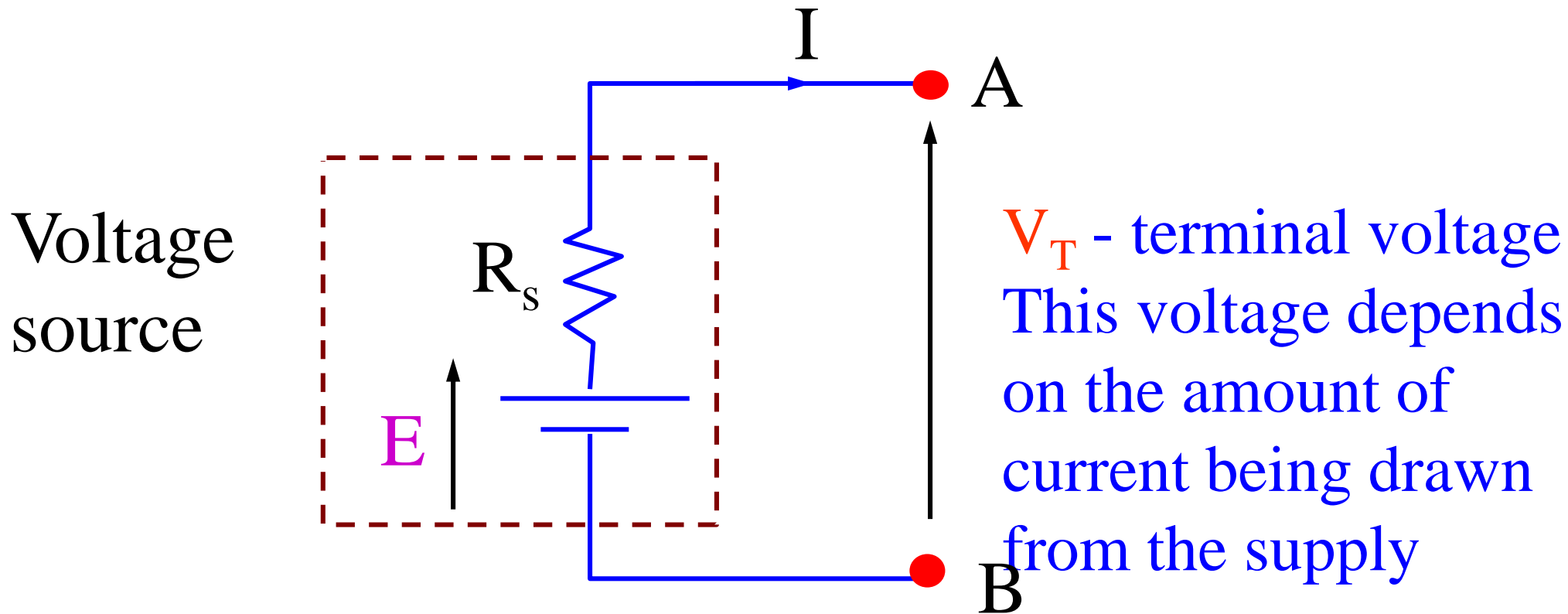

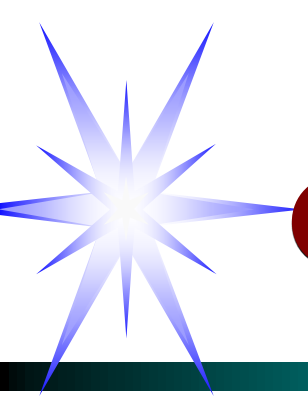


Constant Voltage Source

↩ Representation of voltage source

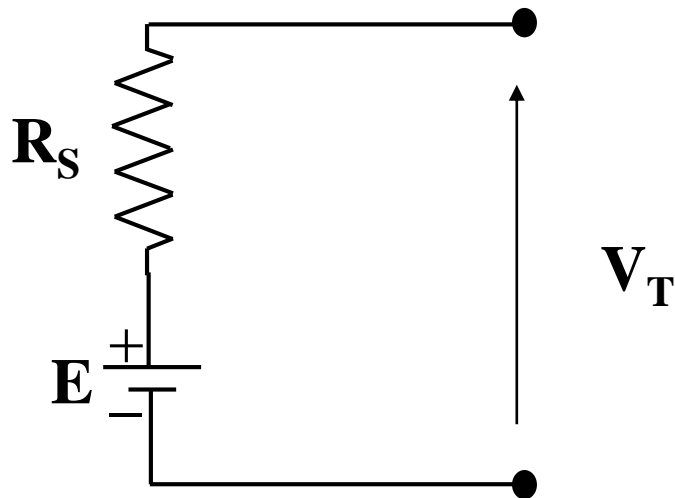


(a) Voltage source

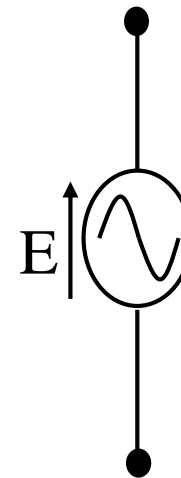

(b) Other symbol



Constant Voltage Source

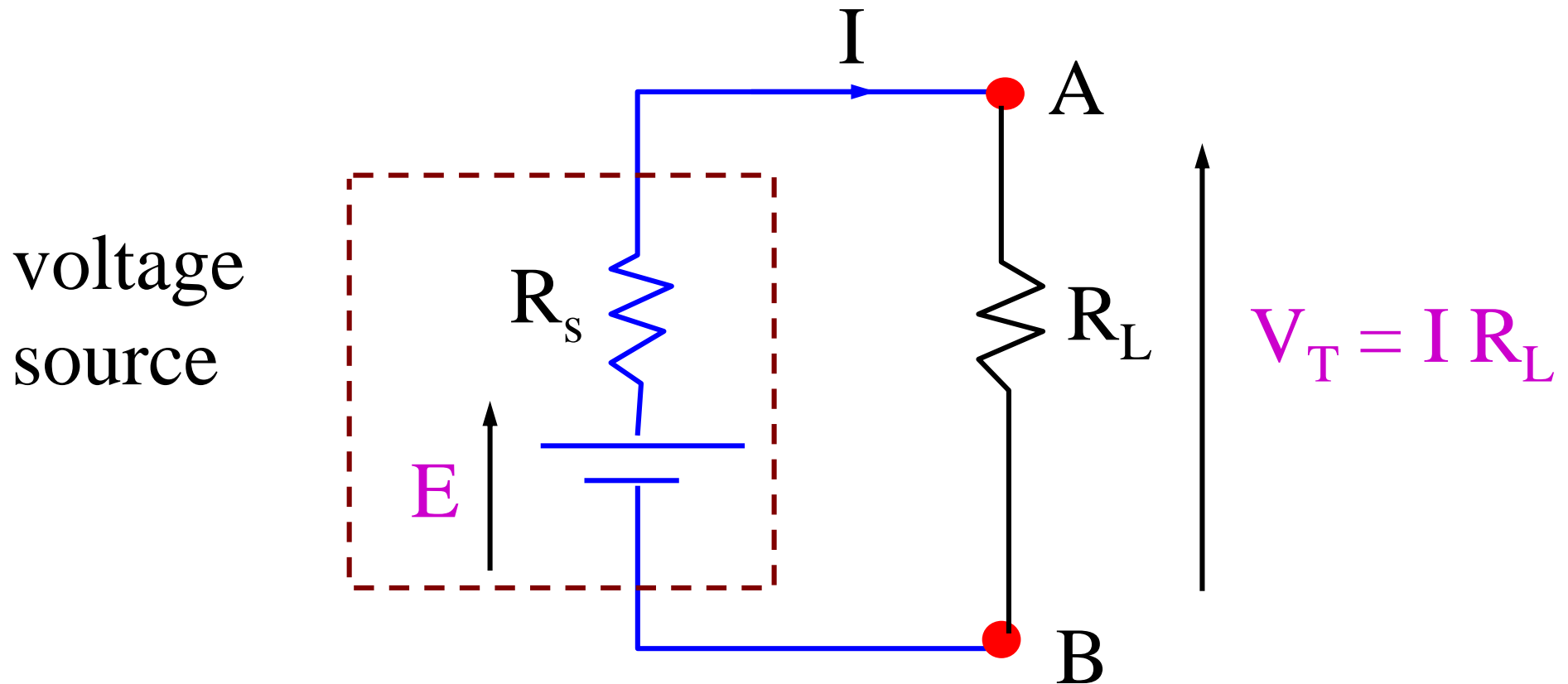


By KVL, $E = I R_s + V_T = I R_s + I R_L$



Constant Current Source

Current
Source

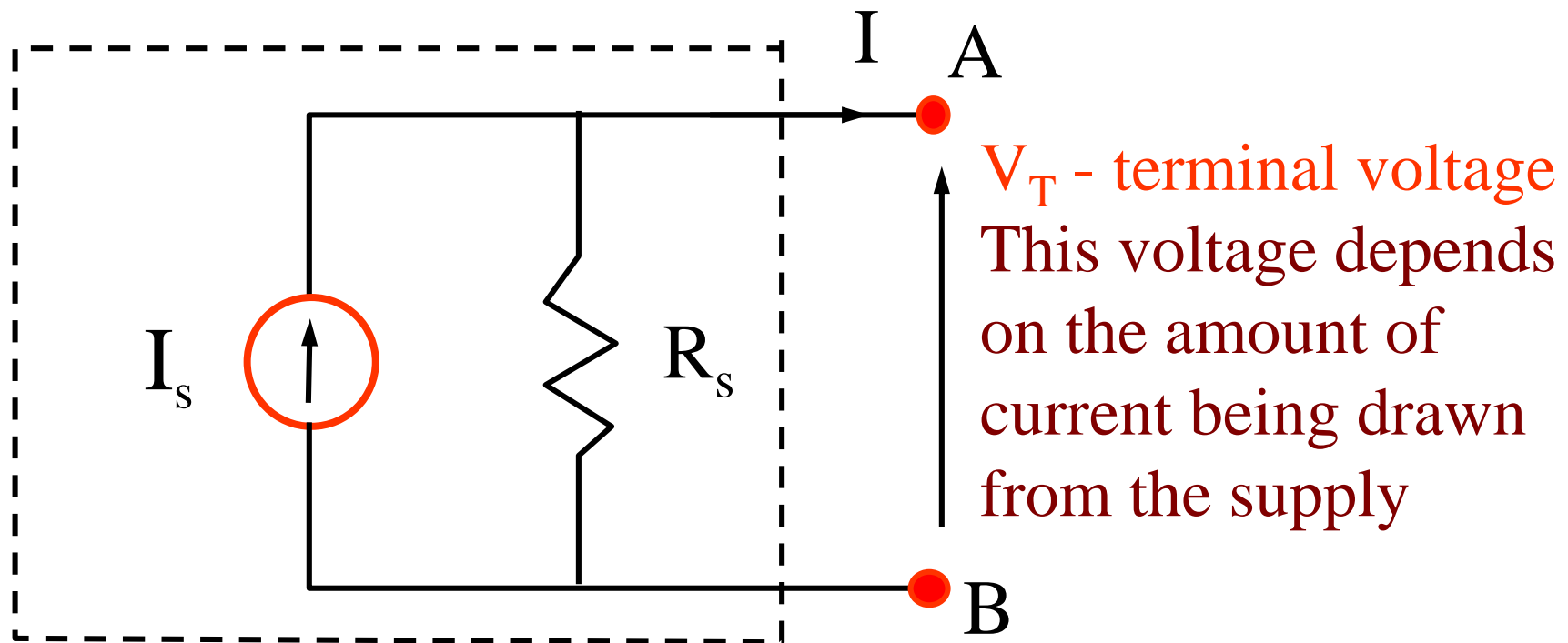


I_s = constant current, independent of the load

R_s = internal resistance


I = load current




Constant Current Source

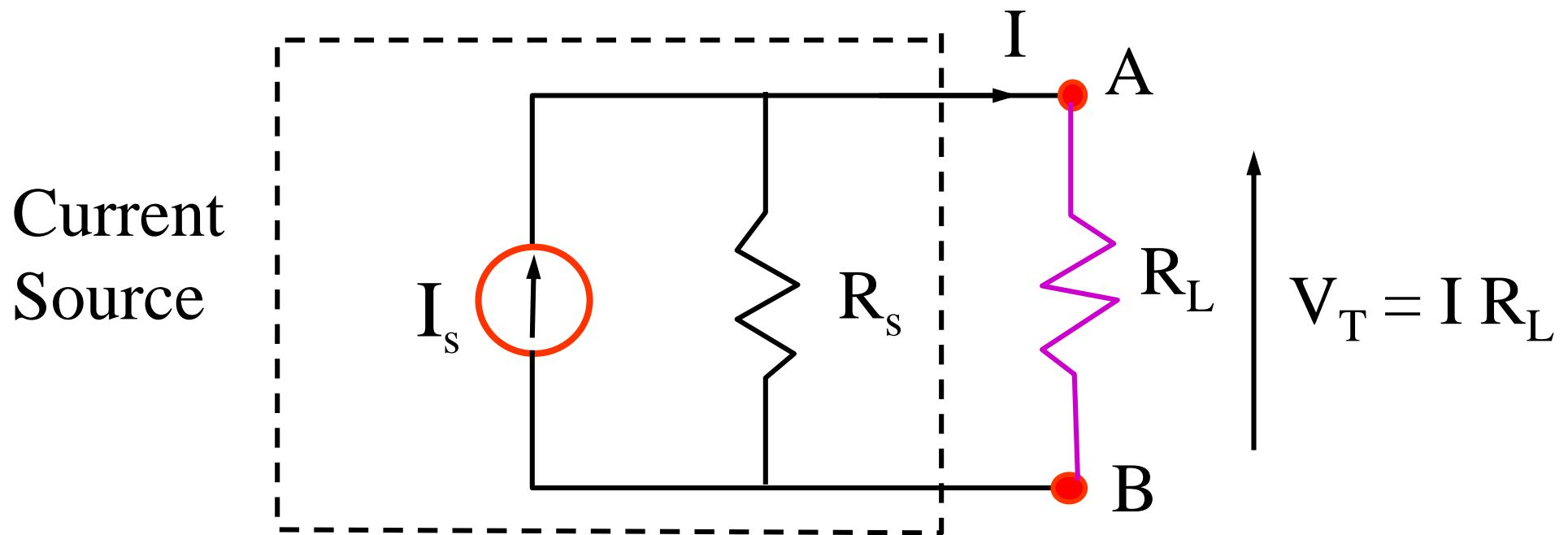

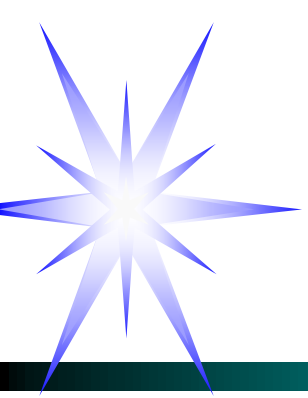
Assume that a resistor R_L is connected across the terminals A & B such that $V_T = I R_L$ and $I = I_s \times [R_s / (R_s + R_L)]$ (current divider)



Source Conversion

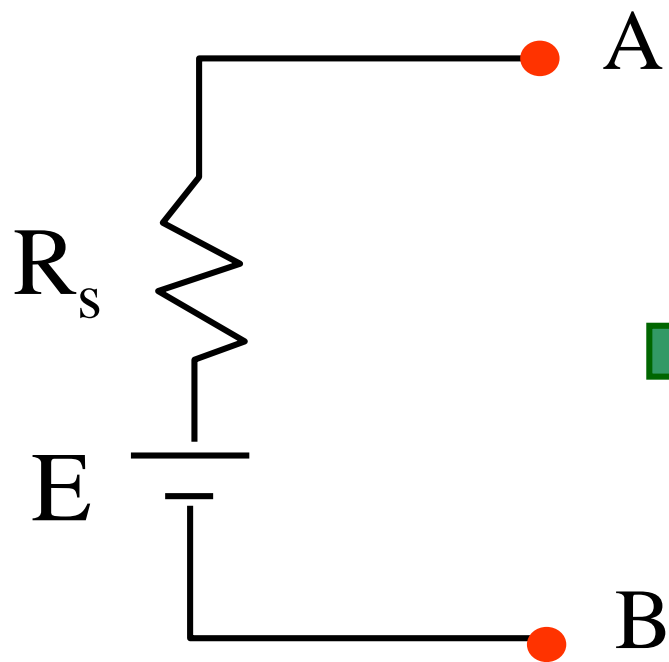


Voltage source

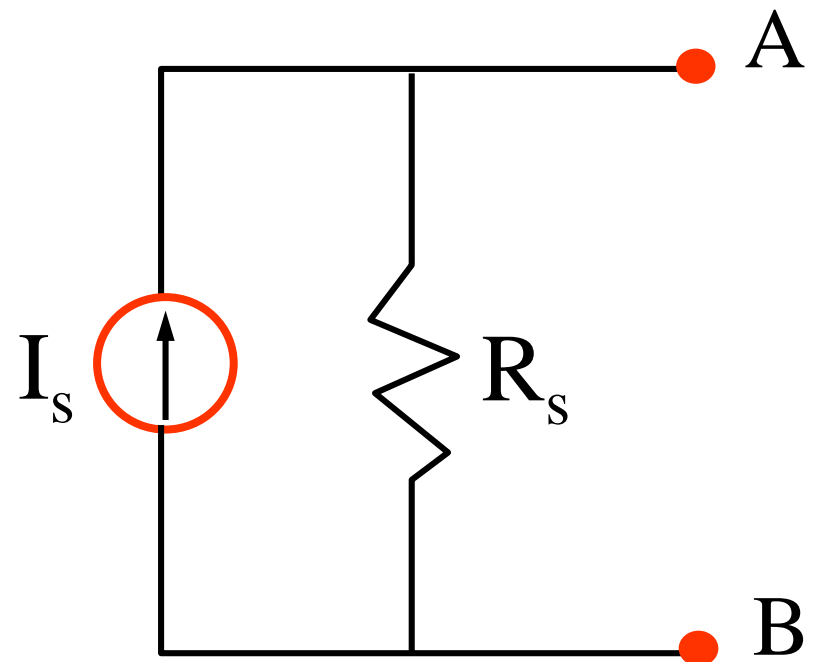


Current source


$$I_s = E / R_s$$

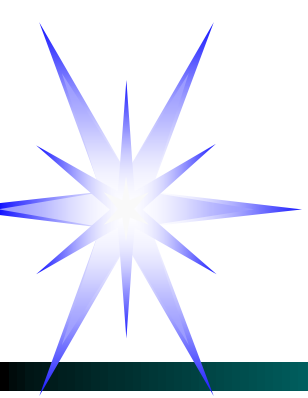


Source Conversion

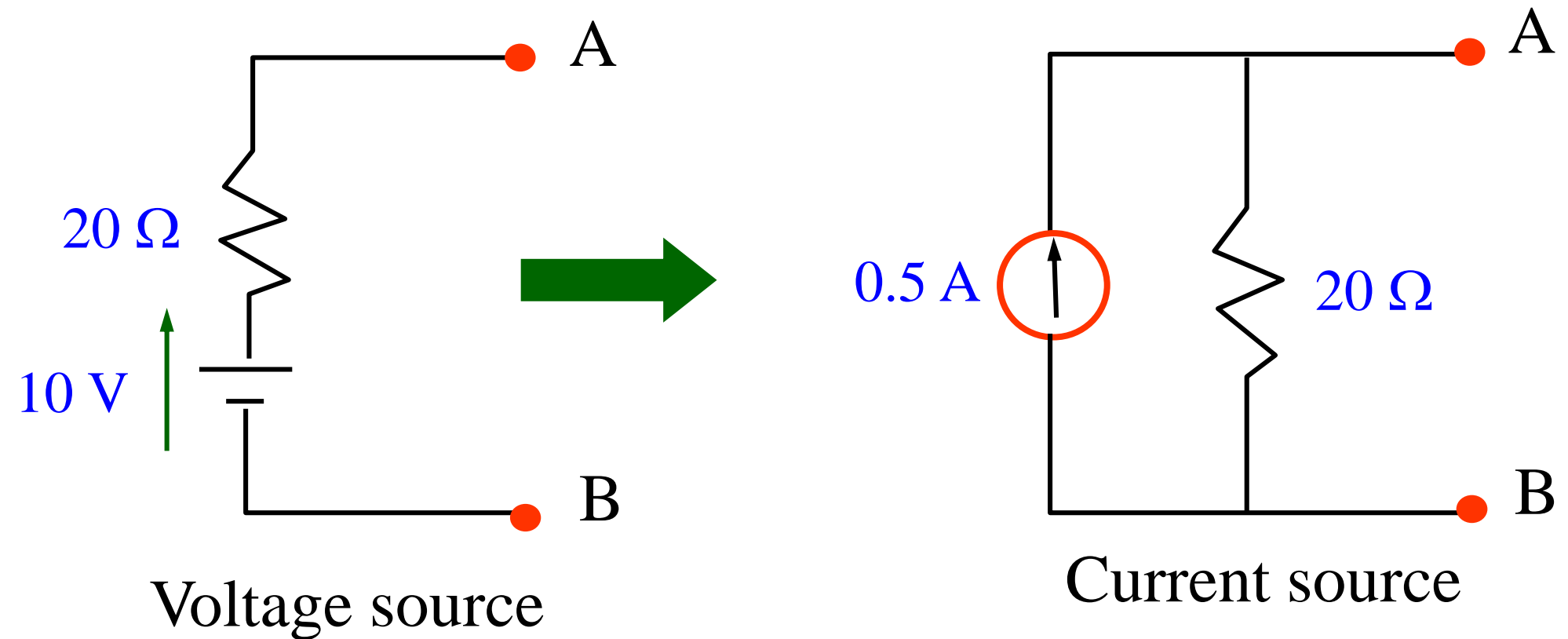

$$I_s = 10/20 = 0.5 \text{ A}$$

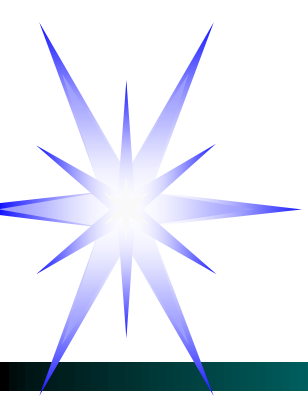


Source Conversion

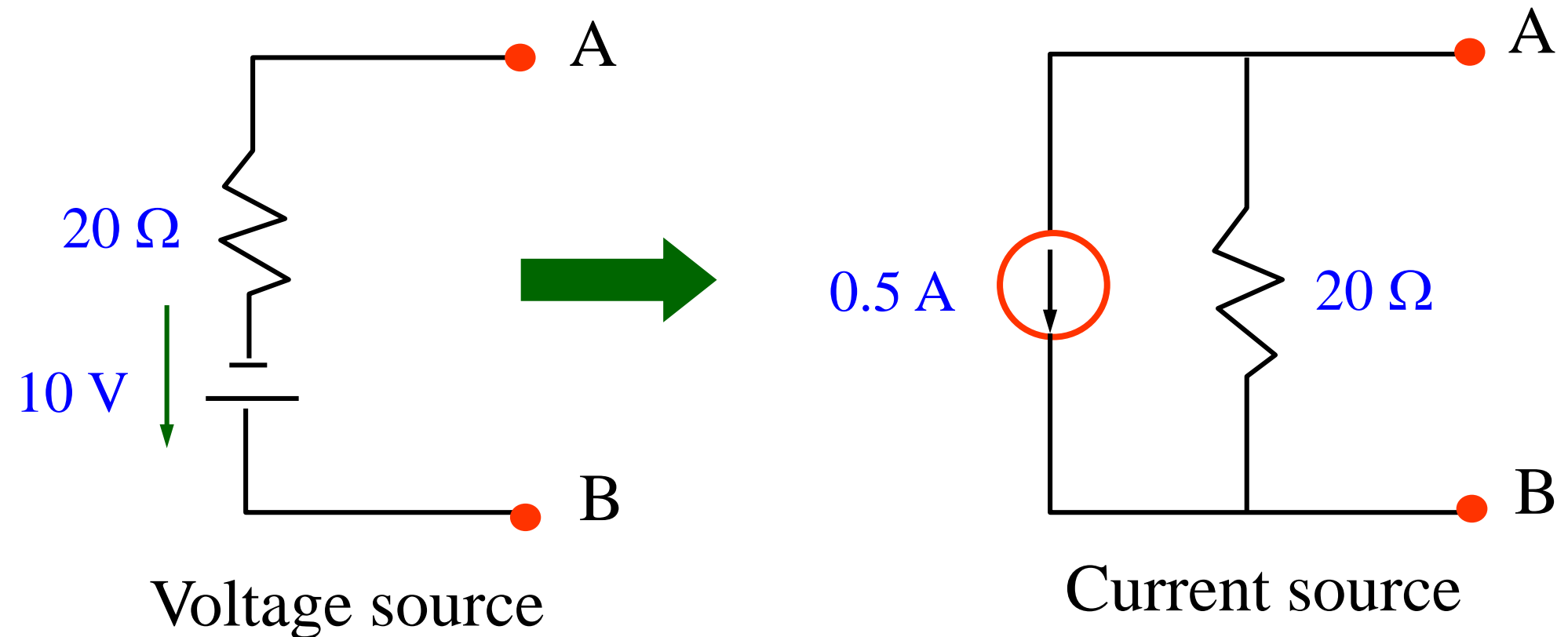



$$I_s = 10/20 = 0.5 \text{ A}$$



Source Conversion

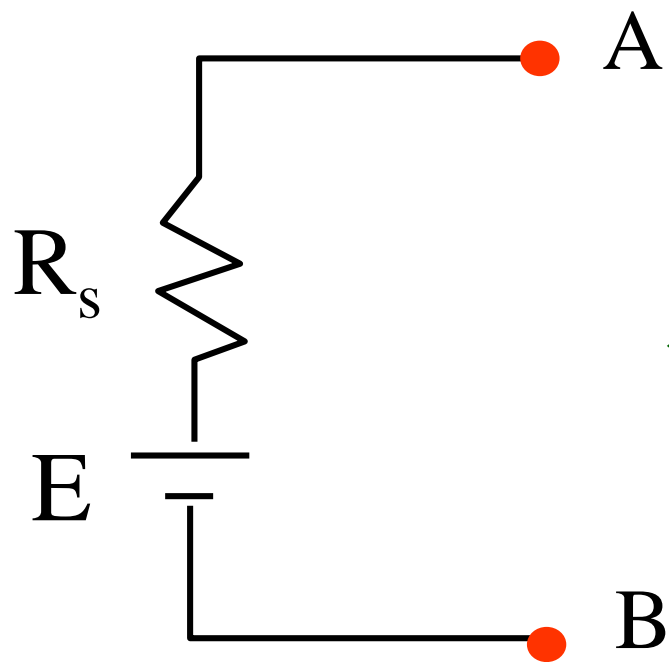


Voltage source

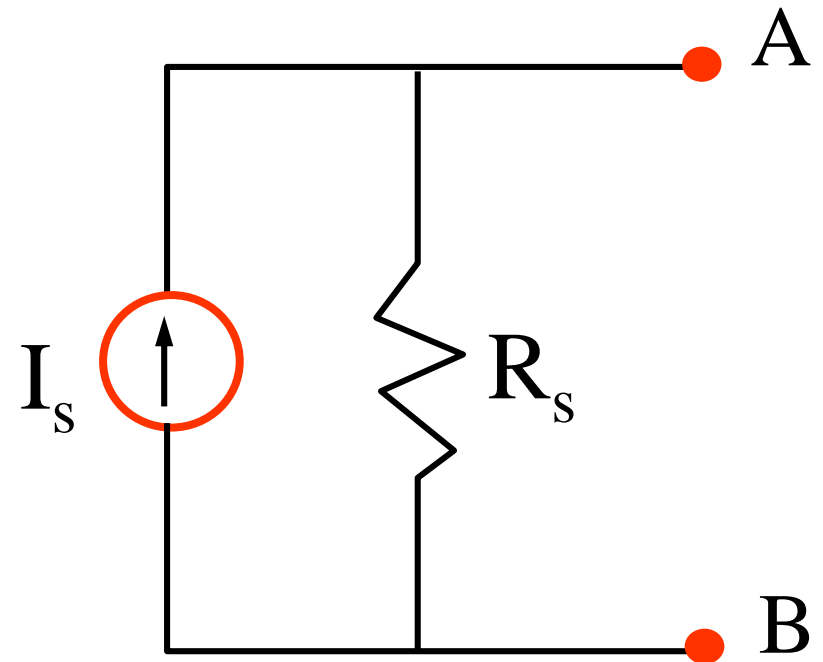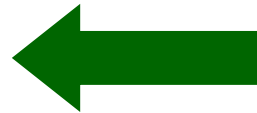


Current source


$$E = I_s R_s$$

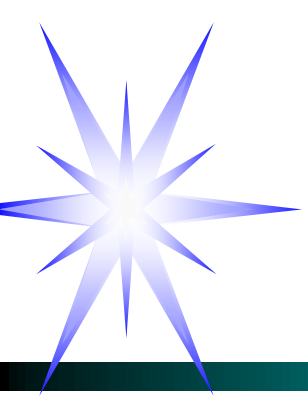

Source Conversion

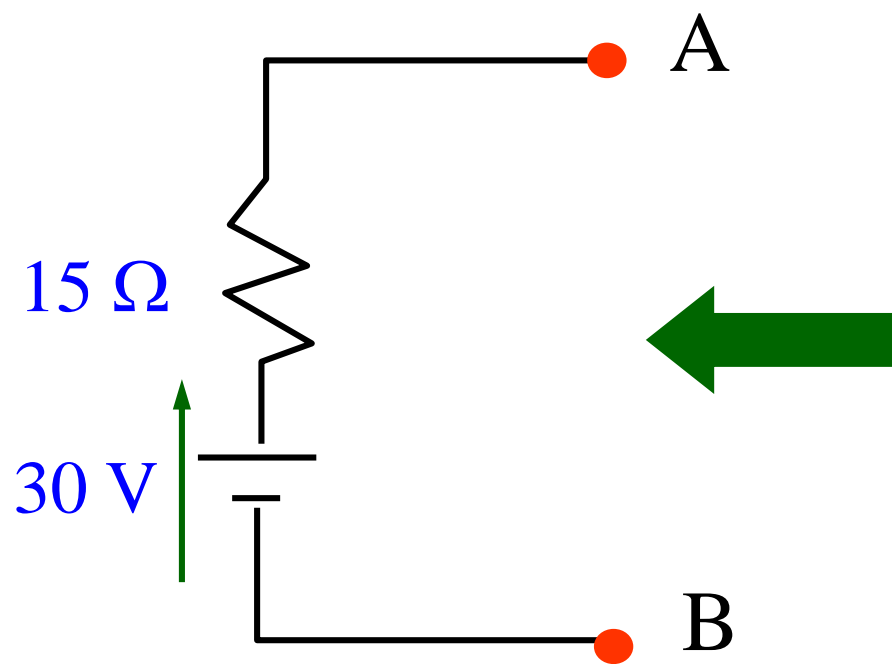

Voltage source

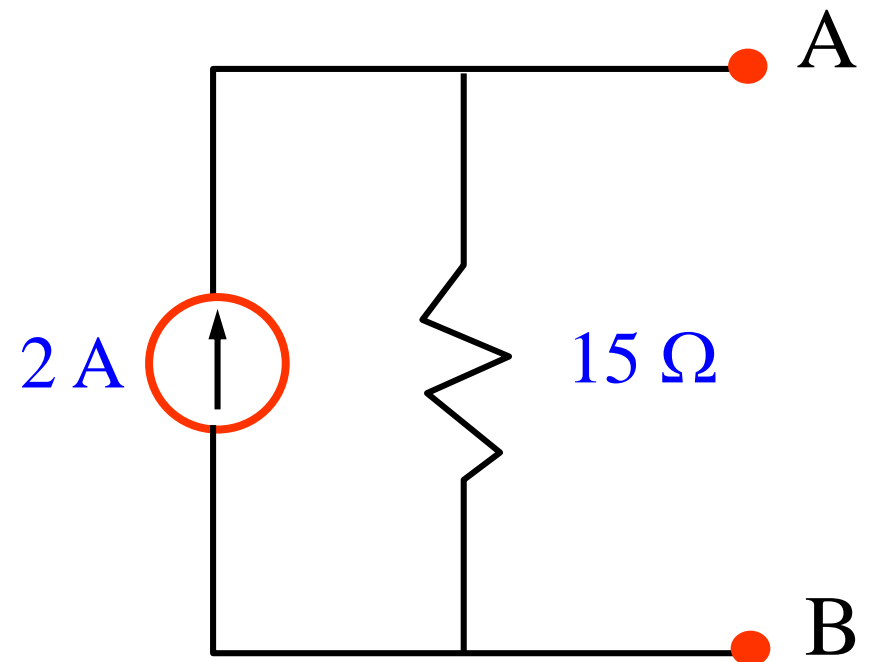


Current source

$$E = 2 \times 15 = 30 \text{ V}$$




Source Conversion

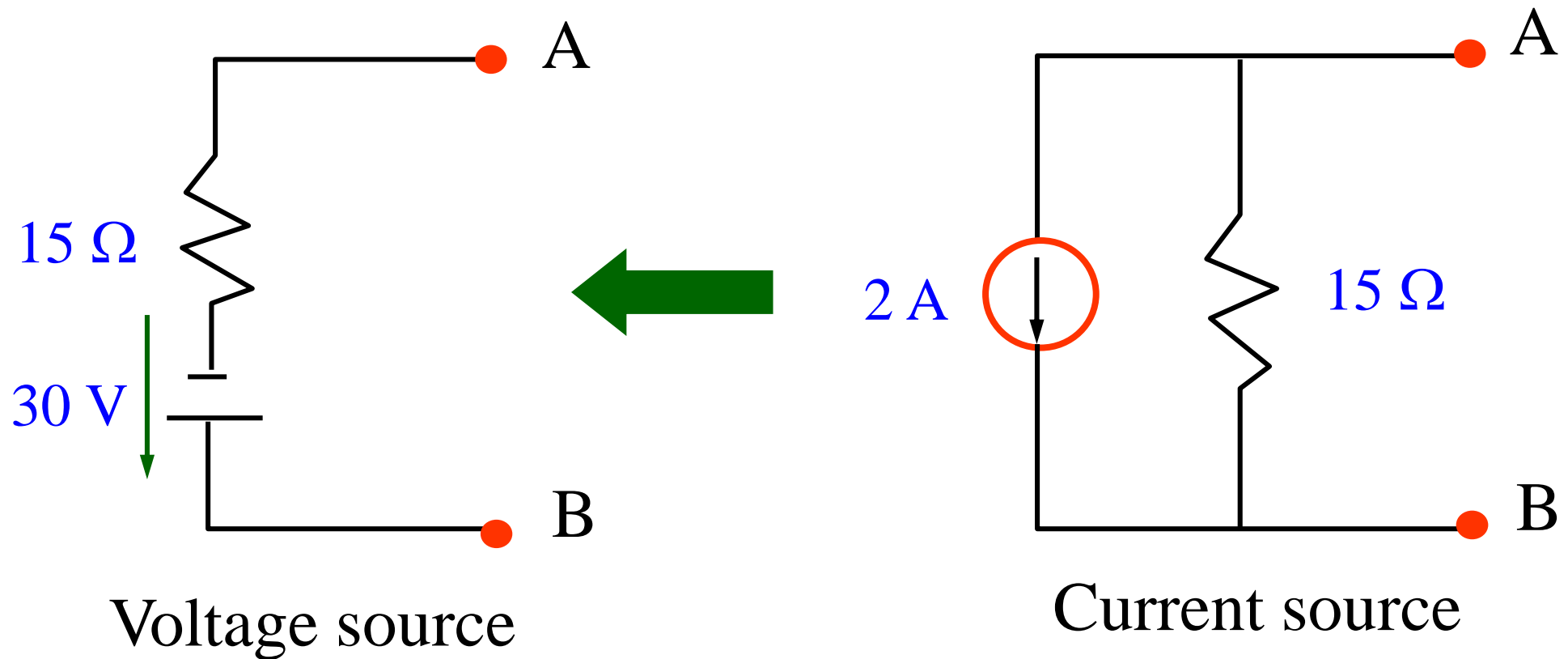

$$E = 2 \times 15 = 30 \text{ V}$$



Tutorial 1, Question 1

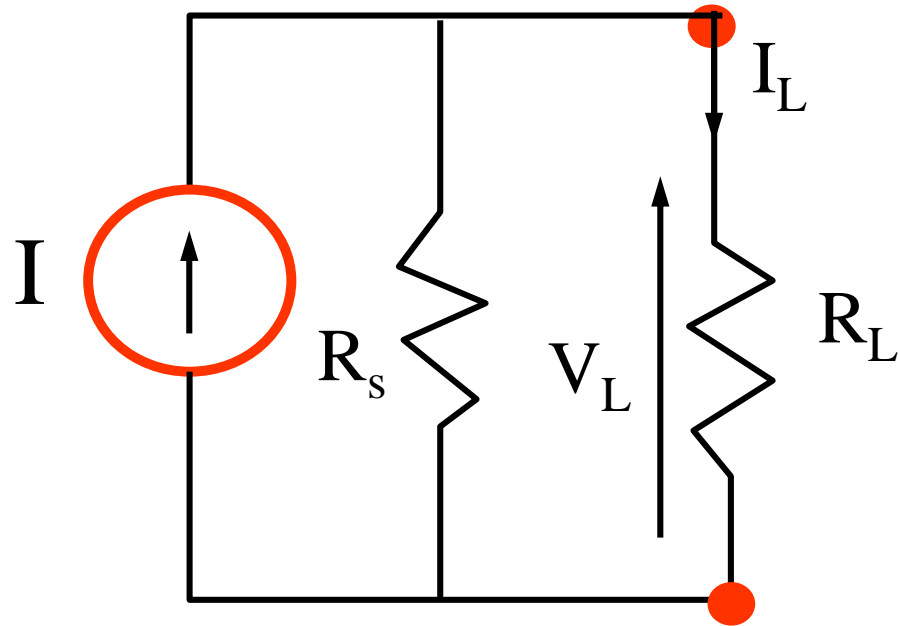

Constant current source


$$I = 12 \text{ A}, R_s = 2 \, \Omega \text{ and } R_L = 6 \, \Omega$$

$$I_L = 12 \times [2 / (2+6)] = 3 \text{ A and}$$

$$V_L = 3 \times 6 = 18 \text{ V}$$




Tutorial 1, Question 1

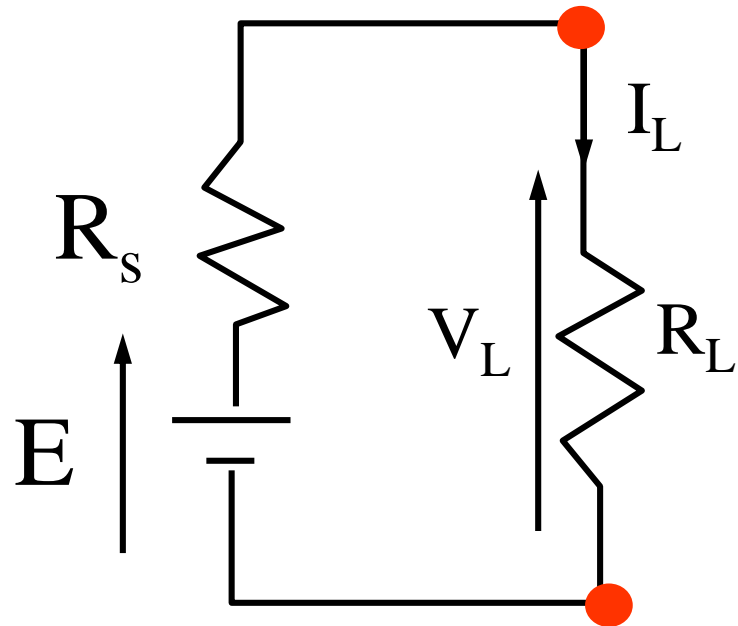


Constant voltage
source
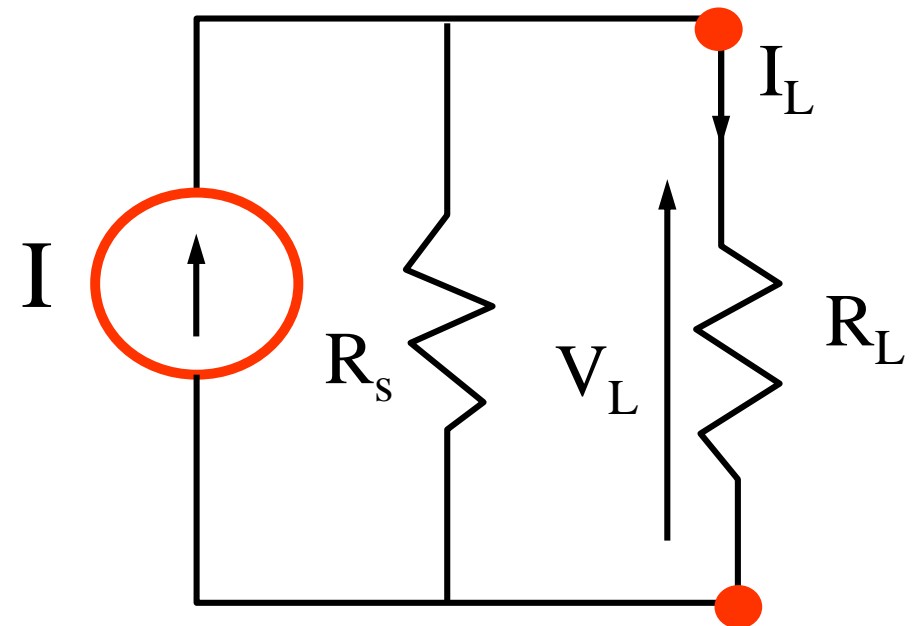
$$E = I \times R_s = 12 \times 2 = 24 \text{ V}$$




Constant current
source
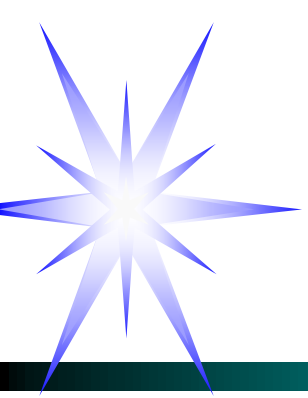
$$I = 12 \text{ A}, R_s = 2 \Omega \text{ and } R_L = 6 \Omega$$




Tutorial 1, Question 1

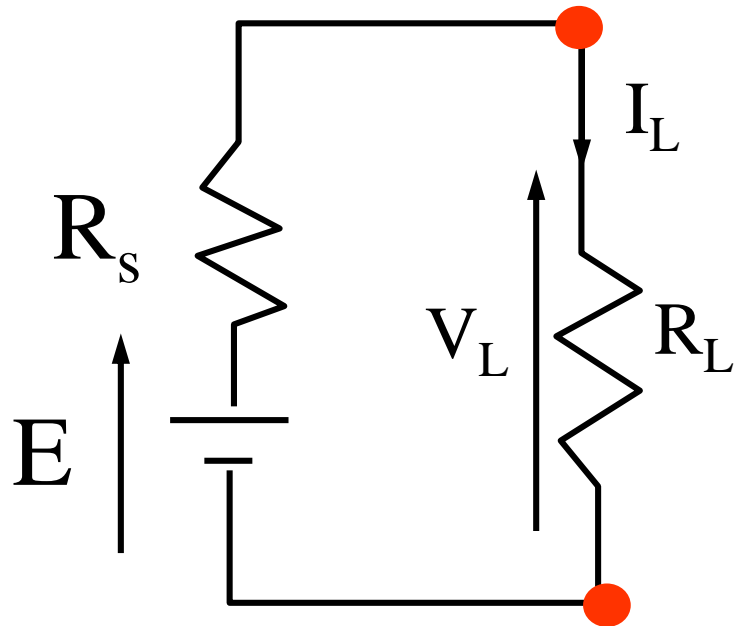


Constant voltage
source
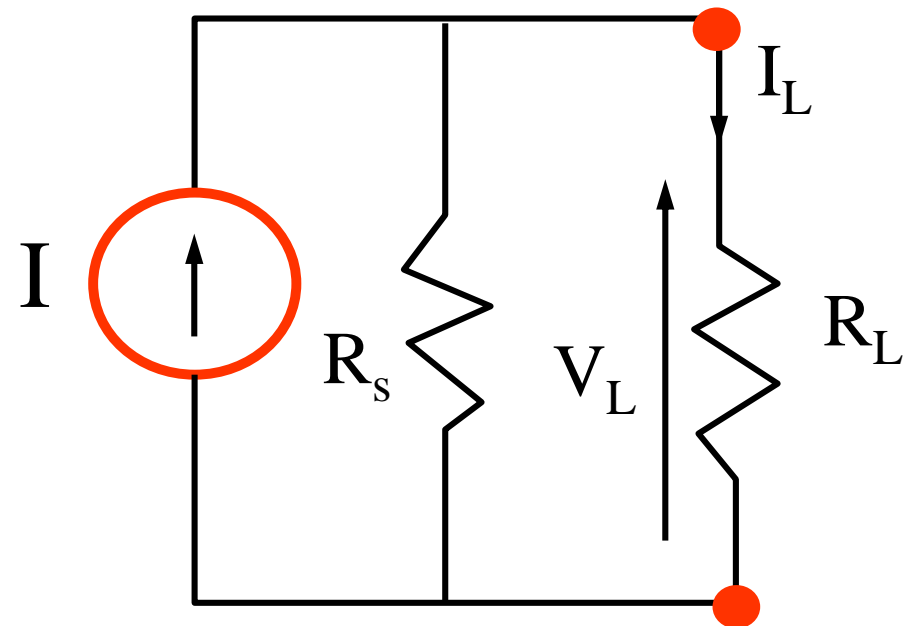
$$E = I \times R_s = 12 \times 2 = 24 \text{ V}$$
$$I_L = 24 / (2 + 6) = 3 \text{ A and}$$
$$V_L = 3 \times 6 = 18 \text{ V}$$





Constant current
source
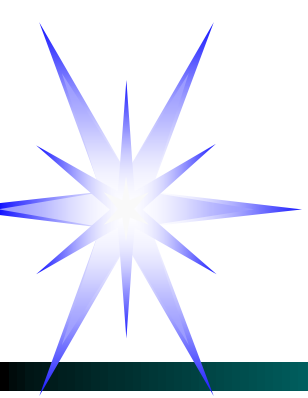
$$I = 12 \text{ A, } R_s = 2 \Omega \text{ and } R_L = 6 \Omega$$
$$I_L = 12 \times 2 / (2 + 6) = 3 \text{ A and}$$
$$V_L = 3 \times 6 = 18 \text{ V}$$




Voltage sources in series

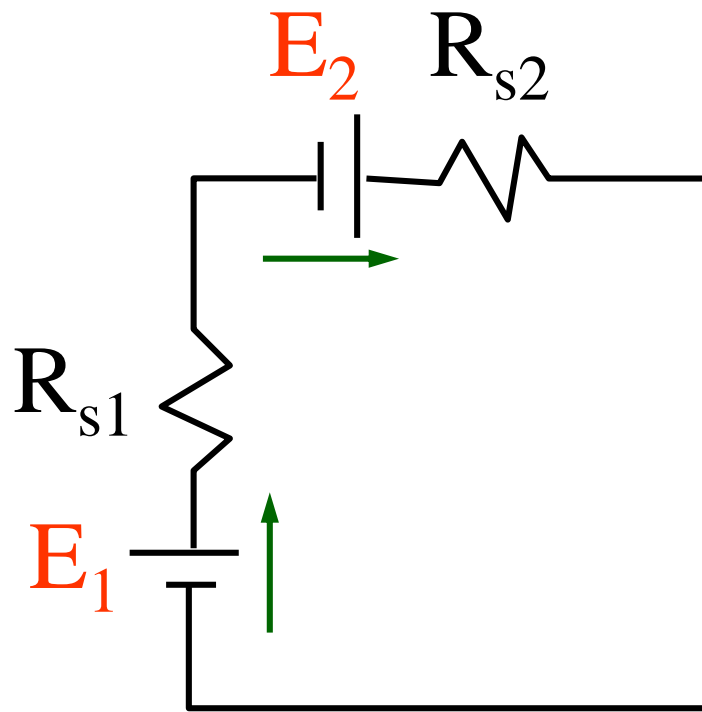

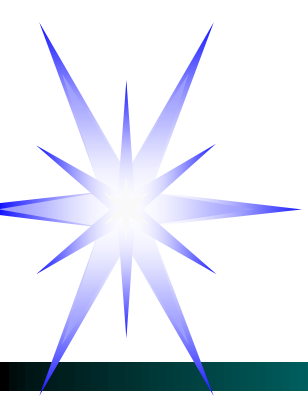


Voltage sources in series

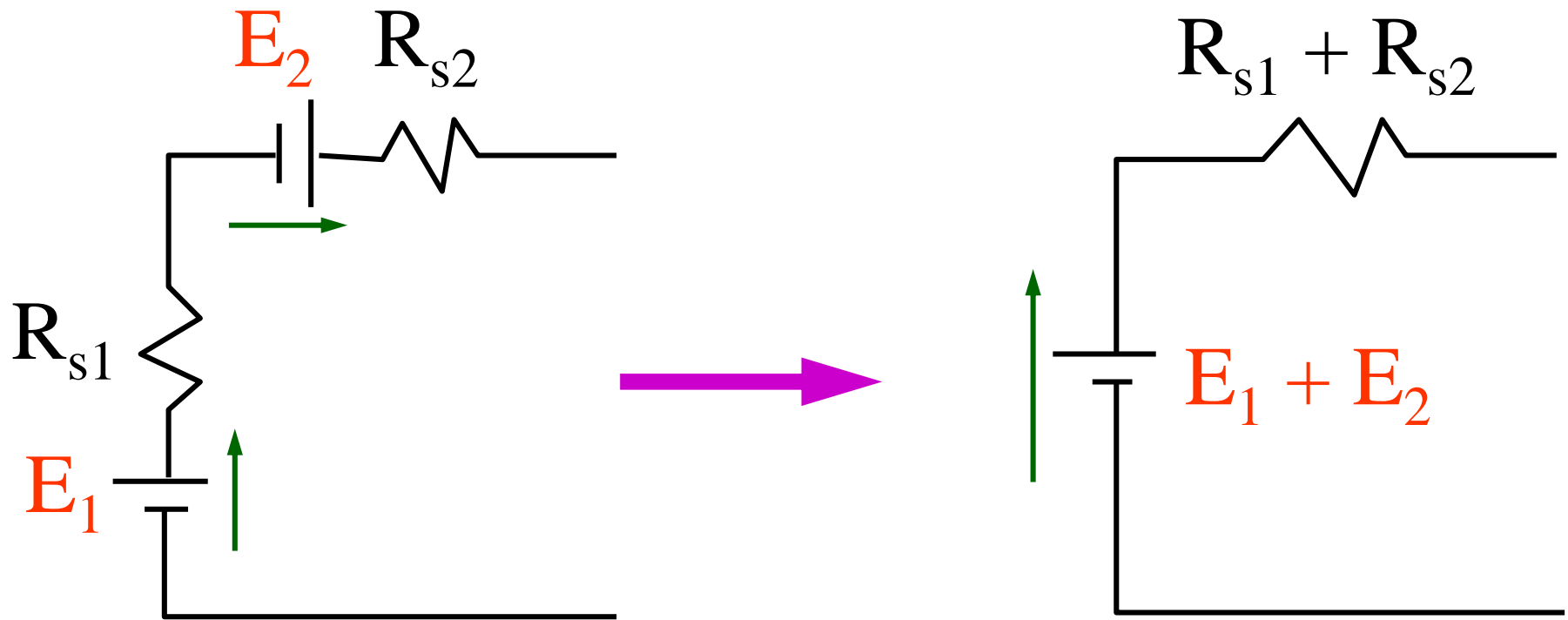


Series-aiding voltage sources




Voltage sources in series

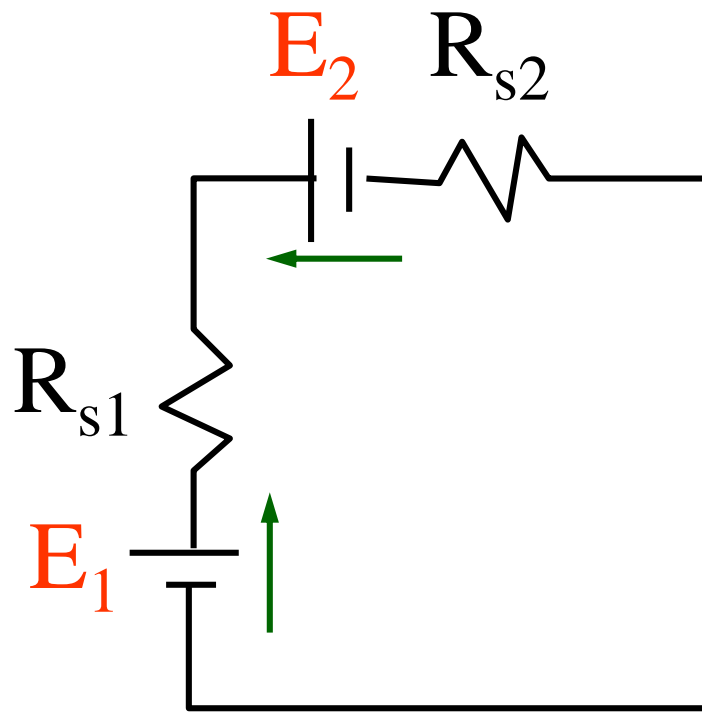

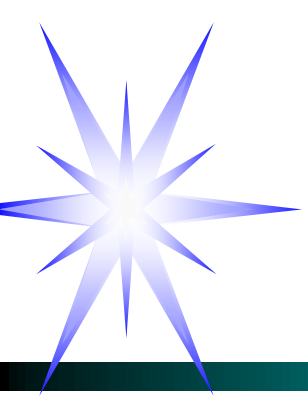

Voltage sources in series

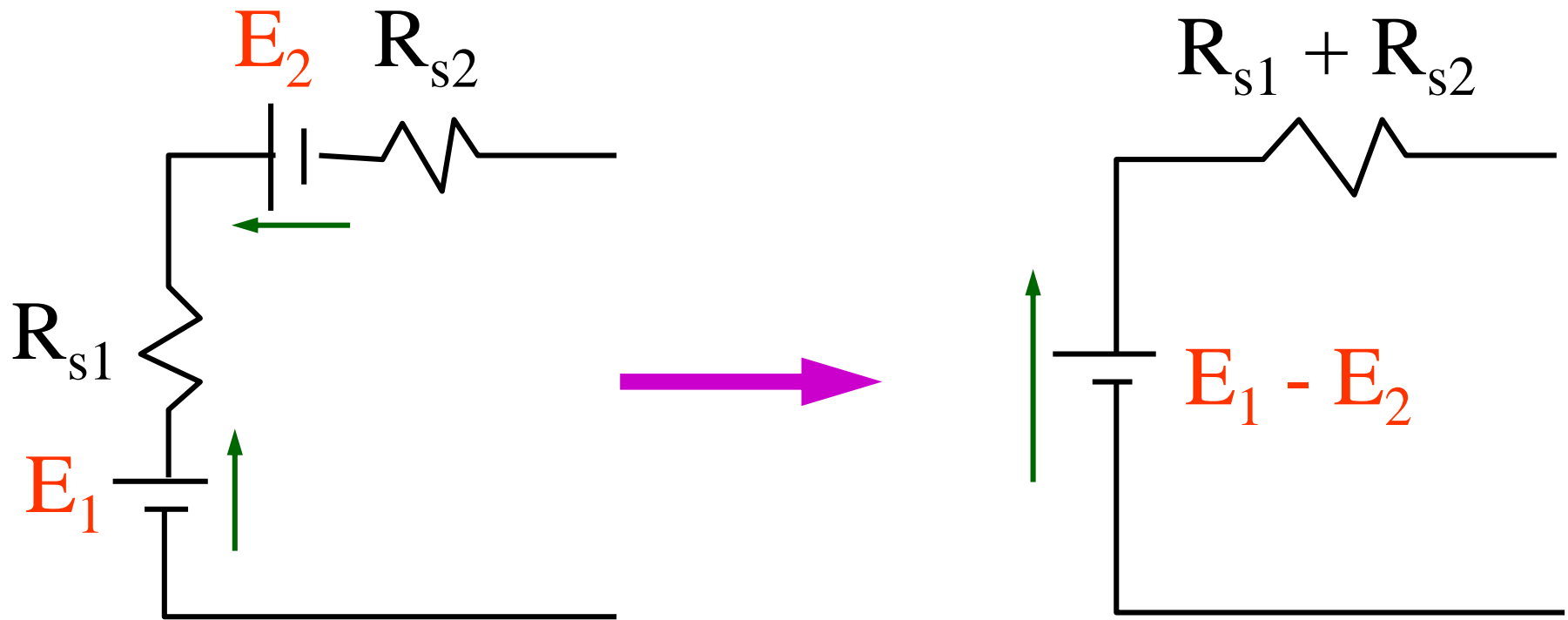


Series-opposing voltage sources



Voltage sources in parallel

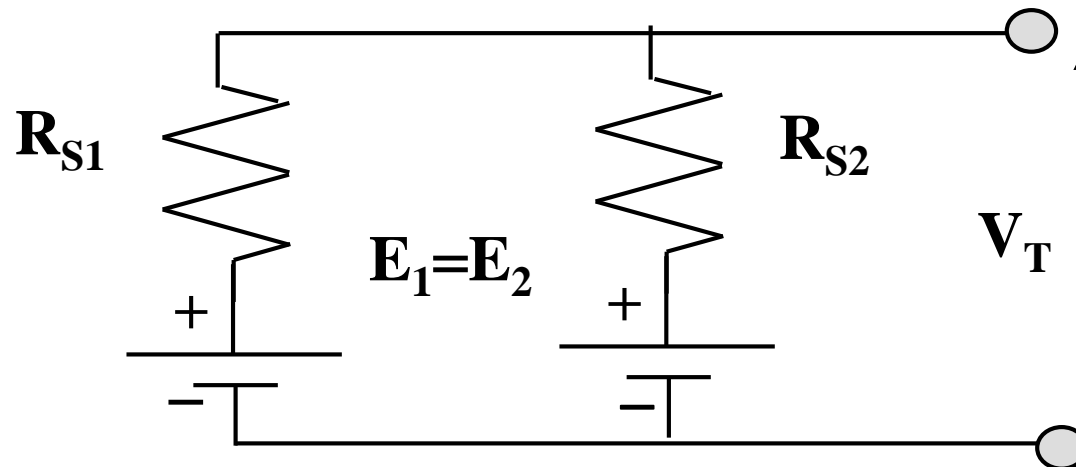- ⌚ Parallel operation of voltage sources with different voltages not possible.
- ⌚ Parallel operation of identical voltage sources for higher output current.






Current sources in series


- ⌚ **Series operation of different current sources are not practical**




Current sources in parallel

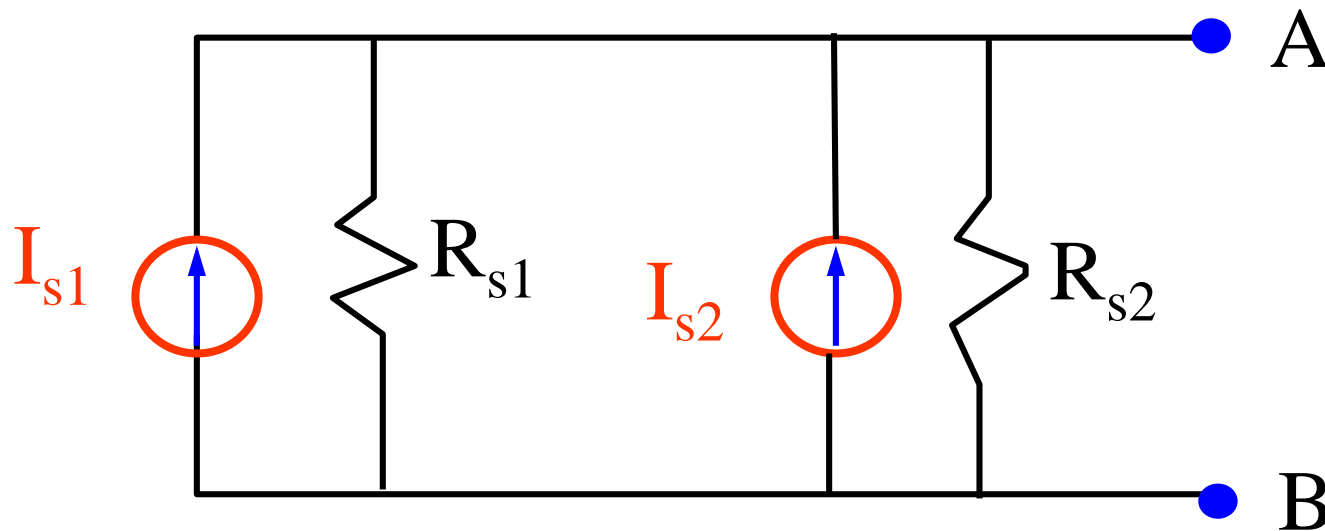


Parallel-aiding
current sources


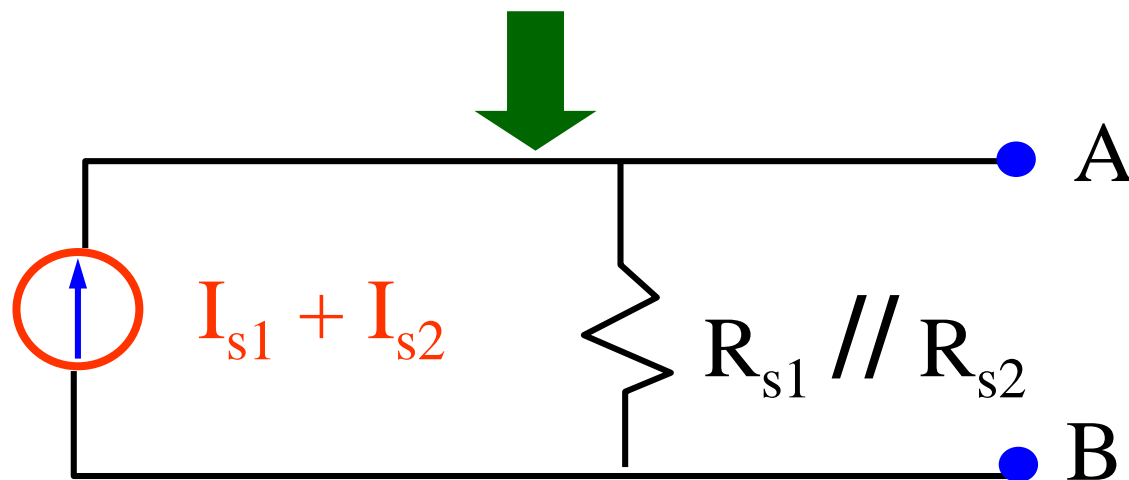


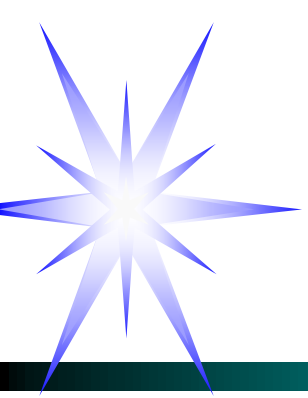

Current sources in parallel

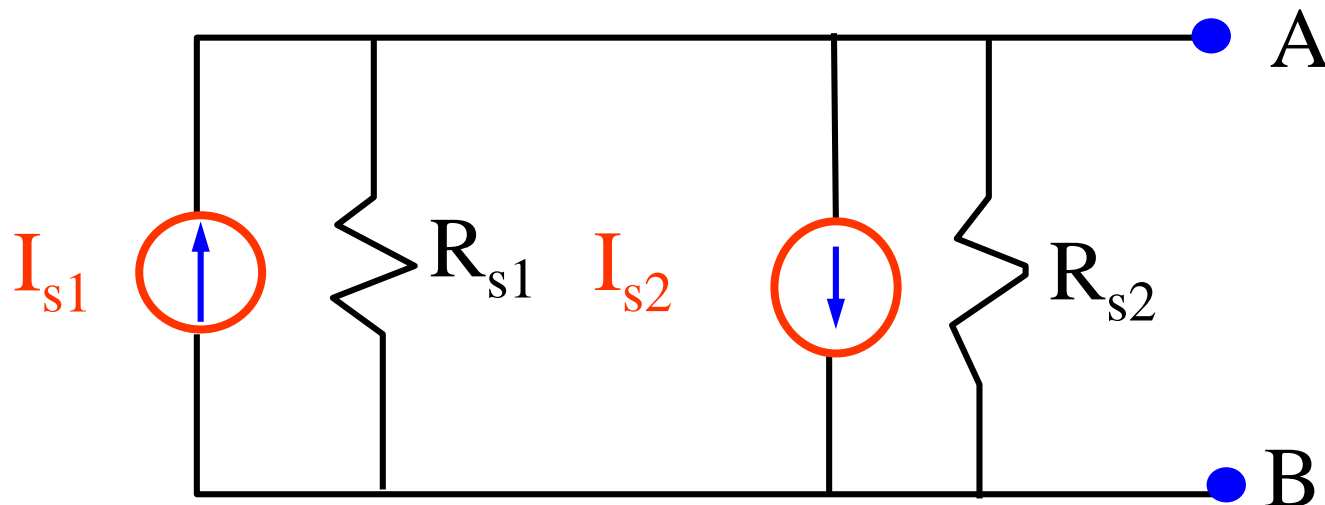

Parallel-opposing
current sources

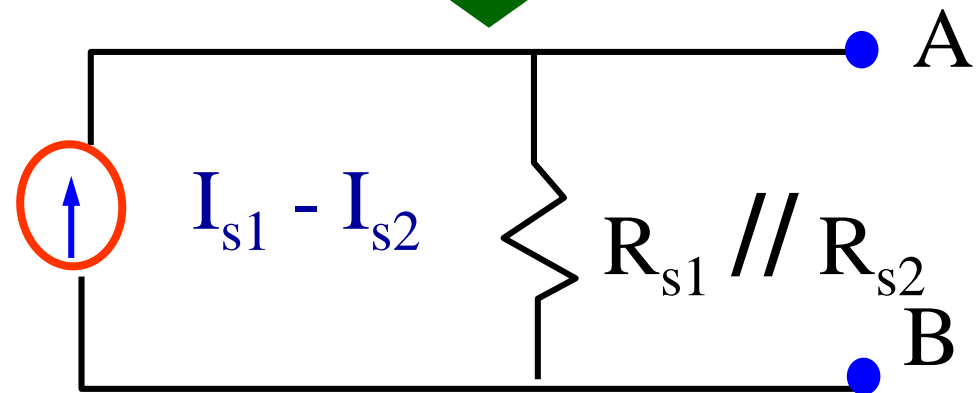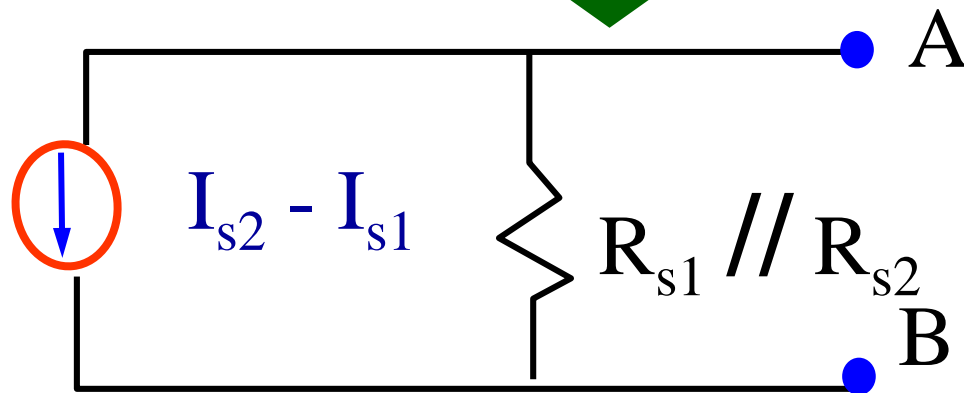



Procedure for finding the equivalent current source or voltage source

- ❖ *When two voltage sources are in parallel or when a voltage source is in parallel with a current source.*
 - ✎ *Always first convert the voltage source to its equivalent current sources with appropriate current direction.*



Procedure for finding the equivalent current source or voltage source

✎ Identify the type of parallel connection as either

▲ Parallel aiding current sources or

▲ Parallel opposing current sources.

✎ Simplify the circuit to find the single equivalent current source with appropriate current direction.



Procedure for finding the equivalent current source or voltage source

- ❖ *When two current sources are in series or when a current source is in series with a voltage source.*
- ✎ *Always first convert the current source to its equivalent voltage sources with appropriate voltage direction.*



Procedure for finding the equivalent current source or voltage source


✎ Identify the type of series connection as either

- ▲ Series aiding voltage sources or*
- ▲ Series opposing voltage sources.*

✎ Simplify the circuit to find the single equivalent voltage source with appropriate voltage direction.




Example 1.2

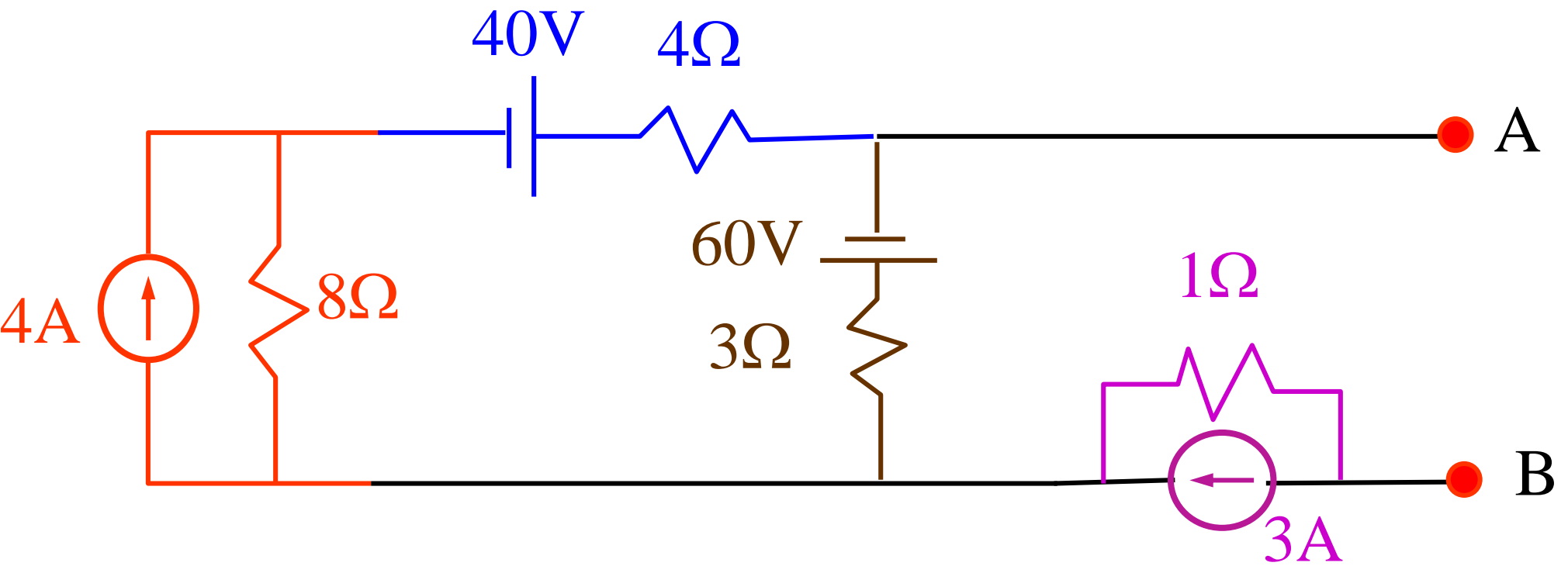

Simplify the above into an equivalent current source




Example 1.2

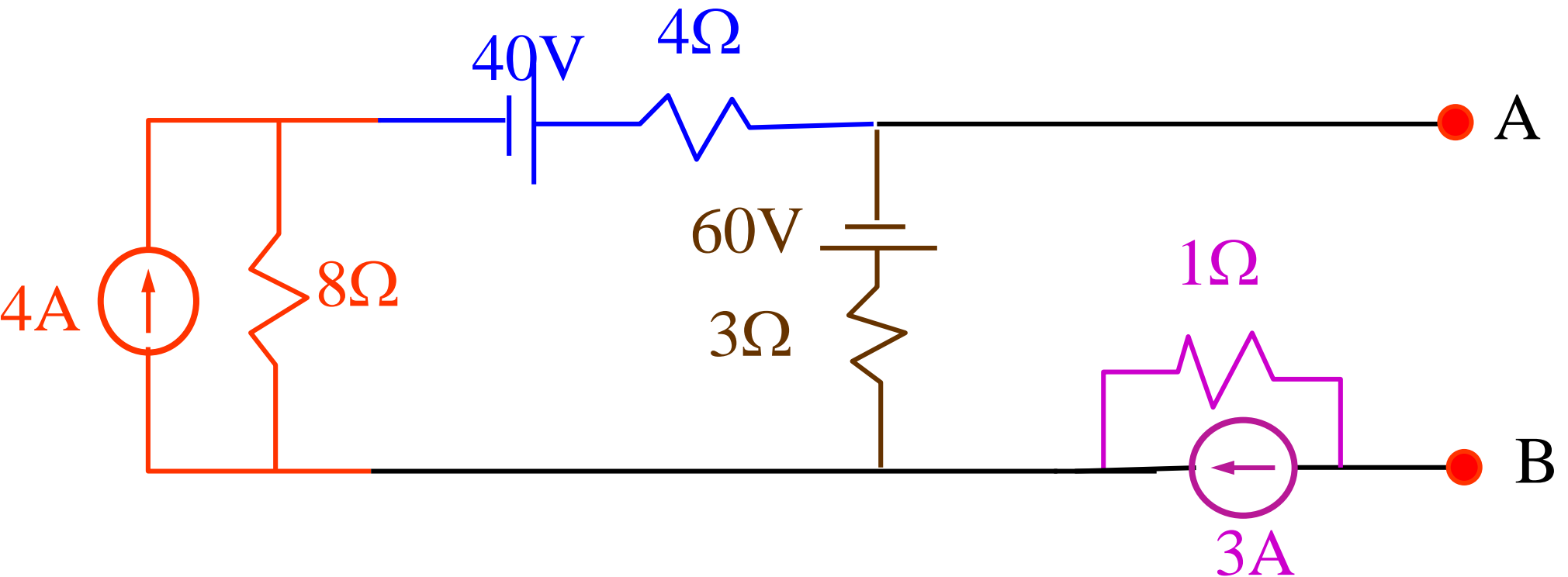


Convert the parallel $4A$, 8Ω into series voltage source of $4 \times 8 = 32$ volts with 8Ω as the series resistor




Example 1.2

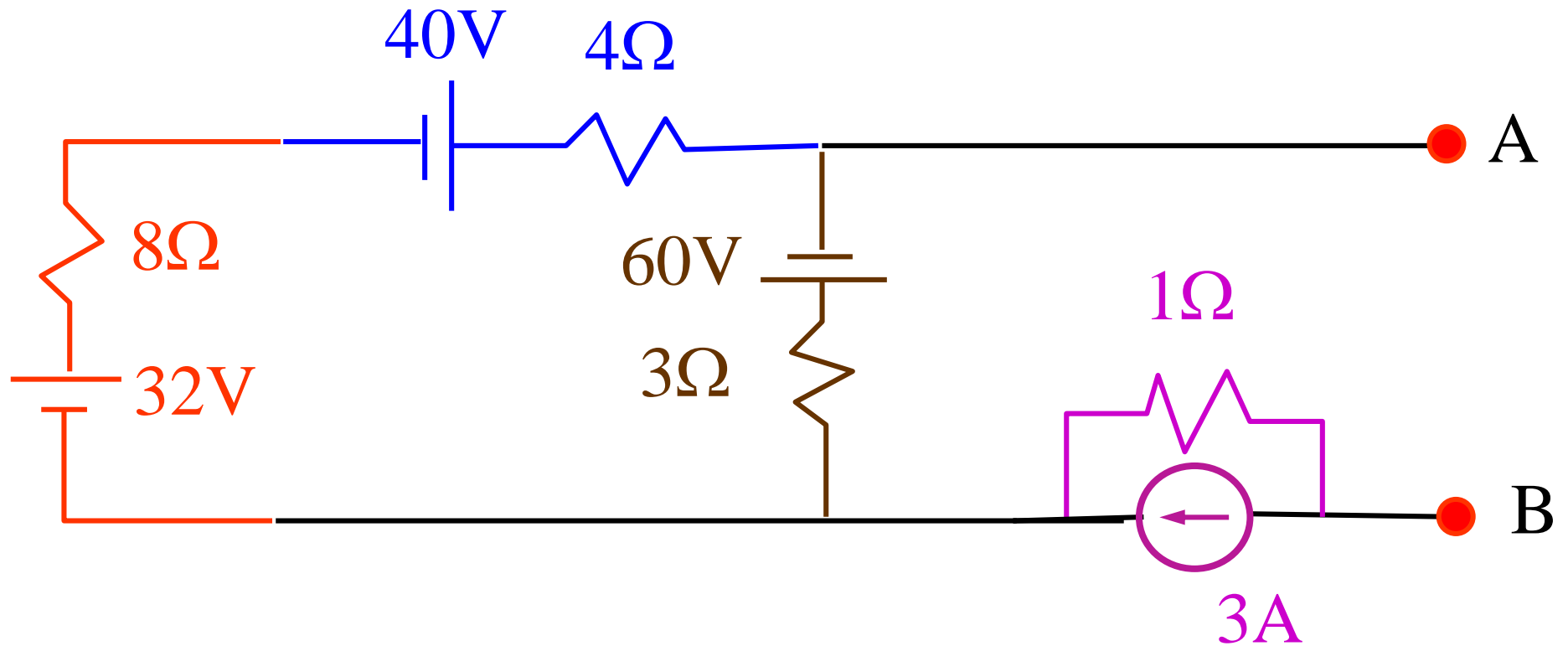


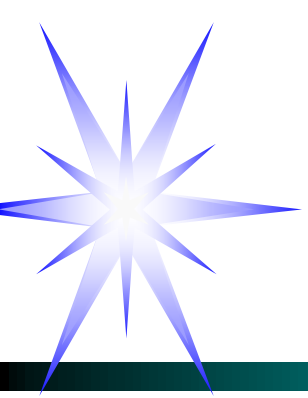


Example 1.2

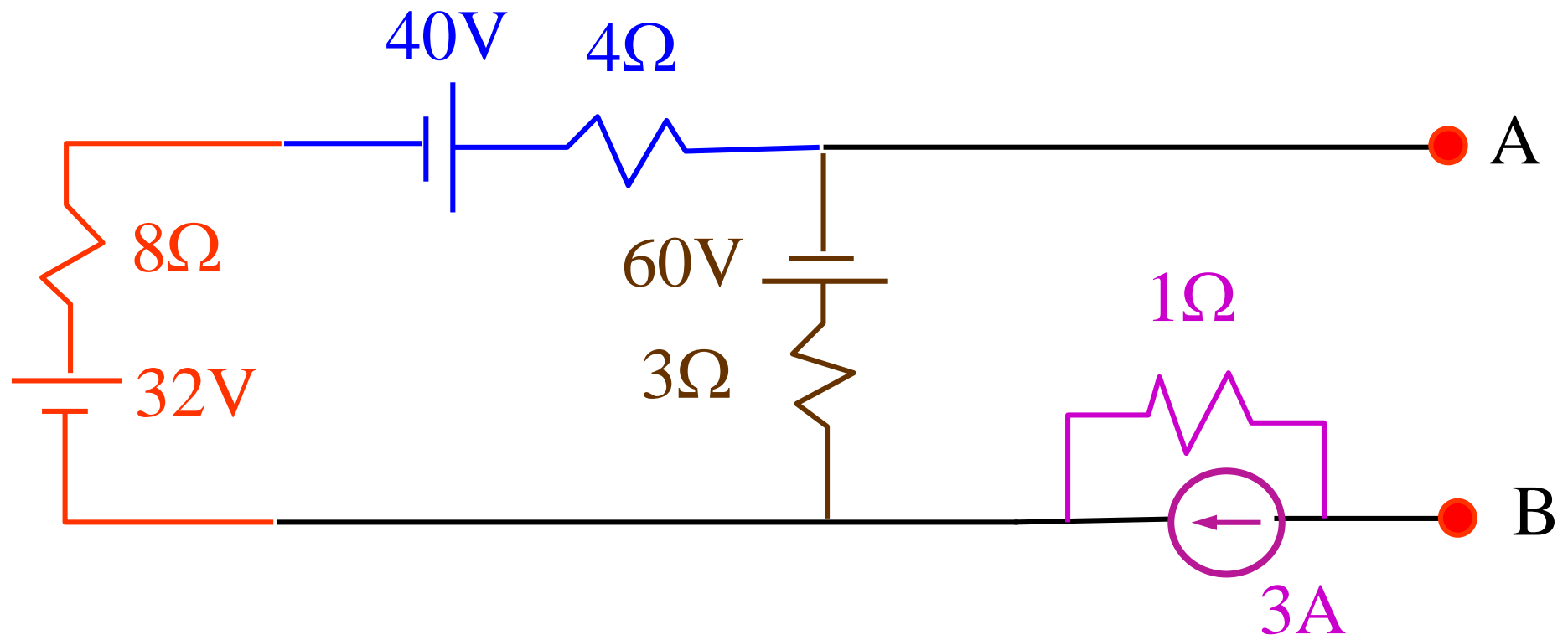


Now combine the 32V and 8Ω with the 40V and 4Ω to form a total of 72V and 12Ω series circuit

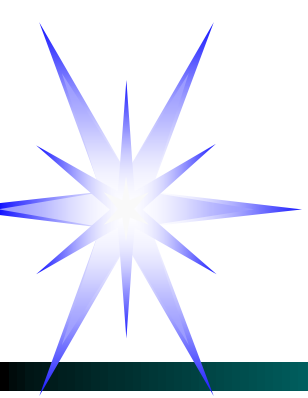


Example 1.2

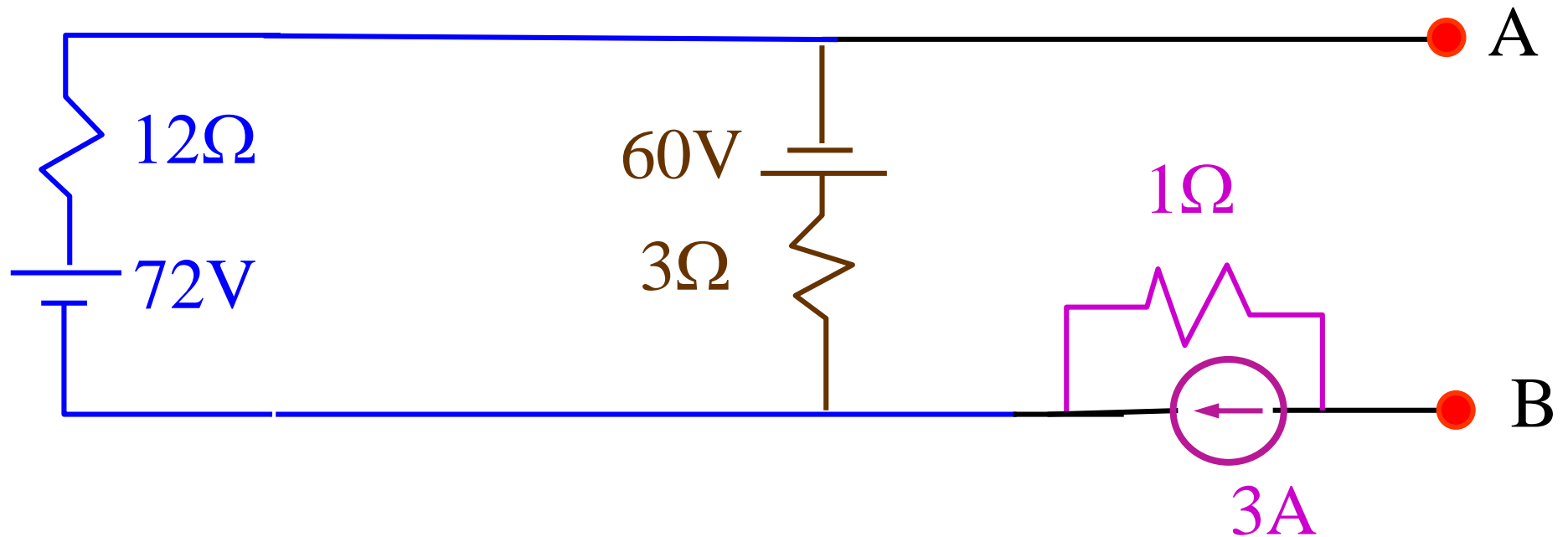

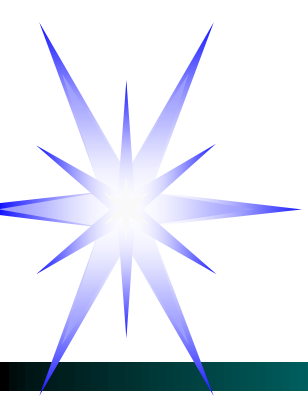


Example 1.2

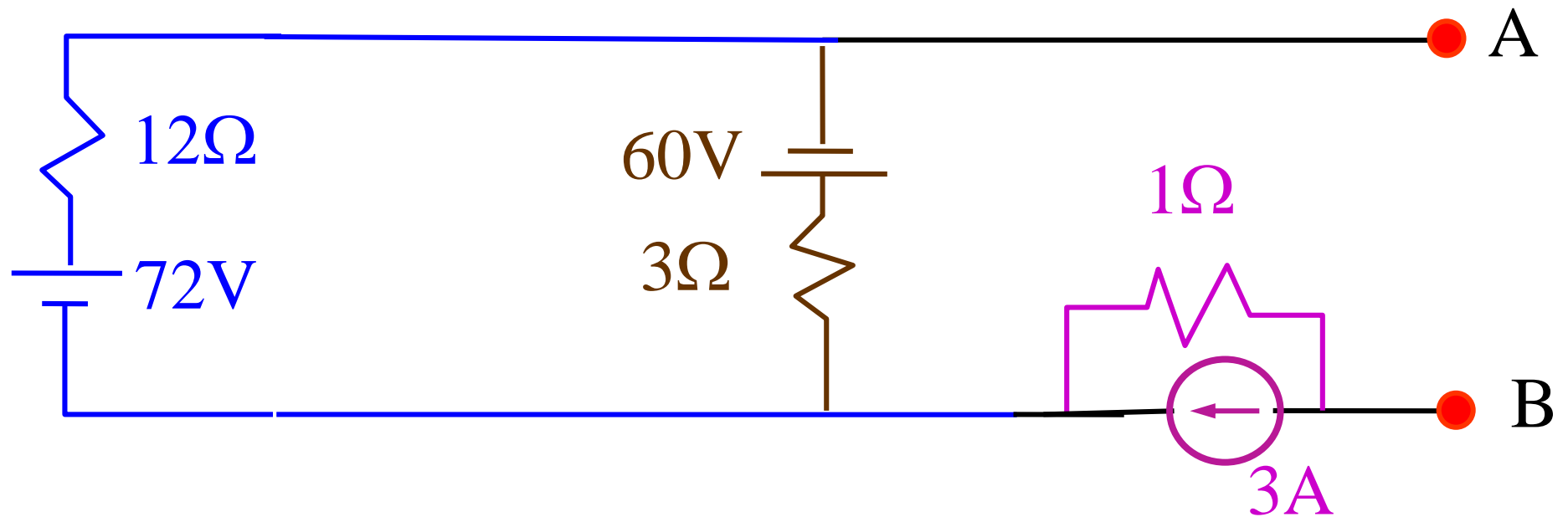


The 72V , 12Ω and 60V , 3Ω must both be converted into current sources before they can be combined




Example 1.2

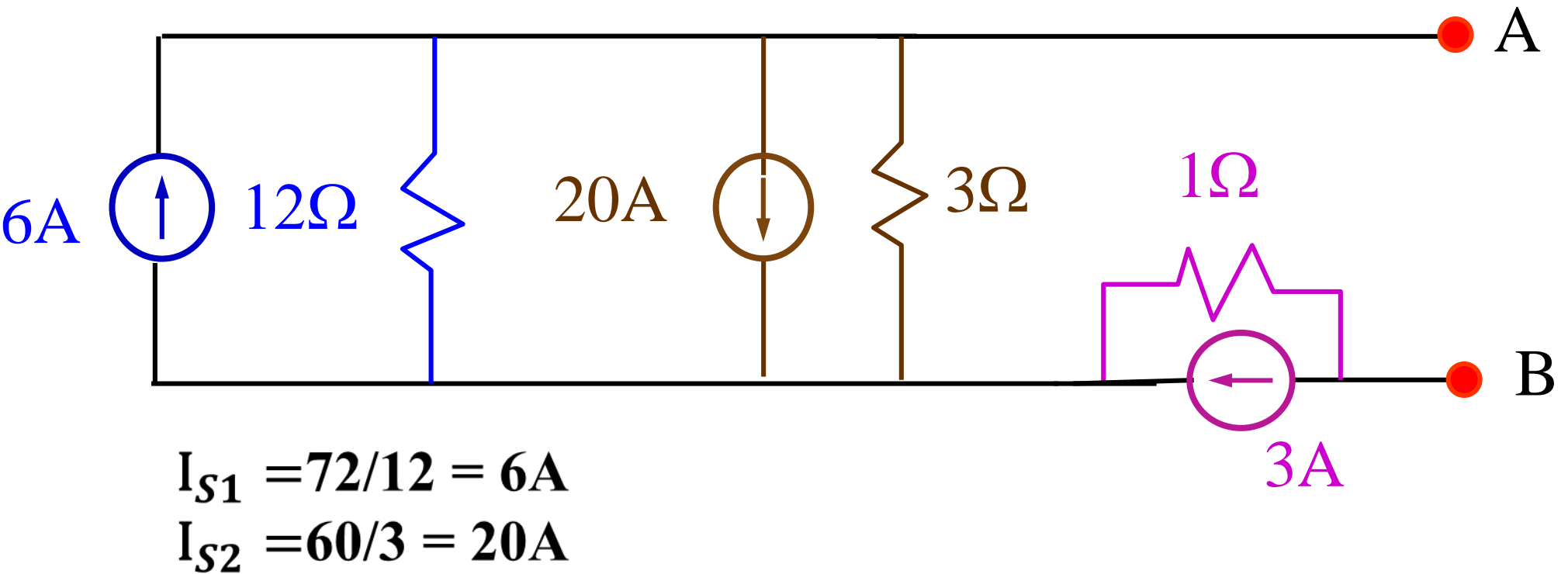

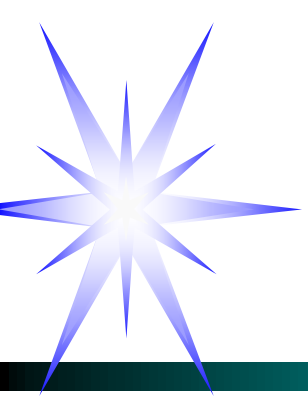


Example 1.2

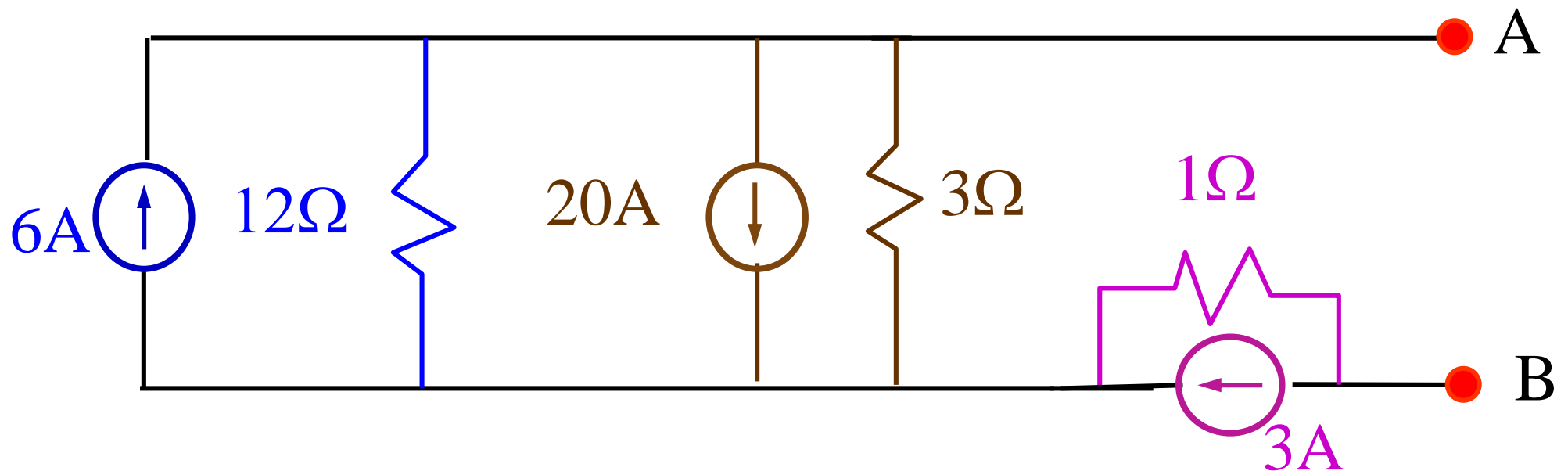

Now combine the $6A$, 12Ω with the $20A$, 3Ω into one single current source with a parallel resistor equals to $12//3 = 2.4\Omega$




Example 1.2

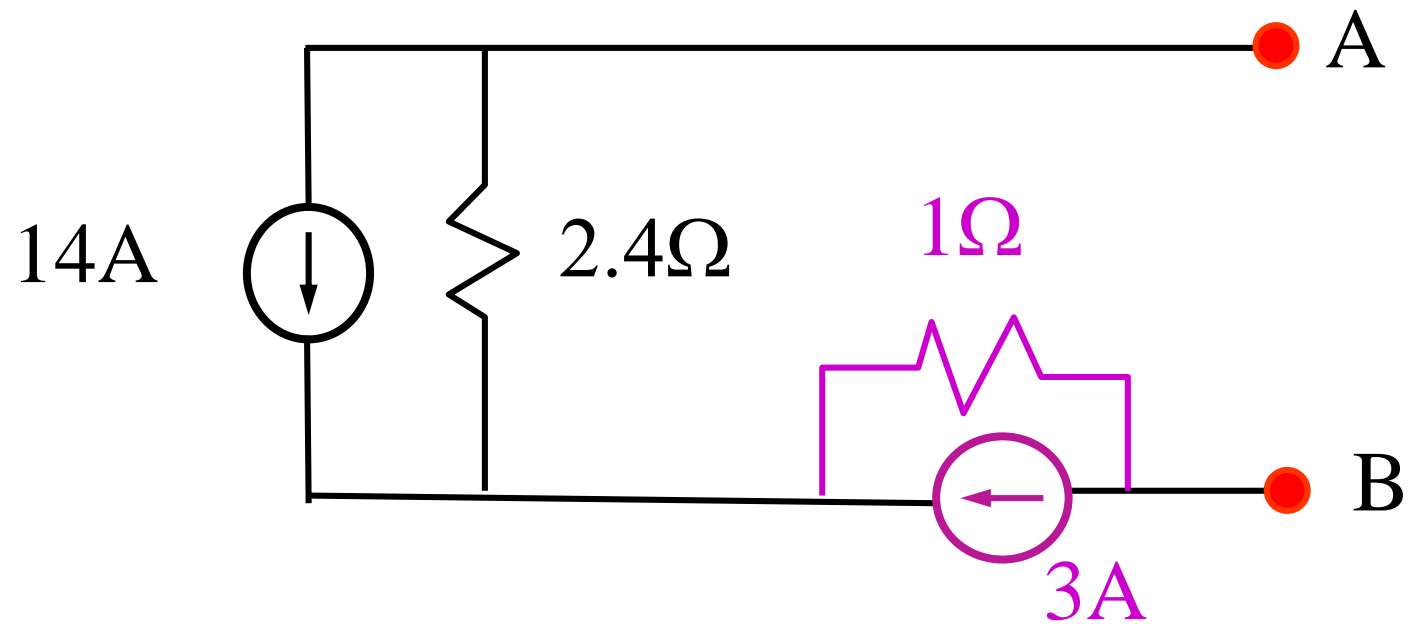




Example 1.2

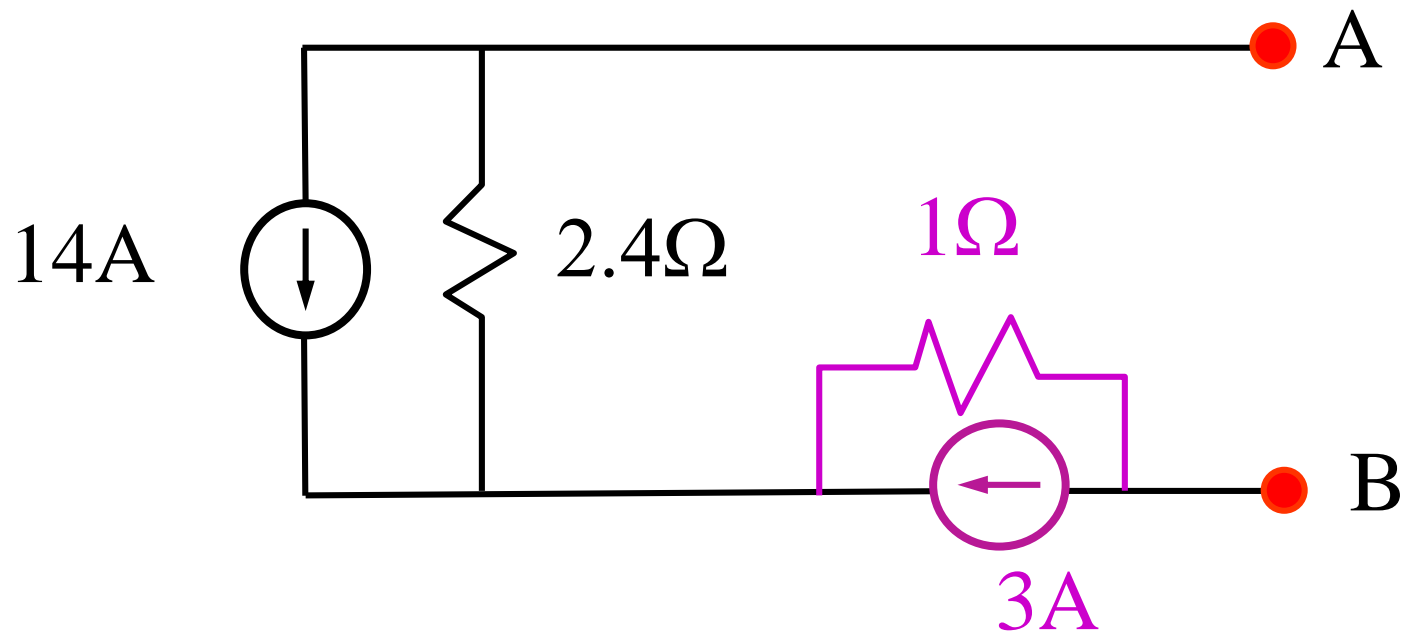


To combine these two current sources, both must first be converted into voltage sources.




Example 1.2

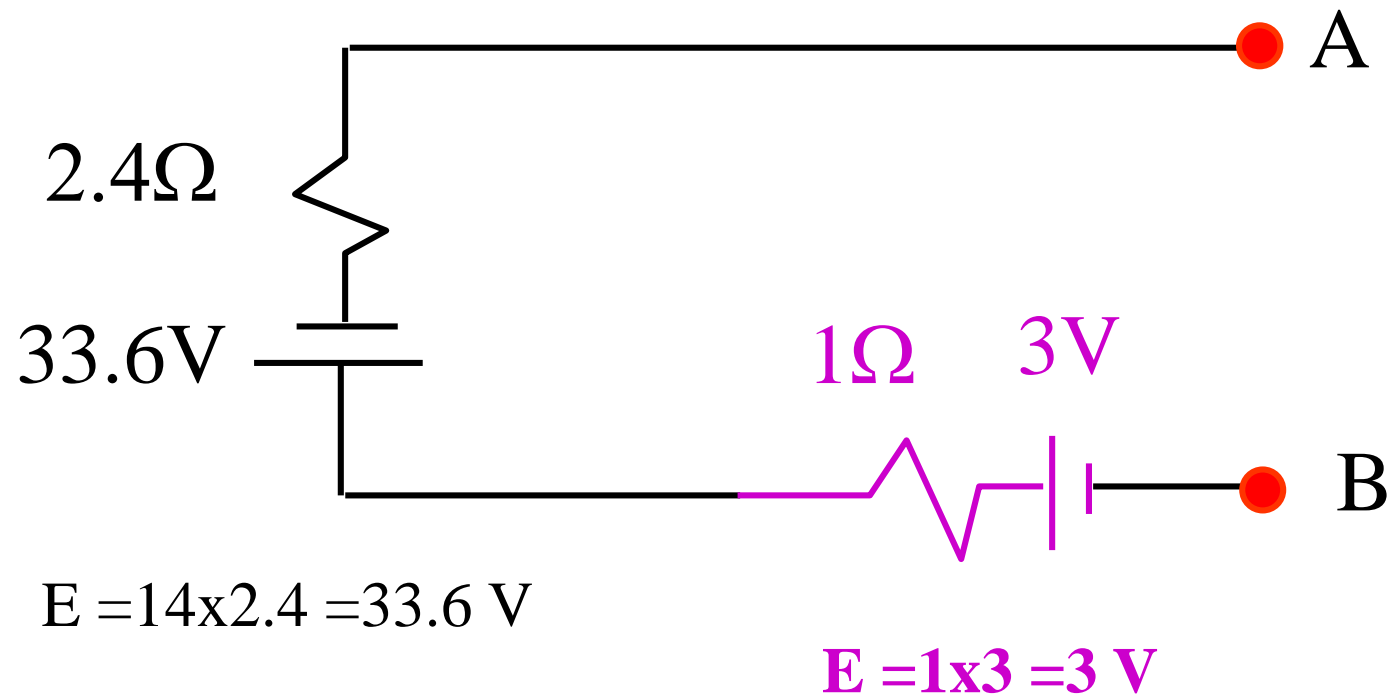


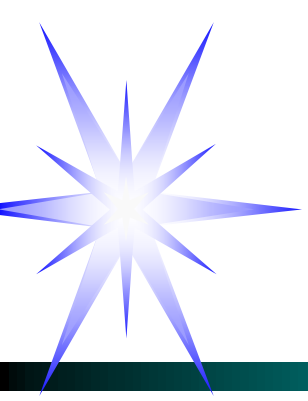


Example 1.2

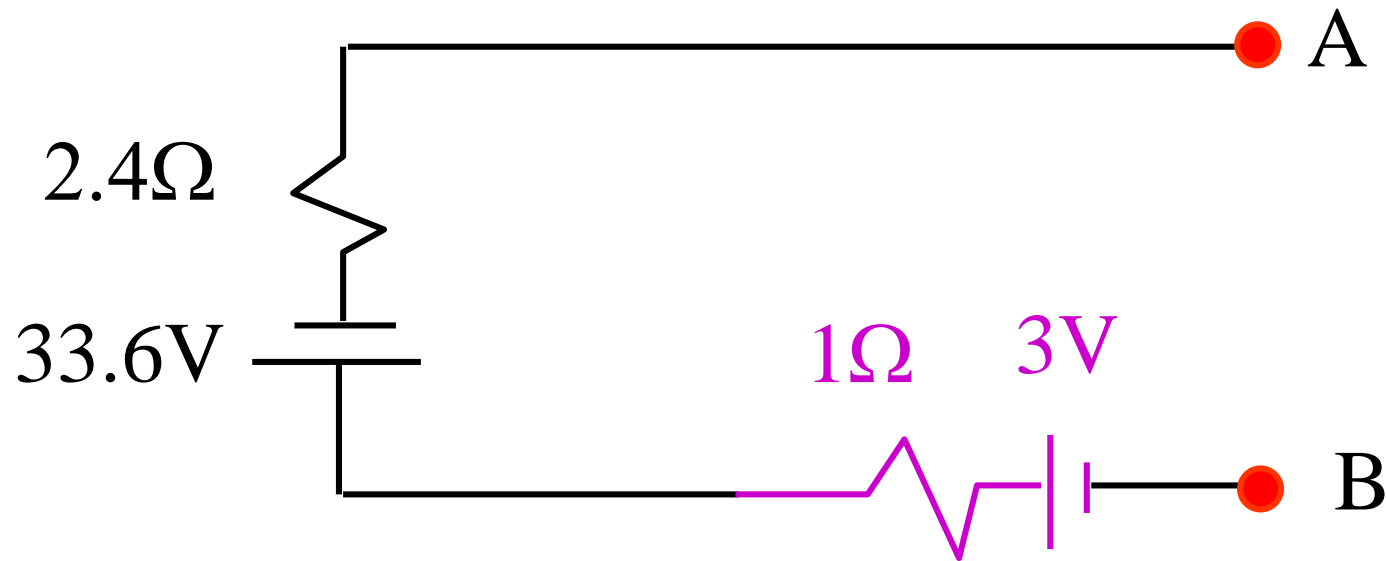


Now these two voltage sources can be combined to form a voltage source of 30.6 V & $3.4\ \Omega$

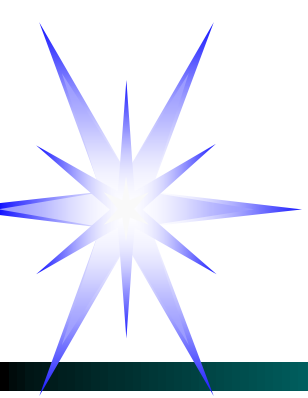


Example 1.2

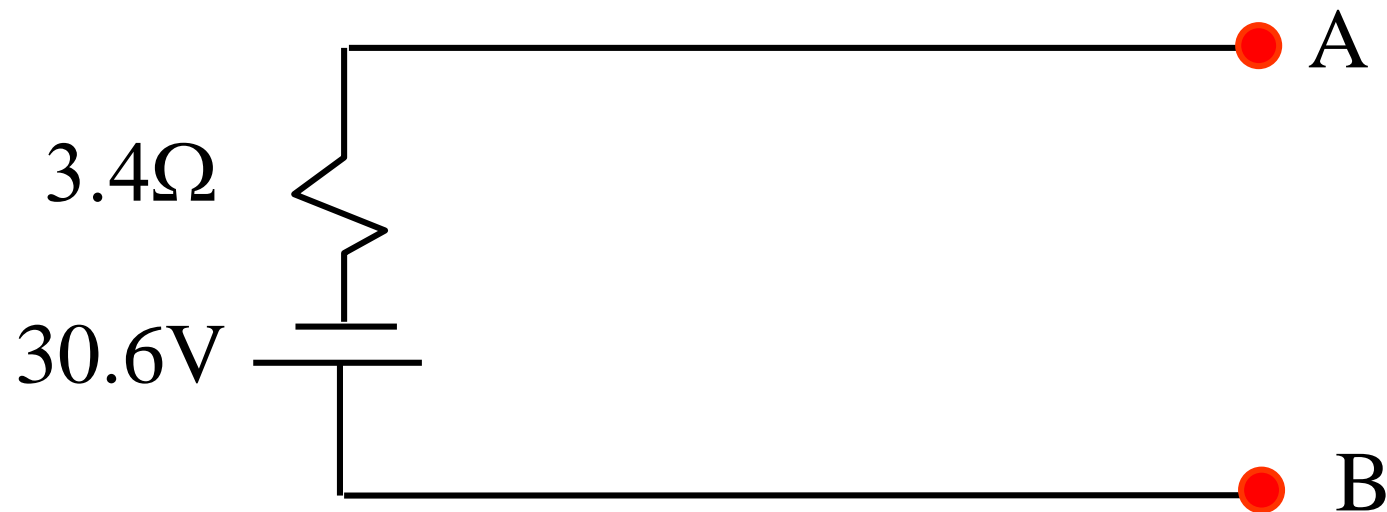

This can be the answer if an equivalent voltage source is required.

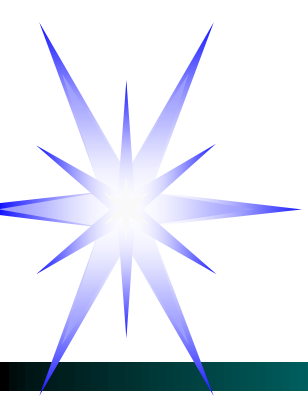

Example 1.2

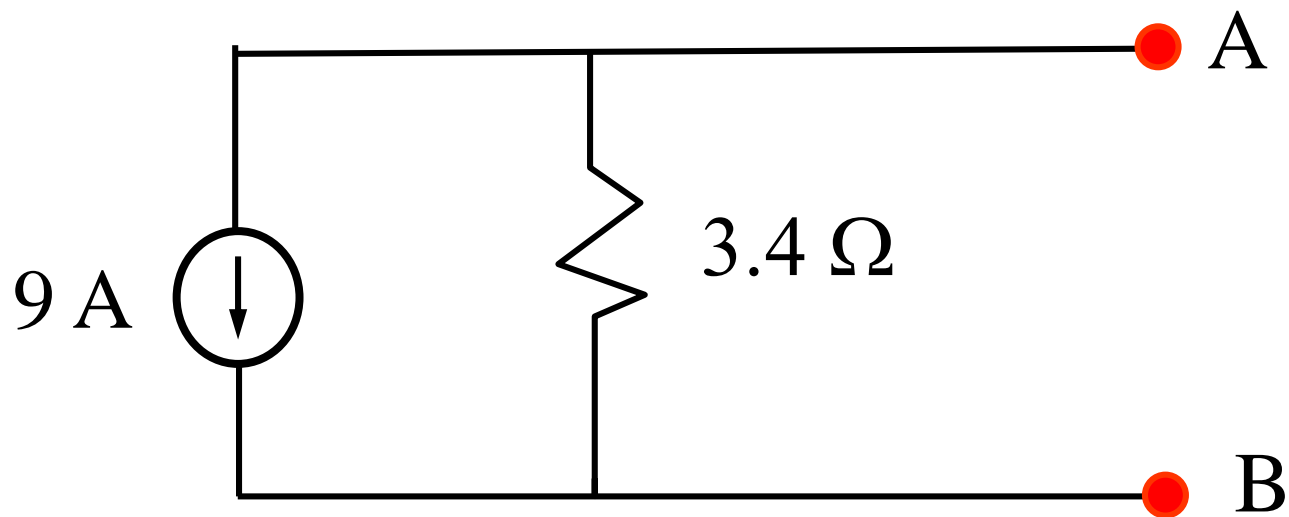

This is the final required equivalent current source

...next topic

Mesh/Loop Analysis

Nurturing Curious Minds, Producing Passionate Engineers

Lee M L

Office: T12A522

School of EEE

Tel: 6879-0657