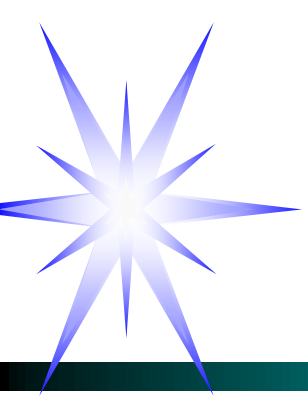




# Circuit Theory & Analysis

---

## **NODAL ANALYSIS**



# Objectives

- ❖ Analyse a given circuit using nodal analysis method.
- ❖ Write nodal equations by inspection and solve for the unknown loop voltages using Cramer's rule.



# Nodal Analysis

---


Nodal Analysis has a lot in common with the Mesh Analysis.

Mesh Analysis - is to replace KVL

Nodal Analysis - is to replace KCL




# Nodal Analysis

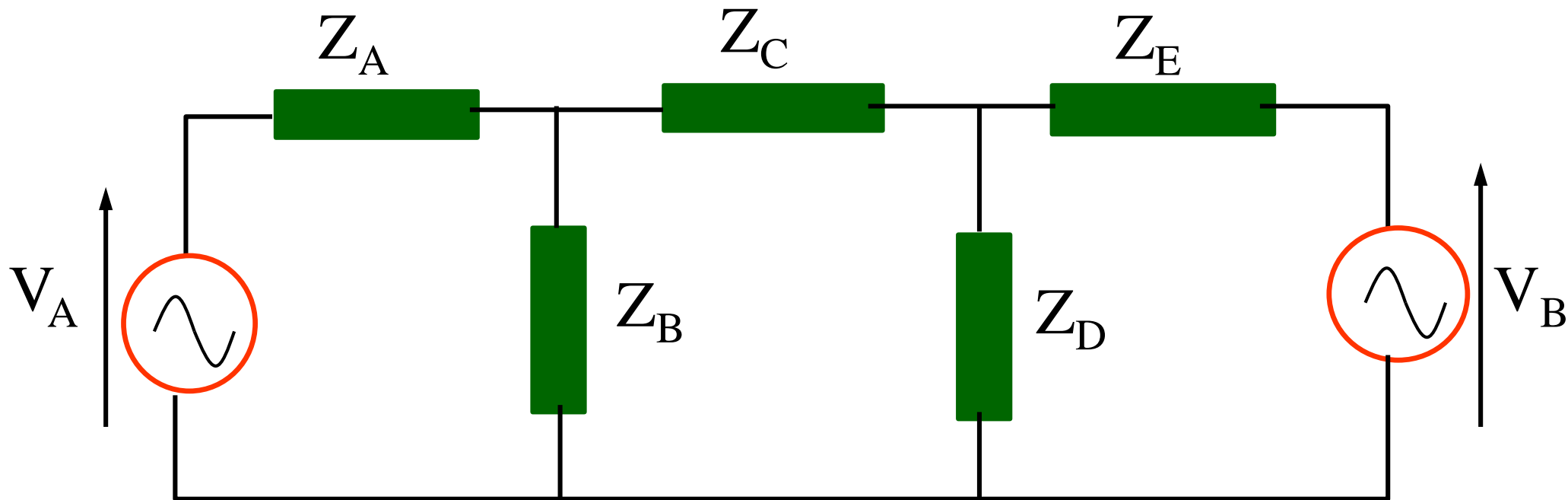


Given a circuit, first determine the number of nodes, hence determine the number of independent equations by KCL.




# Nodal Analysis

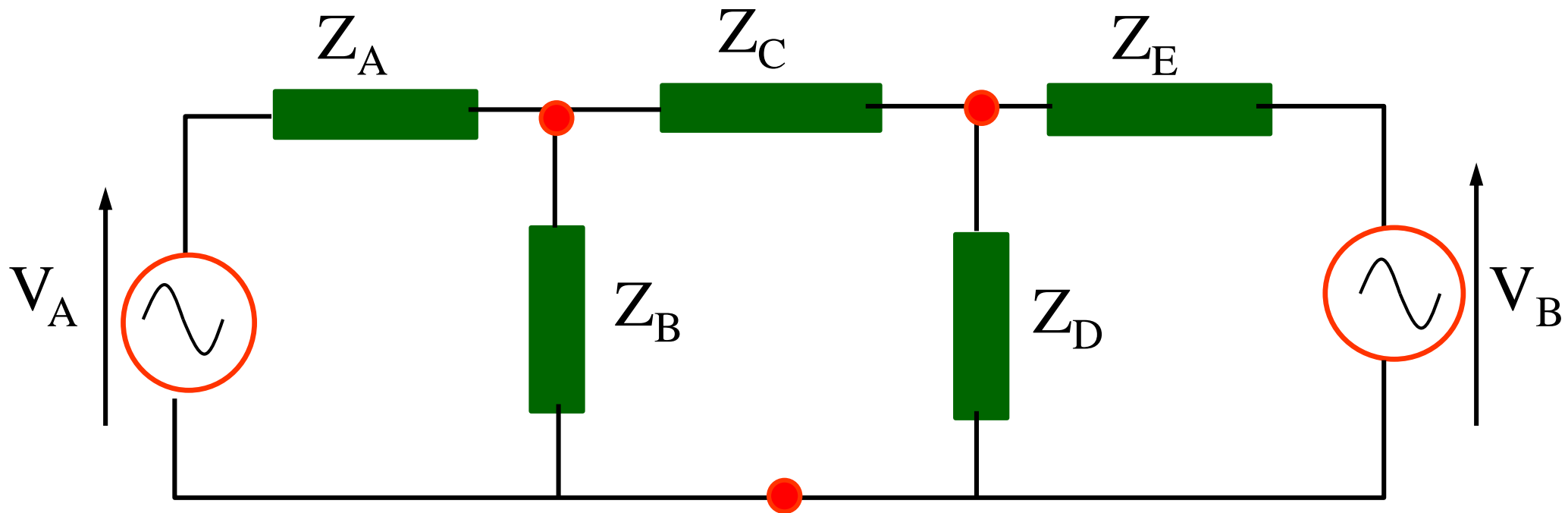

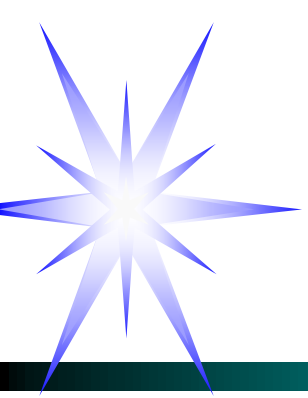
Nodes are junctions of branches in a circuit.




# Nodal Analysis

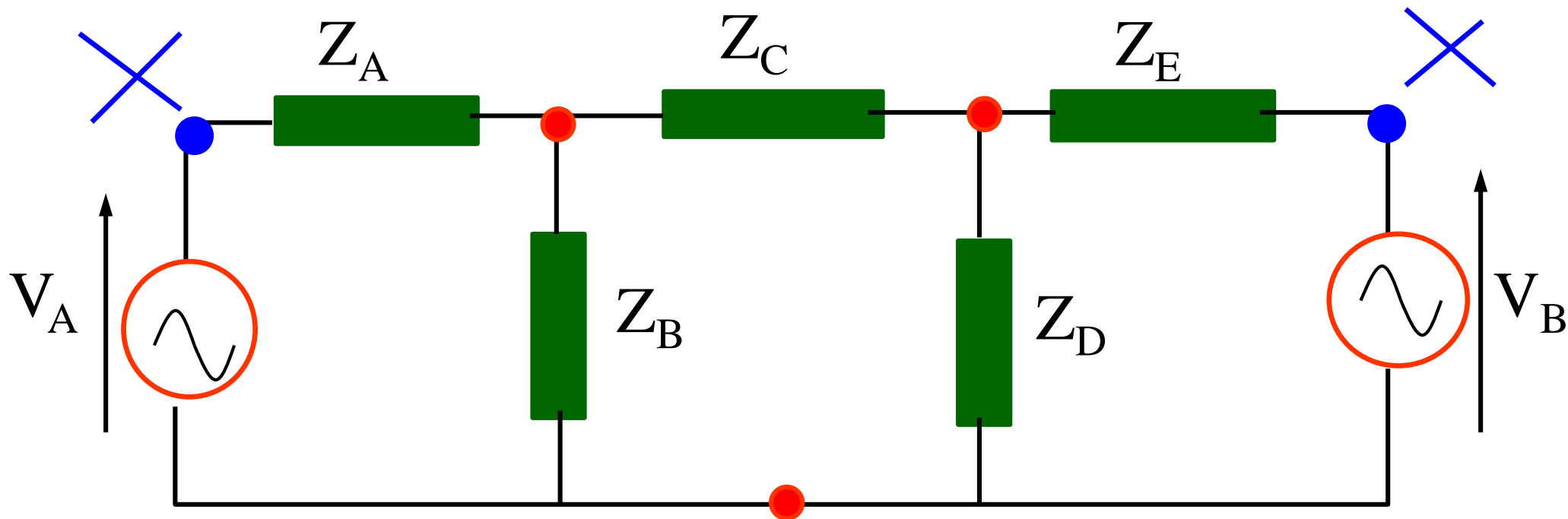

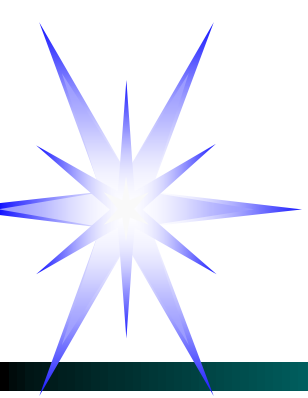Nodes are junctions of branches in a circuit.  
Choose nodes such that no isolated voltage or current source appears between any 2 nodes.




# Nodal Analysis

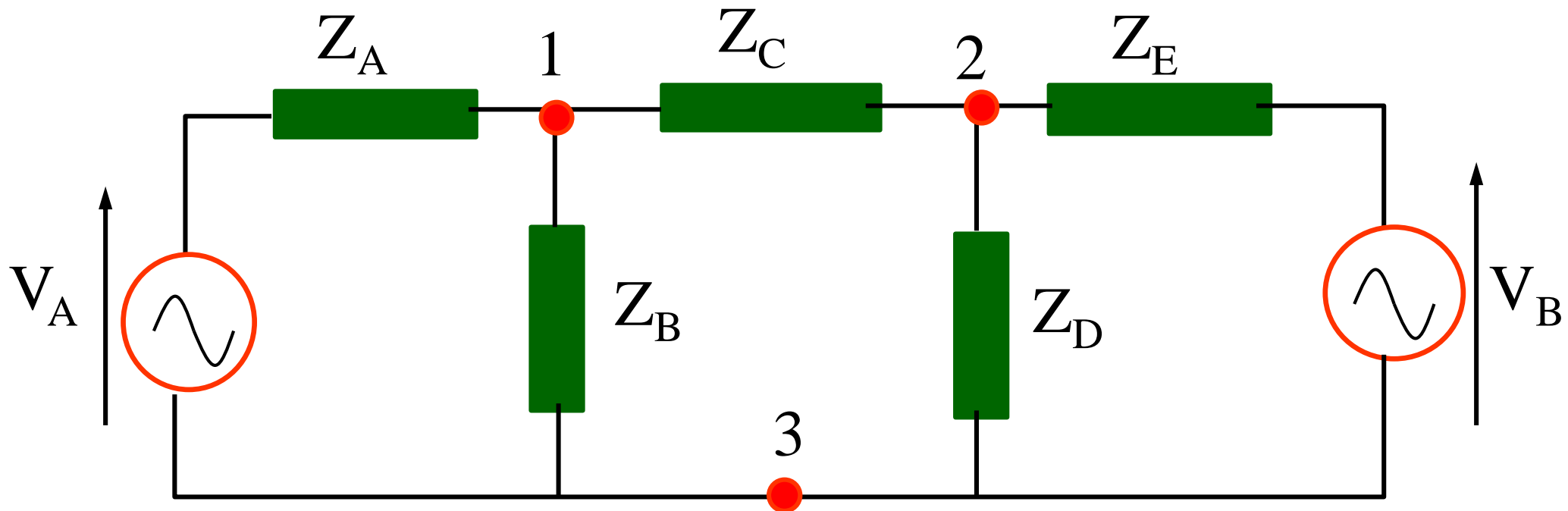


Choose the nodes and number them.

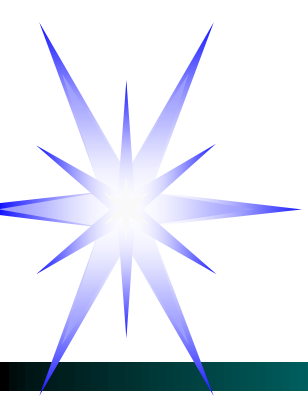Take one of the nodes as reference, say, node 3.



# Nodal Analysis

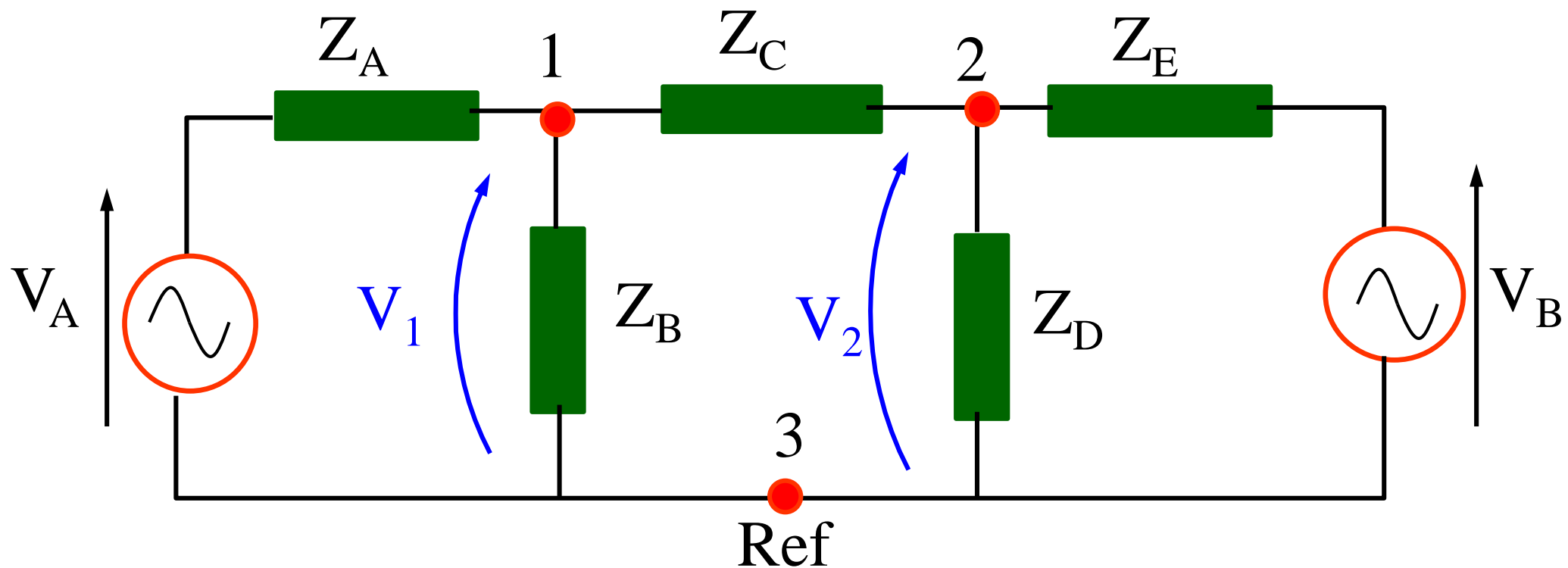

The voltages of the other two nodes 1 & 2, namely  $V_1$  and  $V_2$ , are then measured with respect to this reference node 3.






# Nodal Analysis

---

Started with 3 nodes.

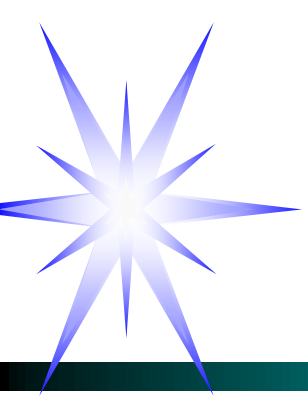After taking 1 node as the reference, 2 nodes are left. This indicates that the number of equations by KCL will also be 2.



# Nodal Analysis

The 2 equations are again shown here:

$$\frac{V_1 - V_A}{Z_A} + \frac{V_1}{Z_B} + \frac{V_1 - V_2}{Z_C} = 0$$

$$\frac{V_2 - V_1}{Z_C} + \frac{V_2}{Z_D} + \frac{V_2 - V_B}{Z_E} = 0$$

Rearranging to give:

$$\left( \frac{1}{Z_A} + \frac{1}{Z_B} + \frac{1}{Z_C} \right) V_1 - \frac{1}{Z_C} V_2 = \frac{V_A}{Z_A}$$
$$-\frac{1}{Z_C} V_1 + \left( \frac{1}{Z_C} + \frac{1}{Z_D} + \frac{1}{Z_E} \right) V_2 = \frac{V_B}{Z_E}$$




# Nodal Analysis

Rewritten in matrix form to give:-

$$\begin{bmatrix} \left( \frac{1}{Z_A} + \frac{1}{Z_B} + \frac{1}{Z_C} \right) & -\left( \frac{1}{Z_C} \right) \\ -\left( \frac{1}{Z_C} \right) & \left( \frac{1}{Z_C} + \frac{1}{Z_D} + \frac{1}{Z_E} \right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{V_A}{Z_A} \\ \frac{V_B}{Z_E} \end{bmatrix}$$



# Nodal Analysis

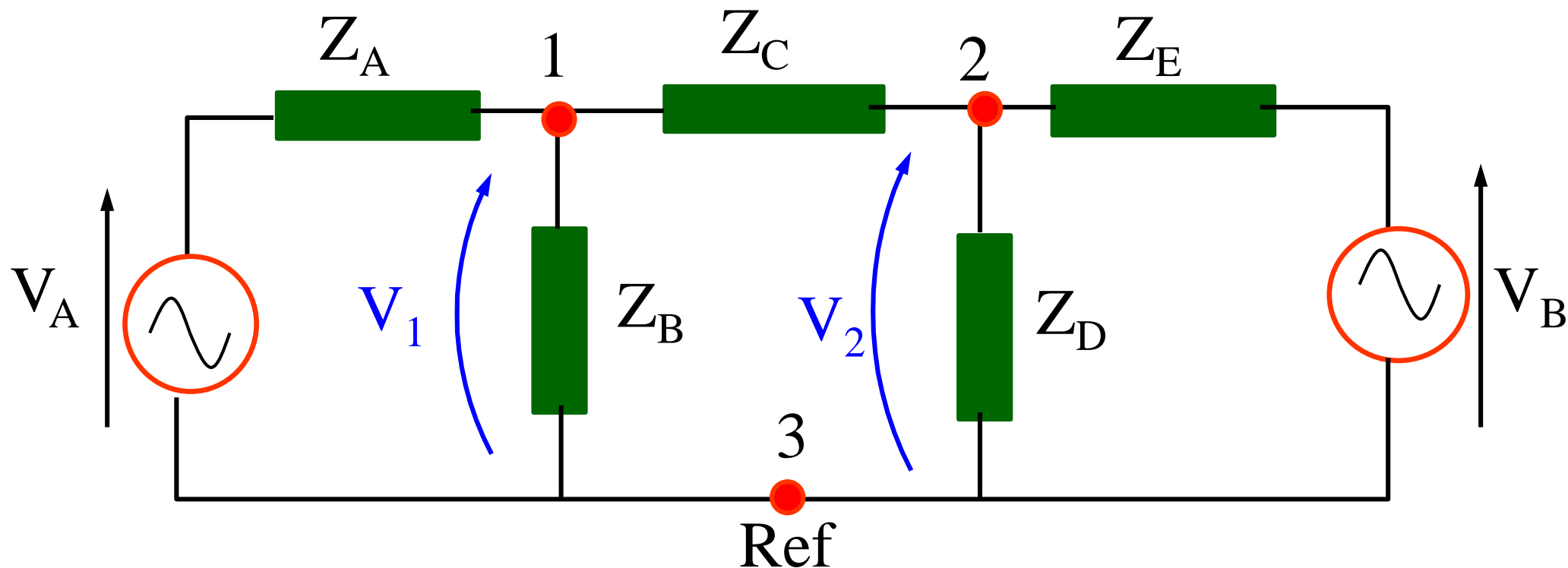


The general nodal matrix equation is therefore:


$Y \times V = I$  where  $Y$  is a  $2 \times 2$  admittance matrix (for a 3 nodes circuit) and  $V$  &  $I$  are  $2 \times 1$  vectors



# Nodal Analysis by Inspection

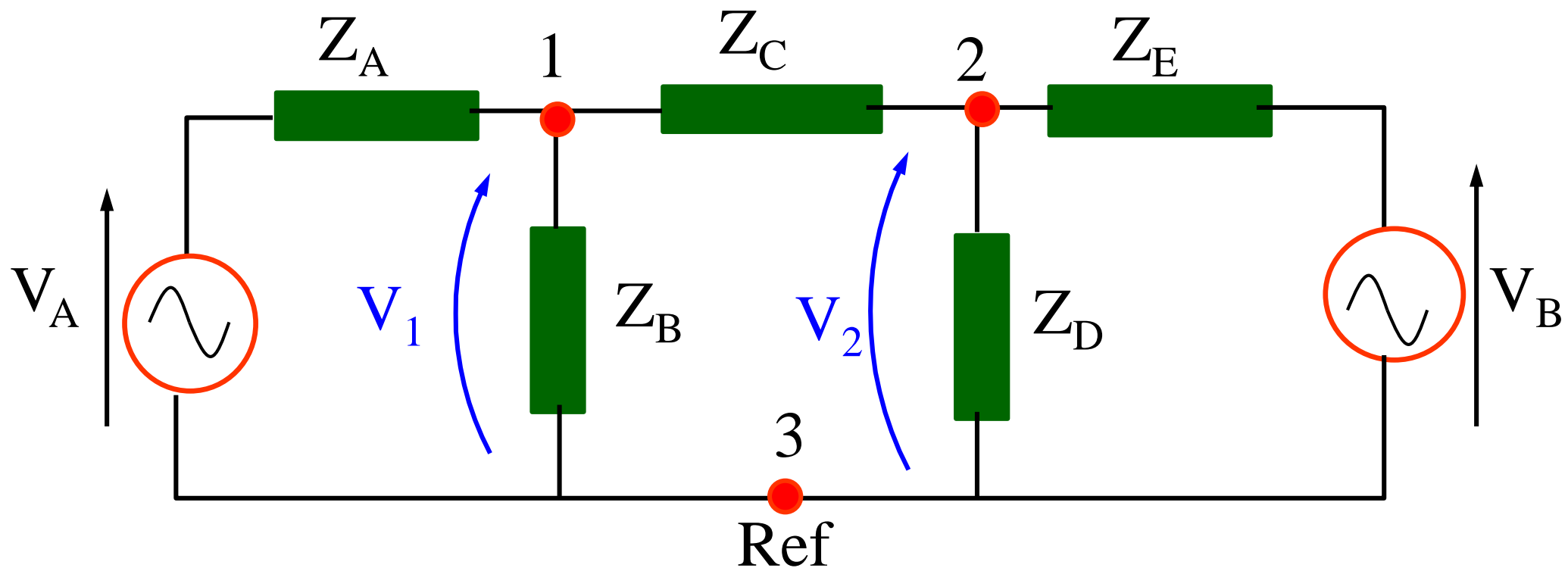

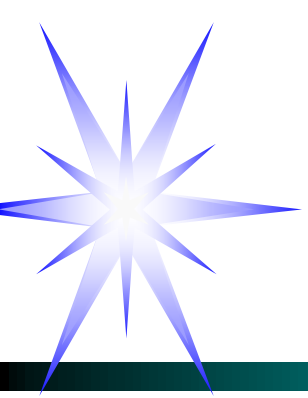The purpose of nodal analysis is to be able to write this matrix equation  $Y \times V = I$  by **INSPECTION** on the circuit without using KCL.




# Nodal Analysis by Inspection

Let's look at the nodal matrix again:-  $Y \times V = I$

$$\begin{bmatrix} \left( \frac{1}{Z_A} + \frac{1}{Z_B} + \frac{1}{Z_C} \right) & -\left( \frac{1}{Z_C} \right) \\ -\left( \frac{1}{Z_C} \right) & \left( \frac{1}{Z_C} + \frac{1}{Z_D} + \frac{1}{Z_E} \right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{V_A}{Z_A} \\ \frac{V_B}{Z_E} \end{bmatrix}$$

In general, the matrix  $Y \times V = I$  can be expressed as:

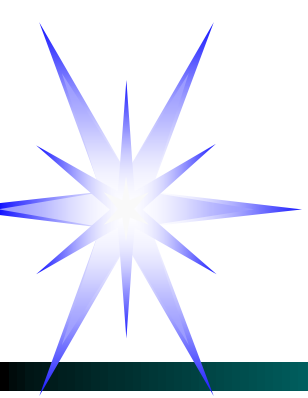
$$\begin{bmatrix} +(\mathbf{Y}_{11}) & -(\mathbf{Y}_{12}) \\ -(\mathbf{Y}_{21}) & +(\mathbf{Y}_{22}) \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$


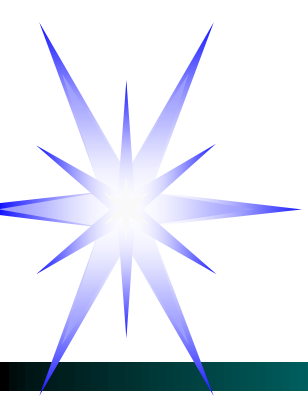
# Nodal Analysis by Inspection

Here comes the regulations to follow in order to write the nodal matrix equation by inspection *without using Kirchhoff's Current Law.*

This is then followed by the use of Cramer's Rule to solve for the nodal voltages  $V_1$ ,  $V_2$  etc.




# Nodal Analysis by Inspection

Self-admittances (those in the diagonal)

$Y_{11}$  = sum of all admittances connected to node 1

$$= (1/Z_A + 1/Z_B + 1/Z_C)$$

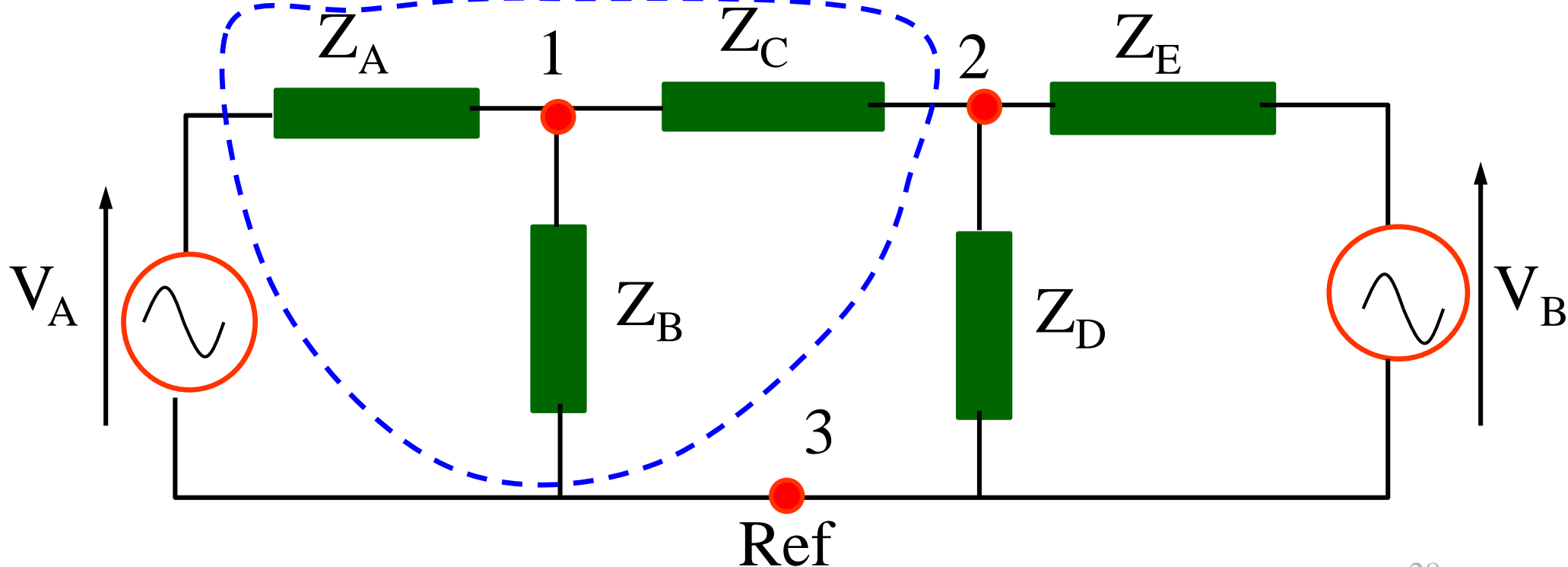






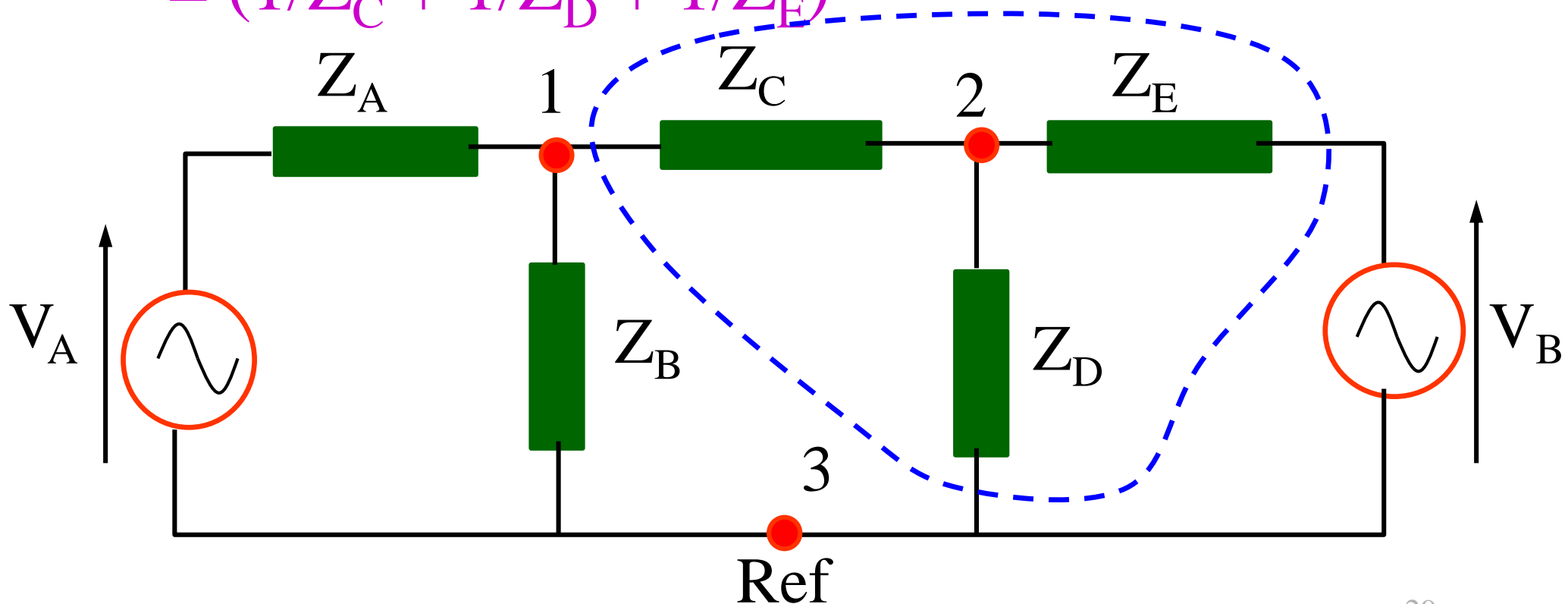
# Nodal Analysis by Inspection

Self-admittances (those in the diagonal)

$Y_{22}$  = sum of all admittances connected to node 2  
 $= (1/Z_C + 1/Z_D + 1/Z_E)$



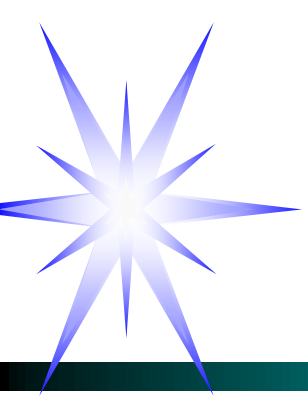

# Nodal Analysis by Inspection

Self-admittances (those in the diagonal)

$Y_{11} = (1/Z_A + 1/Z_B + 1/Z_C) =$  sum of all  
admittances connected to node 1

$Y_{22} = (1/Z_C + 1/Z_D + 1/Z_E) =$  sum of all  
admittances connected to node 2

If the admittance matrix were a 3 x 3 matrix (for a four nodes circuit, taking node 4, say, as the reference), then


$Y_{33} =$  sum of all admittances connected to node 3


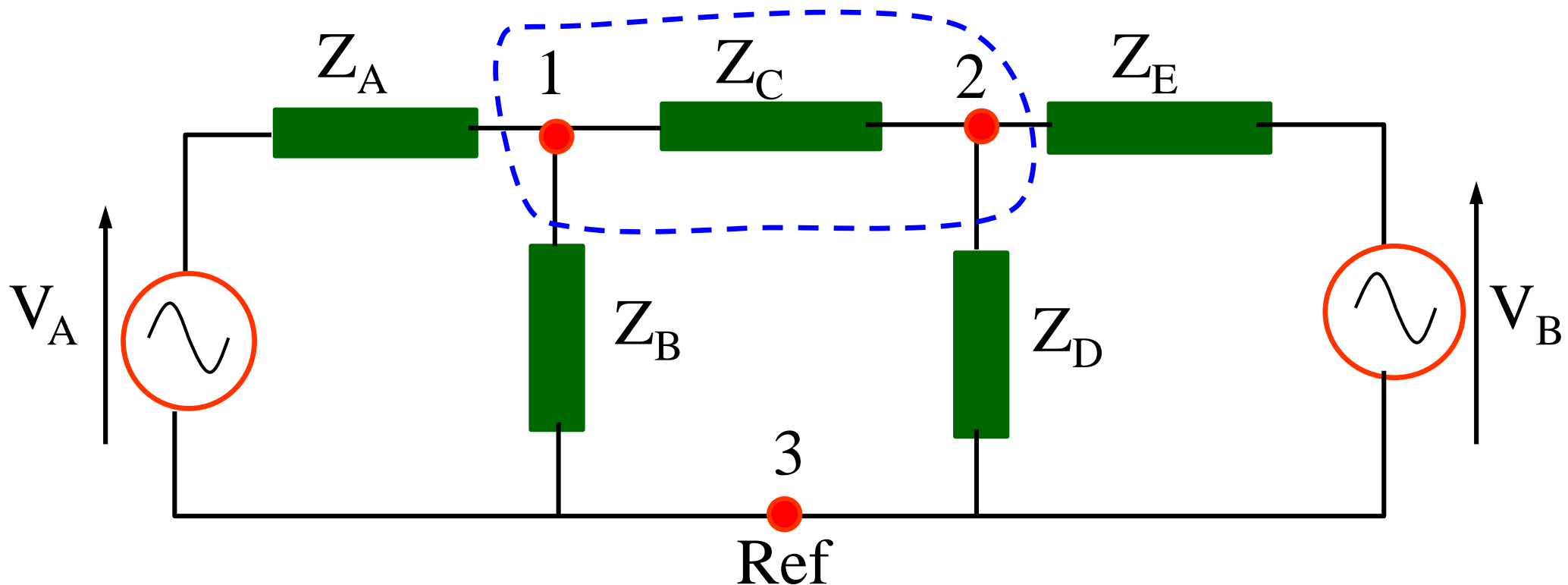
# Nodal Analysis by Inspection

Coupling-admittances (those off the diagonal)

$Y_{12} = Y_{21} = \textit{minus}$  the sum of all admittances connected between node 1 & 2 =  $-1 / Z_C$





# Nodal Analysis by Inspection


If the admittance matrix were a 3 x 3 matrix (for a four nodes circuit, taking node 4 as the reference), then

$Y_{13} = Y_{31} = \textit{minus}$  the sum of all admittances connected between nodes 1 & 3


$Y_{23} = Y_{32} = \textit{minus}$  the sum of all admittances connected between nodes 2 & 3




# Nodal Analysis by Inspection

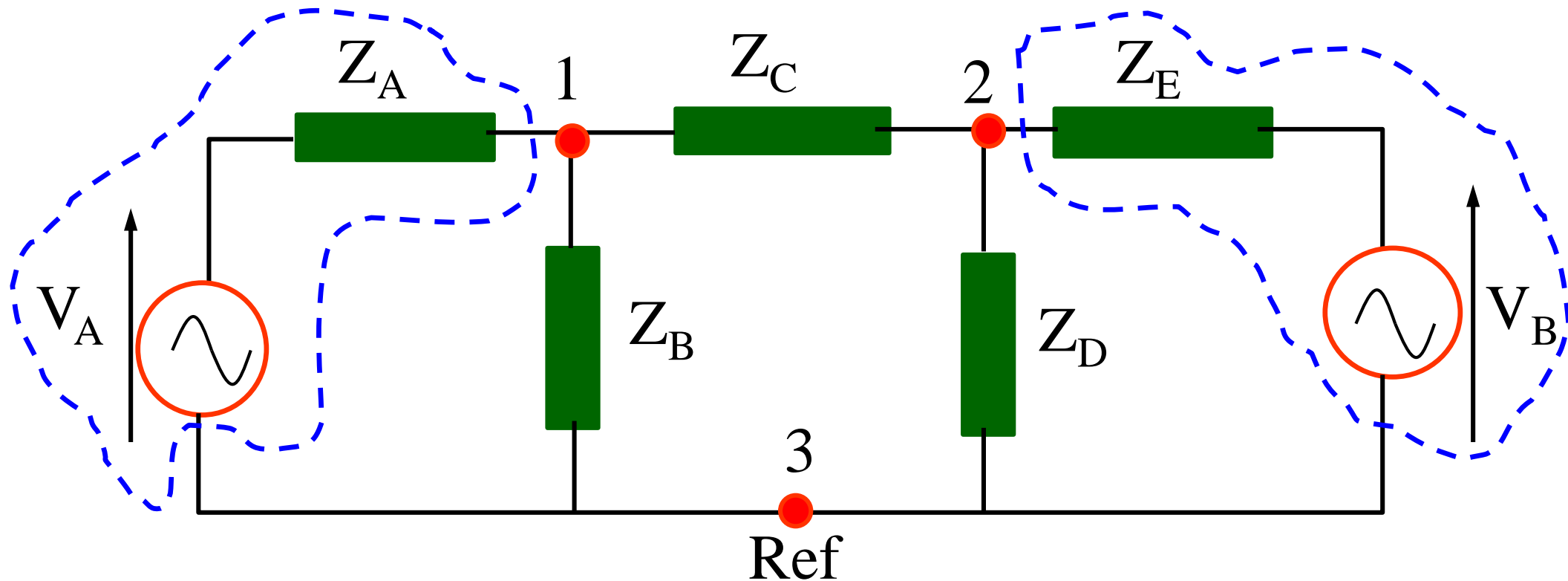


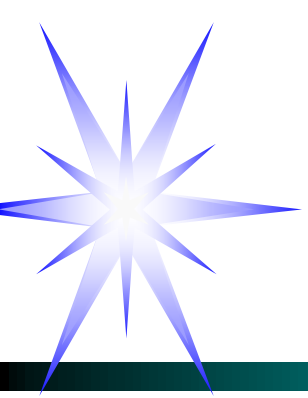A **positive** sign should be applied on a current source if the current is flowing toward the node.  
**Negative** when flowing away from the node.




# Nodal Analysis by Inspection

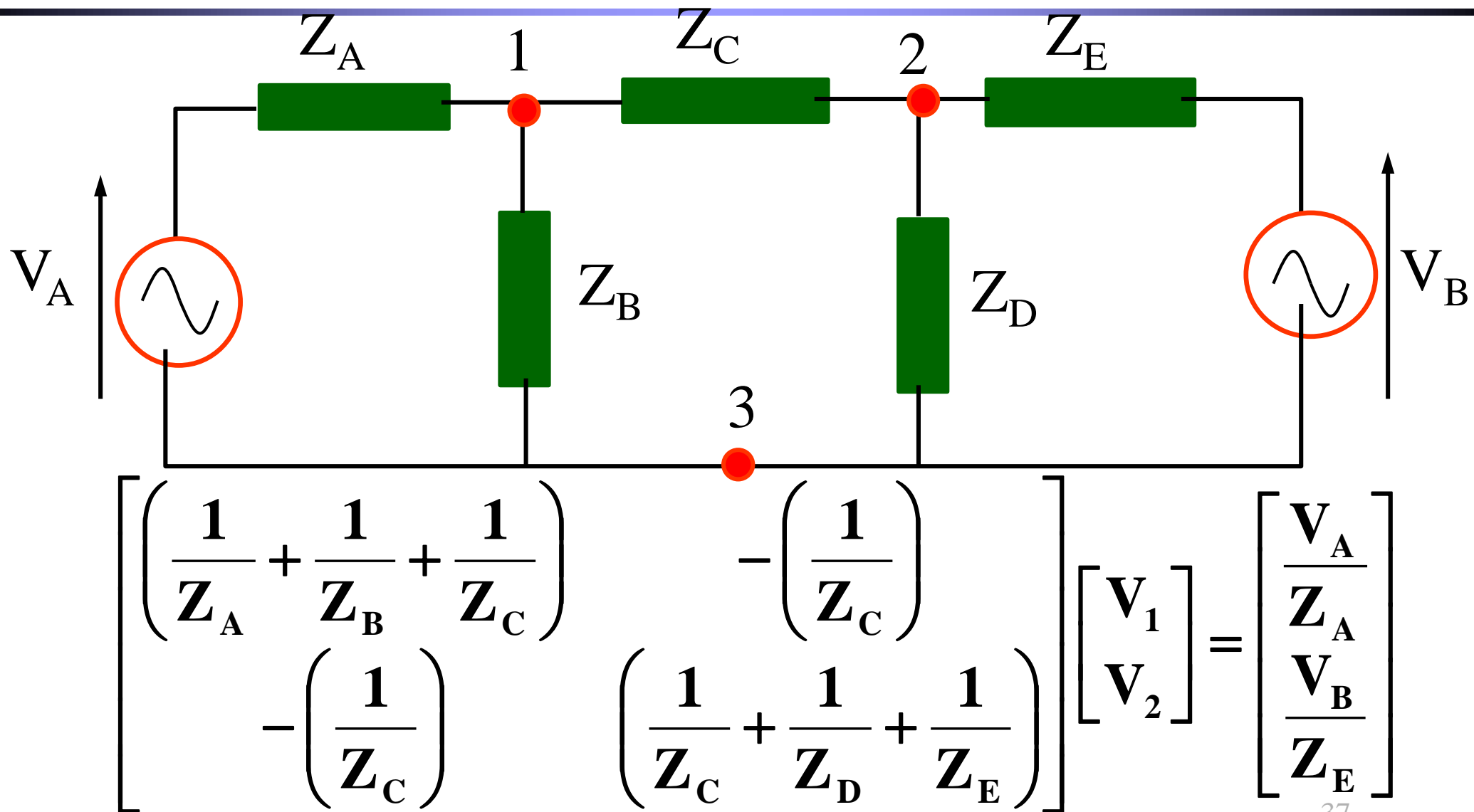


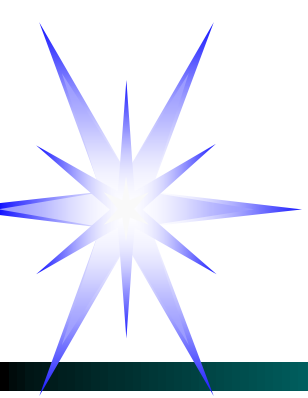


## Example 1.5

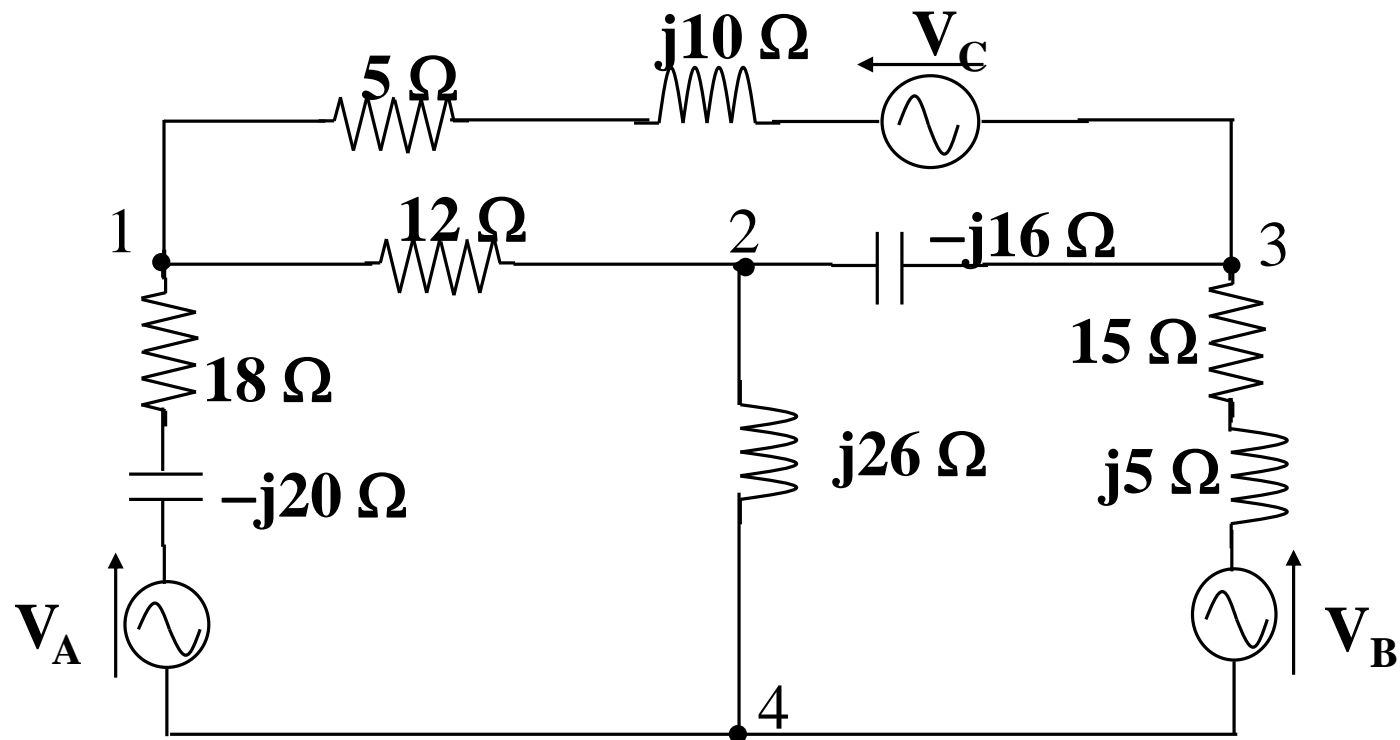

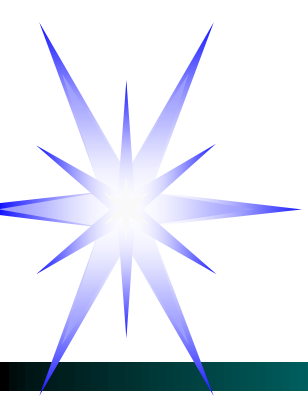Write the nodal voltage equation by inspection for the circuit shown.



## Example 1.5

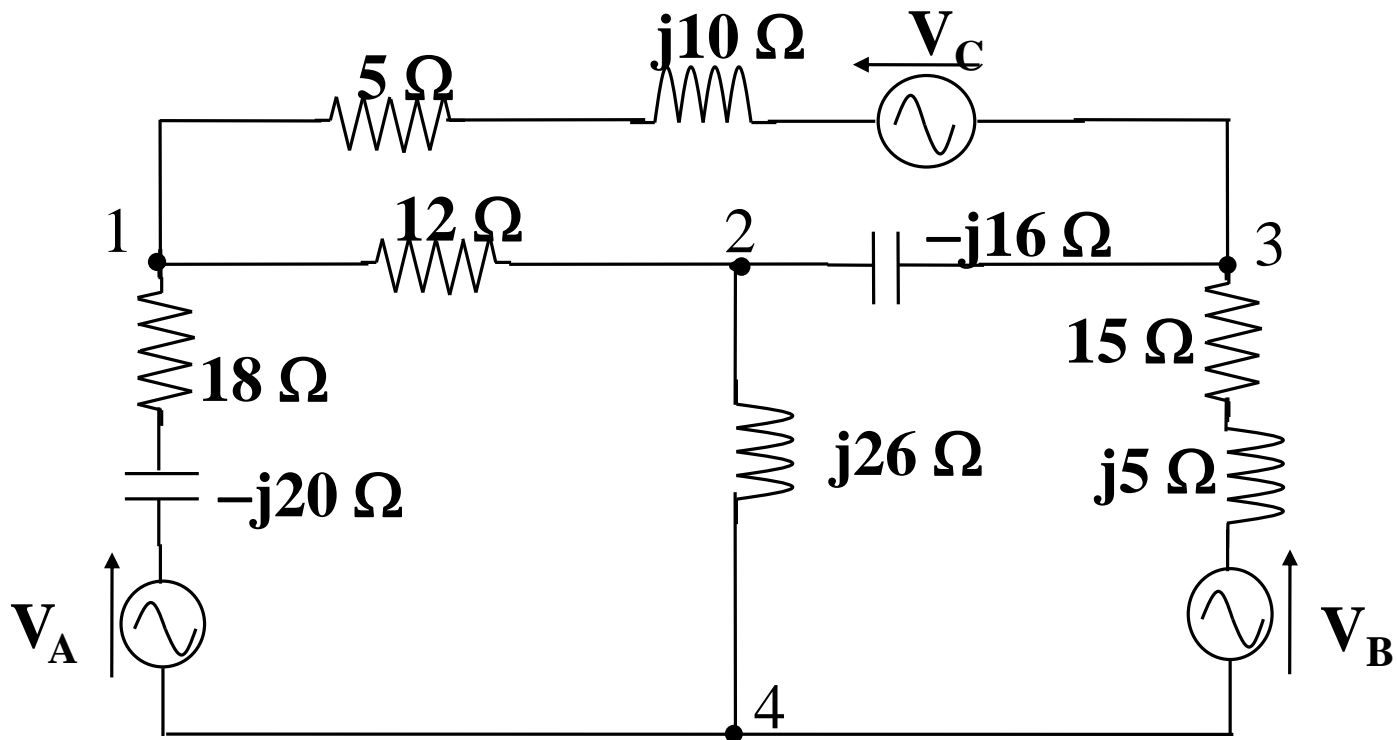


For a four nodes circuit, taking node 4 as the reference, the admittance matrix is a  $3 \times 3$  matrix







# Example 1.5

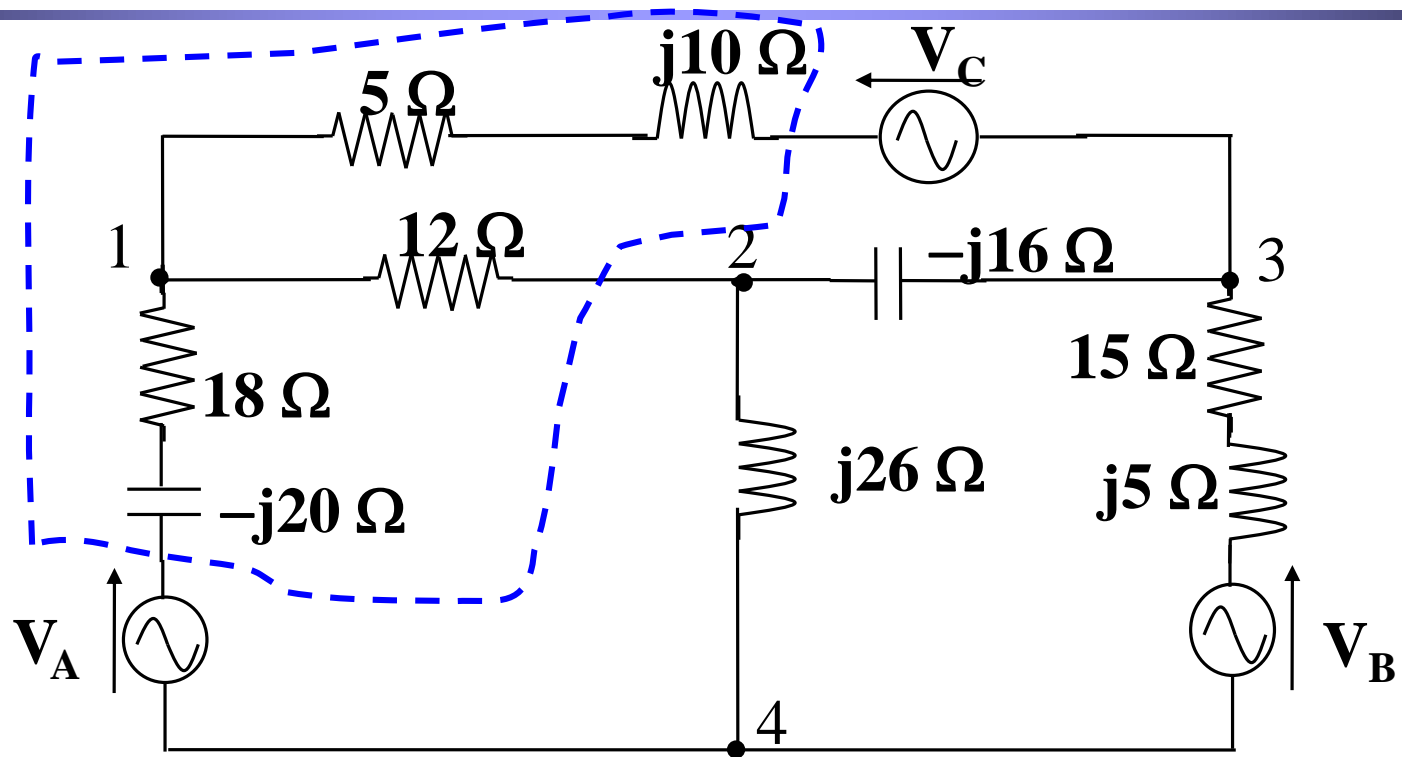
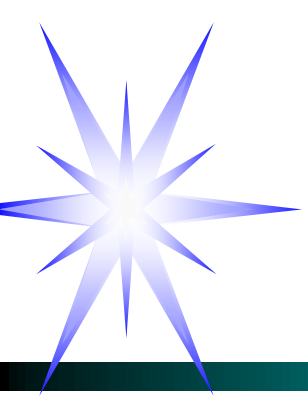
$$\left[ \left( \frac{1}{18 - j20} + \frac{1}{12} + \frac{1}{5 + j10} \right) \right] \begin{bmatrix} \phantom{0} \\ \phantom{0} \end{bmatrix} = \begin{bmatrix} \phantom{0} \\ \phantom{0} \end{bmatrix}$$




# Example 1.5

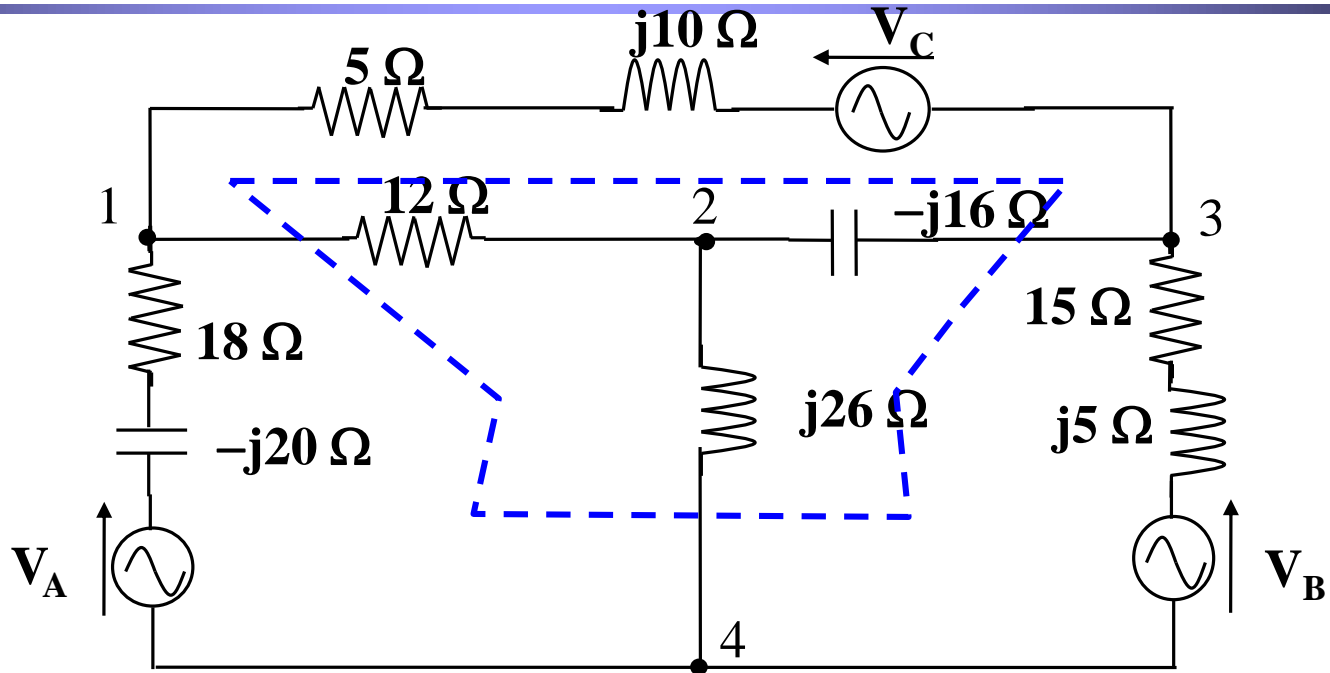

$$\begin{bmatrix} \left( \frac{1}{18 - j20} + \frac{1}{12} + \frac{1}{5 + j10} \right) \\ \left( \frac{1}{12} + \frac{1}{-j16} + \frac{1}{j26} \right) \end{bmatrix} \begin{bmatrix} V_A \\ V_C \end{bmatrix} = \begin{bmatrix} V_B \\ 0 \end{bmatrix}$$




# Example 1.5

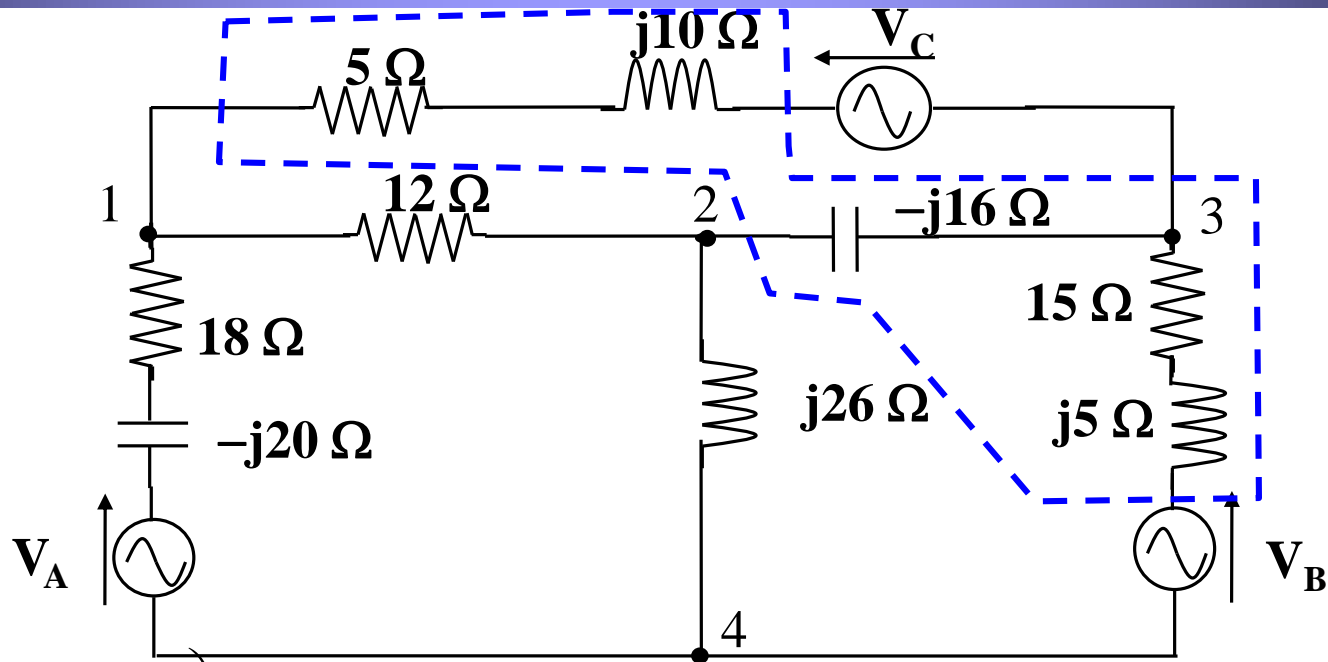

$$\begin{bmatrix} \left( \frac{1}{18 - j20} + \frac{1}{12} + \frac{1}{5 + j10} \right) & \left( \frac{1}{12} + \frac{1}{-j16} + \frac{1}{j26} \right) & \left( \frac{1}{5 + j10} + \frac{1}{-j16} + \frac{1}{15 + j5} \right) \end{bmatrix} \begin{bmatrix} V_A \\ V_C \\ V_B \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$




# Example 1.5

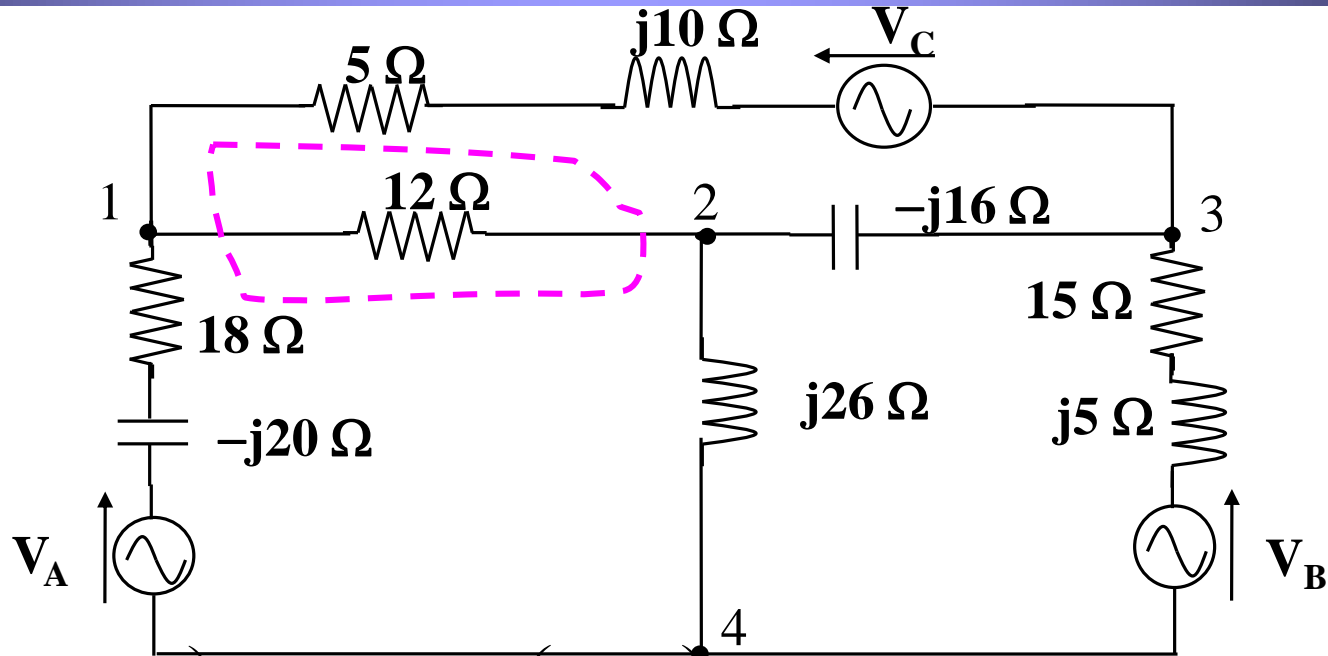


$$\begin{bmatrix} \left( \frac{1}{18 - j20} + \frac{1}{12} + \frac{1}{5 + j10} \right) & - \left( \frac{1}{12} \right) & 0 \\ \left( \frac{1}{12} + \frac{1}{-j16} + \frac{1}{j26} \right) & 0 & 0 \\ 0 & \left( \frac{1}{5 + j10} + \frac{1}{-j16} + \frac{1}{15 + j5} \right) & 0 \end{bmatrix} \begin{bmatrix} V_A \\ V_C \\ V_B \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$




# Example 1.5

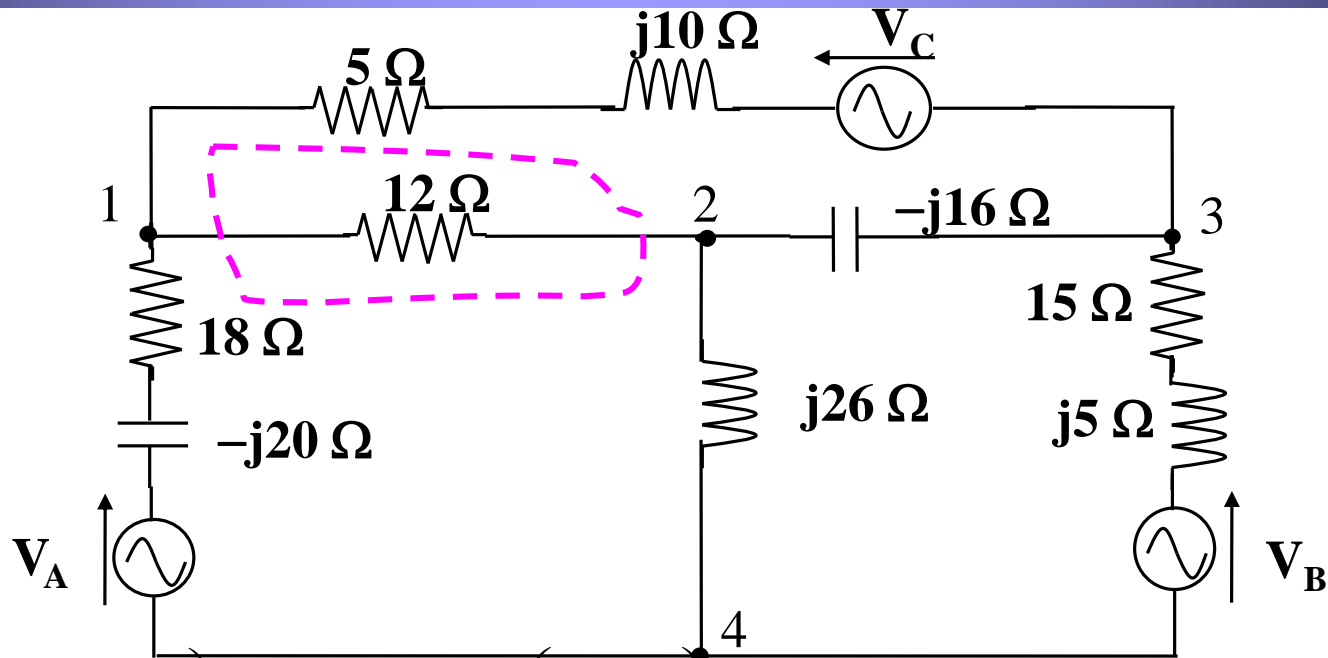

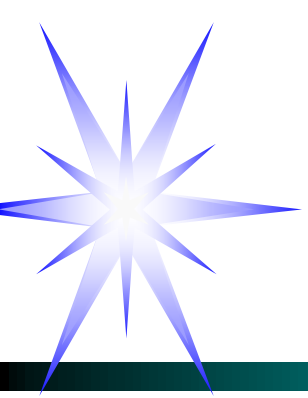
$$\begin{bmatrix} \left( \frac{1}{18 - j20} + \frac{1}{12} + \frac{1}{5 + j10} \right) & - \left( \frac{1}{12} \right) \\ - \left( \frac{1}{12} \right) & \left( \frac{1}{12} + \frac{1}{-j16} + \frac{1}{j26} \right) \end{bmatrix} \begin{bmatrix} V_A \\ V_C \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$




# Example 1.5

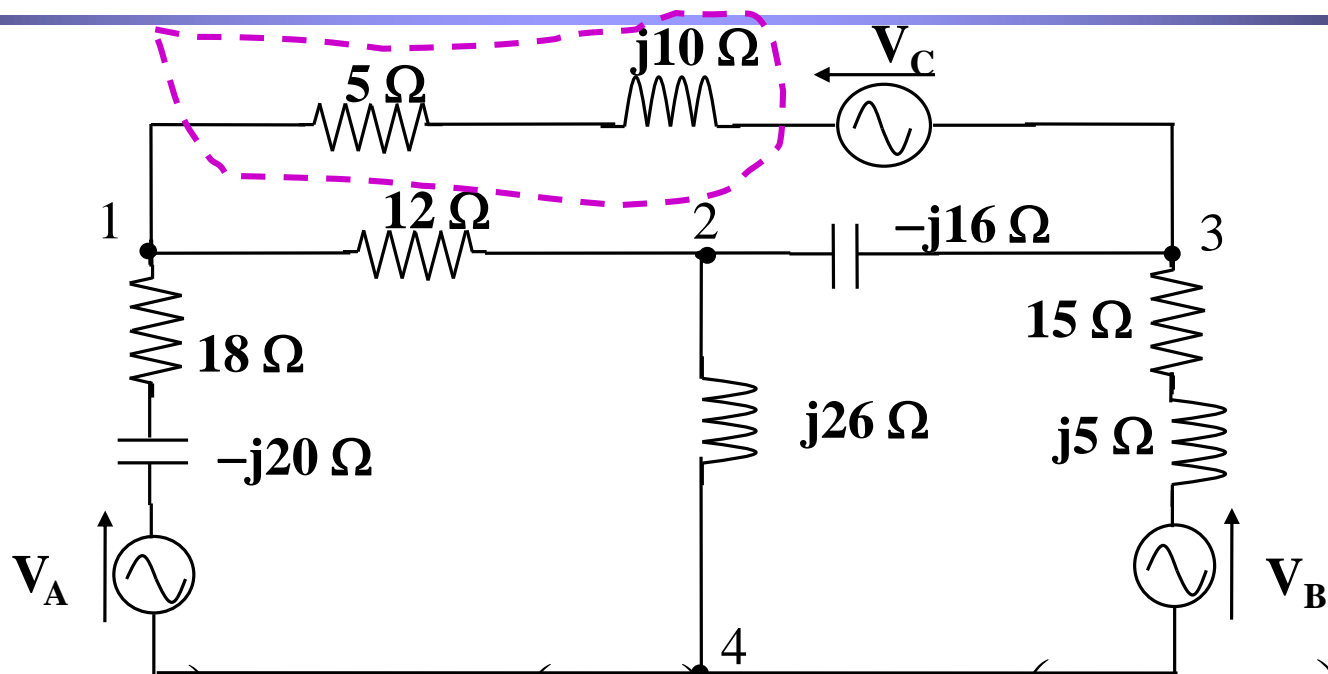


$$\begin{bmatrix} \left( \frac{1}{18 - j20} + \frac{1}{12} + \frac{1}{5 + j10} \right) & - \left( \frac{1}{12} \right) & - \left( \frac{1}{5 + j10} \right) \\ - \left( \frac{1}{12} \right) & \left( \frac{1}{12} + \frac{1}{-j16} + \frac{1}{j26} \right) & \left( \frac{1}{5 + j10} + \frac{1}{-j16} + \frac{1}{15 + j5} \right) \end{bmatrix} \begin{bmatrix} V_A \\ V_C \\ V_B \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

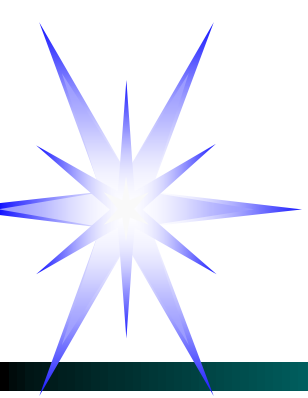


# Example 1.5

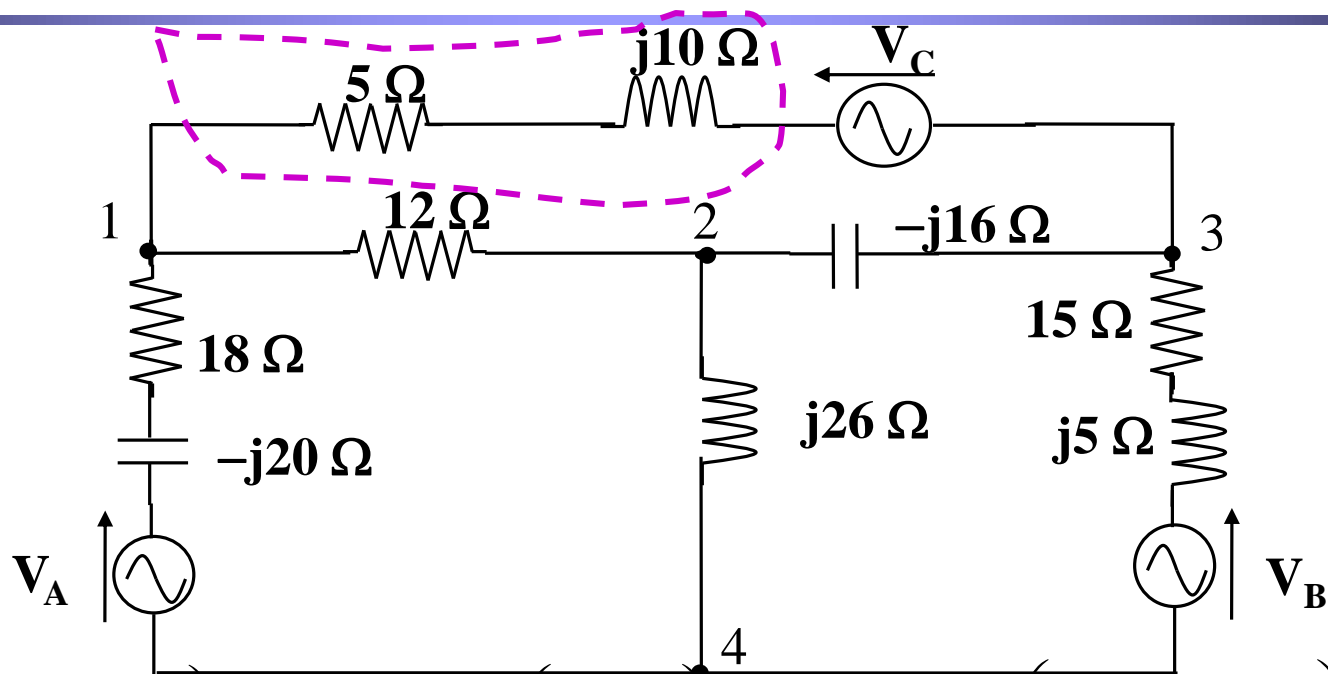

$$\begin{bmatrix} \left( \frac{1}{18 - j20} + \frac{1}{12} + \frac{1}{5 + j10} \right) & - \left( \frac{1}{12} \right) & - \left( \frac{1}{5 + j10} \right) \\ - \left( \frac{1}{12} \right) & \left( \frac{1}{12} + \frac{1}{-j16} + \frac{1}{j26} \right) & \left( \frac{1}{5 + j10} + \frac{1}{-j16} + \frac{1}{15 + j5} \right) \\ - \left( \frac{1}{5 + j10} \right) & \left( \frac{1}{5 + j10} + \frac{1}{-j16} + \frac{1}{15 + j5} \right) & \end{bmatrix} \begin{bmatrix} V_A \\ V_C \\ V_B \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

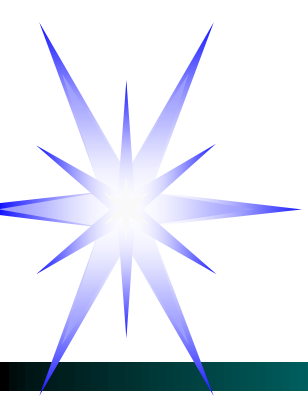

# Example 1.5

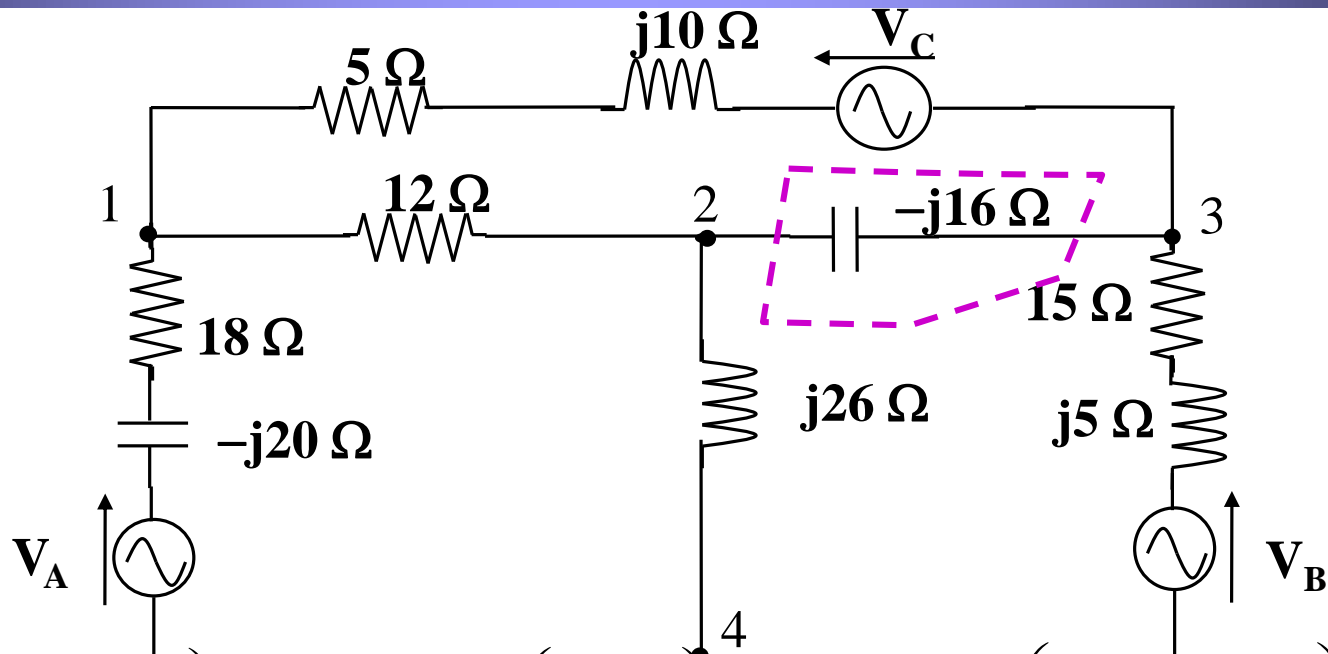


$$\begin{bmatrix} \left( \frac{1}{18 - j20} + \frac{1}{12} + \frac{1}{5 + j10} \right) & - \left( \frac{1}{12} \right) & - \left( \frac{1}{5 + j10} \right) \\ - \left( \frac{1}{12} \right) & \left( \frac{1}{12} + \frac{1}{-j16} + \frac{1}{j26} \right) & - \left( \frac{1}{-j16} \right) \\ - \left( \frac{1}{5 + j10} \right) & - \left( \frac{1}{-j16} \right) & \left( \frac{1}{5 + j10} + \frac{1}{-j16} + \frac{1}{15 + j5} \right) \end{bmatrix} \begin{bmatrix} V_A \\ V_C \\ V_B \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$







# Example 1.5

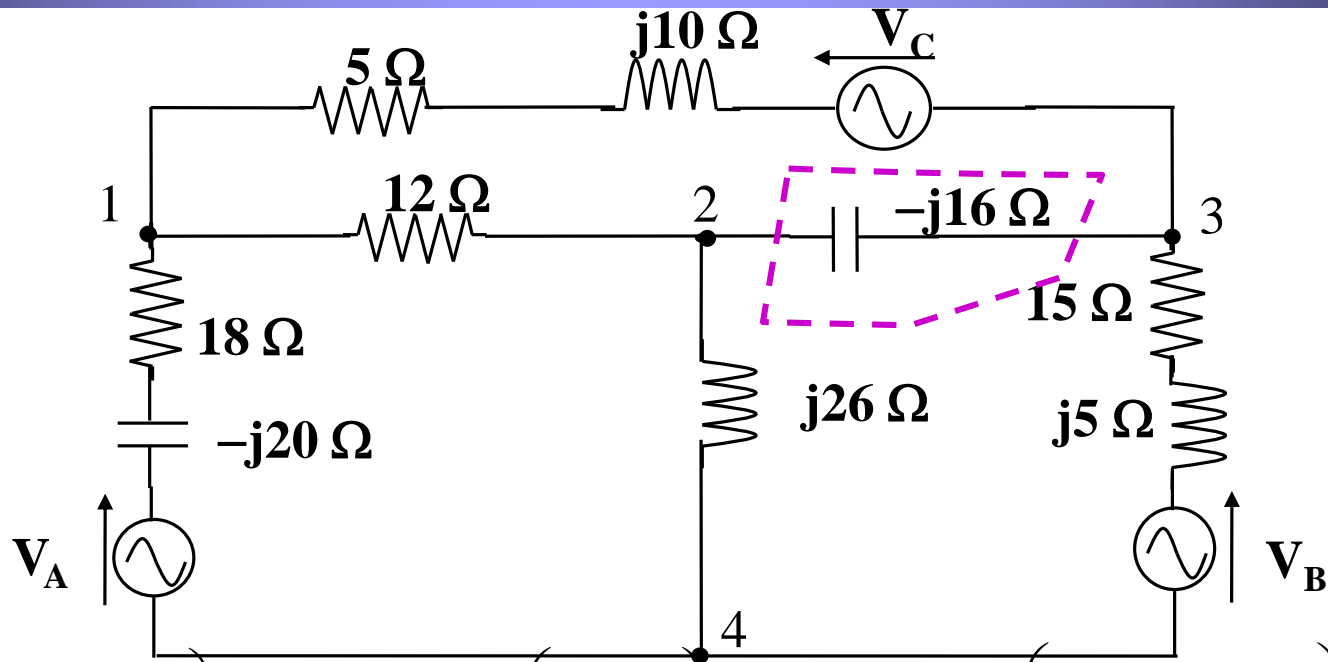

$$\begin{bmatrix} \left( \frac{1}{18 - j20} + \frac{1}{12} + \frac{1}{5 + j10} \right) & - \left( \frac{1}{12} \right) & - \left( \frac{1}{5 + j10} \right) \\ - \left( \frac{1}{12} \right) & \left( \frac{1}{12} + \frac{1}{-j16} + \frac{1}{j26} \right) & - \left( \frac{1}{-j16} \right) \\ - \left( \frac{1}{5 + j10} \right) & - \left( \frac{1}{-j16} \right) & \left( \frac{1}{5 + j10} + \frac{1}{-j16} + \frac{1}{15 + j5} \right) \end{bmatrix} \begin{bmatrix} V_A \\ V_C \\ V_B \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

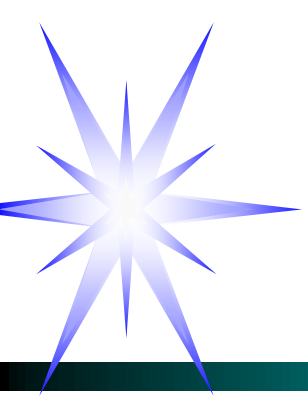


# Example 1.5

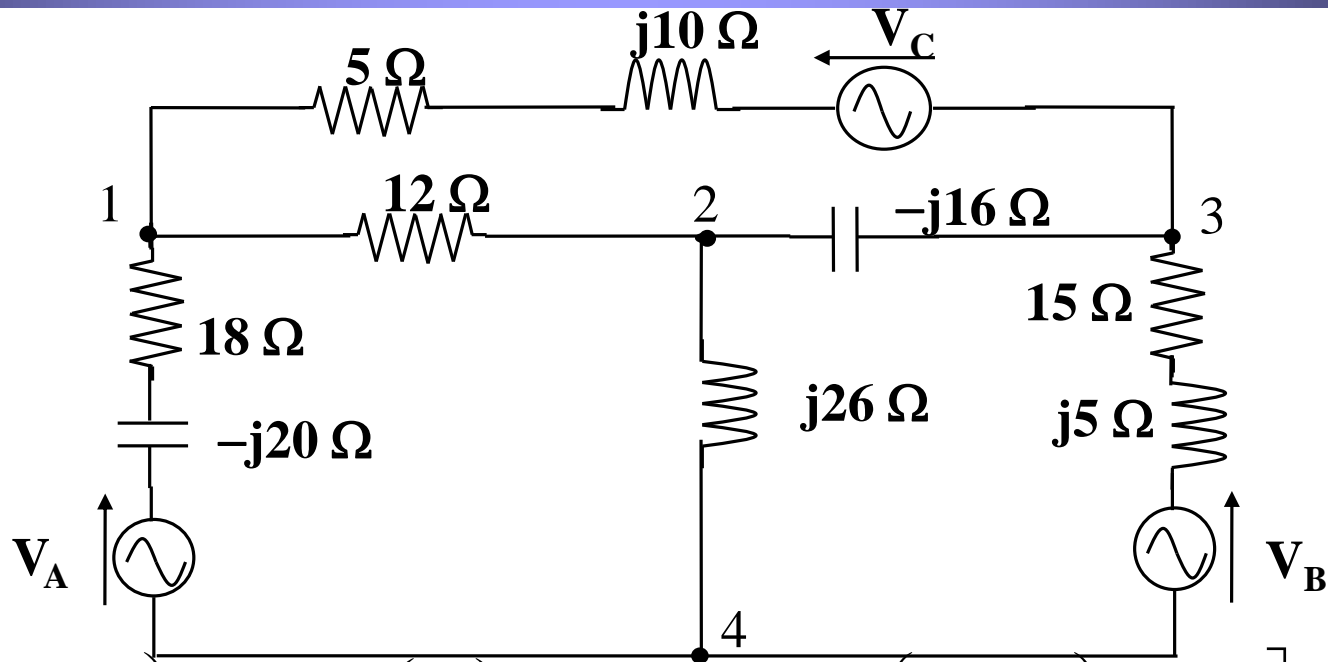

$$\begin{bmatrix} \left( \frac{1}{18-j20} + \frac{1}{12} + \frac{1}{5+j10} \right) & -\left( \frac{1}{12} \right) & -\left( \frac{1}{5+j10} \right) \\ -\left( \frac{1}{12} \right) & \left( \frac{1}{12} + \frac{1}{-j16} + \frac{1}{j26} \right) & -\left( \frac{1}{-j16} \right) \\ -\left( \frac{1}{5+j10} \right) & -\left( \frac{1}{-j16} \right) & \left( \frac{1}{5+j10} + \frac{1}{-j16} + \frac{1}{15+j5} \right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} \\ \\ \end{bmatrix}$$




# Example 1.5

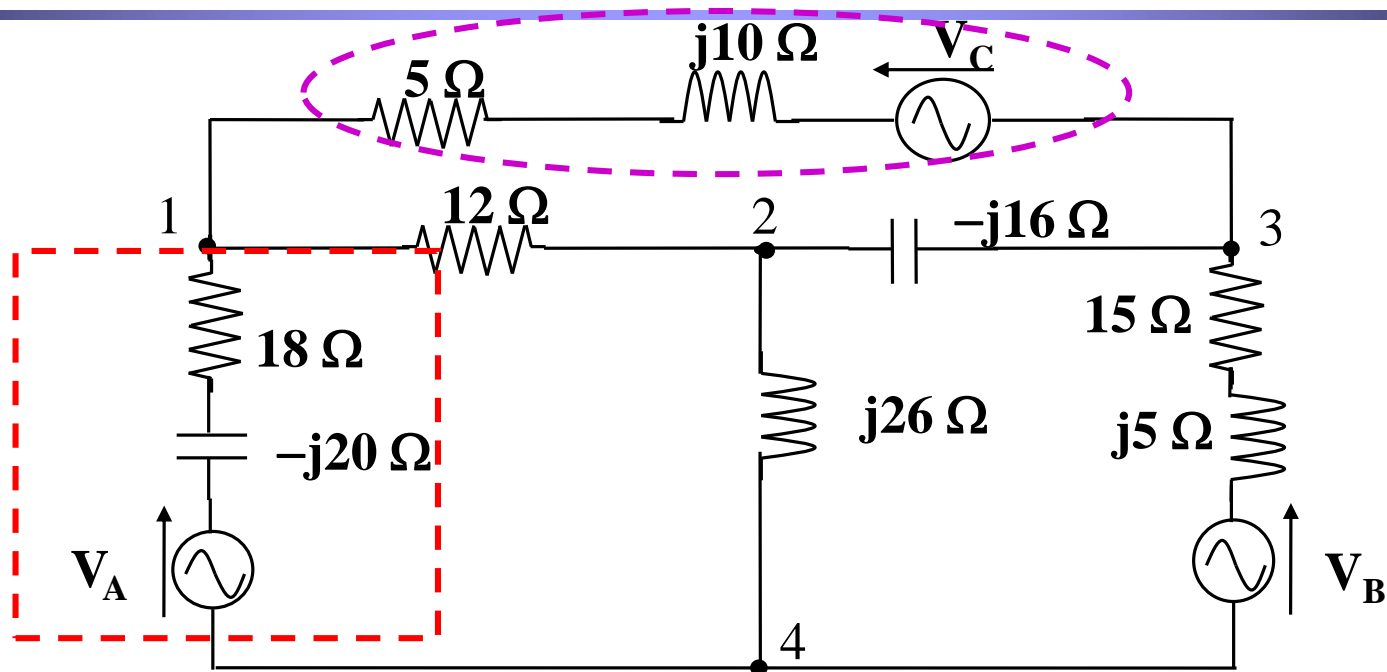

$$\begin{bmatrix} \left( \frac{1}{18-j20} + \frac{1}{12} + \frac{1}{5+j10} \right) & -\left( \frac{1}{12} \right) & -\left( \frac{1}{5+j10} \right) \\ -\left( \frac{1}{12} \right) & \left( \frac{1}{12} + \frac{1}{-j16} + \frac{1}{j26} \right) & -\left( \frac{1}{-j16} \right) \\ -\left( \frac{1}{5+j10} \right) & -\left( \frac{1}{-j16} \right) & \left( \frac{1}{5+j10} + \frac{1}{-j16} + \frac{1}{15+j5} \right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} \frac{V_A}{18-j20} + \frac{V_C}{5+j10} \\ 0 \\ 0 \end{bmatrix}$$




# Example 1.5

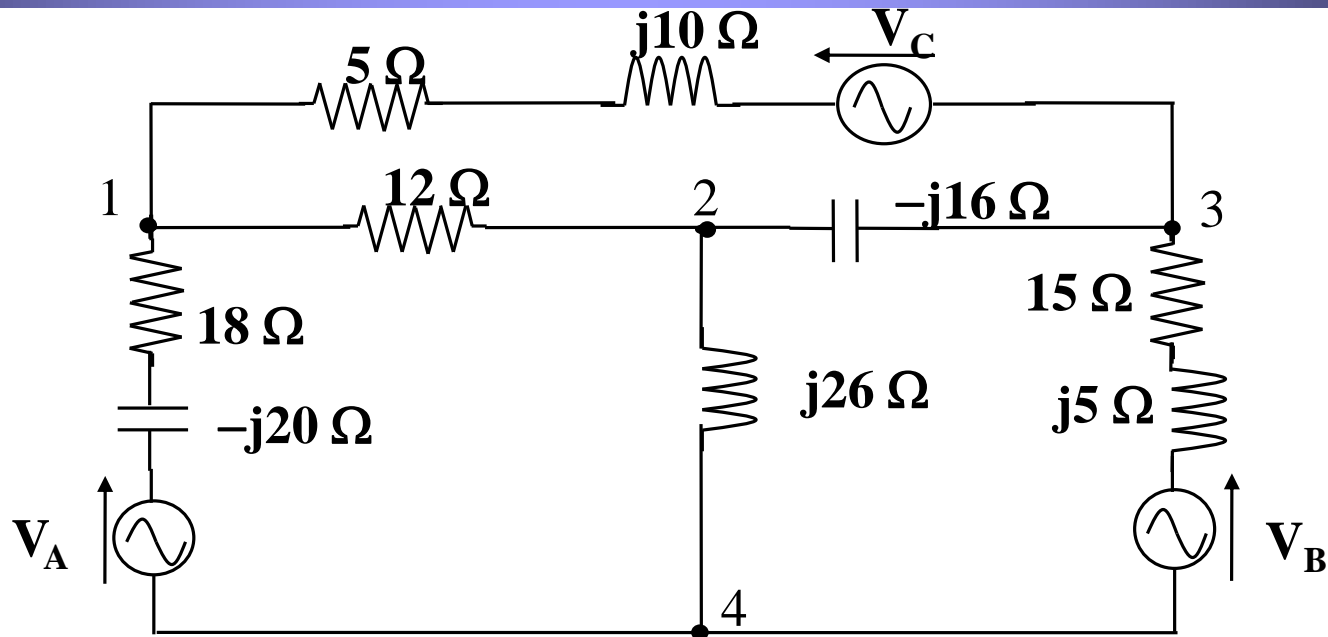


$$\begin{bmatrix} \left( \frac{1}{18-j20} + \frac{1}{12} + \frac{1}{5+j10} \right) & -\left( \frac{1}{12} \right) & -\left( \frac{1}{5+j10} \right) \\ -\left( \frac{1}{12} \right) & \left( \frac{1}{12} + \frac{1}{-j16} + \frac{1}{j26} \right) & -\left( \frac{1}{-j16} \right) \\ -\left( \frac{1}{5+j10} \right) & -\left( \frac{1}{-j16} \right) & \left( \frac{1}{5+j10} + \frac{1}{-j16} + \frac{1}{15+j5} \right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} \frac{V_A}{18-j20} + \frac{V_C}{5+j10} \\ 0 \\ 0 \end{bmatrix}$$




# Example 1.5

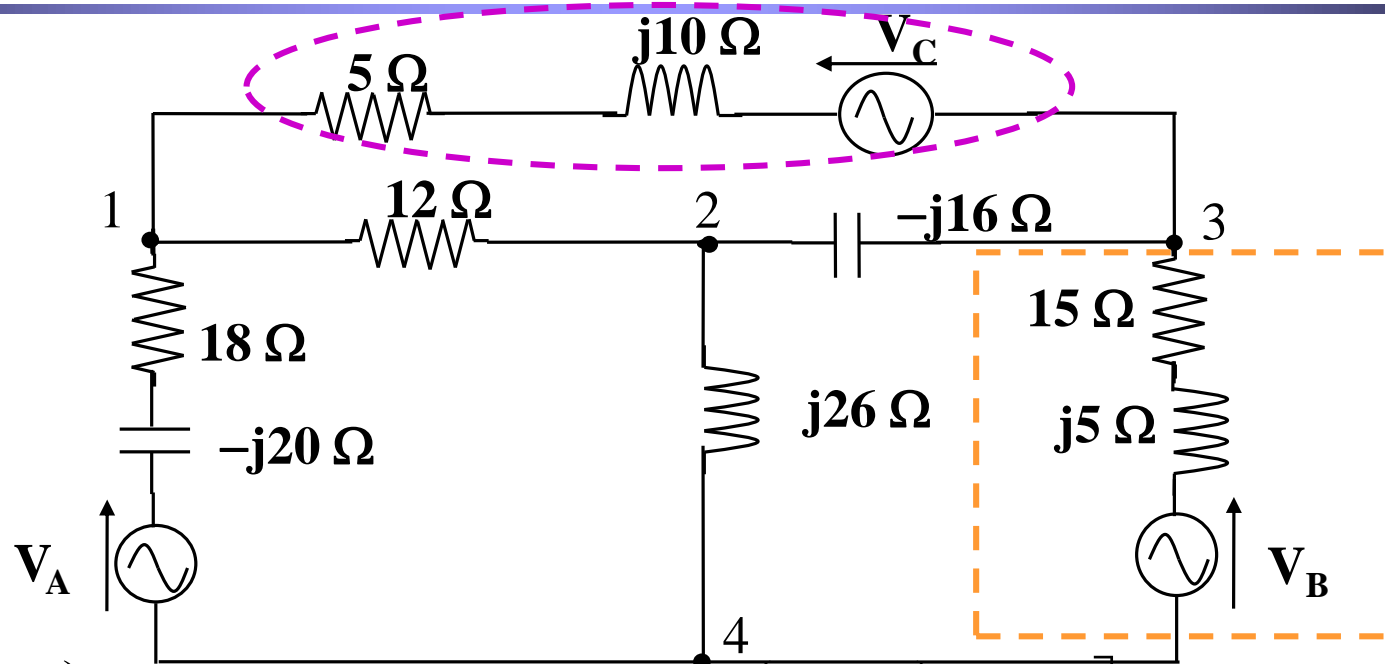


$$\begin{bmatrix} \left( \frac{1}{18-j20} + \frac{1}{12} + \frac{1}{5+j10} \right) & -\left( \frac{1}{12} \right) & -\left( \frac{1}{5+j10} \right) \\ -\left( \frac{1}{12} \right) & \left( \frac{1}{12} + \frac{1}{-j16} + \frac{1}{j26} \right) & -\left( \frac{1}{-j16} \right) \\ -\left( \frac{1}{5+j10} \right) & -\left( \frac{1}{-j16} \right) & \left( \frac{1}{5+j10} + \frac{1}{-j16} + \frac{1}{15+j5} \right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} \frac{V_A}{18-j20} + \frac{V_C}{5+j10} \\ 0 \\ \frac{V_B}{15+j5} - \frac{V_C}{5+j10} \end{bmatrix}$$

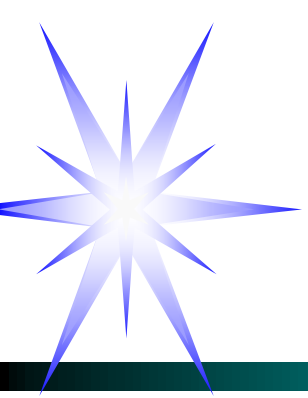


## Example 1.6

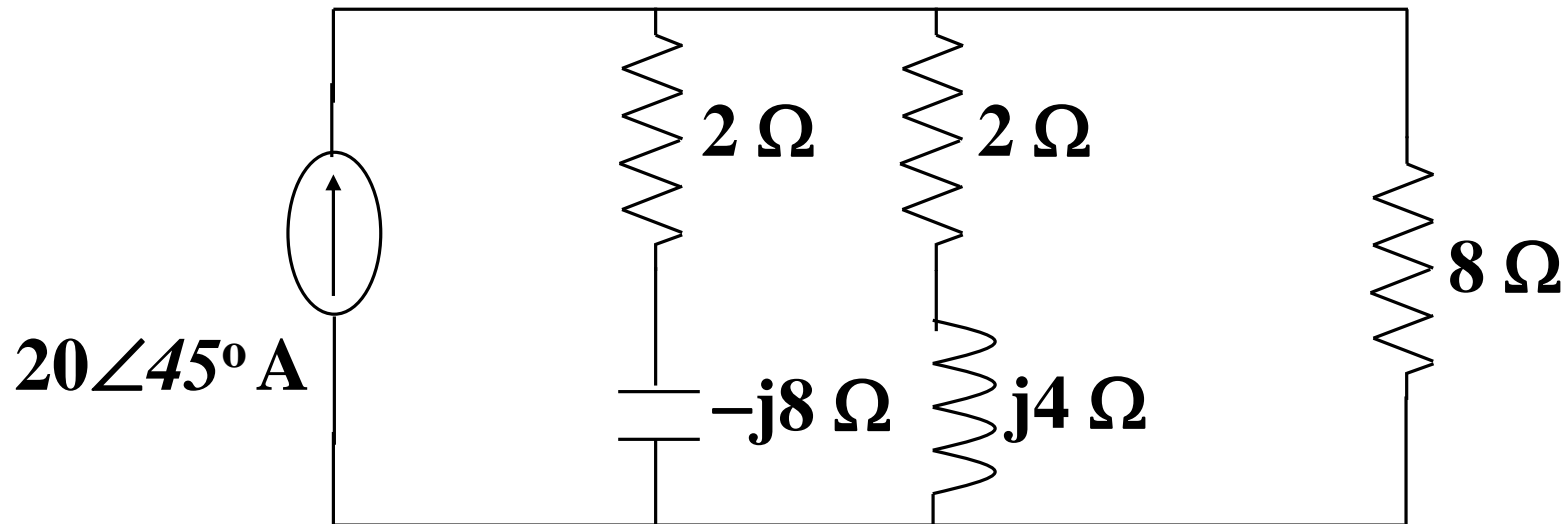

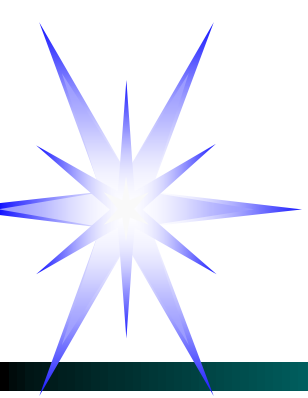
Find the current in the  $8 \Omega$  resistor using node voltage analysis method.




## Example 1.6

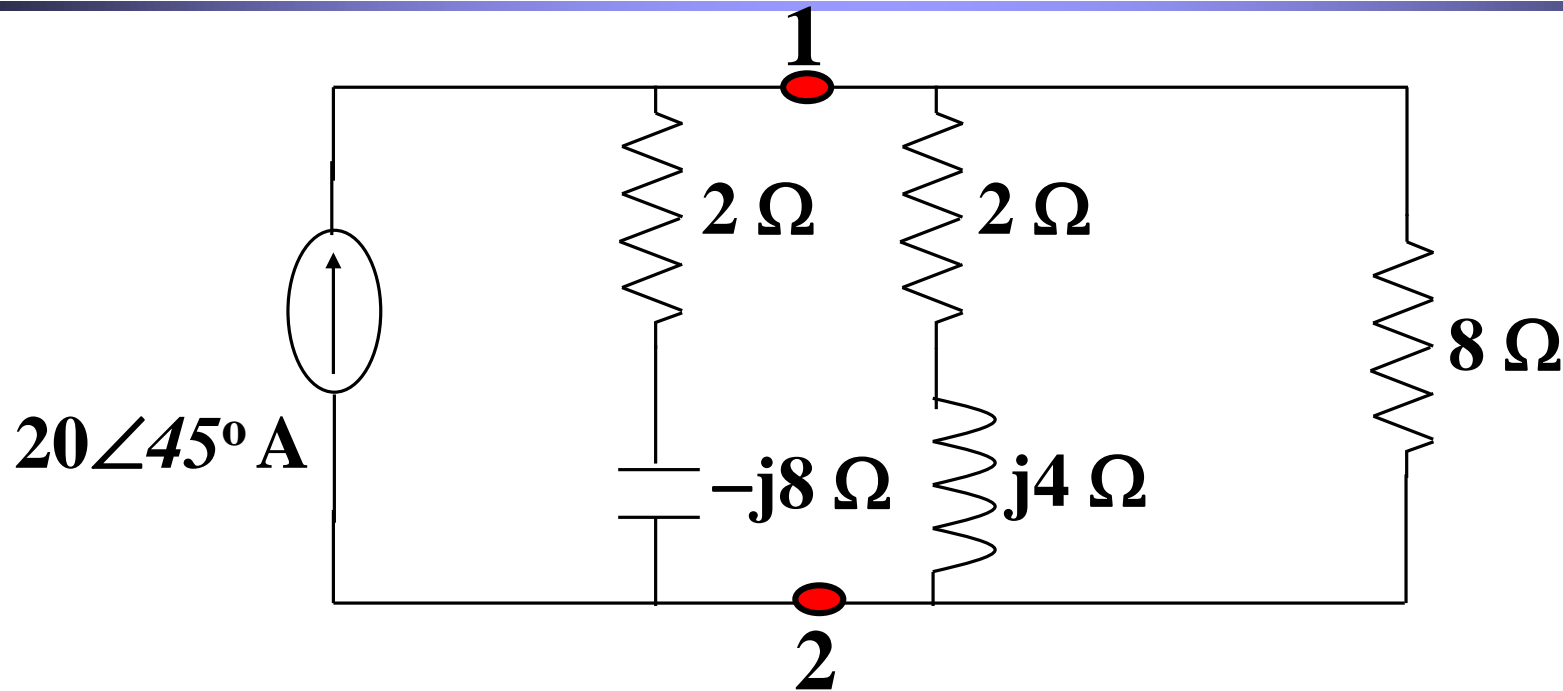

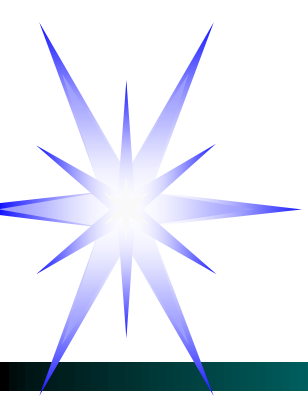Two nodes and taking node 2 as the reference, the admittance matrix is a 1 x 1 matrix.



## Example 1.6

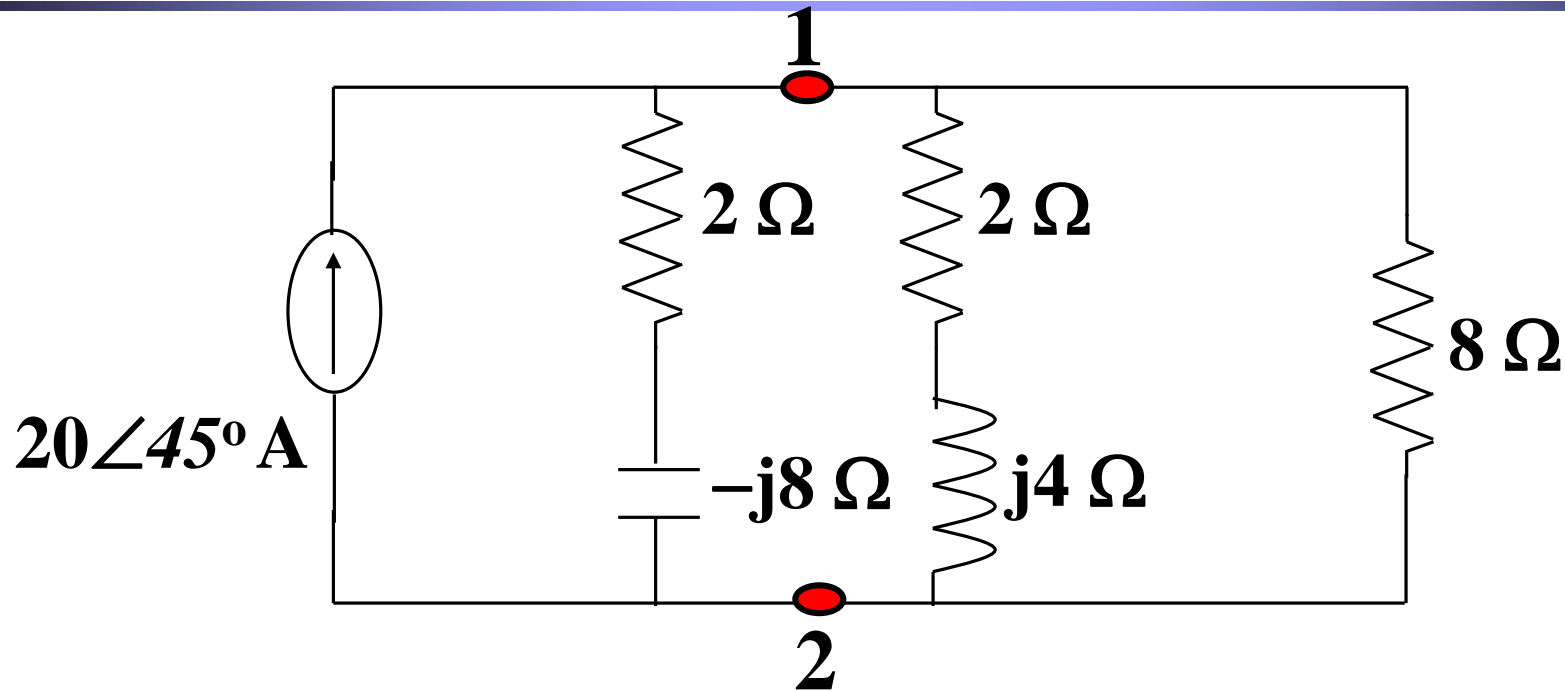

$$\left[ \frac{1}{2 - j8} + \frac{1}{2 + j4} + \frac{1}{8} \right] [V_1] = [20\angle 45^\circ]$$






## Example 1.6

$$\left[ \frac{1}{2 - j8} + \frac{1}{2 + j4} + \frac{1}{8} \right] V_1 = 20 \angle 45^\circ$$

$$\left[ \frac{1}{8.24 \angle -75.96^\circ} + \frac{1}{4.47 \angle 63.43^\circ} + 0.125 \right] V_1 = 20 \angle 45^\circ$$

$$[0.121 \angle 75.96^\circ + 0.224 \angle -63.43^\circ + 0.125] V_1 = 20 \angle 45^\circ$$
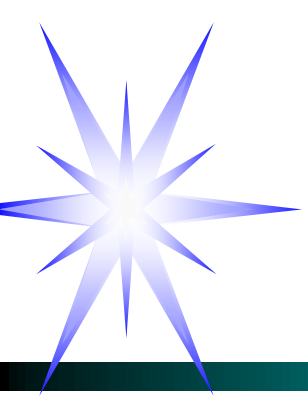
$$[0.029 + j0.117 + 0.1 - j0.2 + 0.125] V_1 = 20 \angle 45^\circ$$



## Example 1.6

$$(0.254 - j0.083)V_1 = 20\angle 45^\circ$$

$$\therefore V_1 = \frac{20\angle 45^\circ}{0.254 - j0.083} = \frac{20\angle 45^\circ}{0.267\angle -18.09^\circ} = 74.9\angle 63.09^\circ$$

$$\text{Hence } I_{8\Omega} = \frac{V_1}{8} = 9.36\angle 63.09^\circ \text{ A}$$

*...next topic*

## *Star-Delta & Delta-Star Transformation*

Nurturing Curious Minds, Producing Passionate Engineers

**Lee M L**

Office: T12A522

School of EEE

Tel: 6879-0657