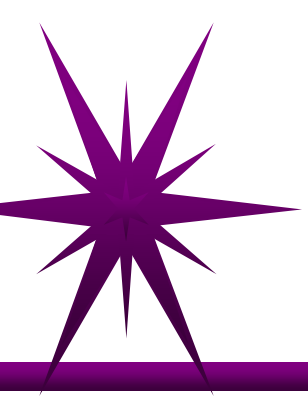



Circuit Theory & Analysis

Star-Delta and Delta-Star Transformation



Objectives

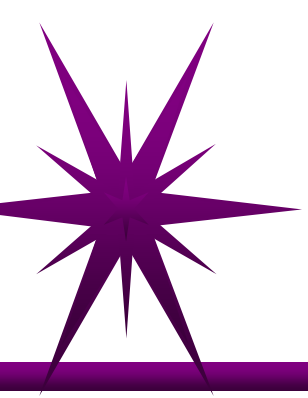- & Derive the relationships for star-delta and delta to star transformation.
- & Use star-delta and delta to star transformation to simplify the given circuit.




Star-Delta and Delta-Star Transformation

Star-Delta transformation is a mathematical tool where circuits connected in Star (Y) are converted into their Delta (Δ) equivalent, or vice versa.


$$Y \rightarrow \Delta$$

and

$$\Delta \rightarrow Y$$

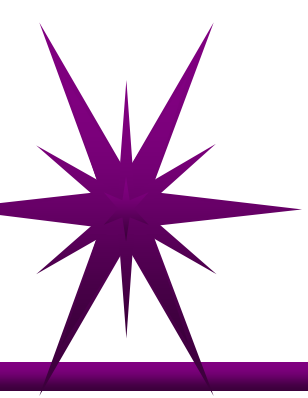


Star-Delta and Delta-Star Transformation

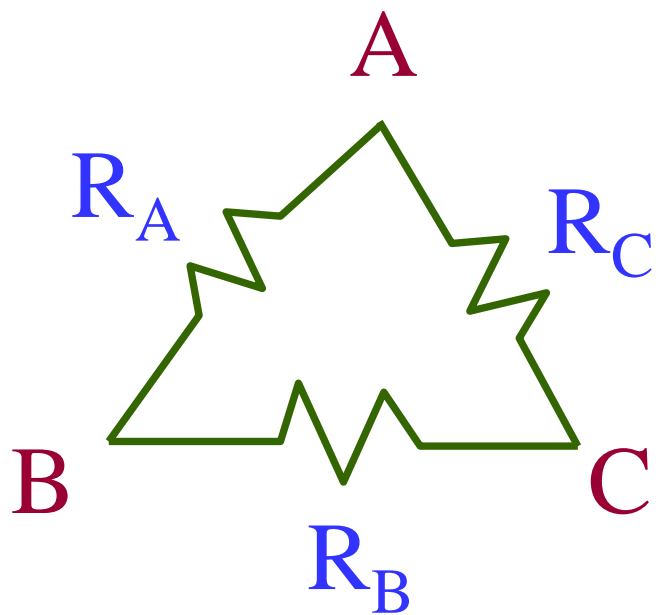


Delta circuit

\equiv

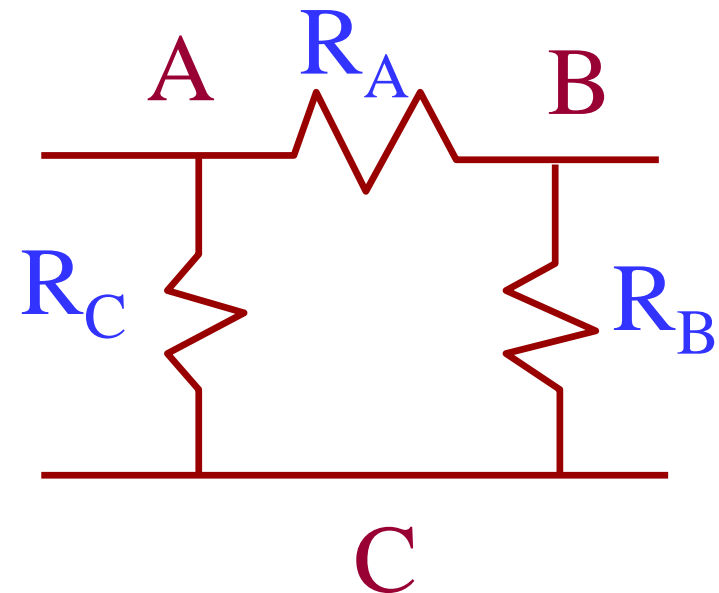


*also
called*


Π circuit

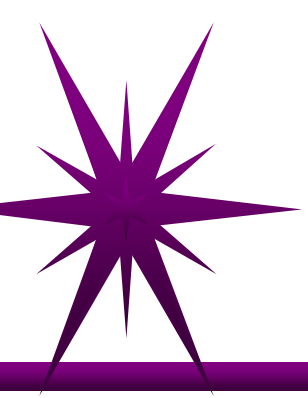

Star-Delta and Delta-Star Transformation

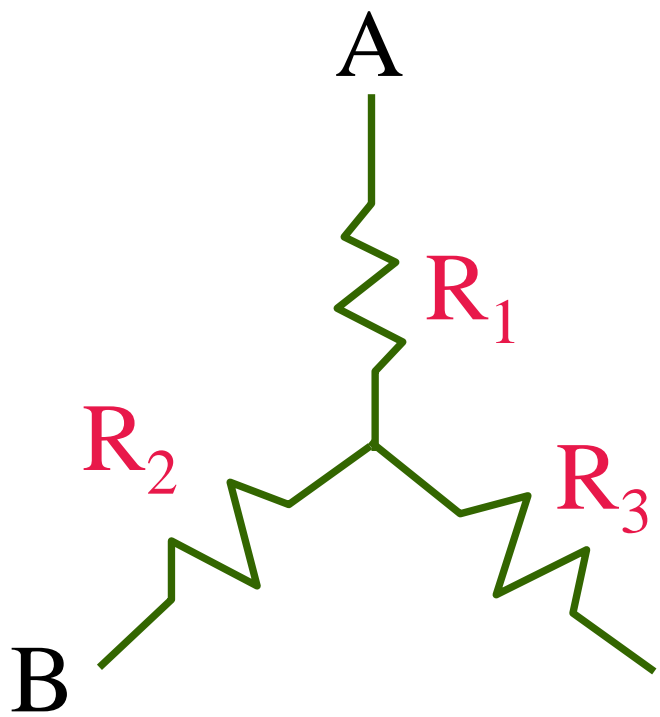


\equiv

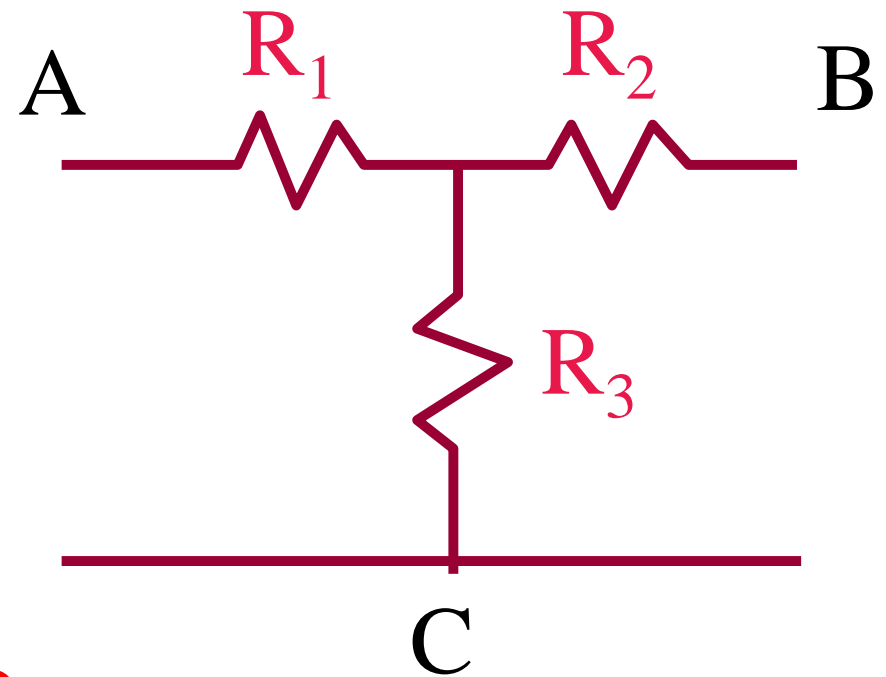


*also
called*

Star circuit


T circuit

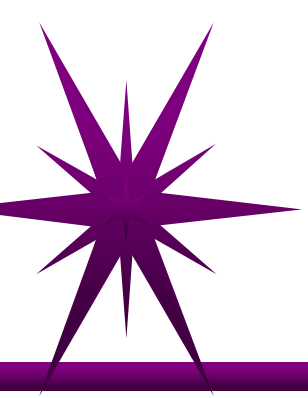


Star-Delta and Delta-Star Transformation

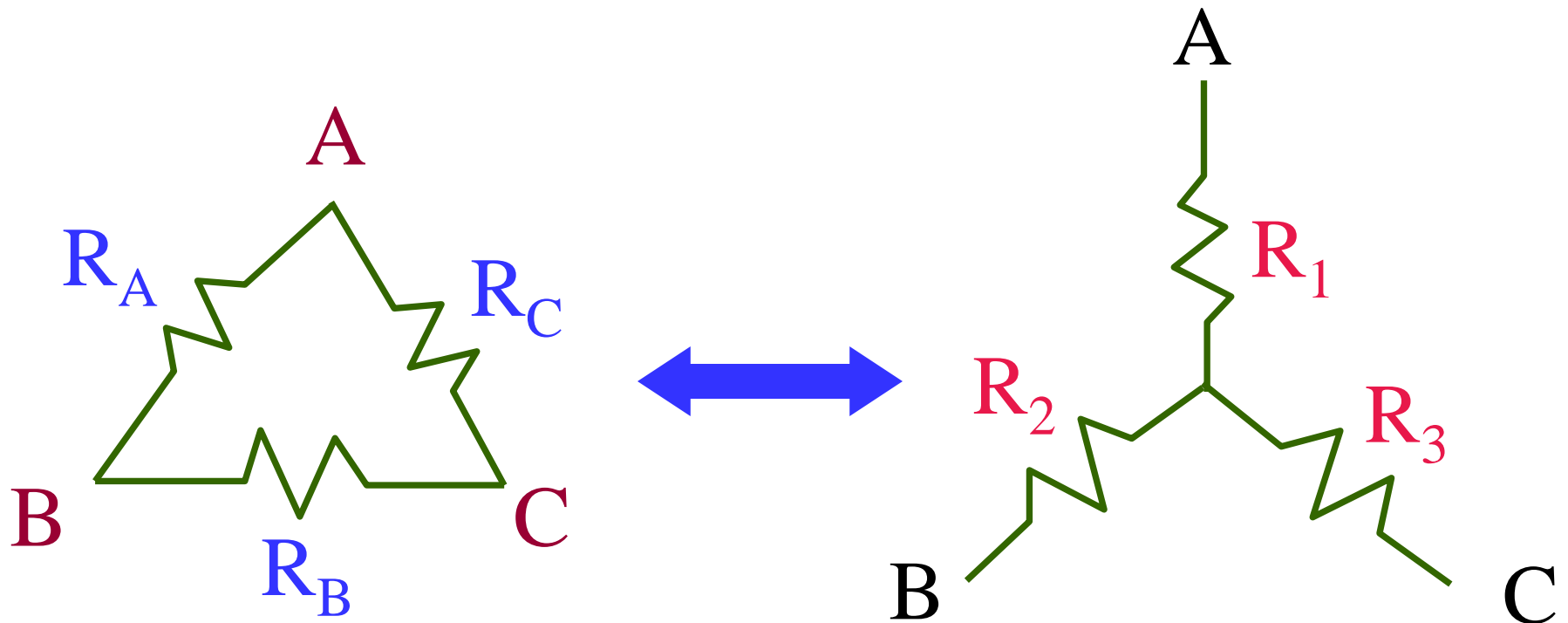

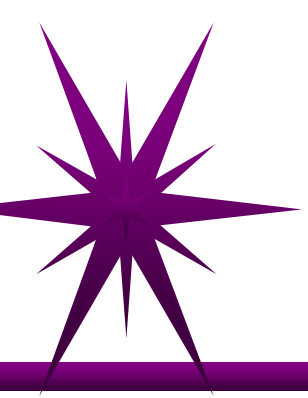
To make the Δ and the Y equivalent, the impedance across any two terminals in the Δ must be equal to that across the corresponding terminals in the Y.




Star-Delta and Delta-Star Transformation

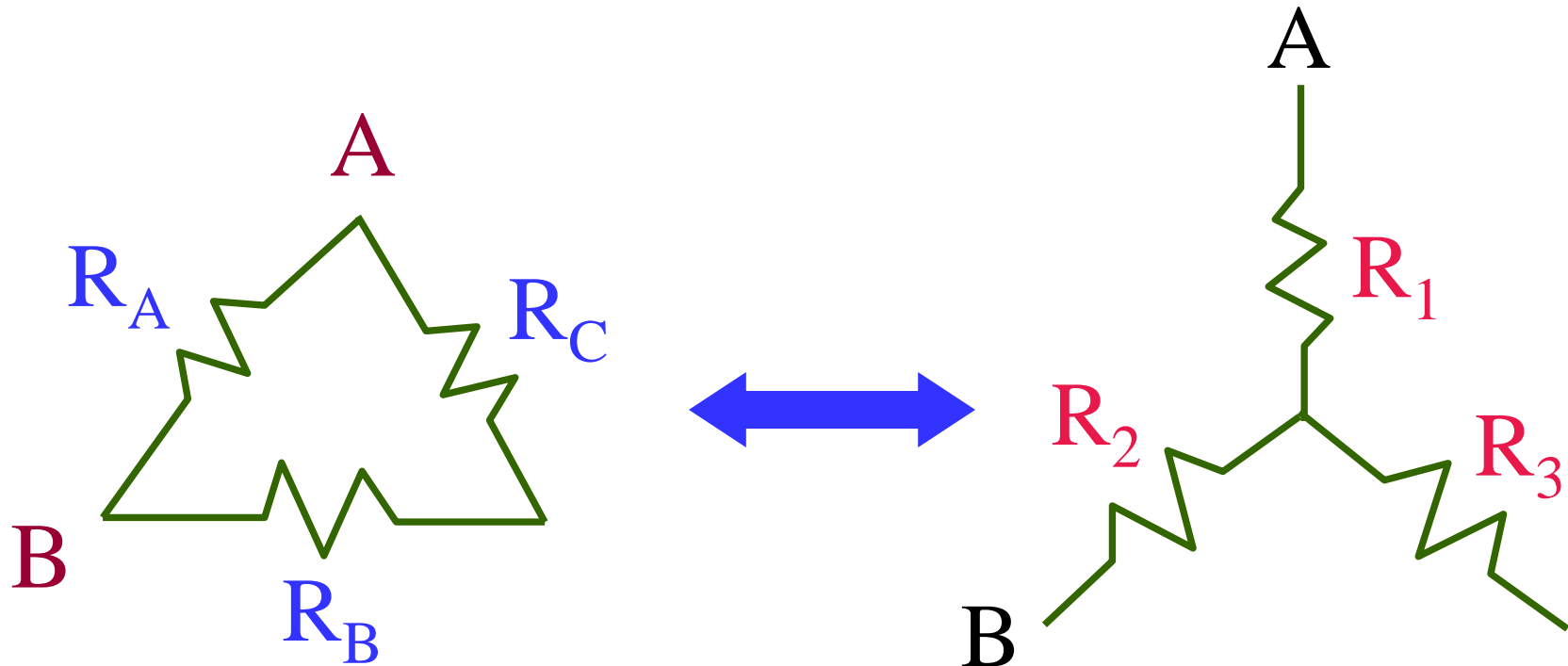

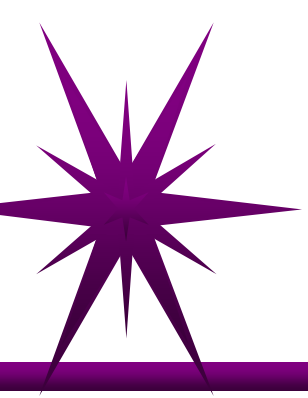
$$R_{AB} = R_A // (R_B + R_C) \text{ *Equals* } R_{AB} = R_1 + R_2$$
$$= \frac{R_A (R_B + R_C)}{R_A + R_B + R_C}$$




Star-Delta and Delta-Star Transformation

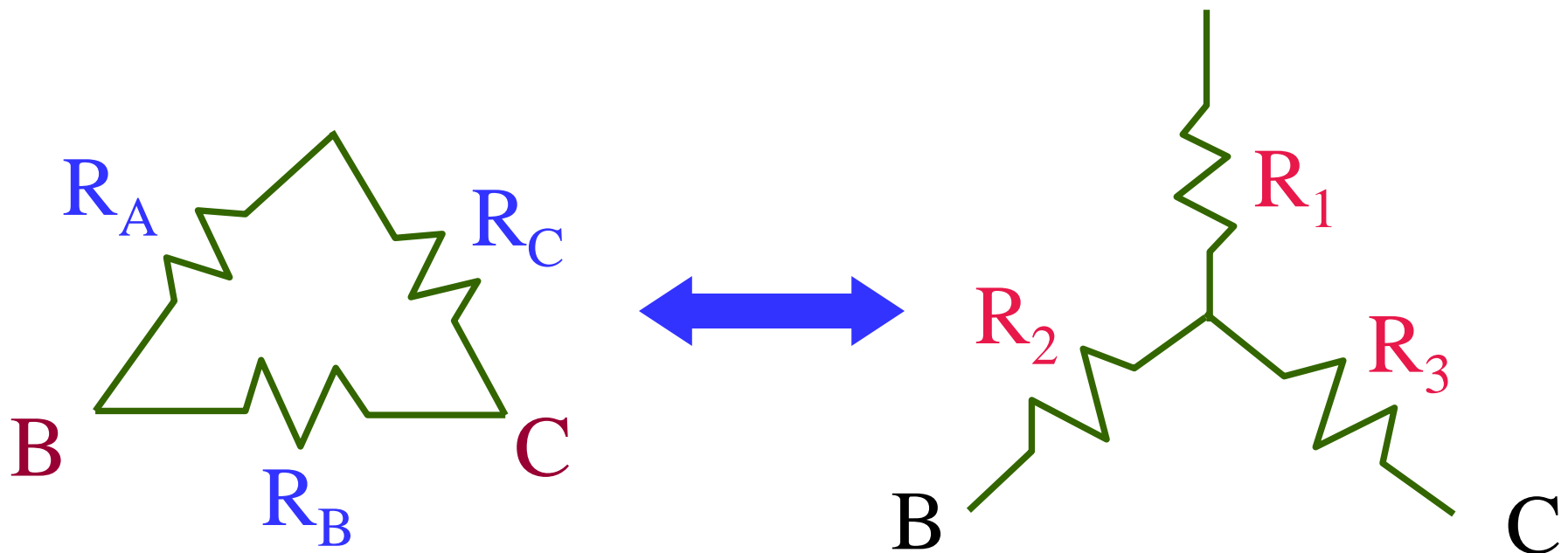

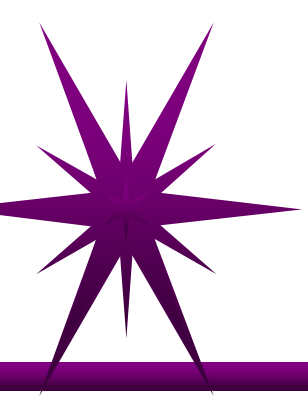
$$\mathbf{R_{BC} = R_B // (R_A + R_C) \text{ Equals } R_{BC} = R_2 + R_3}$$
$$= \frac{R_B (R_A + R_C)}{R_A + R_B + R_C}$$



Star-Delta and Delta-Star Transformation

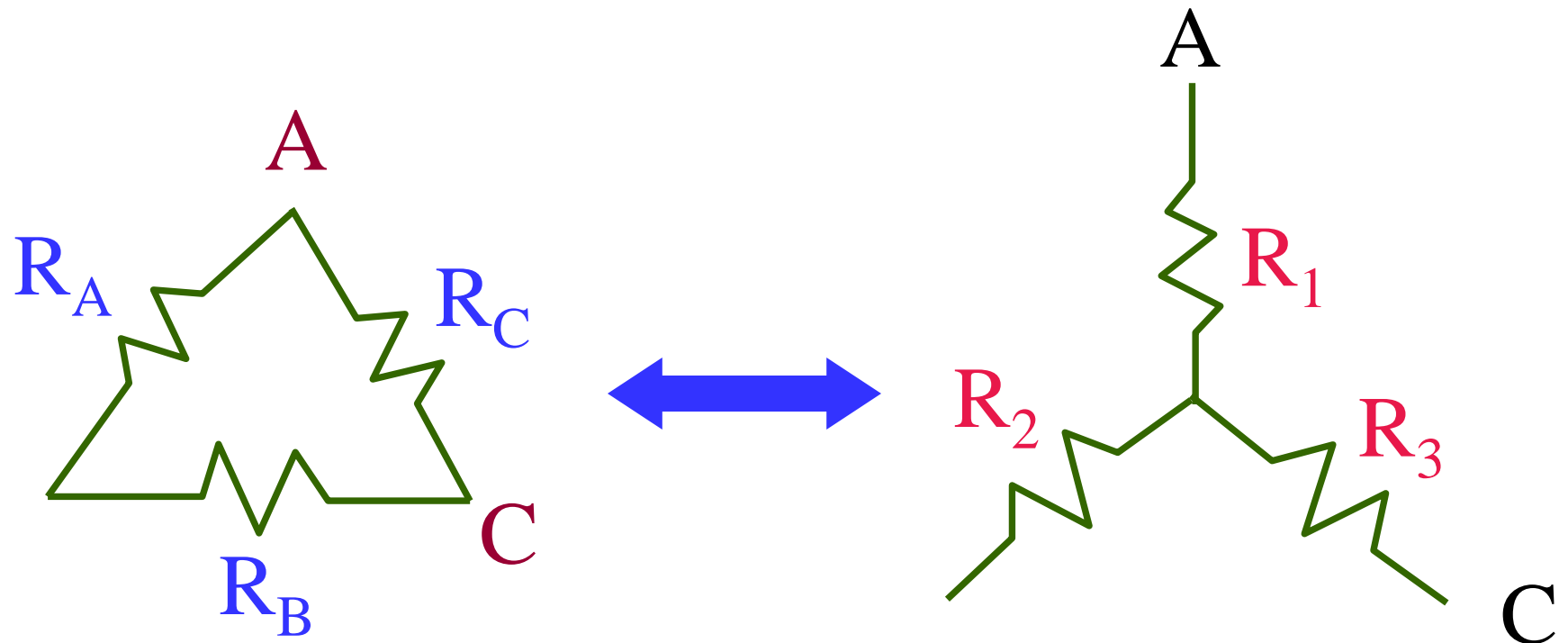

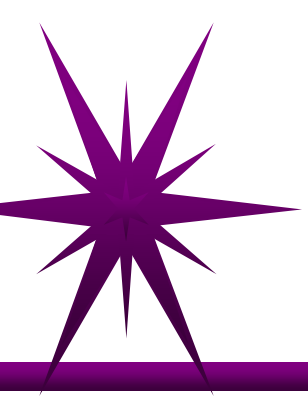
$$R_{CA} = R_C // (R_A + R_B) \text{ *Equals* } R_{CA} = R_1 + R_3$$
$$= \frac{R_C (R_A + R_B)}{R_A + R_B + R_C}$$



Star-Delta and Delta-Star Transformation

For the Δ and the Y to be equivalent, the following three equations must therefore be satisfied *at the same time*.

For terminals AB	$\frac{R_A R_B + R_A R_C}{R_A + R_B + R_C} = R_1 + R_2 \dots (12)$
For terminals BC	$\frac{R_A R_B + R_B R_C}{R_A + R_B + R_C} = R_2 + R_3 \dots (13)$
For terminals CA	$\frac{R_A R_C + R_B R_C}{R_A + R_B + R_C} = R_1 + R_3 \dots (14)$

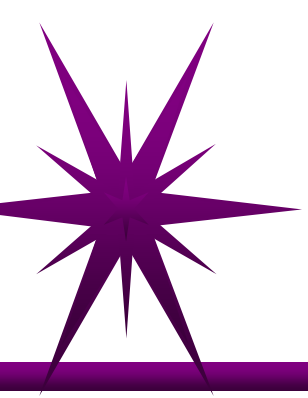

Delta-Star Transformation

Equations (12) - (13) + (14) results in


$$2R_1 = \frac{2R_A R_C}{R_A + R_B + R_C} \quad \text{or} \quad R_1 = \frac{R_A R_C}{R_A + R_B + R_C} \quad \dots(15)$$

Equations (13) - (14) + (12) results in


$$2R_2 = \frac{2R_A R_B}{R_A + R_B + R_C} \quad \text{or} \quad R_2 = \frac{R_A R_B}{R_A + R_B + R_C} \quad \dots(16)$$

Equations (14) - (12) + (13) results in
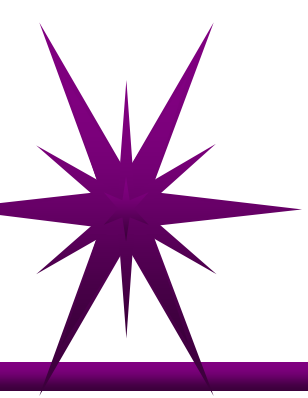
$$2R_3 = \frac{2R_B R_C}{R_A + R_B + R_C} \quad \text{or} \quad R_3 = \frac{R_B R_C}{R_A + R_B + R_C} \quad \dots(17)$$



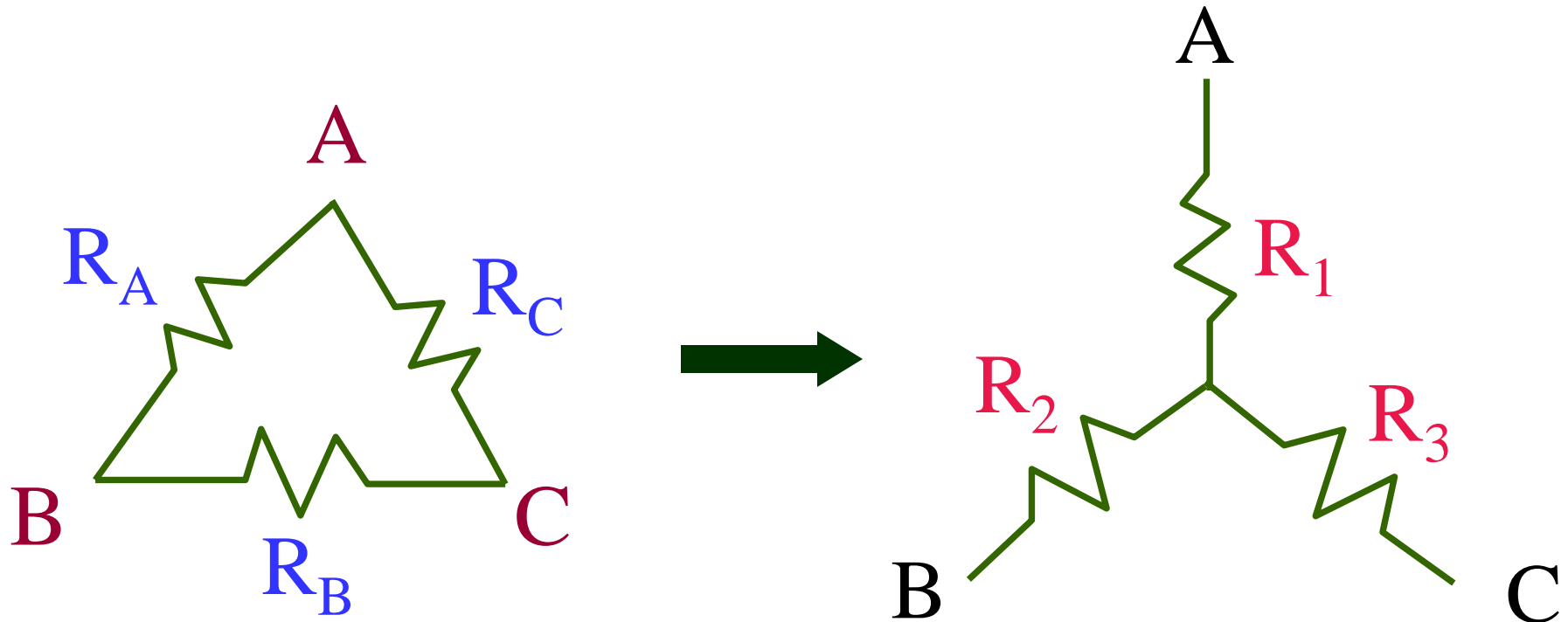
Equations for Delta to *Star* Transformation



$$R_1 = (R_A R_C) / (R_A + R_B + R_C) \dots (15)$$

$$R_2 = (R_A R_B) / (R_A + R_B + R_C) \dots (16)$$
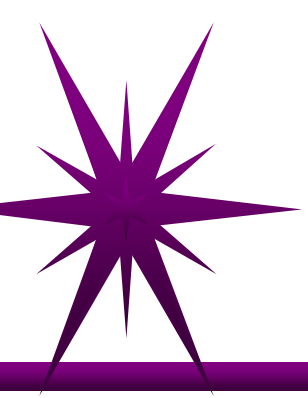
$$R_3 = (R_B R_C) / (R_A + R_B + R_C) \dots (17)$$



Star-Delta Transformation

Equations (17) divided by (15) will result in


$$R_B = \frac{R_A R_3}{R_1} \dots\dots\dots(18)$$

Equations (17) divided by (16) will result in

$$R_C = \frac{R_A R_3}{R_2} \dots\dots\dots(19)$$

Substituting (18) and (19) into (17) will result in
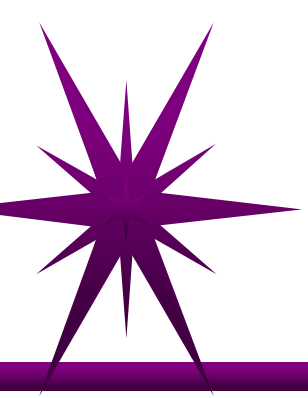
$$R_3 = \frac{\left(\frac{R_A R_3}{R_1}\right)\left(\frac{R_A R_3}{R_2}\right)}{R_A + \frac{R_A R_3}{R_1} + \frac{R_A R_3}{R_2}} = \frac{R_A^2 R_3^2}{R_A R_1 R_2 + R_A R_2 R_3 + R_A R_1 R_3}$$



Star-Delta Transformation


$$1 = \frac{R_A R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

$$R_A = R_1 + R_2 + \frac{R_1 R_2}{R_3} \dots\dots\dots(20)$$


Similarly with the same approach, we can solve for R_B and R_C .

$$R_B = R_2 + R_3 + \frac{R_2 R_3}{R_1} \dots\dots\dots(21)$$
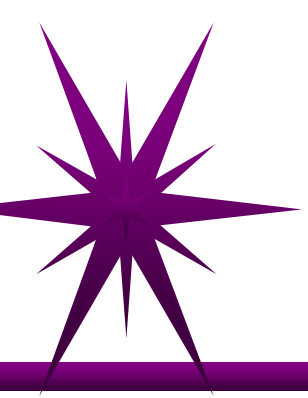
$$R_C = R_1 + R_3 + \frac{R_1 R_3}{R_2} \dots\dots\dots(22)$$



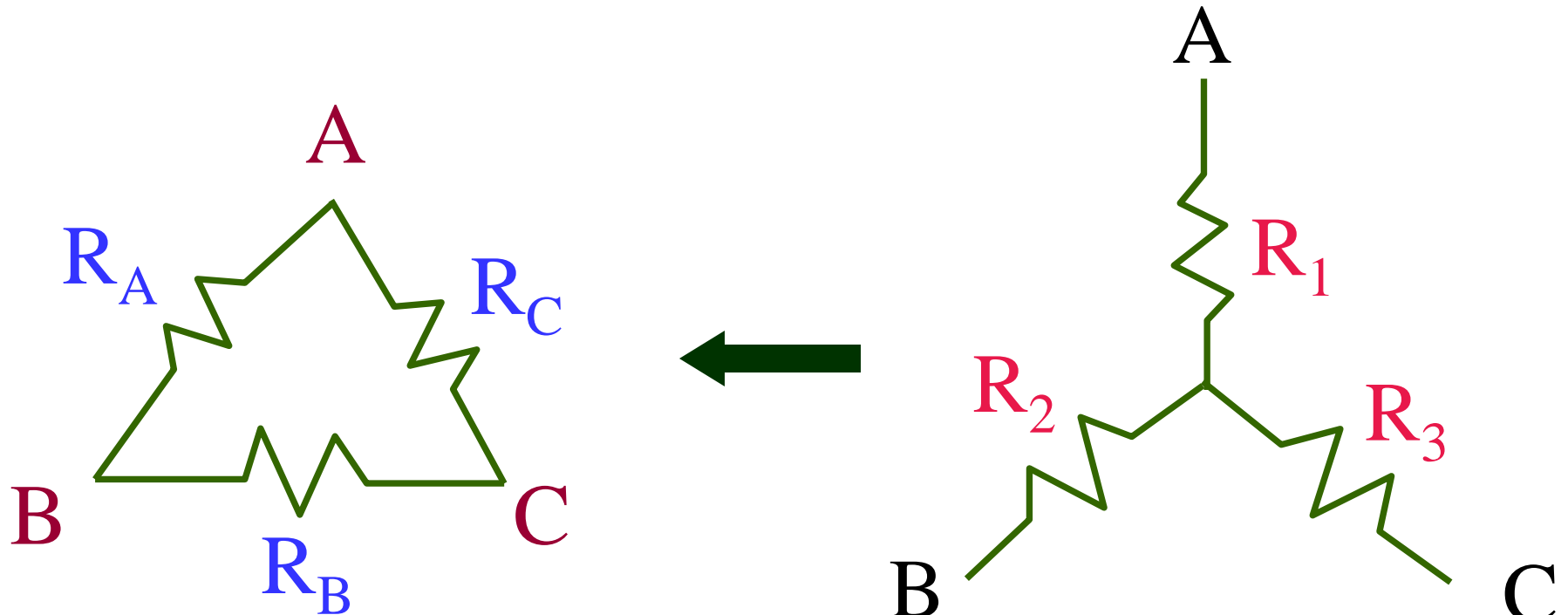Equations for *Star to Delta* Transformation



$$R_A = R_1 + R_2 + (R_1 R_2) / R_3 \dots\dots\dots(20)$$


$$R_B = R_2 + R_3 + (R_2 R_3) / R_1 \dots\dots\dots(21)$$

$$R_C = R_1 + R_3 + (R_1 R_3) / R_2 \dots\dots\dots(22)$$



Summary of transformation rules:

Delta to star

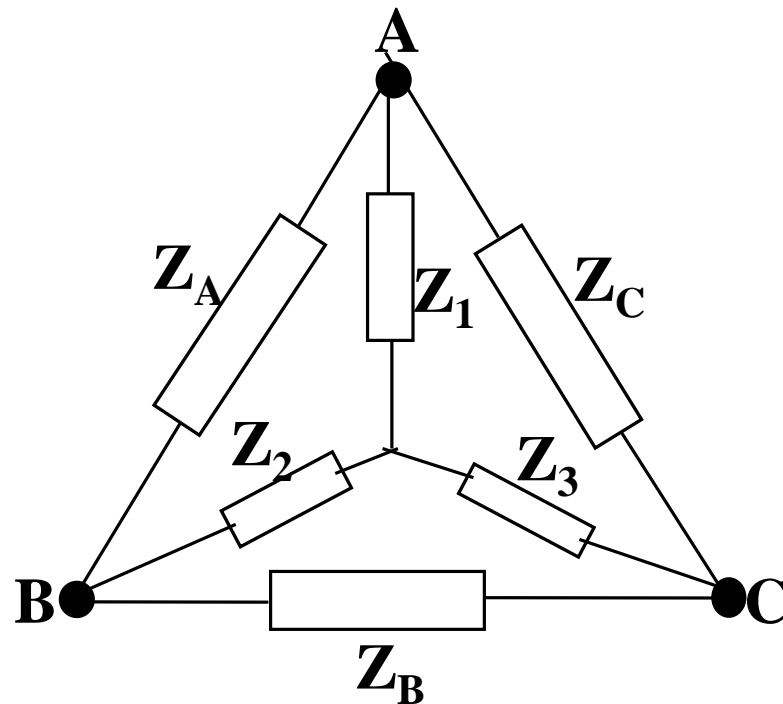

$$Z_1 = \frac{Z_A Z_C}{Z_A + Z_B + Z_C}$$


$$Z_2 = \frac{Z_A Z_B}{Z_A + Z_B + Z_C}$$

$$Z_3 = \frac{Z_B Z_C}{Z_A + Z_B + Z_C}$$



Summary of transformation rules:


Star to delta

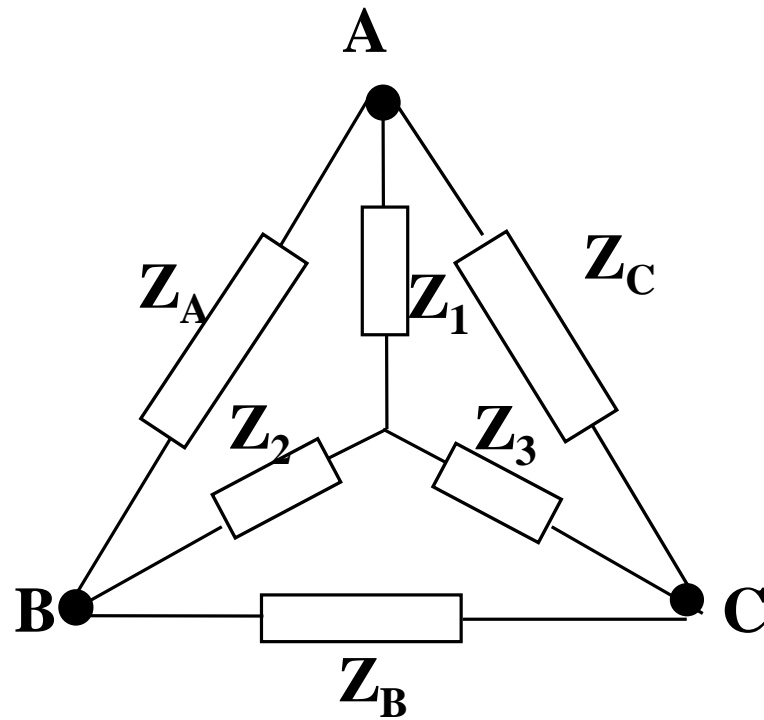


$$Z_A = Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3}$$

$$Z_B = Z_2 + Z_3 + \frac{Z_2 Z_3}{Z_1}$$
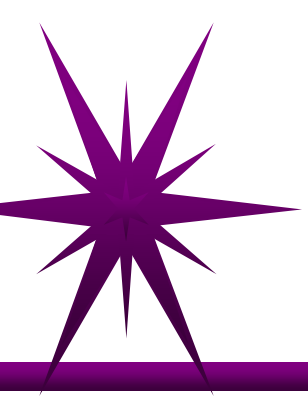
$$Z_C = Z_1 + Z_3 + \frac{Z_1 Z_3}{Z_2}$$



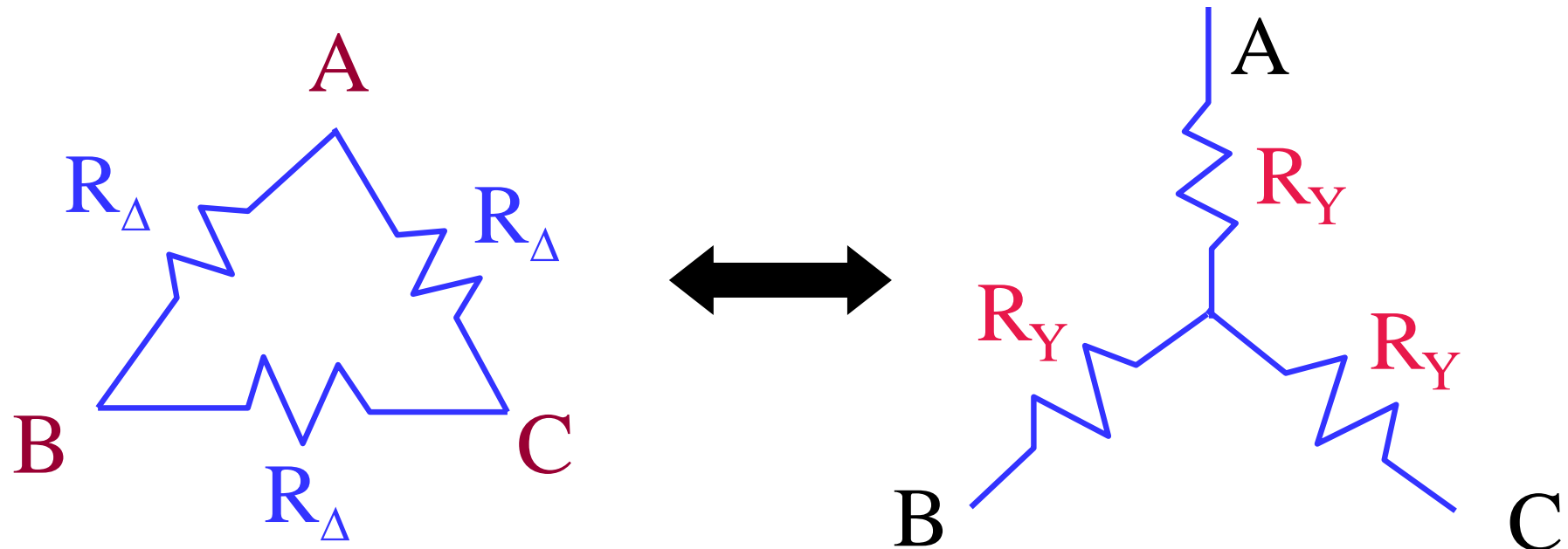Equations for Balanced Star to Delta or Balanced Delta to Star Transformation



When the Δ or the Y circuit is balanced


$$R_{\Delta} = R_Y + R_Y + (R_Y R_Y) / R_Y$$

$$\text{giving } R_{\Delta} = 3 R_Y \quad \text{or} \quad Z_{\Delta} = 3 Z_Y$$




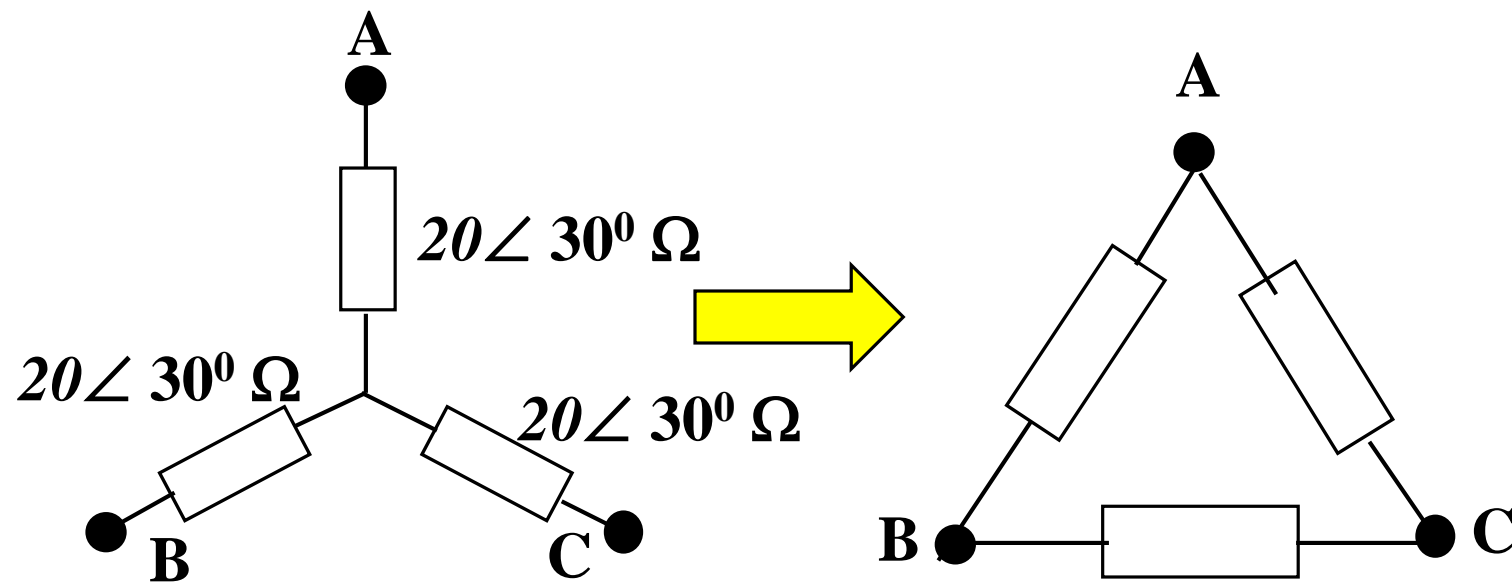Example 1.7


 Find the delta equivalent of the balanced star network.




✓ Solution: $Z_D = 3 \times Z_S = 3 \times 20 \angle 30^\circ \Omega = 60 \angle 30^\circ \Omega$

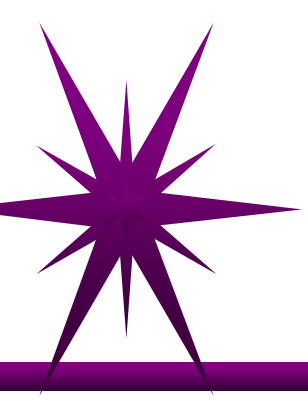


Example 1.8

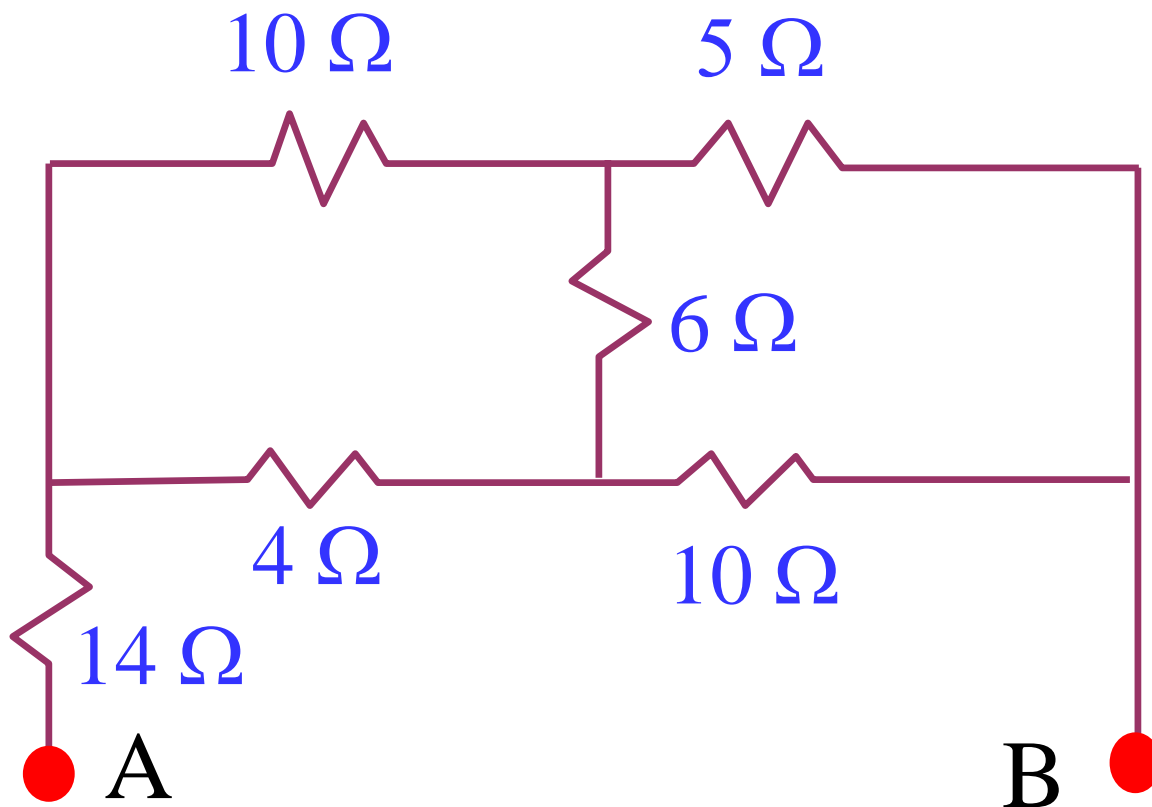

Find R_{AB}

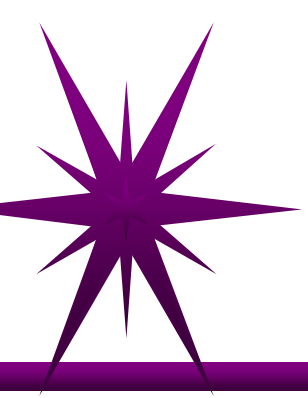

Example 1.8

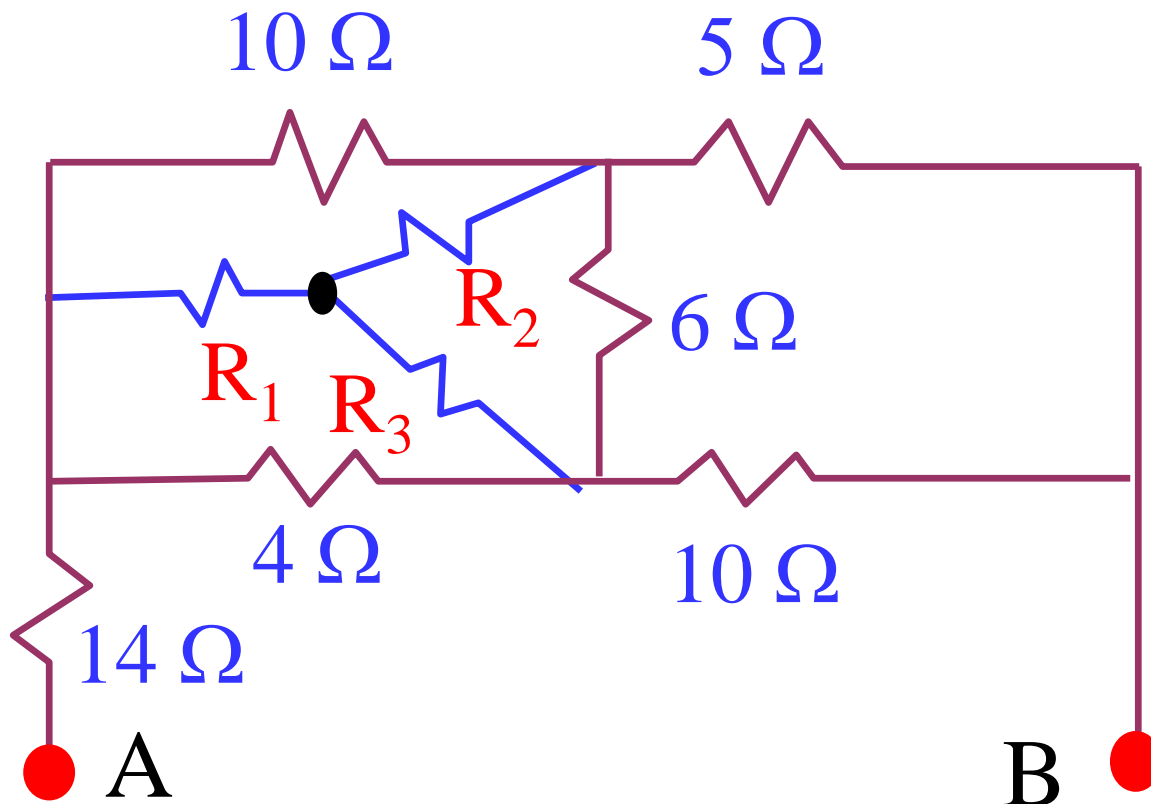


The Δ formed by the $10\ \Omega$, $6\ \Omega$ and $4\ \Omega$ resistors is transformed to Y formed by R_1 , R_2 and R_3


$$R_1 = (10 \times 4) / (10 + 6 + 4) = 2\ \Omega$$

$$R_2 = (10 \times 6) / (10 + 6 + 4) = 3\ \Omega$$


$$R_3 = (4 \times 6) / (10 + 6 + 4) = 1.2\ \Omega$$

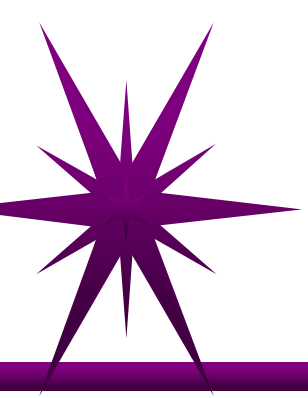


Example 1.8

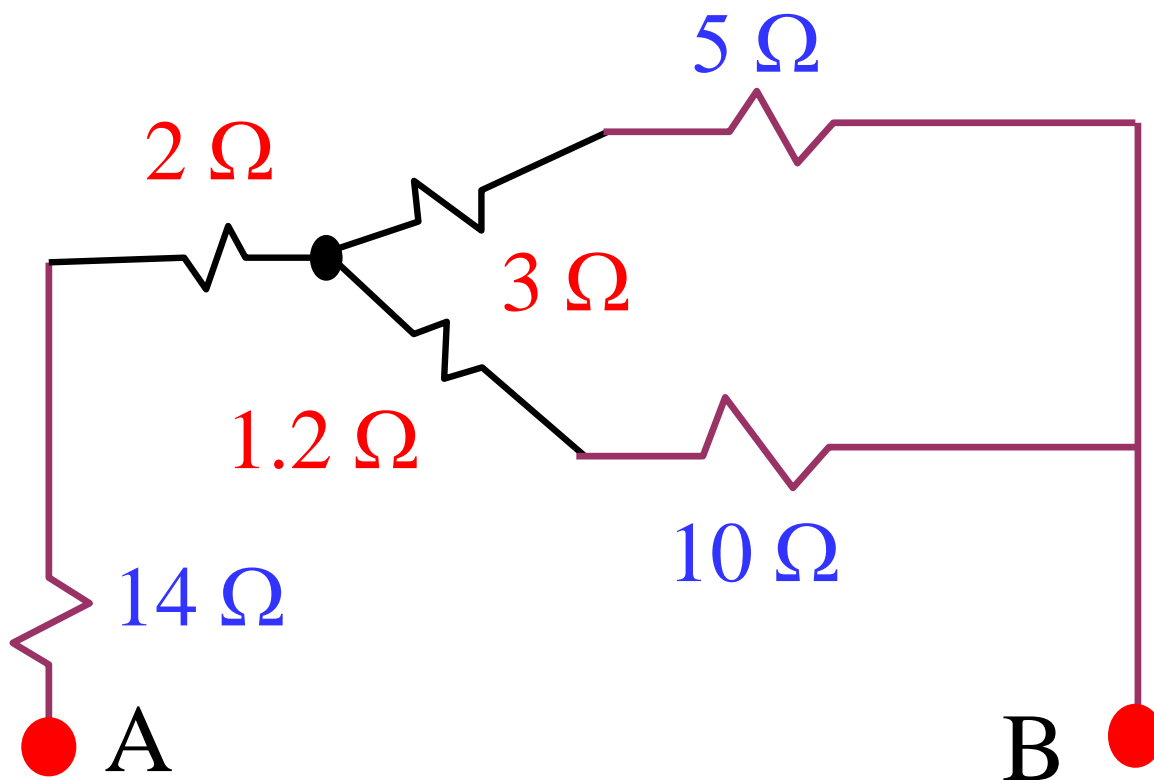


The $10\ \Omega$, $6\ \Omega$ and $4\ \Omega$ resistors in Delta are now replaced by the R_1 , R_2 and R_3 in Star

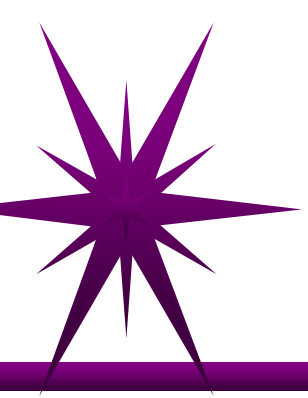


Example 1.8

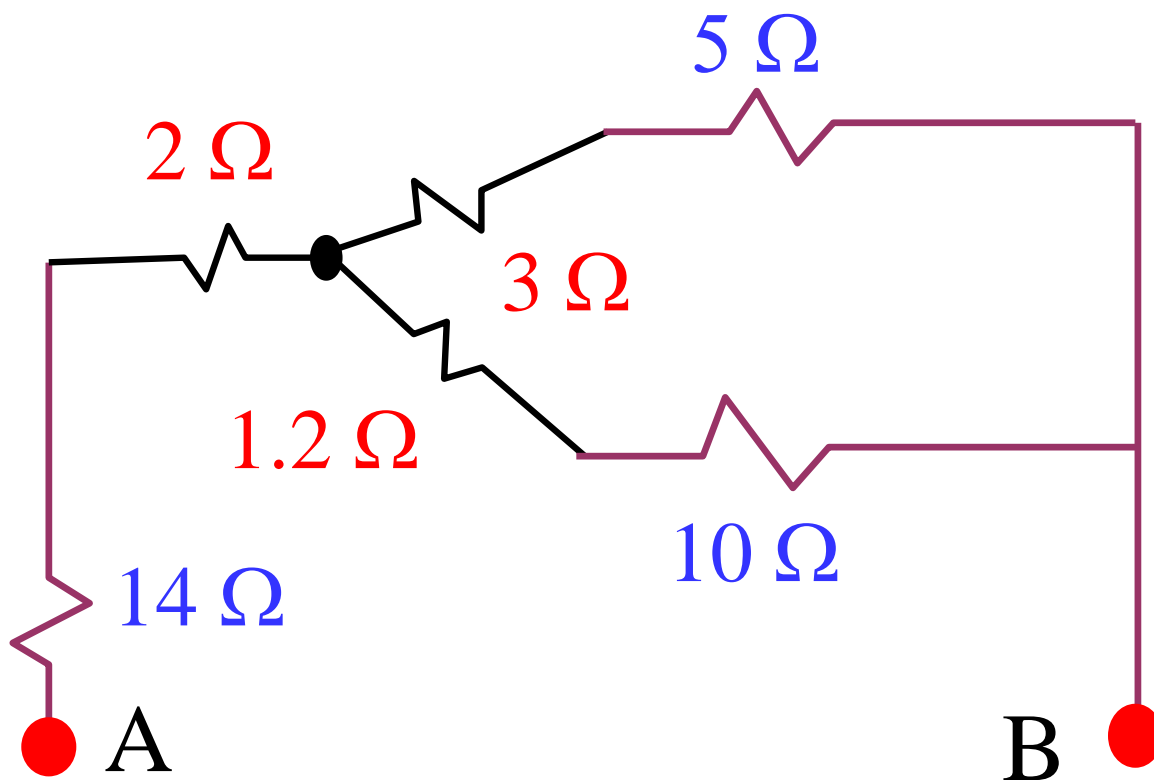


Now add the series resistors together, the circuit then becomes.....

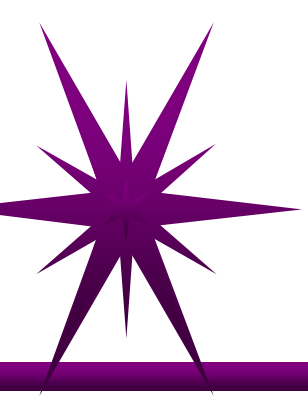

Example 1.8

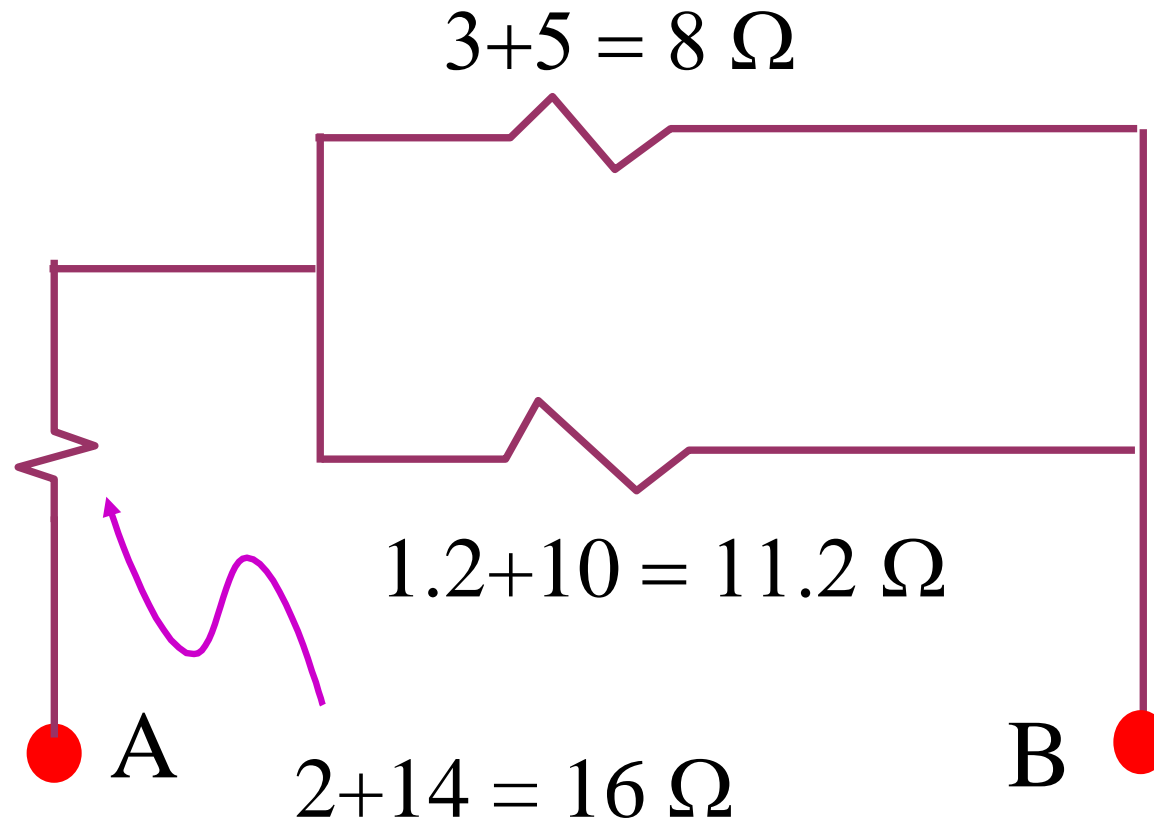

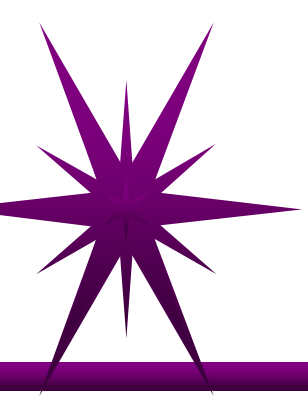
Finally, $R_{AB} = 16 + (8 // 11.2) = 20.67 \, \Omega$




Tutorial 3, Question 1

A network is arranged as shown in Figure 1. Calculate the equivalent resistance between A & C using star-delta transformation.

Figure 1

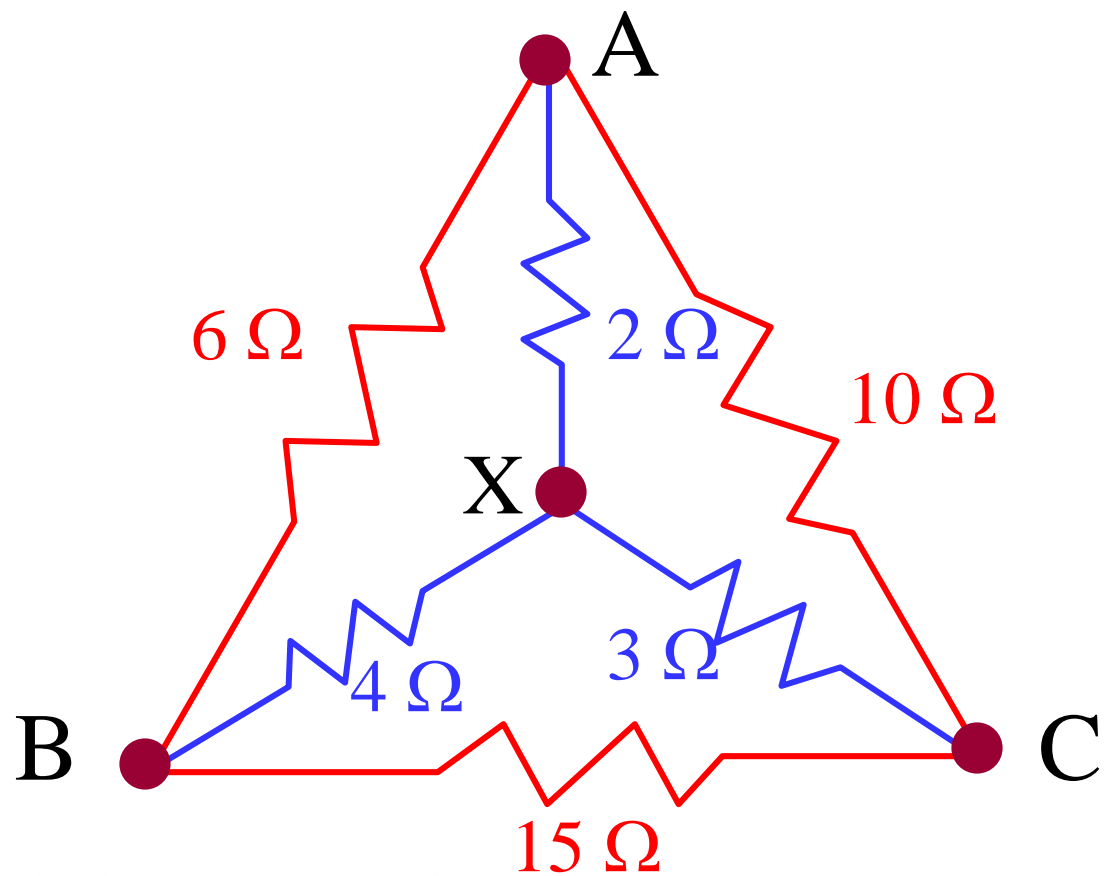

Tutorial 3, Question 1

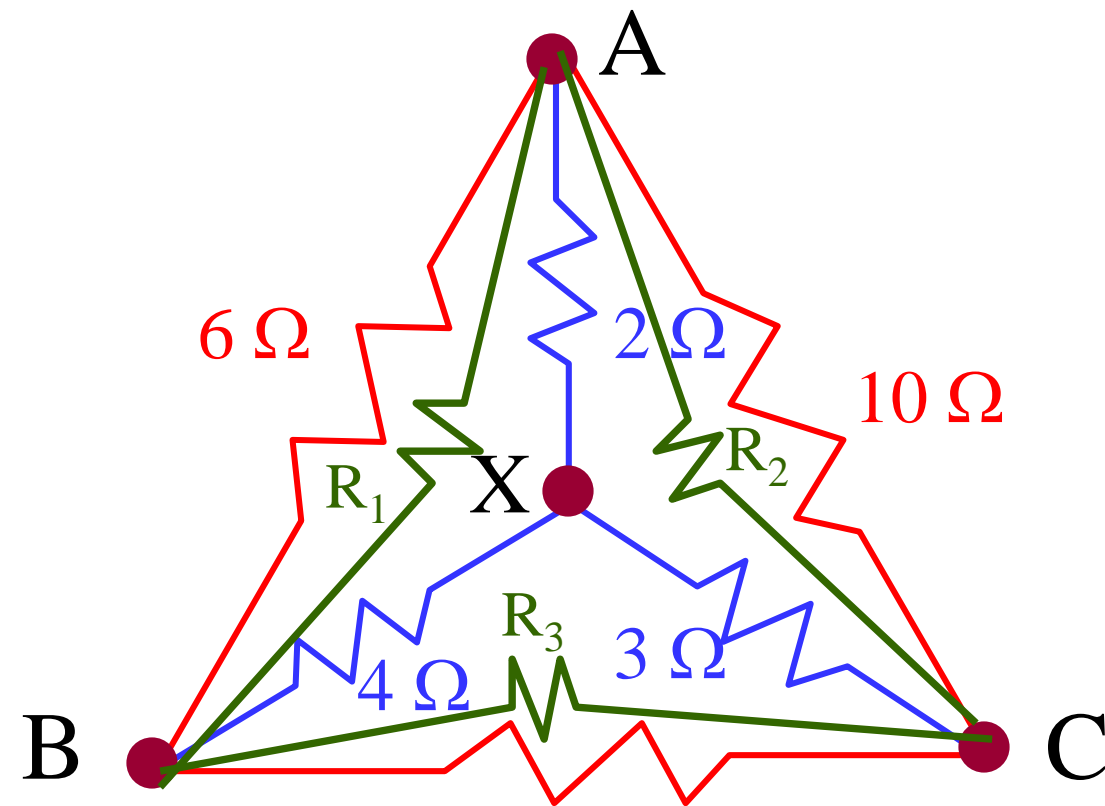


Transform the **blue** star into the **green** delta.

$$\begin{aligned} \mathbf{R}_1 &= 2 + 4 + (2 \times 4) / 3 \\ &= 8.667 \, \Omega \end{aligned}$$

$$\begin{aligned} \mathbf{R}_2 &= 2 + 3 + (2 \times 3) / 4 \\ &= 6.5 \, \Omega \end{aligned}$$

$$\begin{aligned} \mathbf{R}_3 &= 3 + 4 + (3 \times 4) / 2 \\ &= 13 \, \Omega \end{aligned}$$

Tutorial 3, Question 1

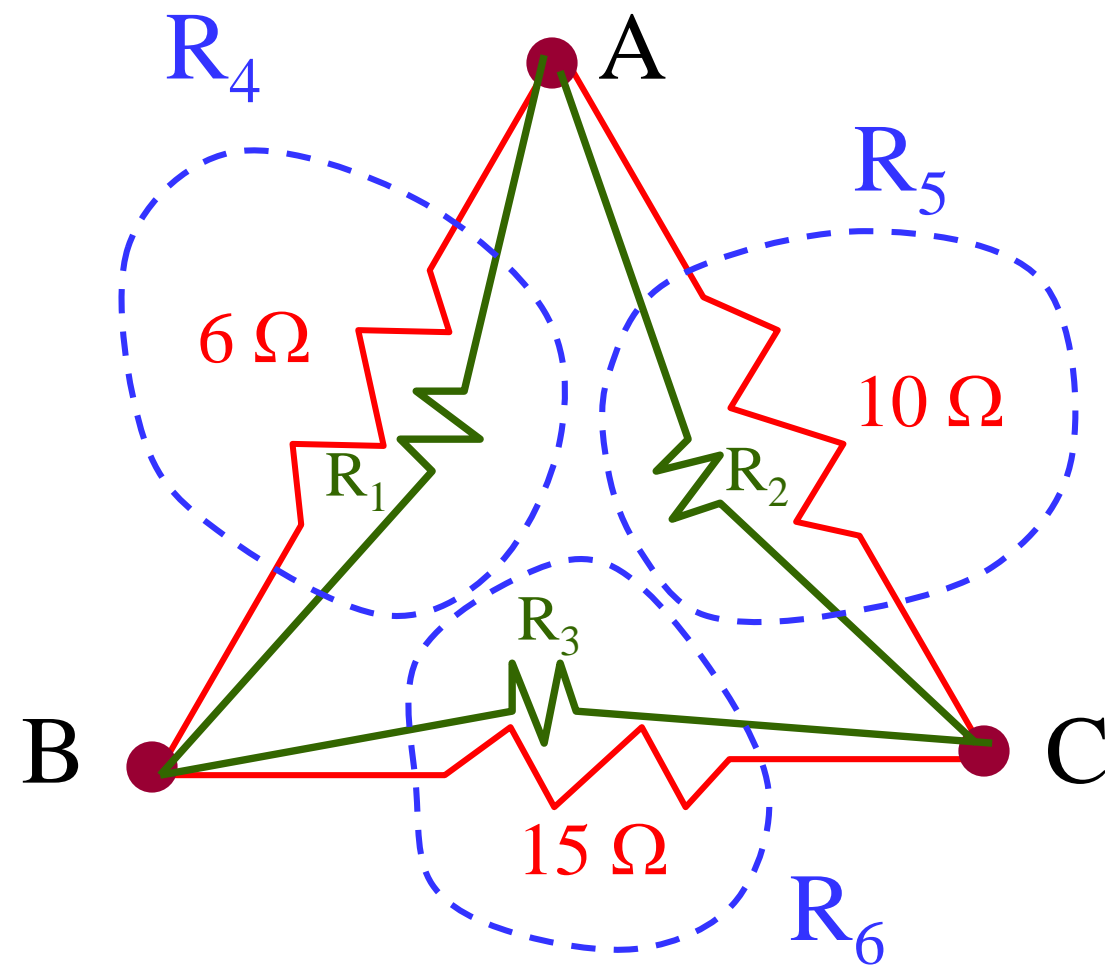


Now the $6\ \Omega$ resistor is parallel to R_1 . Similarly for the $10\ \Omega$ & R_2

and $15\ \Omega$ & R_3


$$R_4 = (6 \times 8.667) / (6 + 8.667) = 3.55\ \Omega$$

$$R_5 = (10 \times 6.5) / (10 + 6.5) = 3.94\ \Omega$$
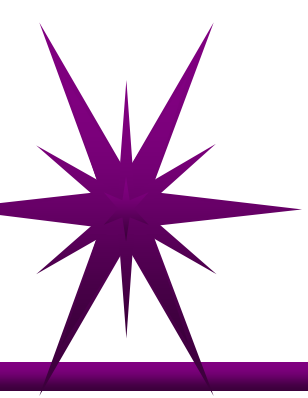
$$R_6 = (15 \times 13) / (15 + 13) = 6.96\ \Omega$$



Tutorial 3, Question 1

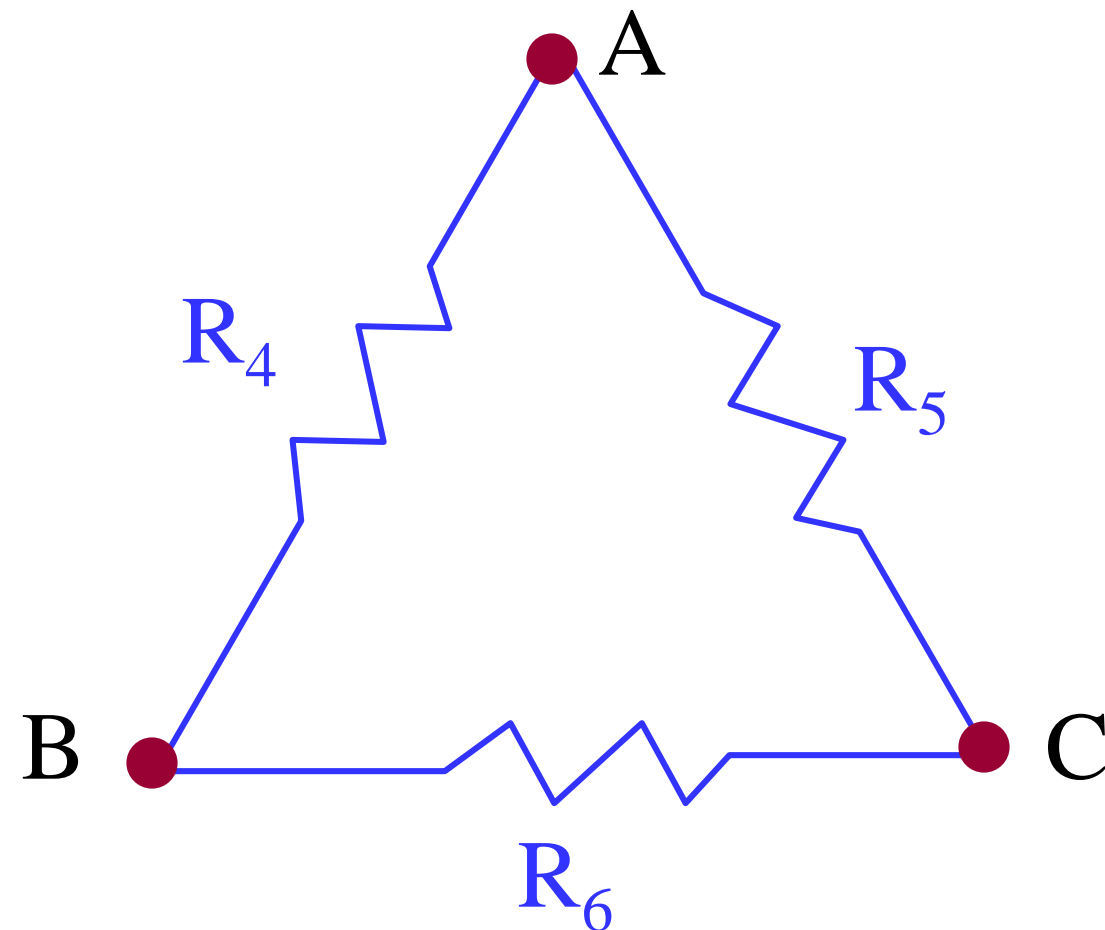


And the circuit becomes


$$R_4 = 3.55 \, \Omega$$

$$R_5 = 3.94 \, \Omega$$

$$R_6 = 6.96 \, \Omega$$

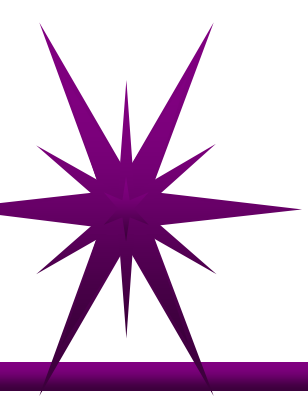

Tutorial 3, Question 1

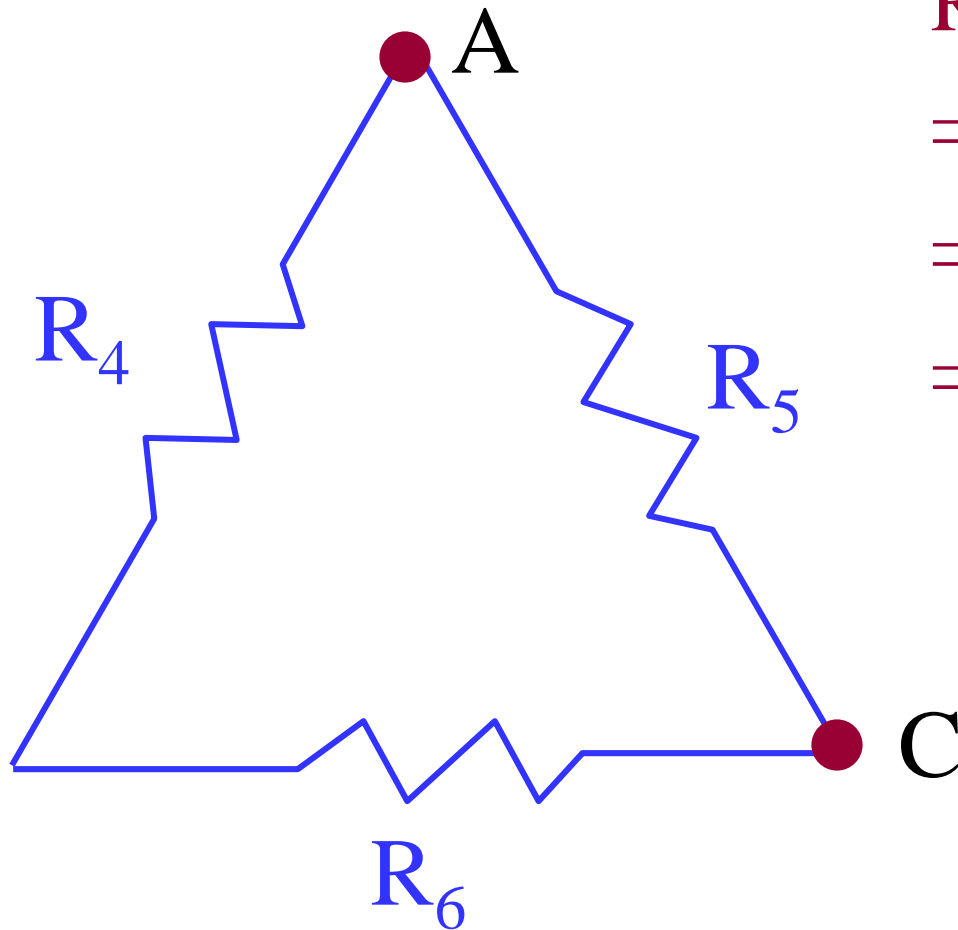

$$\begin{aligned} \text{Resistance between A \& C} \\ &= (R_4 + R_6) // R_5 \\ &= 10.51 \times 3.94 / (10.51 + 3.94) \\ &= 2.86 \, \Omega \end{aligned}$$

...next topic

Thevenin's Theorem

Nurturing Curious Minds, Producing Passionate Engineers

Lee M L

Office: T12A522

School of EEE

Tel: 6879-0657