Formulae

Energy, Work Done, Charge, Power:

$$W = QV$$

$$P = \frac{W}{t} \qquad \qquad I = \frac{Q}{t}$$

$$I = \frac{Q}{t}$$

The maximum of number of electrons in a shell (band) = $2N^2$

 6.25×10^{18} electrons $\rightarrow 1C$ of negative charge

Diodes:

Forward voltage drop V_F is 0.7 V for silicon diode and 0.3 V for germanium diode

Zener dynamic resistance
$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z}$$

AC Voltages and Currents:

$$I_{rms} = I_p / \sqrt{2} = 0.7071 I_p$$

$$I_{p-p}=2I_p$$

$$I_{avg} = 2I_{p} / \pi = 0.637I_{p}$$

$$V_{rms} = V_p / \sqrt{2} = 0.7071 V_p$$
 $V_{p-p} = 2V_p$

$$V_{p-p} = 2V_1$$

$$V_{avg} = 2V_p / \pi = 0.637 V_p$$

Half-Wave Rectifier:

$$V_{out(p)} = V_{\sec(p)} - 0.7V$$
 $V_{AVG} = \frac{V_{out(p)}}{\pi}$ $PIV = V_{\sec(p)}$

$$V_{AVG} = \frac{V_{out(p)}}{\pi}$$

$$PIV = V_{\sec(p)}$$

Centre-Tapped Full-Wave Rectifier:

$$V_{out(p)} = \frac{V_{sec(p)}}{2} - 0.7V$$

$$V_{out(p)} = \frac{V_{sec(p)}}{2} - 0.7V$$
 $V_{AVG} = \frac{2V_{out(p)}}{\pi}$ $PIV = 2V_{out(p)} + 0.7V$

Full-Wave Bridge Rectifier:

$$V_{out(p)} = V_{\sec(p)} - 1.4 \ V \ V_{AVG} = \frac{2V_{out(p)}}{\pi} \ PIV = V_{out(p)} + 0.7 \ V$$

$$PIV = V_{out(p)} + 0.7 V$$

Ripple Factor:

$$r = \frac{V_{r(rms)}}{V_{DC}}$$
 where $V_{r(rms)} = \frac{V_{r(p-p)}}{2\sqrt{3}}$

Line Regulation =
$$\left(\frac{\Delta V_{OUT}}{\Delta V_{IN}}\right)$$
100%

$$\textbf{Line Regulation} = \left(\frac{\Delta V_{OUT}}{\Delta V_{IN}}\right) 100\% \qquad \textbf{Load Regulation} = \left(\frac{V_{NL} - V_{FL}}{V_{FL}}\right) 100\%$$

Transistors:

$$\begin{split} I_E &= I_C + I_B \quad \beta_{DC} = \frac{I_C}{I_B} \quad \alpha_{DC} = \frac{I_C}{I_E} \quad \beta_{DC} = \frac{\alpha_{DC}}{1 - \alpha_{DC}} \\ V_{BE} &= 0.7V \quad V_{CC} = V_{CE} + I_C R_C \\ V_{BB} &= V_{BE} + I_B R_B \quad V_{CE} = V_{CB} + V_{BE} \end{split}$$

$$V_{BB} = V_{BE} + I_B R_B$$

$$egin{aligned} oldsymbol{v}_{CC} &= oldsymbol{v}_{CE} + oldsymbol{I}_{CI} \ oldsymbol{V}_{CE} &= oldsymbol{V}_{CR} + oldsymbol{V}_{RE} \end{aligned}$$