

Formulae List

The maximum number of electrons in a shell (band) = $2N^2$

6.25×10^{18} electrons \rightarrow 1C of negative charge

Ohm's Law for ac:

$$\bar{V} = \bar{I}\bar{Z} \quad \bar{I} = \frac{\bar{V}}{\bar{Z}} = \bar{V}\bar{Y} \quad \bar{Z} = \frac{\bar{V}}{\bar{I}}$$

Capacitors:

Capacitive reactance, $X_C = \frac{1}{2\pi fC}$ in ohms

Inductors:

Inductive reactance, $X_L = 2\pi fL$ in ohms

AC Voltages and Currents:

$$I_{rms} = I_p / \sqrt{2} = 0.7071 I_p$$

$$I_{p-p} = 2I_p$$

$$I_{av} = 2I_p / \pi = 0.637I_p$$

$$V_{rms} = V_p / \sqrt{2} = 0.7071 V_p$$

$$V_{p-p} = 2V_p$$

$$V_{av} = 2V_p / \pi = 0.637V_p$$

AC Impedance/Admittance:

Series circuit,

$$\bar{Z}_R = R \quad \bar{Z}_C = -jX_C = -j\frac{1}{\omega C} = \frac{1}{\omega C} \angle -90^\circ \quad \bar{Z}_L = jX_L = j\omega L = \omega L \angle 90^\circ \quad \omega = 2\pi f$$

$$\bar{Z} = \bar{Z}_1 + \bar{Z}_2 + \bar{Z}_3 + \dots \quad \phi = \angle \bar{Z} = \angle \bar{I} = \tan^{-1} \frac{X_{tot}}{R_{tot}}$$

Parallel circuit,

$$\bar{Y}_R = G \quad \bar{Y}_C = jB_C = j\omega C = \omega C \angle 90^\circ \quad \bar{Y}_L = -jB_L = -j\frac{1}{\omega L} = \frac{1}{\omega L} \angle -90^\circ \quad \omega = 2\pi f$$

$$\bar{Y} = \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 + \dots \quad \phi = \angle \bar{Y} = \angle \bar{V}_S = \tan^{-1} \frac{B_{tot}}{G_{tot}}$$

AC Power:

$$S = V_S I = I^2 Z \quad P = V_S I \cos \phi = I^2 R \quad Q = V_S I \sin \phi = I^2 X \quad \cos \phi = \frac{P}{S}$$

Diodes:

Forward voltage drop is 0.7 V for silicon diode and 0.3 V for germanium diode

Zener impedance $Z_Z = \frac{\Delta V_Z}{\Delta I_Z}$

Half-Wave Rectifier:

$$V_{out(p)} = V_{sec(p)} - 0.7 V \quad V_{AVG} = \frac{V_{out(p)}}{\pi} \quad PIV = V_{sec(p)}$$

Centre-Tapped Full-Wave Rectifier:

$$V_{out(p)} = \frac{V_{sec(p)}}{2} - 0.7 V \quad V_{AVG} = \frac{2V_{out(p)}}{\pi} \quad PIV = 2V_{out(p)} + 0.7 V$$

Full-Wave Bridge Rectifier:

$$V_{out(p)} = V_{sec(p)} - 1.4 V \quad V_{AVG} = \frac{2V_{out(p)}}{\pi} \quad PIV = V_{out(p)} + 0.7 V$$

Ripple Factor:

$$r = \frac{V_{r(rms)}}{V_{DC}} \text{ where } V_{r(rms)} = \frac{V_{r(p-p)}}{2\sqrt{3}}$$

$$\text{Line Regulation} = \left(\frac{\Delta V_{OUT}}{\Delta V_{IN}} \right) 100\% \quad \text{Load Regulation} = \left(\frac{V_{NL} - V_{FL}}{V_{FL}} \right) 100\%$$

Transistors:

$$I_E = I_C + I_B \quad \beta_{DC} = \frac{I_C}{I_B} \quad \alpha_{DC} = \frac{I_C}{I_E} \quad \beta_{DC} = \frac{\alpha_{DC}}{1 - \alpha_{DC}}$$

$$V_{BE} = 0.7V \quad V_{CC} = V_{CE} + I_C R_C$$

$$V_{BB} = V_{BE} + I_B R_B \quad V_{CE} = V_{CB} + V_{BE}$$

Operational Amplifiers

$$\text{Voltage Gain of Inverting Amplifier: } -\frac{R_f}{R_i}$$

$$\text{Voltage Gain of Non-inverting Amplifier: } 1 + \frac{R_f}{R_i}$$

Output voltage of summing amplifier:

$$V_O = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \dots + \frac{R_f}{R_n} V_n \right) \text{ for "n" inputs}$$

Threshold Voltages for comparator with positive feedback:

$$\text{Upper Trigger Point (UTP)} = \frac{R_2}{R_1 + R_2} (+V_{O[\max]})$$

$$\text{Lower Trigger Point (LTP)} = \frac{R_2}{R_1 + R_2} (-V_{O[\max]})$$