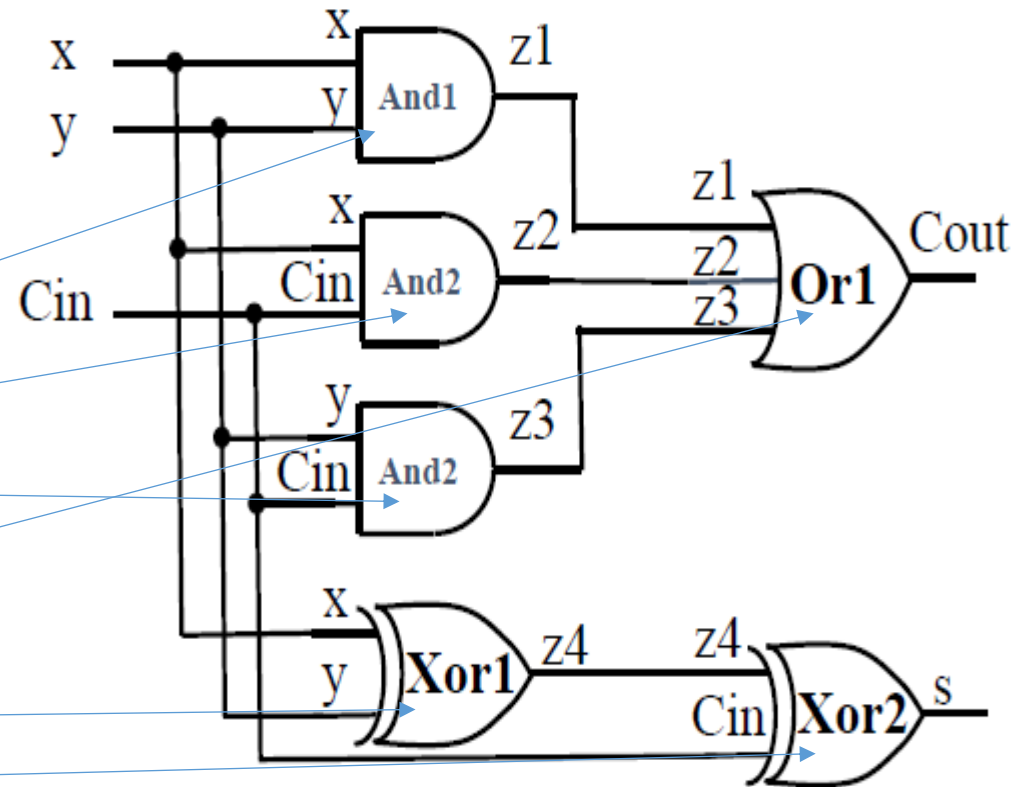


Gate Instantiations (Note Ch.2 p.15)

Pre-defined modules for logic gates

```
module fulladd(Cin,x,y,s,Cout);  
  input Cin,x,y;  
  output s,Cout;  
  
  wire z1,z2,z3,z4;  
  
  and And1(z1,x,y);  
  and And2(z2,x,Cin);  
  and And3(z3,y,Cin);  
  
  or Or1(Cout,z1,z2,z3);  
  
  xor Xor1(z4,x,y);  
  xor Xor2(s,z4,Cin);  
endmodule
```




The first one is output
while the rest are inputs

The instance name is optional.

The order of execution statements is not important unless inside an **always** block.

 (Another example from: “Quick Start Guide to Verilog” p.54)



The output is always listed first in the port mapping when using gate level primitives.

```
module SystemX (output wire F,  
                input wire A, B, C);  
  
    wire An, Bn, Cn; // internal nets  
    wire m0, m2, m6;  
  
    not U0 (An, A);           // Not's  
    not U1 (Bn, B);  
    not U2 (Cn, C);  
  
    and U3 (m0, An, Bn, Cn);  // AND's  
    and U4 (m2, An, B, Cn);  
    and U5 (m6, A, B, Cn);  
  
    or U6 (F, m0, m2, m6);   // OR  
  
endmodule
```


Note these statements are concurrent and their order is not important (since they are not enclosed in any **always** / **initial** block).

Note Ch.2 p.16

Name	Description	Usage
and	$f = (a \cdot b \cdot \dots)$	and (f, a, b, \dots)
nand	$f = \overline{(a \cdot b \cdot \dots)}$	nand (f, a, b, \dots)
or	$f = (a + b + \dots)$	or (f, a, b, \dots)
nor	$f = \overline{(a + b + \dots)}$	nor (f, a, b, \dots)
xor	$f = (a \oplus b \oplus \dots)$	xor (f, a, b, \dots)
xnor	$f = (a \odot b \odot \dots)$	xnor (f, a, b, \dots)
not	$f = \bar{a}$	not (f, a)
buf	$f = a$	buf (f, a)
notif0	$f = (!e ? \bar{a} : 'bz)$	notif0 (f, a, e)
notif1	$f = (e ? \bar{a} : 'bz)$	notif1 (f, a, e)
bufif0	$f = (!e ? a : 'bz)$	bufif0 (f, a, e)
bufif1	$f = (e ? a : 'bz)$	bufif1 (f, a, e)

Hi-Z of any bits

From DE2:

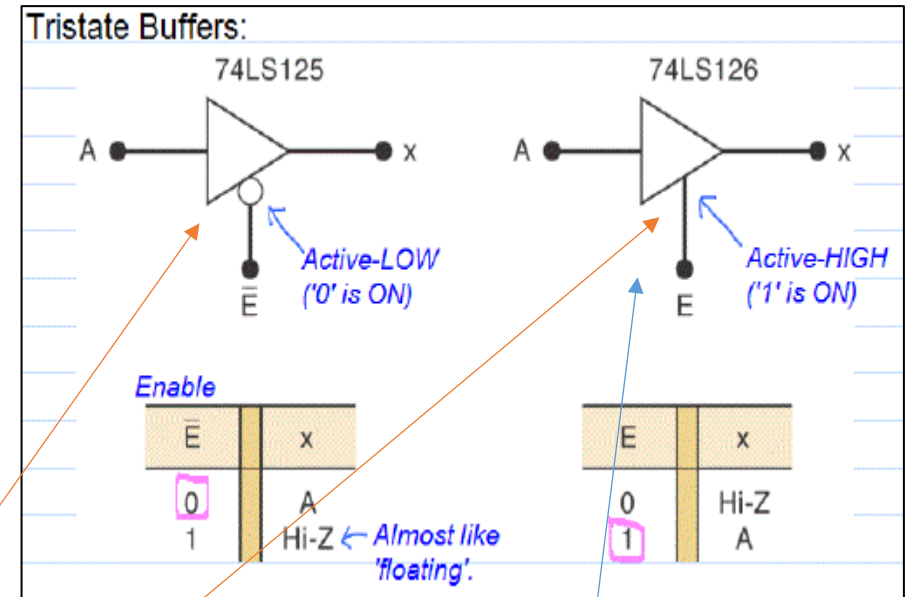

Tristate Inverters

Tristate Buffers, e.g.: **bufif1**(x, A, E);

Sub-circuit (Note Ch.2 p.17)

```

module adder4(carryin,X,Y,S, carryout);
    input carryin; input [3:0] X, Y; output [3:0] S; output carryout; wire [3:1] C;


    fulladd stage0 (carryin, X[0], Y[0], S[0], C[1]);
    fulladd stage1 (C[1], X[1], Y[1], S[1], C[2]);
    fulladd stage2 (C[2], X[2], Y[2], S[2], C[3]);
    fulladd stage3 (.Cout(carryout), .s(S[3]), .y(Y[3]), .x(X[3]), .Cin(C[3]));
endmodule

```

Positional port mapping:
Following the order of ports
as defined in **fulladd**


Explicit port mapping

 Module defined on p.15: **module** fulladd(Cin,x,y,s,Cout);



(Another example from: “Quick Start Guide to Verilog” p.52-53)

 Verilog Structural Design using Explicit Port Mapping



```
module Sub1 (output wire F1, F2,
             input wire A, B);
    // behavior here...
endmodule
```


```
module Sub2 (output wire W,
             input wire A, B);
    // behavior here...
endmodule
```

```
module System3 (output wire Z,
                input wire X, Y);
    wire n1, n2;
    Sub1 U0 (.F1(n1), .F2(n2), .A(X), .B(Y));
    Sub2 U1 (.W(Z), .A(n1), .B(n2));
endmodule
```

The lower-level port name is explicitly listed (preceded by a period).

The signal being connected to the lower-level port is listed inside of parenthesis.

 Verilog Structural Design using Positional Port Mapping



```
module Sub1 (output wire F1, F2,
             input wire A, B);
    // behavior here...
endmodule
```

```
module Sub2 (output wire W,
             input wire A, B);
    // behavior here...
endmodule
```

```
module System3 (output wire Z,
                input wire X, Y);
    wire n1, n2;
    Sub1 U0 (n1, n2, X, Y);
    Sub2 U1 (Z, n1, n2);
endmodule
```

The signals to be connected to the lower-level module must be listed in the same order as they were defined in the lower-level system.

Verilog for Combinational Circuits (Ch.2, p.18)

- Simple combinational circuits - use continuous assignments (**assign**).
- Complicated circuits - use blocking assignments (**=**) in **always** block.

```
module mux2to1(w0,w1,s,f);  
  input w0, w1, s;  
  output f;  
  assign f = s ? w1 : w0;  
endmodule
```

If $s == \text{true}$ then $f = w1$; else $f = w0$;

```
module mux2to1(w0,w1,s,f);  
  input w0, w1, s; output reg f;  
  always @ (w0, w1, s)  
    f = s ? w1 : w0;  
endmodule
```


Can be replaced by: **if (s==1) f = w1; else f = w0;** (Not allowed in **assign**.)

s	w1	w0	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$s = 0$ (false) → $f = w0$

$s = 1$ (true) → $f = w1$


(Ch.2, p.19)

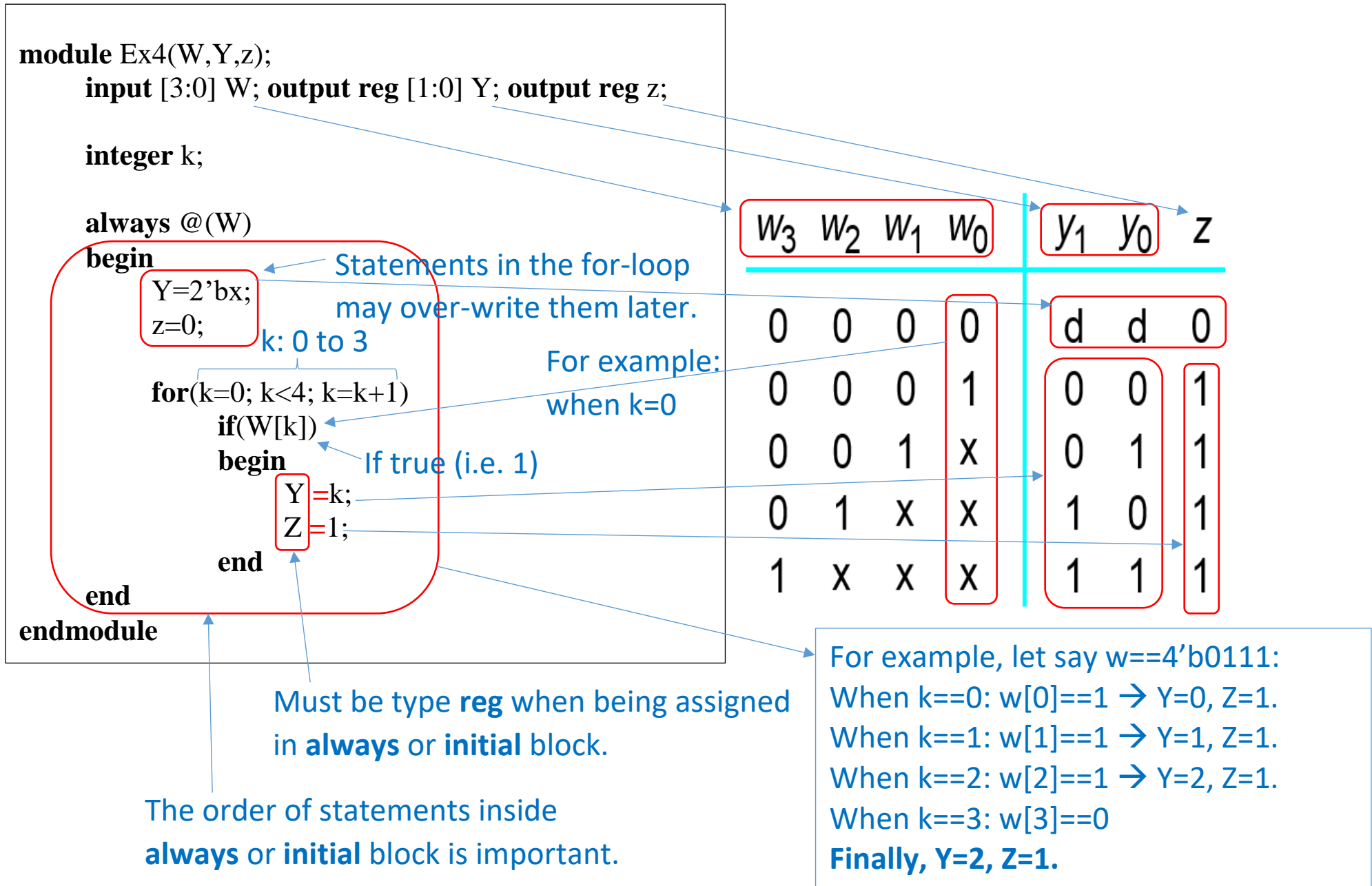

Verilog for Sequential Circuits (Ch.2, p.19)

- Sequential circuits - use non-blocking assignments (**<=**) in **always** block.
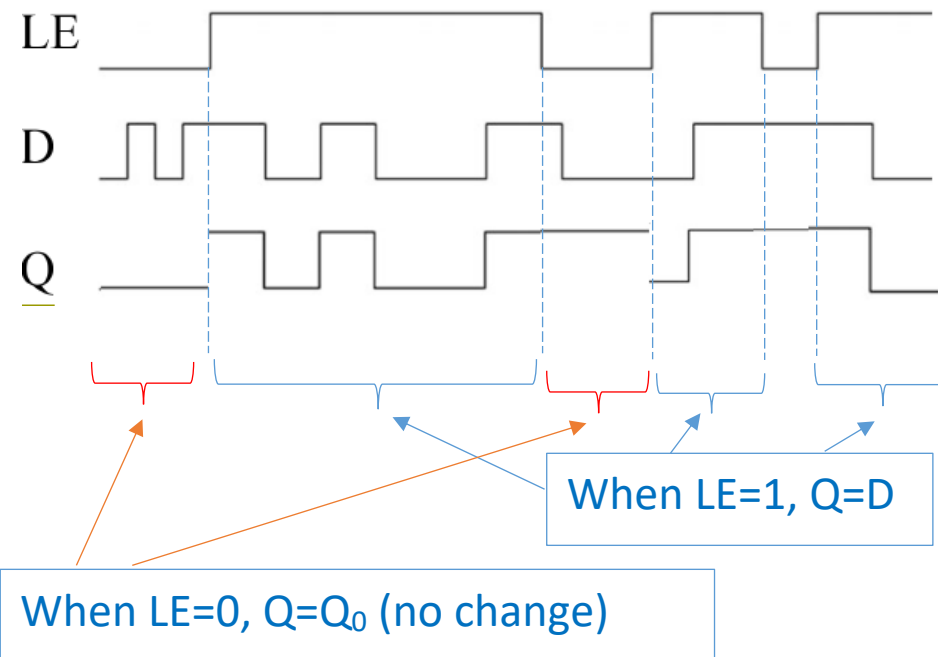
```
module D_latch(D, LE, Q);  
input D, LE;  
output reg Q;  
  
always @(D or LE)  
begin  
    if (LE) Q <= D;  
end  
endmodule
```



(Another example from: “Quick Start Guide to Verilog” p.72)

```
module BlockingEx4
(output reg F,
 input wire A,
 input wire Clock);

reg B;

always @ (posedge Clock)
begin
  B = A;    // statement 1
  F = B;    // statement 2
end

endmodule
```

WRONG




```
module NonBlockingEx4
(output reg F,
 input wire A,
 input wire Clock);

reg B;

always @ (posedge Clock)
begin
  B <= A;   // statement 1
  F <= B;   // statement 2
end

endmodule
```

CORRECT

   


It is like...

```
begin
  B_temp = A;
  F_temp = B;


  //At the end:
  B = B_temp;
  F = F_temp;
end
```

Ch.2, p.20

When $L==1$
Parallel load:

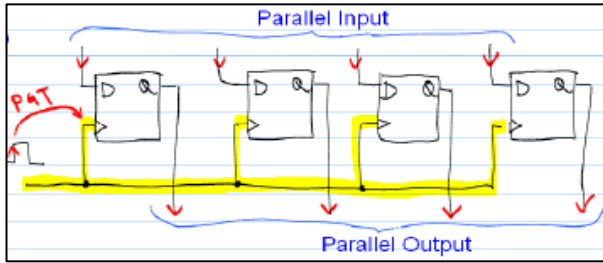

When
 $L==0$
Shift:

 

```
module Ex6 (R, L, w, Clk, Q);
  input [3:0] R;
  input L, w, Clk;
  output reg [3:0] Q;
  integer k;
  always@(posedge Clk)
```

```
    if (L) Q <= R;
```

```
    else
```

k: 0 to 2

```
    begin
```

```
        for(k=0; k<3; k=k+1)
```


```
            Q[k] <= Q[k+1];
```

```
        Q[3] <= w;
```

```
    end
```

```
endmodule
```

If $L==1$ then
Parallel load

 

For example, let say, $Q==4'b1101$ initially:

When $k==0$: $Q[0] <= Q[1] \rightarrow Q[0] <= 0$.

When $k==1$: $Q[1] <= Q[2] \rightarrow Q[1] <= 1$.


When $k==2$: $Q[2] <= Q[3] \rightarrow Q[2] <= 1$.

$Q[3] <= w$; (w is either 0 or 1.)

Finally, Q becomes w110.
(Q has been shifted right.)

*Use unblocking assignment ($<=$) in
always blocks for sequential circuits.*

Fig. 2-18 (Ch.2, p.20)

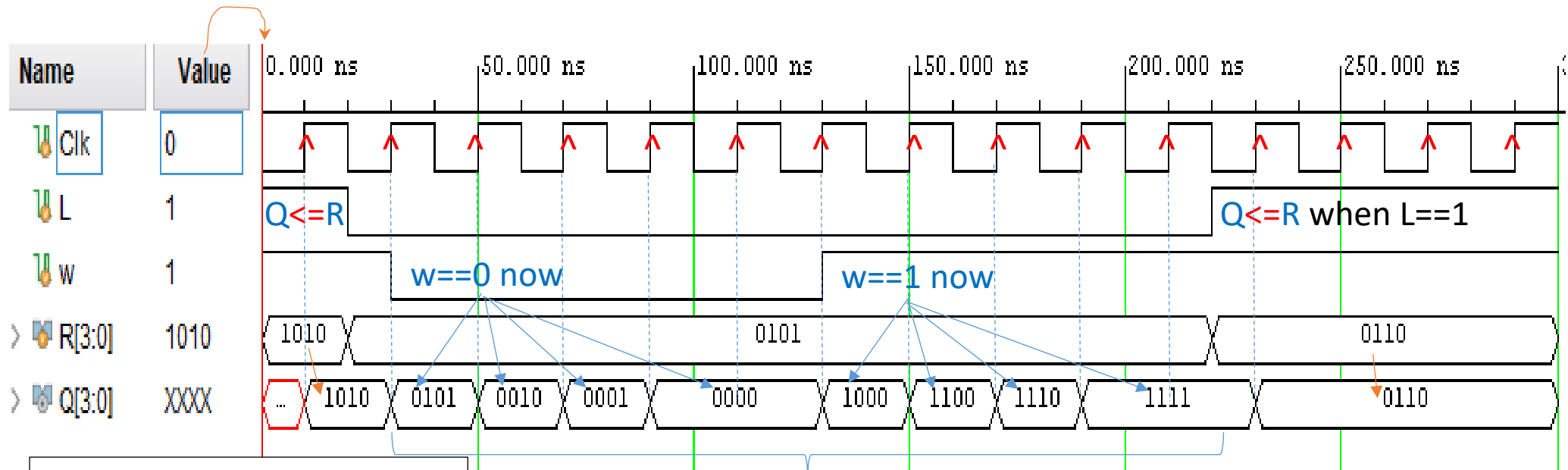

```
`timescale 1ns / 1ps
```

```
module Ex6_tb();
  reg Clk=0, L=0, w=0; reg [3:0] R;
  wire [3:0] Q;
  Ex6 dut (R, L, w, Clk, Q);
```

```
always #10 Clk = ~Clk;
```

```
initial
```

```
begin
```

```
L=1; w=1; R=10;
#20 L=0; R=5;
#10 w=0;
#100 w=1;
#90 L=1; R=6;
```

```
end
```

```
endmodule
```

Generating
clock pulses

Test sequence

Q will shift right while L==0

When L==0:

$Q[0] \leq Q[1]$

$Q[1] \leq Q[2]$

$Q[2] \leq Q[3]$

$Q[3] \leq w$

The test-bench module generating the
above signals for testing Ex6.

(See Fig. 2.20 on p.23 for another method.)

Simulation (Notes p. 21-23) – see also notes for Lab 1

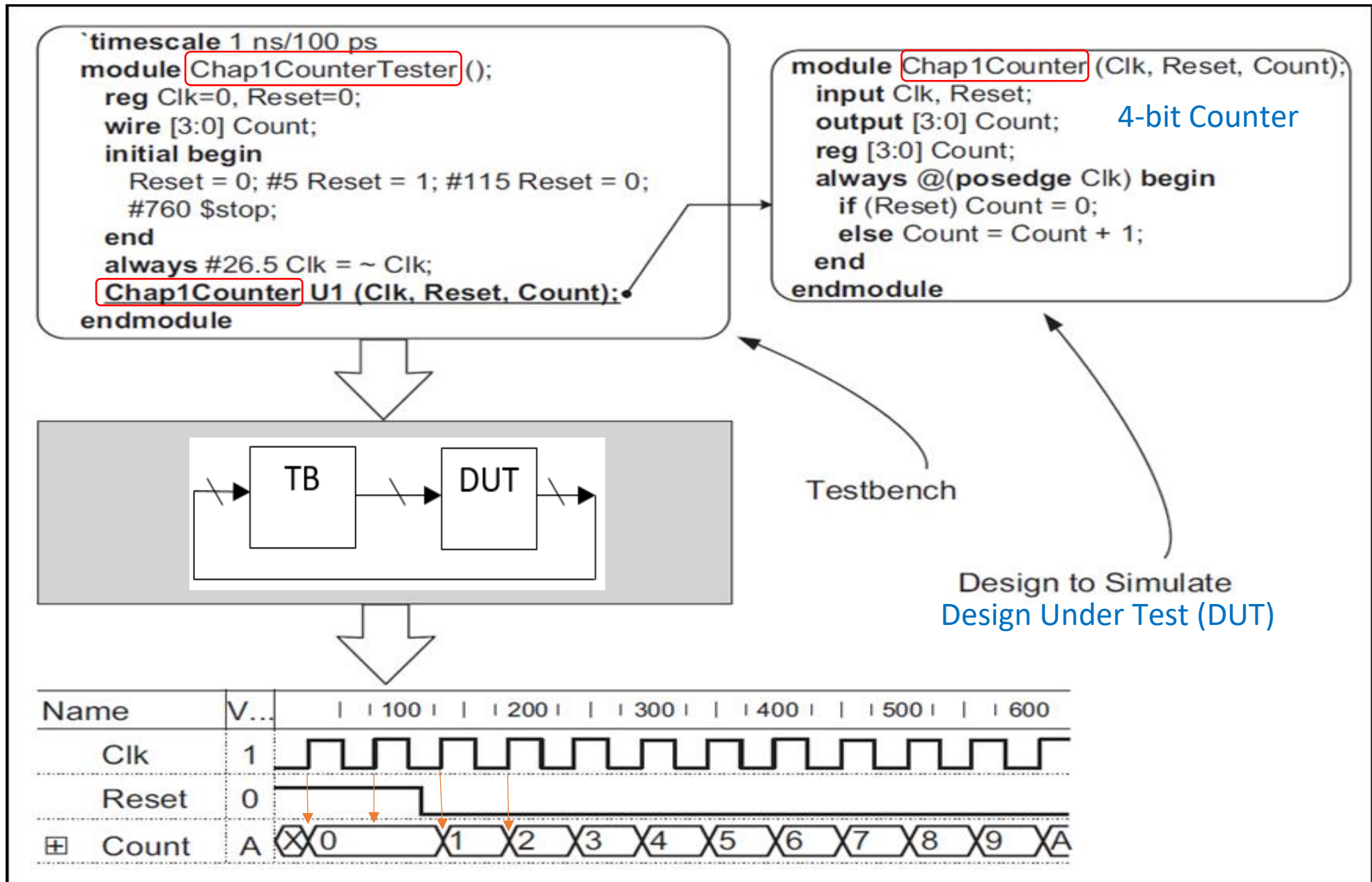


Figure 20 - Verilog testbench for Ex6 in Figure 18

```

`timescale 1ns / 1ps // simulator time unit = 1 ns and precision = 1 ps
module Ex6_tb(); // module name Ex6_tb, input and output is optional here
  wire [3:0] Q; // output in design become input in test-bench
  reg [3:0] R; // input in design become output in test-bench
  reg L;
  reg w;
  reg Clk=0; // Clk is initialized with logic '0'
  initial // initial block is not synthesizable, meant for simulation only
  begin
    L=1; // Initially L= '1'
    #20 L=0; // 20 ns later L= '0'
    #200 L=1; // another 200 ns later L= '1'
  end
  initial
  begin
    w=1; // Initially w = '1'
    #30 w=0; // 30 ns later w= '0'
    #100 w=1; // another 100 ns later w= '1'
  end
  initial
  begin
    R=4'b1010; // Initially R = "1010"
    #20 R=4'b0011; // 20 ns later R = "0011"
    #200 R=4'b0110; // another 200 ns R = "0110"
  end
  always #10 Clk=~Clk; // Clock pulse train of period = 10 + 10 ns = 20 ns

  Ex6 dut(R,L,w,Clk,Q); //an instance of Ex6 is added and called dut
endmodule


```

initial block for L

initial block for w

initial block for R

always block for clock pulses at Clk

 

This method uses separate blocks for the test signals. (Easier to control timing.)

