


SAMPLE DE1 EXAM Solution

: DIGITAL MODULE ELECTRONICS 1MOD. CODE: ET1003

No	SOLUTION												
A	<p><u>SECTION – A</u> (2 marks each)</p> <p>1) (c) 2) (b) 3) (c) 4) (c) 5) (d)</p> <p>6) (a) 7) (a) 8) (c) 9) (c) 10) (a)</p> <p><u>SECTION – B</u> (10 marks each)</p>												
B1													
a)	<p>Decimal 7788_{10} to Binary and Hexadecimal. As number is quite large, it is better to convert to hex first & then to binary.</p> <table><tr><td>16</td><td>7788</td><td>Remainder</td></tr><tr><td>16</td><td>486</td><td>C</td></tr><tr><td></td><td>30</td><td>6</td></tr><tr><td></td><td>1</td><td>E</td></tr></table> <p>Thus $7788_{10} = 1\text{ E }6\text{ C}_H = 1\ 1110\ 0110\ 1100_2$</p>	16	7788	Remainder	16	486	C		30	6		1	E
16	7788	Remainder											
16	486	C											
	30	6											
	1	E											
(b)	<p>Binary 10110011_2 to Decimal or base 10.</p> $10110011_2 = (1 * 128) + 0 + (1 * 32) + 1 * 16 + 0 + 0 + (1 * 2) + 1$ $= 128 + 32 + 16 + 2 + 1 = \mathbf{179_{10}}$ <p>Octal 56271 to decimal</p> $= 5 * 8^4 + 6 * 8^3 + 2 * 8^2 + 7 * 8^1 + 1$ $= 23737_{10}$ <p>Hex 3FAD to decimal</p> $= 3 * 16^3 + 15 * 16^2 + 10 * 16 + 13$ $= 16301_{10}$												

SAMPLE DE1 EXAM Solution

: DIGITAL MODULE ELECTRONICS 1MOD. CODE: ET1003

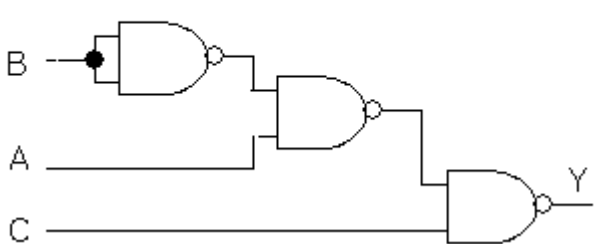No	SOLUTION															
B2	<p>Boolean Equation from truth table is</p> <p>(a) $Y = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + A\overline{B}C + A\overline{B}\overline{C}$</p> <p>(b) $Y = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + A\overline{B}C + A\overline{B}\overline{C}$ $= \overline{C}(\overline{A}\overline{B} + \overline{A}B + A\overline{B} + AB) + A\overline{B}\overline{C}$ $= \overline{C} + A\overline{B}\overline{C}$ $= \overline{C} + A\overline{B}$</p> <p>Or</p> <table><tr><td>Y</td><td>$\overline{B}\overline{C}$</td><td>$\overline{B}C$</td><td>BC</td><td>$B\overline{C}$</td></tr><tr><td>\overline{A}</td><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>A</td><td>1</td><td>1</td><td>0</td><td>1</td></tr></table> <p>$Y = \overline{C} + A\overline{B}$</p> <p>(C) $Y = \overline{\overline{\overline{\overline{C} + A\overline{B}}}} = \overline{\overline{\overline{C}} \cdot \overline{\overline{A\overline{B}}}} = \overline{\overline{C} \cdot \overline{A\overline{B}}}$</p> 	Y	$\overline{B}\overline{C}$	$\overline{B}C$	BC	$B\overline{C}$	\overline{A}	1	0	0	1	A	1	1	0	1
Y	$\overline{B}\overline{C}$	$\overline{B}C$	BC	$B\overline{C}$												
\overline{A}	1	0	0	1												
A	1	1	0	1												



SAMPLE DE1 EXAM Solution

: DIGITAL MODULE ELECTRONICS 1MOD. CODE: ET1003

No	SOLUTION																																			
B3	<table><tr><th>CLK</th><th>J</th><th>K</th><th>Q1</th><th>Q2</th></tr><tr><td>L</td><td>L</td><td>L</td><td>H</td><td>H</td></tr><tr><td>↓</td><td>L</td><td>L</td><td>H</td><td>H</td></tr><tr><td>↑</td><td>L</td><td>H</td><td>L</td><td>H</td></tr><tr><td>↑</td><td>H</td><td>L</td><td>H</td><td>H</td></tr><tr><td>↓</td><td>H</td><td>H</td><td>H</td><td>H</td></tr><tr><td>↑</td><td>H</td><td>H</td><td>L</td><td>H</td></tr></table>	CLK	J	K	Q1	Q2	L	L	L	H	H	↓	L	L	H	H	↑	L	H	L	H	↑	H	L	H	H	↓	H	H	H	H	↑	H	H	L	H
CLK	J	K	Q1	Q2																																
L	L	L	H	H																																
↓	L	L	H	H																																
↑	L	H	L	H																																
↑	H	L	H	H																																
↓	H	H	H	H																																
↑	H	H	L	H																																
B4	<p>Boolean Equation is</p> $Z = \overline{(\overline{A+B}).C.C\overline{D}}$ <p><i>Simplifying</i></p> $Z = \overline{(\overline{A+B+C}).C\overline{D}}$ $Z = (A+B+\overline{C}).C\overline{D}$ $Z = ACD\overline{D} + BC\overline{D} + \overline{C}CD$ $Z = ACD\overline{D} + BC\overline{D}$																																			
(a)																																				
(b)	<table><tr><td>Z</td><td>$\overline{C}\overline{D}$</td><td>$\overline{C}D$</td><td>CD</td><td>$C\overline{D}$</td></tr><tr><td>$\overline{A}\overline{B}$</td><td>1</td><td>1</td><td>1</td><td>1</td></tr><tr><td>$\overline{A}B$</td><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>AB</td><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>$A\overline{B}$</td><td>1</td><td>1</td><td>1</td><td>1</td></tr></table> <p>$Z = \overline{B} + \overline{D}$</p>	Z	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$	$\overline{A}\overline{B}$	1	1	1	1	$\overline{A}B$	1	0	0	1	AB	1	0	0	1	$A\overline{B}$	1	1	1	1										
Z	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$																																
$\overline{A}\overline{B}$	1	1	1	1																																
$\overline{A}B$	1	0	0	1																																
AB	1	0	0	1																																
$A\overline{B}$	1	1	1	1																																

SAMPLE DE1 EXAM Solution



: DIGITAL MODULE ELECTRONICS 1MOD. CODE: ET1003

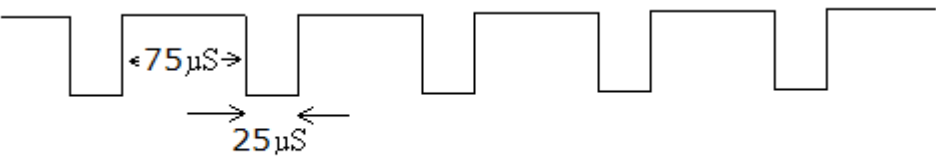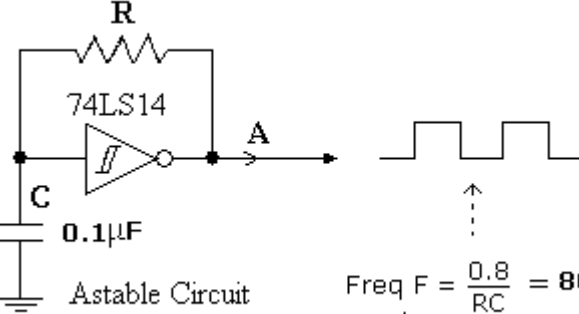No	SOLUTION
B5 a)	<p>Given:</p>  <p style="text-align: center;">Figure B5.1</p> <p>Frequency = $1/(\text{period})$ $= 1/(75+25) \mu\text{s} = 10,000 \text{ Hz or } 10\text{kHz}.$</p> <p>Duty Cycle = $75/(25+75) * 100$ $= 75\%$</p> <p>To change the duty cycle without changing the CLK frequency a monostable or one-shot can be used for this purpose.</p> <p>b)</p>  <p style="text-align: center;">Astable Circuit</p> <p style="text-align: center;">Freq $F = \frac{0.8}{RC} = 80 \text{ kHz}$</p> <p>$F = \frac{0.8}{RC} = 80000 \text{ Hz}$ Therefore $R = 0.8/(80000 * 10^{-7}) = 100 \text{ Ohms}$</p>

SAMPLE DE1 EXAM Solution

: DIGITAL MODULE ELECTRONICS 1MOD. CODE: ET1003

B6

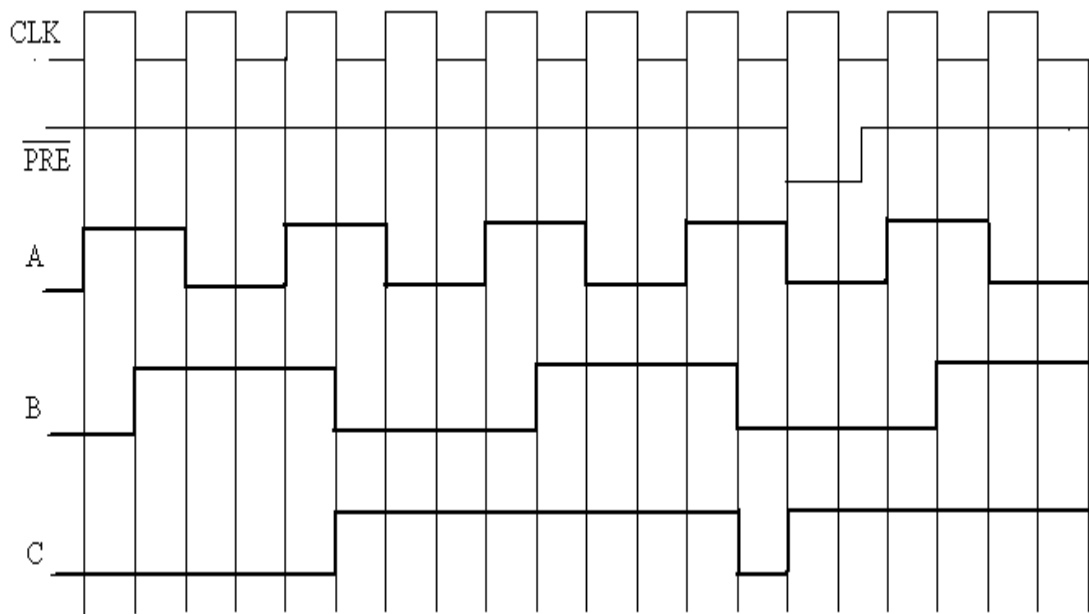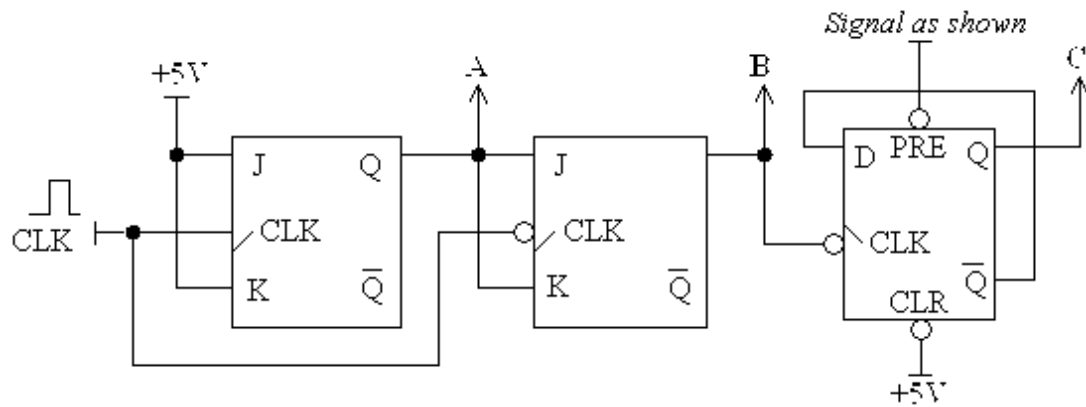

SAMPLE DE1 EXAM Solution

: DIGITAL MODULE ELECTRONICS 1MOD. CODE: ET1003

No	SOLUTION																																																																																										
C1	Required Truth-table is as shown:																																																																																										
(a)	<table><tr><th colspan="4">Inputs</th><th>Output</th></tr><tr><th>D</th><th>C</th><th>B</th><th>A</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr></table> <p style="text-align: center;"><u>Table C1</u></p> <p>Boolean expression for output is therefore:</p> $Z = \overline{D}\overline{C}\overline{B}\overline{A} + \overline{D}\overline{C}B\overline{A} + \overline{D}C\overline{B}A + D\overline{C}\overline{B}\overline{A} + D\overline{C}B\overline{A} + DC\overline{B}A + DCBA + \overline{D}CBA$	Inputs				Output	D	C	B	A	Z	0	0	0	0	1	0	0	0	1	0	0	0	1	0	1	0	0	1	1	0	0	1	0	0	0	0	1	0	1	1	0	1	1	0	0	0	1	1	1	1	1	0	0	0	1	1	0	0	1	0	1	0	1	0	1	1	0	1	1	0	1	1	0	0	0	1	1	0	1	1	1	1	1	0	0	1	1	1	1	1
Inputs				Output																																																																																							
D	C	B	A	Z																																																																																							
0	0	0	0	1																																																																																							
0	0	0	1	0																																																																																							
0	0	1	0	1																																																																																							
0	0	1	1	0																																																																																							
0	1	0	0	0																																																																																							
0	1	0	1	1																																																																																							
0	1	1	0	0																																																																																							
0	1	1	1	1																																																																																							
1	0	0	0	1																																																																																							
1	0	0	1	0																																																																																							
1	0	1	0	1																																																																																							
1	0	1	1	0																																																																																							
1	1	0	0	0																																																																																							
1	1	0	1	1																																																																																							
1	1	1	0	0																																																																																							
1	1	1	1	1																																																																																							

SAMPLE DE1 EXAM Solution

: DIGITAL MODULE ELECTRONICS 1

MOD. CODE: ET1003

No	SOLUTION
C1 (b)	<p>Using the K-Map,</p> <p>$Z = AC + \bar{A}\bar{C}$</p> <p>Or, if Boolean theorems are used instead, then the solution is:</p> $Z = \bar{D}\bar{C}\bar{B}\bar{A} + \bar{D}\bar{C}B\bar{A} + \bar{D}C\bar{B}\bar{A} + \bar{D}CBA + D\bar{C}\bar{B}\bar{A} + D\bar{C}B\bar{A} + DC\bar{B}\bar{A} + DCBA$ $Z = \bar{C}\bar{A}(\bar{D}\bar{B} + \bar{D}B + D\bar{B} + DB) + CA(\bar{D}\bar{B} + \bar{D}B + D\bar{B} + DB)$ $= \bar{C}\bar{A} + CA$ <p>Implementing with the least possible number of gates, the simplified equation is the Boolean expression of an XOR gate.</p> <p>Thus:</p> $Z = \bar{C}\bar{A} + CA$ $= \overline{C \oplus A}$

SAMPLE DE1 EXAM Solution

: DIGITAL MODULE ELECTRONICS 1MOD. CODE: ET1003

No	SOLUTION
	<p>Double complementing the expression and applying DeMorgan's theorems, the NAND gate implementation is:</p> $Z = \overline{\overline{C} \overline{A} + CA}$ $= \overline{\overline{C} \overline{A}} \overline{CA}$ <p>Hence the circuit is as shown:</p> 