 


Tutorial 3

B1. Write a Verilog program for the circuit in Figure 1 using gate instantiation.

```
module Figure1 (A, B, C, Y);  
  input A,B,C;  
  output Y; Structural description  
  wire z1,z2;  
  and Gate1 (z1 , A, B);  
  not Gate2 (z2, C);  
  nor Gate3 (Y, z1, z2);  
endmodule
```



The above statements can be replaced by its *behaviour description* equivalent:

```
assign Y = ~(A & B | ~C);
```

In boolean equation:

$$Y = \overline{A \cdot B + \bar{C}}$$

B2. Figure 2 shows the testbench for Figure 1.

Draw the waveform of A, B, C and Y after simulation for 80 ns.

```
`timescale 1ns / 1ps
module Figure1_tb();
  wire Y;
  reg A=0;
  reg B=0;
  reg C=0;
  always #40 A=~A;
  always #20 B=~B;
  always #10 C=~C;
  Figure1 dut(A,B,C,Y);
endmodule
```

$Y = \sim(A \& B \mid \sim C)$

In boolean equation:

$$Y = A.B + \overline{C}$$

$$\overline{Y} = A.B + \overline{C}$$

Y=0 when either:

- A=1 & B=1
- C=0

