

This diagram is for answering Q6 to Q10

Q6 Given that A is a North pole and B, a South pole, what is the direction of the current, if any, when the rod is moved at a velocity forward?

The current flows from left to right/right to left / no current at the point marked by 1. Same situation as Qs and we have seen that the tre charges move to the right towards Yend. In Q6, the circuit is now closed and the chargescan continue to flow and form a current. Given that A is a North pole and B, a South pole, what is the polarity of VR when the

rod is moved at a velocity forward? V_R is is negative/positive.

actual voltage Because the actual voltage is opposite to the direction we measure it. direction direction Given that A is a South pole and B a North pole, what is the polarity of V_R when the Use the same reasonings employed for Q68Q7.

rod is moved at a velocity forward? The only difference is the reversal of the V_R is is negative/positive magantic field the charges

Given that A is a North pole and B, a South pole, what is the direction of the Lorentz Q9 force generated that acts on the rod, if any, when the rod is moved at a velocity

forward?

The rod experiences a force forward backward upward/downward/no force

0.2Testa A downward pointing uniform magnetic field of 0.2 Tesla is created by the magnetic poles A and B and the rod is 0.1 m long. Determine the direction and the magnitude of the force on the rod when the current is 10 A flowing from left to right at point to the right marked by I.

Q7

08

210

OIM

10A

As the charge moves to the forther?


right, another force is generated

which is the the Page 2 of 3

direction into the paper (backwards).

That is, the rod will experience a backward force.

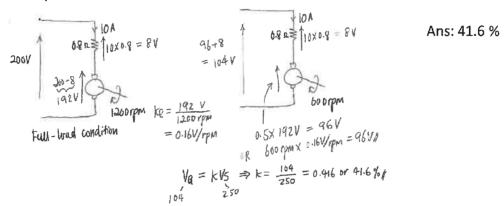Q11 A 200 V, 10 A, 1200 rpm separately-excited dc motor has an armature resistance of 0.8 Ω . It is driven by a chopper taking its supply from a 250 V dc source. Determine the duty cycle of the chopper when the motor is exerting the full-load torque at ½ the rated speed. The armature current is assumed to be continuous.



Q12 A 200 V, 10 A, 1200 rpm separately-excited dc motor has an armature resistance of 0.8 Ω . It is driven by a chopper taking its supply from a 250 V dc source. Determine the duty cycle of the chopper when the motor is exerting 60 % of full-load torque at the rated speed. The armature current is assumed to be continuous.

Ans: 78.7 %

Q13 A 200 V, 10 A, 1200 rpm separately-excited dc motor has an armature resistance of 0.8 Ω . It is driven by a chopper taking its supply from a 250 V dc source. Determine the duty cycle of the chopper when the motor is exerting 60 % of full-load torque at ½ the rated speed. The armature current is assumed to be continuous.

Ans: 40.3 %

$$V_{0.8V} = \frac{162}{48V} V_{0.8V} = \frac{100.8}{250} = 0.403 \text{ or } 40.3\%, p$$

$$V_{0.8V} = \frac{162}{250} = 0.403 \text{ or } 40.3\%, p$$

$$V_{0.8V} = \frac{162}{250} = 0.403 \text{ or } 40.3\%, p$$

$$V_{0.8V} = \frac{162}{250} = 0.403 \text{ or } 40.3\%, p$$

$$V_{0.8V} = \frac{162}{250} = 0.403 \text{ or } 40.3\%, p$$