

B1. Figure 2 shows a state-assigned table for a finite state machine.

- (a) Is this a Moore's or Mealy's finite state machine? Support your answer with reason.

Answer: Mealy's since output depends on present states as well as input.

- (b) Derive the excitation table using flips.

Present state	Next state		Output	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
$y_2 y_1$	$Y_2 Y_1$	$Y_2 Y_1$	z	z
00	01	11	0	0
01	01	11	1	0
11	01	11	0	1

Excitation table – truth table/K-map for generating the Next State and Output(s):

Input & Present State			Next State		Output
w	$y_2 (Q_2)$	$y_1 (Q_1)$	$Y_2 (D_2)$	$Y_1 (D_1)$	z
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	x	x	x
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	1	1	0
1	1	0	x	x	x
1	1	1	1	1	1


This state is not used.

(The following is not required in the question.)

From K-map or inspection:

- $D_2 = w$
- $D_1 = 1$
- $Z = w' \cdot Q_2' \cdot Q_1 + w \cdot Q_2$

		Q2 Q1			
		00	01	11	10
w	0	0	1	0	x
	1	0	0	1	x

 

B2. Write the Verilog code for the FSM in Figure 2. You may assume that the reset state is “00” and the Reset is asynchronous active low signal and Clock is an active low signal.

One possible solution:

Present state	Next state		Output	
	w = 0	w = 1	w = 0	w = 1
y ₂ y ₁	Y ₂ Y ₁	Y ₂ Y ₁	z	z
A 00	B 01	C 11	0	0
B 01	B 01	C 11	1	0
C 11	B 01	C 11	0	1

```
module Tut5B2 (Clock, Reset, w, z);
```

```
  input wire Clock, Reset, w;
```

```
  output reg z;
```

```
  reg [2:1] y, Y; // Present & Next State
```

```
  parameter [2:1] A=0, B=1, C=3; // State codes
```

```
  // Define the next state and output combinational circuit:
```

```
  always @(w,y)
```

```
    case (y)
```

```
      A: if (w==1) begin z=0; Y=C; end  
        else begin z=0; Y=B; end
```

```
      B: if (w==1) begin z=0; Y=C; end  
        else begin z=1; Y=B; end
```

```
      C: if (w==1) begin z=1; Y=C; end  
        else begin z=0; Y=B; end
```

The unused state(s)

```
      default: begin z=1'b0; Y=A; end
```

```
    endcase
```

Set next state to be the reset state instead of don't care (as in the notes).

```
  // Define the sequential block:
```

```
  always @(negedge Resetn, negedge Clock)
```

```
    if (Resetn==0) y<=A;
```

```
    else y <= Y;
```

```
      // The next state now (Y) will become the
```

```
      // present state (y) one clock cycle later.
```

```
endmodule
```