

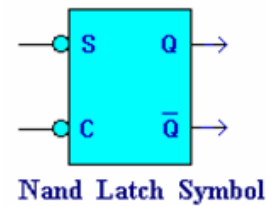
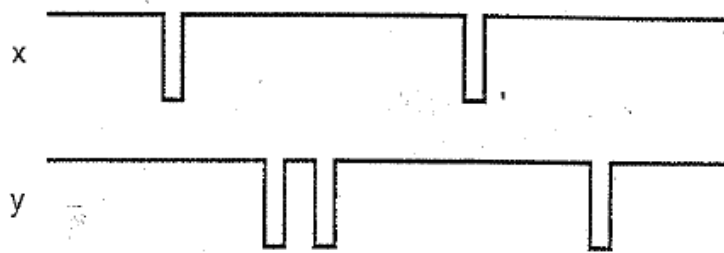


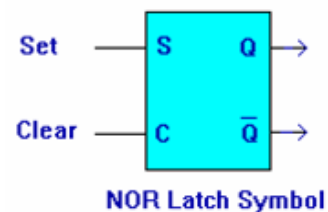5-1. Assuming that  $Q = 0$  initially, apply the  $x$  and  $y$  waveforms of Figure 5-73 to the SET and CLEAR inputs of a NAND latch, and determine the  $Q$  and  $\bar{Q}$  waveforms.




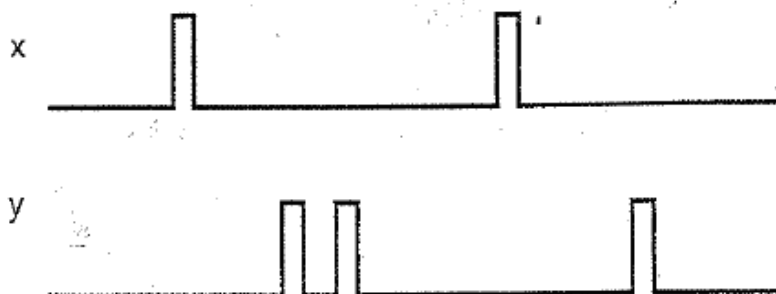5-2. Invert the  $x$  and  $y$  waveforms of Figure 5-73, apply them to the SET and CLEAR inputs of a NOR latch, and determine the  $Q$  and  $\bar{Q}$  waveforms. Assume that  $Q = 0$  initially.



p.182 : Debounced switch using NAND latch

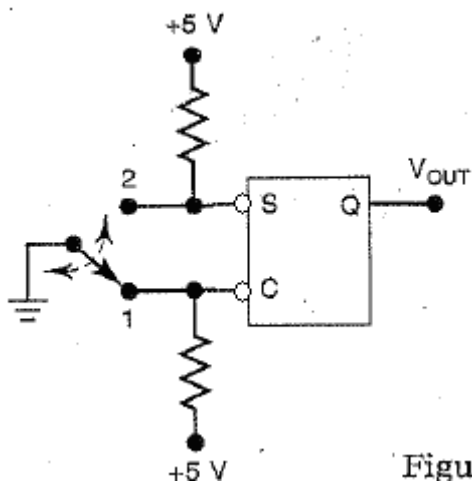→ 5-4. Modify the circuit of Figure 5-9 to use a NOR gate latch.



Figure

5-9. Apply the waveforms of Figure 5-76 to the FF of Figure 5-17 and determine the waveform at  $Q$ . Assume  $Q = 0$  initially.

Figure 5-76

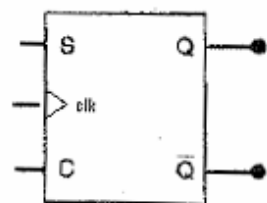
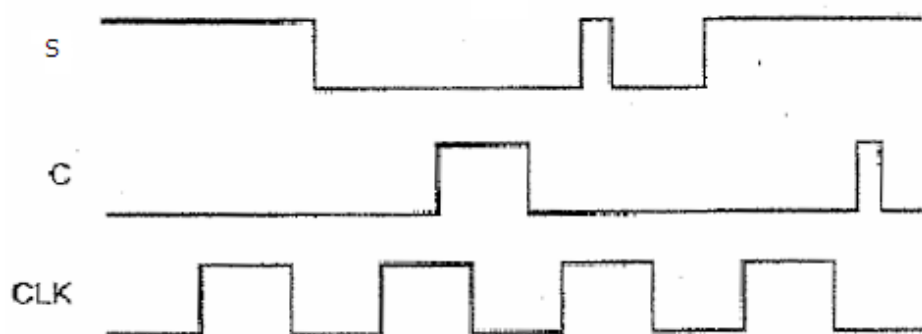


Fig 5.17

Repeat for the FF of Figure 5-18. Assume  $Q = 0$  initially.



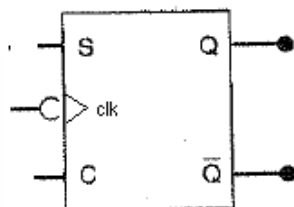
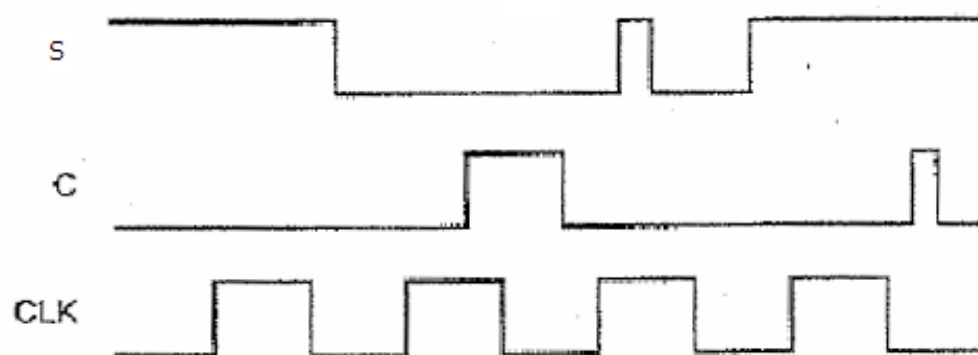


Fig. 5.18

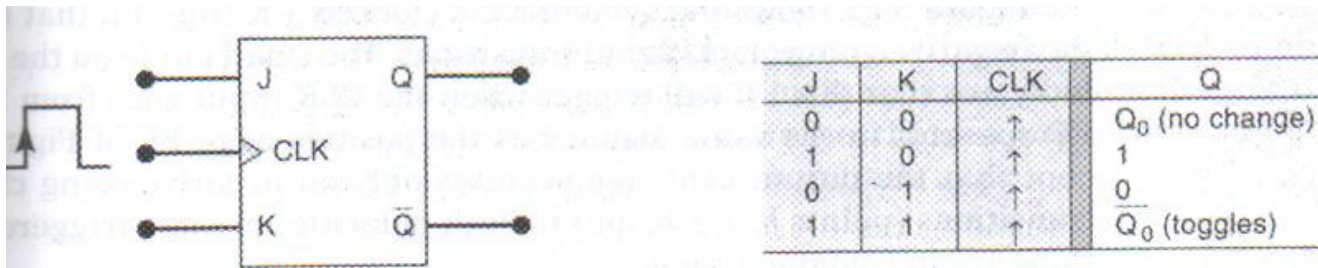→ 5-10. Apply the  $J$ ,  $K$ , and  $CLK$  waveforms of Figure 5-21 to the FF of Figure 5-22. Assume that  $Q = 1$  initially, and determine the  $Q$  waveform.




(a)

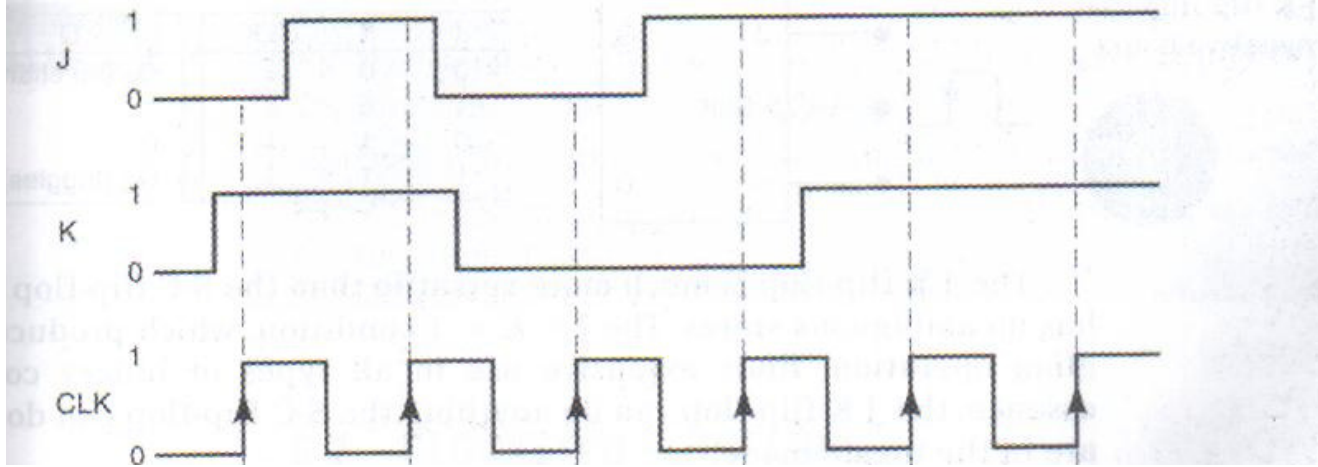


- 5-11. (a) Show how a J-K flip-flop can operate as a *toggle* FF (changes states on each clock pulse). Then apply a 10-kHz clock signal to its *CLK* input and determine the waveform at *Q*.
- (b) Connect *Q* from this FF to the *CLK* input of a second J-K FF that also has  $J = K = 1$ . Determine the frequency of the signal at this FF's output.

5-13. A D FF is sometimes used to *delay* a binary waveform so that the binary information appears at the output a certain amount of time after it appears at the *D* input.

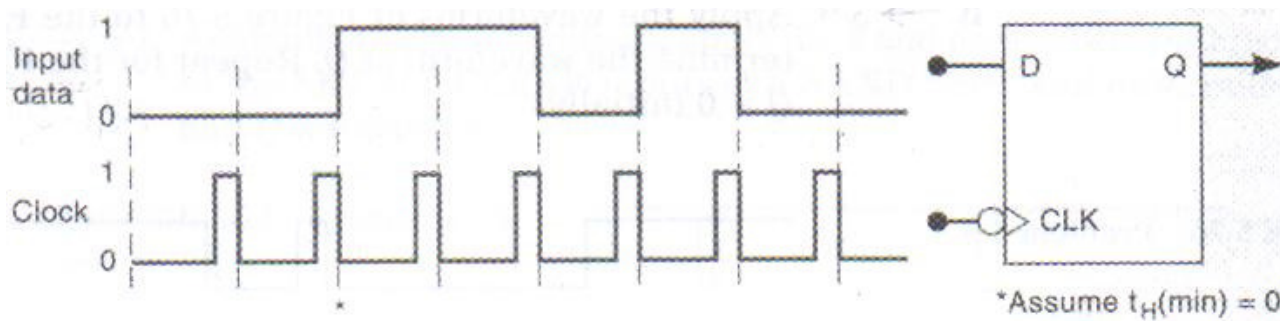- (a) Determine the *Q* waveform in Figure 5-78, and compare it with the input waveform. Note that it is delayed from the input by one clock period. (below)
- (b) How can a delay of two clock periods be obtained?



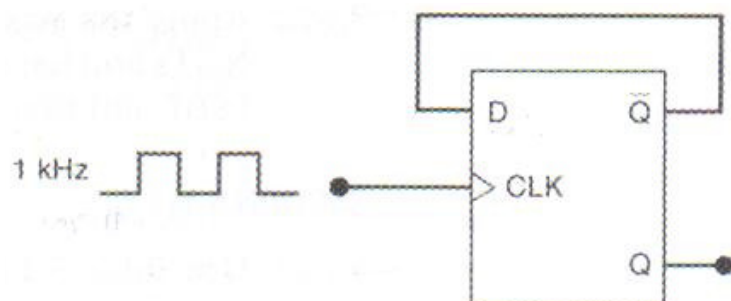5-15. An edge-triggered D flip-flop can be made to operate in the toggle mode by connecting it as shown in Figure 5-79. Assume that  $Q = 0$  initially, and determine the  $Q$  waveform. (below)



→ 5-18. Compare the operation of the *D* latch with a negative-edge-triggered *D* flip-flop by applying the waveforms of Figure 5-80 to each and determining the *Q* waveforms. (below)

