
 


LAB1 Part 7

7 Extra Practice: Design a 74LS147 Decimal-to-BCD Priority Encoder

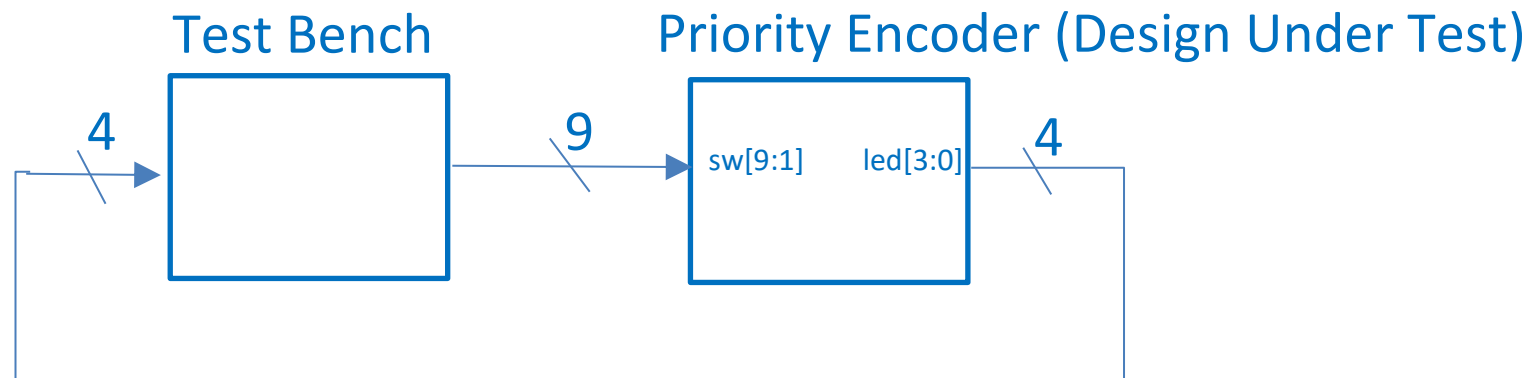

The 4-bit BCD output will indicate which of the 9 inputs is ON.
 If 2 or more inputs are ON, it will indicate the highest of them.
 Both the inputs and outputs are inverted.



First attempt - ignore inverted inputs and inverted outputs, apply 2^9 input combinations to test:

```
module Priority_Encoder(  
    input wire [9:1] sw,  
    output reg [3:0] led  
);  
  
always @(sw) // if value in sw changes,  
begin  
    casex(sw)  
        9'b1xxx_xxx_xxx: led=9;  
        9'b01x_xxx_xxx: led=8;  
        9'b001_xxx_xxx: led=7;  
        9'b000_1xx_xxx: led=6;  
        9'b000_01x_xxx: led=5;  
        9'b000_001_xxx: led=4;  
        9'b000_000_1xx: led=3;  
        9'b000_000_01x: led=2;  
        9'b000_000_001: led=1;  
        default: led=0; //Default output  
    endcase  
end  
endmodule
```

Time unit Resolution Test Bench


```
`timescale 1ns / 1ps  
  
module Priority_Encoder_tb();  
  
    reg [9:1] sw;  
    wire [3:0] led;  
  
    Priority_Encoder dut(.led(led),.sw(sw));  
  
    initial  
    begin  
        for (integer i=0; i < 2**9; i=i+1)  
            #10 sw = i;  
        end  
    end  
endmodule
```

Design Under Test

Execute once only at the beginning

Delay 10 time units

Simulation results:

 

Second attempt – still ignore inverted inputs and inverted outputs, but apply only 10 input combinations with don't-cares 'x' to test:

```
`timescale 1ns / 1ps

module Priority_Encoder_tb();

    reg [9:1] sw;
    wire [3:0] led;


    Priority_Encoder dut(.led(led),.sw(sw));

    initial
    begin
        //      for (integer i=0; i < 2**9; i=i+1)
        //          #10 sw = i;

        #10 sw = 9'b1xx_xxx_xxx;
        #10 sw = 9'b01x_xxx_xxx;
        #10 sw = 9'b001_xxx_xxx;
        #10 sw = 9'b000_1xx_xxx;
        #10 sw = 9'b000_01x_xxx;
        #10 sw = 9'b000_001_xxx;
        #10 sw = 9'b000_000_1xx;
        #10 sw = 9'b000_000_01x;
        #10 sw = 9'b000_000_001;
        #10 sw = 9'b000_000_000;

    end

endmodule
```

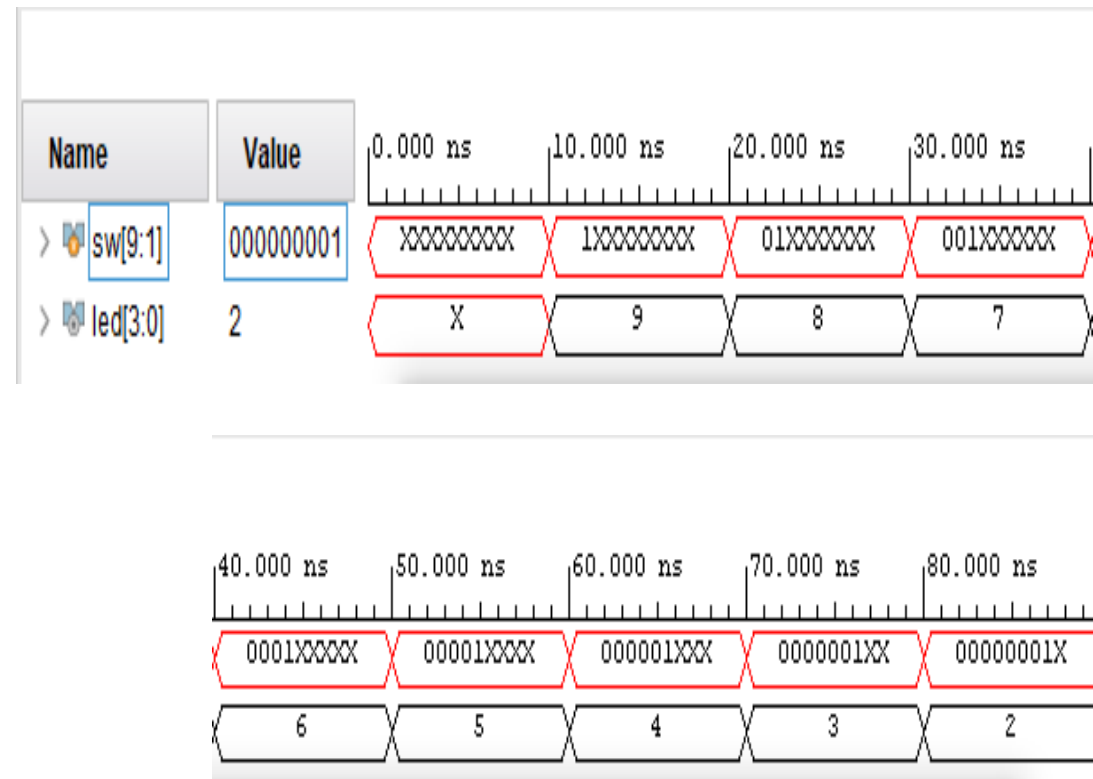

Third attempt – invert the inputs and outputs and apply only 10 inverted input combinations with don't-cares 'x' to test:

```
`timescale 1ns / 1ps

module Priority_Encoder(
    input wire [9:1] sw, //Active-low
    output reg [3:0] led //Active-low
);

always @(sw)
begin
    casex(~sw) //Bits inverted
        9'b1xx_xxx_xxx: led=~9;
        9'b01x_xxx_xxx: led=~8;
        9'b001_xxx_xxx: led=~7;
        9'b000_1xx_xxx: led=~6;
        9'b000_01x_xxx: led=~5;
        9'b000_001_xxx: led=~4;
        9'b000_000_1xx: led=~3;
        9'b000_000_01x: led=~2;
        9'b000_000_001: led=~1;
        default: led=~0;
    endcase
end
endmodule
```

```
`timescale 1ns / 1ps

module Priority_Encoder_tb();

    reg [9:1] sw;
    wire [3:0] led;

    Priority_Encoder dut(.led(led),.sw(sw));

    initial
    begin
        sw = 9'b0xxxxxxxx;
        #10 sw = 9'b10xxxxxxxx;
        #10 sw = 9'b110xxxxxxx;
        #10 sw = 9'b1110xxxxxx;
        #10 sw = 9'b11110xxxxx;
        #10 sw = 9'b111110xxx;
        #10 sw = 9'b1111110xx;
        #10 sw = 9'b11111110x;
        #10 sw = 9'b111111110;
        #10 sw = 9'b111111111;
    end
endmodule
```

Inverted test patterns

Simulation results:

