

2016/2017 SEMESTER TWO EXAMINATION

Diploma in Aerospace Electronics (DASE) 2<sup>nd</sup> Year FT  
Diploma in Engineering with Business (DEB) 3<sup>rd</sup> Year FT  
Diploma in Electrical & Electronic Engineering (DEEE) 2<sup>nd</sup> Year FT  
Diploma in Engineering Systems (DES) 2<sup>nd</sup> Year FT  
Diploma in Energy Systems and Management (DESM) 2<sup>nd</sup> Year FT

**CIRCUIT THEORY & ANALYSIS**

Time Allowed: 2 Hours

---

Instructions to Candidates

1. The examination rules set out on the last page of the answer booklet are to be complied with.
2. This paper consists of **TWO** sections:
  - Section A - 6 Short Questions, 10 marks each.
  - Section B - 2 Long Questions, 20 marks each.
3. **ALL** questions are **COMPULSORY**.
4. All questions are to be answered in the answer booklet. Start each question on a new page.
5. Fill in the Question Numbers in the boxes found on the front cover of the answer booklet under the column "Question Answered".
6. This paper consists of 6 pages, inclusive of the formulae sheet.

**SECTION A: 6 QUESTIONS** (10 marks each)

- A1. Using the source conversion method, simplify the circuit shown in Figure A1 to its equivalent current source across terminals A and B. (10 marks)

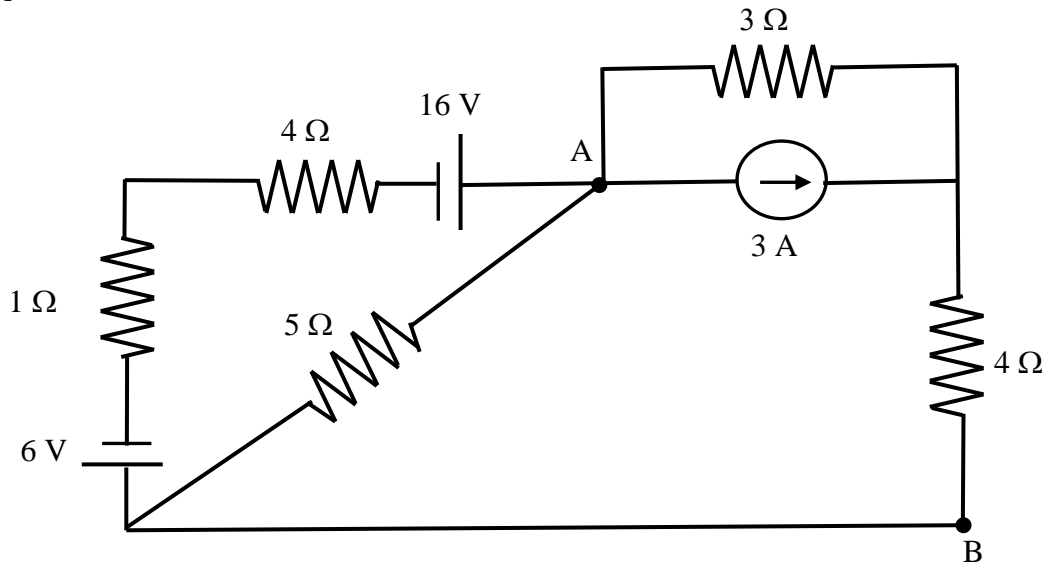


Figure A1

- A2. For the circuit shown in Figure A2,
- convert the delta-connected resistors as shown in the dotted box into an equivalent star-connection, and hence (5 marks)
  - determine the current in the  $20\ \Omega$  resistor. (5 marks)

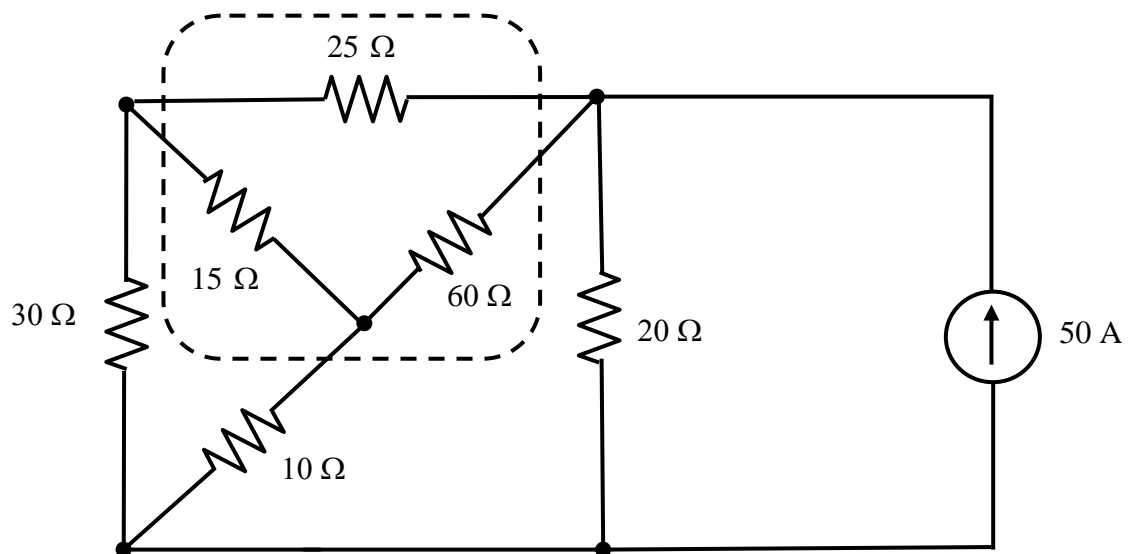


Figure A2

- A3. A balanced star-connected load having a power factor of 0.8 leading, draws 28 A from a 300 V, 50 Hz, three-phase distribution system. Calculate
- (a) the total real and reactive power consumed by the load, and (5 marks)
  - (b) the phase impedance of the star-connected load in polar form. (5 marks)
- A4. A three-phase, 200 V, ABC symmetrical supply serves a balanced delta-connected load of phase impedance  $Z = 8\angle 45^\circ \Omega$ . Taking  $V_{CA}$  as the reference voltage, determine
- (a) the line current  $I_A$ , and (6 marks)
  - (b) draw a phasor diagram showing the reference voltage and line currents. (4 marks)
- A5. A 3-phase star-connected induction motor takes a total power of 25 kW at a power factor of 0.75 lagging from a 3-phase, 400 V, 50 Hz supply. When a three-phase star-connected capacitor bank is added, the overall power factor improves to 0.95 lagging. Calculate:
- (a) the kVAr rating of the capacitor bank, and (6 marks)
  - (b) the phase reactance of the capacitor bank. (4 marks)
- A6. A balanced star-connected load is connected to a 150 V, 50 Hz, three-phase, 3-wire supply. When using the two-wattmeter method to measure the power supplied to the inductive load, the readings on the two wattmeters are 60 W and -24 W respectively. Calculate:
- (a) the power factor and (4 marks)
  - (b) the magnitude of load impedance. (6 marks)

**SECTION B: 2 QUESTIONS** (20 marks each)

- B1(a). Apply Thevenin's Theorem to find the Thevenin equivalent circuit parameters  $V_{TH}$  and  $Z_{TH}$  between terminals A and B for the circuit shown in Figure B1. (Include circuit diagrams for finding  $V_{TH}$  and  $Z_{TH}$ ) (17 marks)
- (b). Draw the Thevenin's equivalent circuit. (3 marks)

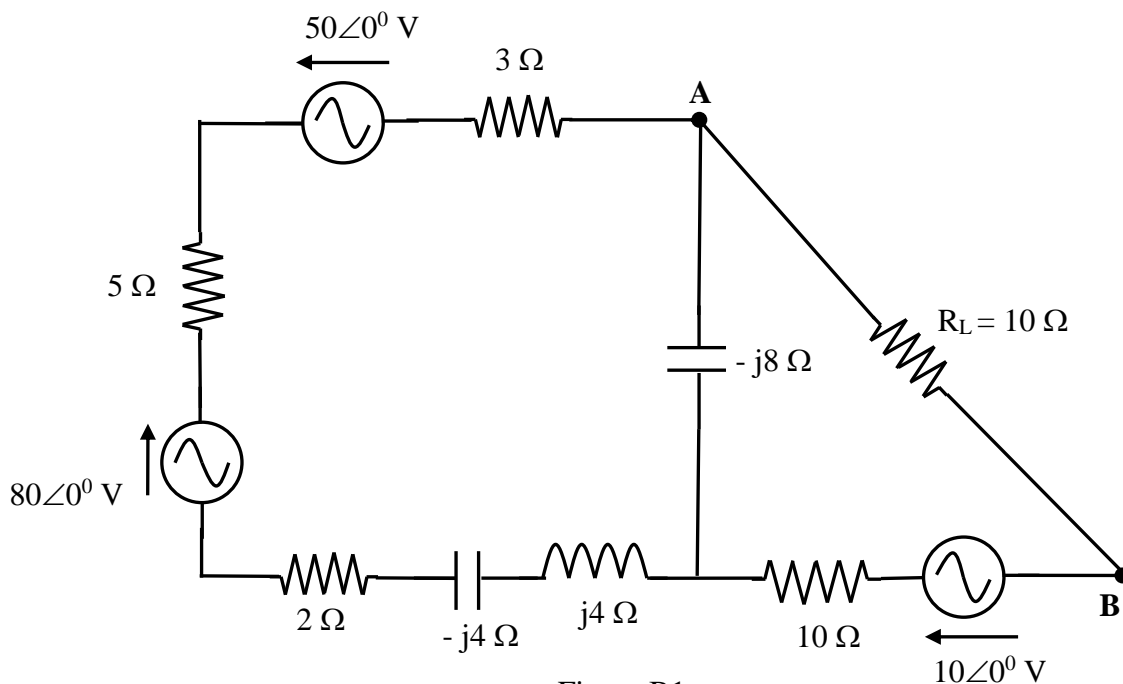


Figure B1

- B2. A 3-phase, ABC sequence, 4 wire, 400 V system has the following loads connected between the Neutral and A, B and C lines respectively:

A to Neutral: 15 kW pure resistive load

B to Neutral: 8 kVAr load at a power factor of 0.8 leading

C to Neutral: 25 kVAr pure inductive load

Taking  $V_{AN}$  as the reference voltage, calculate:

- (a) the line currents ( $I_A$ ,  $I_B$ ,  $I_C$ ), (8 marks)
- (b) the total real, reactive and apparent power, and (10 marks)
- (c) the overall power factor. (2 marks)

- End of Paper -

Formulae

Resistors in series	$R_T = R_1 + R_2 + R_3 + \dots$
Resistors in parallel	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$
Resistors in parallel (for 2 resistors)	$R_T = \frac{R_1 R_2}{R_1 + R_2}$
Voltage Divider Rule	$V_X = \frac{R_X}{R_T} V_S$
Current Divider Rule	$I_1 = \frac{R_2}{R_1 + R_2} I_T$
Source Conversion	$E = I_S R_S \qquad I_S = \frac{E}{R_S}$
Mesh Current Analysis	$[Z] [I] = [V]$
Nodal Voltage Analysis	$[Y] [V] = [I]$
Delta to Star Conversion	$Z_1 = \frac{Z_A Z_C}{Z_A + Z_B + Z_C}$ $Z_2 = \frac{Z_A Z_B}{Z_A + Z_B + Z_C}$ $Z_3 = \frac{Z_B Z_C}{Z_A + Z_B + Z_C}$
Star to Delta Conversion	$Z_A = Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3}$ $Z_B = Z_2 + Z_3 + \frac{Z_2 Z_3}{Z_1}$ $Z_C = Z_1 + Z_3 + \frac{Z_1 Z_3}{Z_2}$
Inductive Reactance	$X_L = 2\pi fL$
Capacitive Reactance	$X_C = \frac{1}{2\pi fC}$
Three Phase Star – Connected Load	$V_L = \sqrt{3} V_{PH}$ $I_L = I_{PH}$ $Z_{PH} = \frac{V_{PH}}{I_{PH}}$

Three Phase Delta - Connected Load	$V_L = V_{PH}$ $I_L = \sqrt{3} I_{PH}$ $Z_{PH} = \frac{V_{PH}}{I_{PH}}$
Three Phase Apparent Power	$S_T = 3 V_{PH} I_{PH} = \sqrt{3} V_L I_L$
Three Phase Active/Real/True Power	$P_T = 3 V_{PH} I_{PH} \cos \phi = \sqrt{3} V_L I_L \cos \phi$
Three Phase Reactive Power	$Q_T = 3 V_{PH} I_{PH} \sin \phi = \sqrt{3} V_L I_L \sin \phi$
Power factor	Power factor = $\cos \phi = \frac{P}{S}$
Two-Wattmeter Method	$W_1 = V_L \times I_L \times \cos (\theta - 30^\circ)$ $W_2 = V_L \times I_L \times \cos (\theta + 30^\circ)$ $P_T = W_1 + W_2$ Power factor = $\cos \left( \tan^{-1} \left[ \sqrt{3} \left( \frac{W_1 - W_2}{W_1 + W_2} \right) \right] \right)$

**ANSWERS:**

A1.  $I_S = 0.71 \text{ A}$ ,  $R = 1.84 \Omega$


A2.  $R_1 = 3.75 \Omega$ ,  $R_2 = 9 \Omega$ ,  $R_3 = 15 \Omega$

$I_{20\Omega} = 28.8 \text{ A}$

A3.  $P_T = 11.64 \text{ kW}$ ,  $Q_T = 8.73 \text{ kVAr}$

$Z = 6.19 \angle -36.87^\circ \Omega$

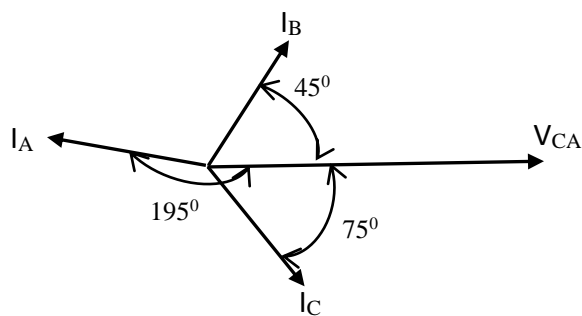
A4.  $I_A = 43.30 \angle -195^\circ \text{ A}$  or  $43.30 \angle 165^\circ \text{ A}$



A5.  $Q_C = 13.84 \text{ kVAr}$ ,  $X_C = 11.57 \Omega$

A6. Power Factor = 0.24 lagging,  $Z_{PH} = 149.31 \Omega$

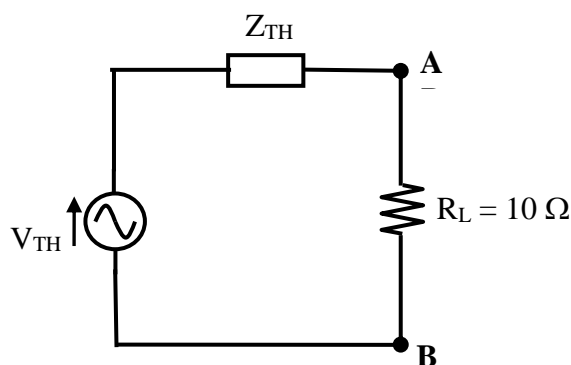B1.  $V_{TH} = 26.16 \angle -33.97^\circ \text{ V}$ ,  $Z_{TH} = 14.74 \angle -19.34^\circ \Omega$



B2.  $I_A = 64.95 \angle 0^\circ \text{ A}$ ,  $I_B = 57.73 \angle -83.13^\circ$ ,  $I_C = 108.25 \angle -330^\circ \text{ A}$  or  $108.25 \angle 30^\circ \text{ A}$

$P_T = 25.67 \text{ kW}$ ,  $Q_T = 17 \text{ kVAr}$ ,  $S_T = 30.79 \text{ kVA}$

Overall power factor = 0.834 lagging