

Tutorial 1


ET0917 / ET0817 / ET0832

RELAY FUNDAMENTALS

MCQ

How many sets of contacts does this relay have?

- a) 1
- b) 2
- c) 3
- d) 4

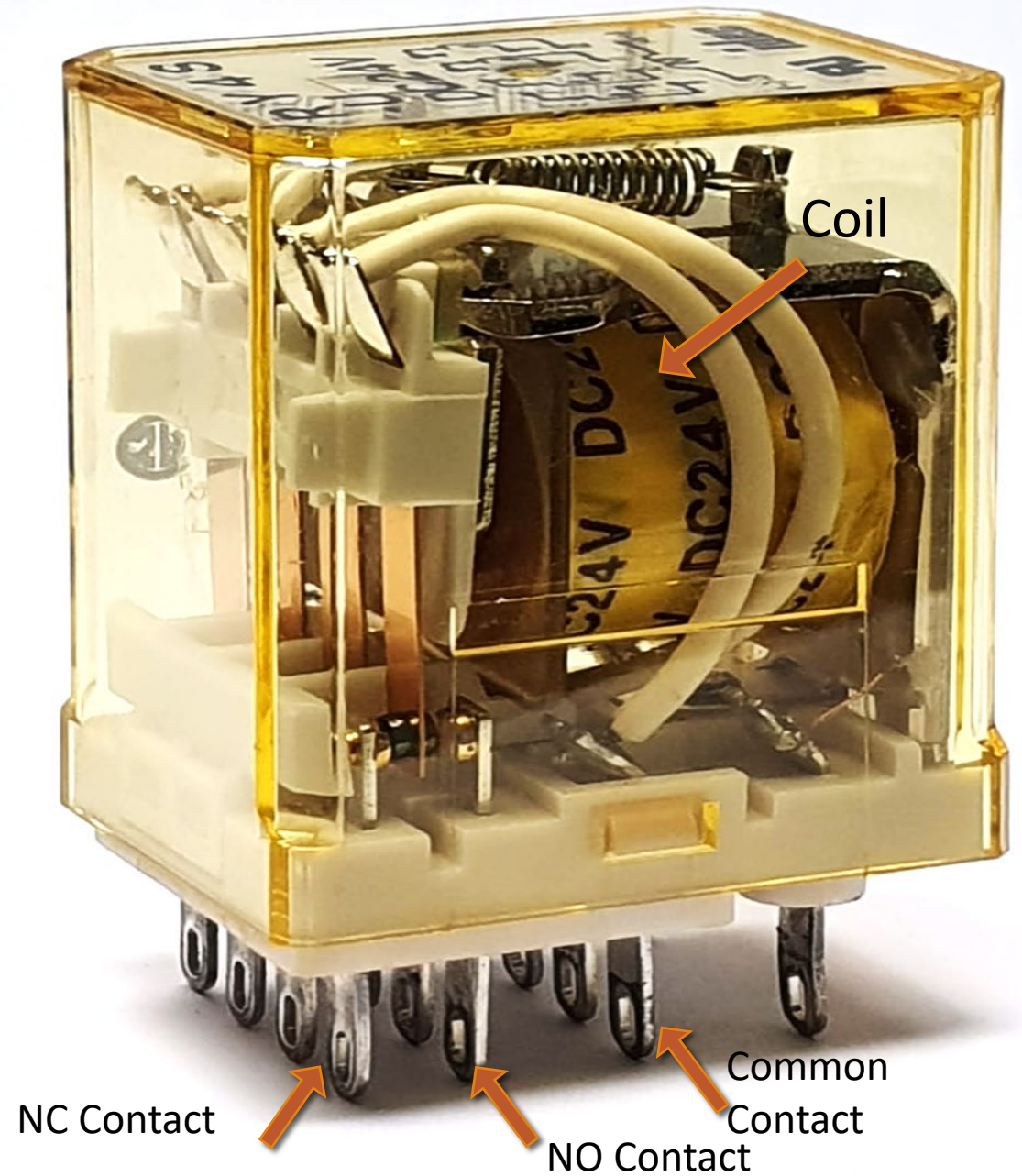


RELAY FUNDAMENTALS

MCQ

This relay is also known as _____ relay.

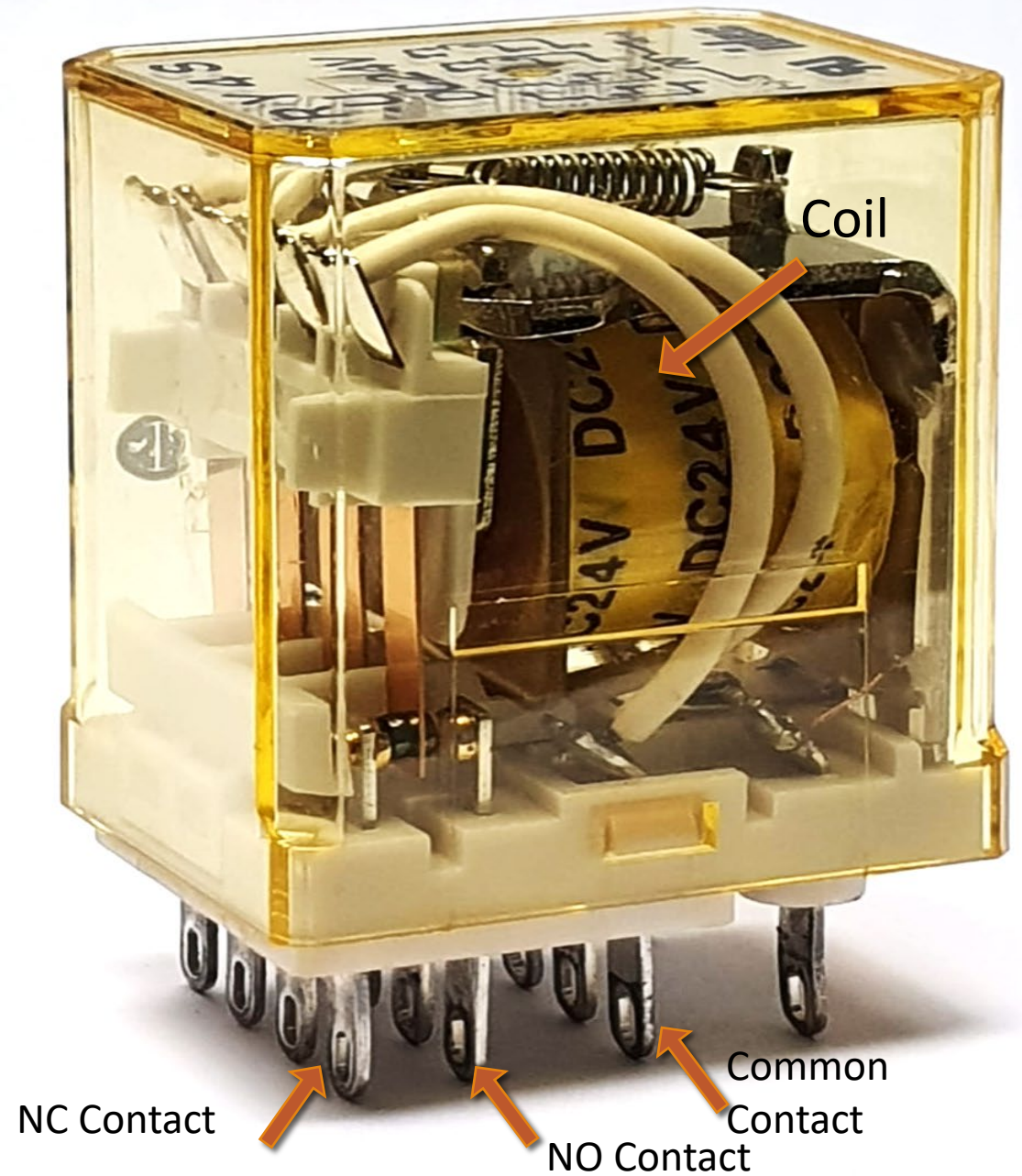- a) SPDT
- b) DPDT
- c) 4PDT
- d) Solid State




RELAY FUNDAMENTALS

MCQ

What is the operating voltage for this relay?

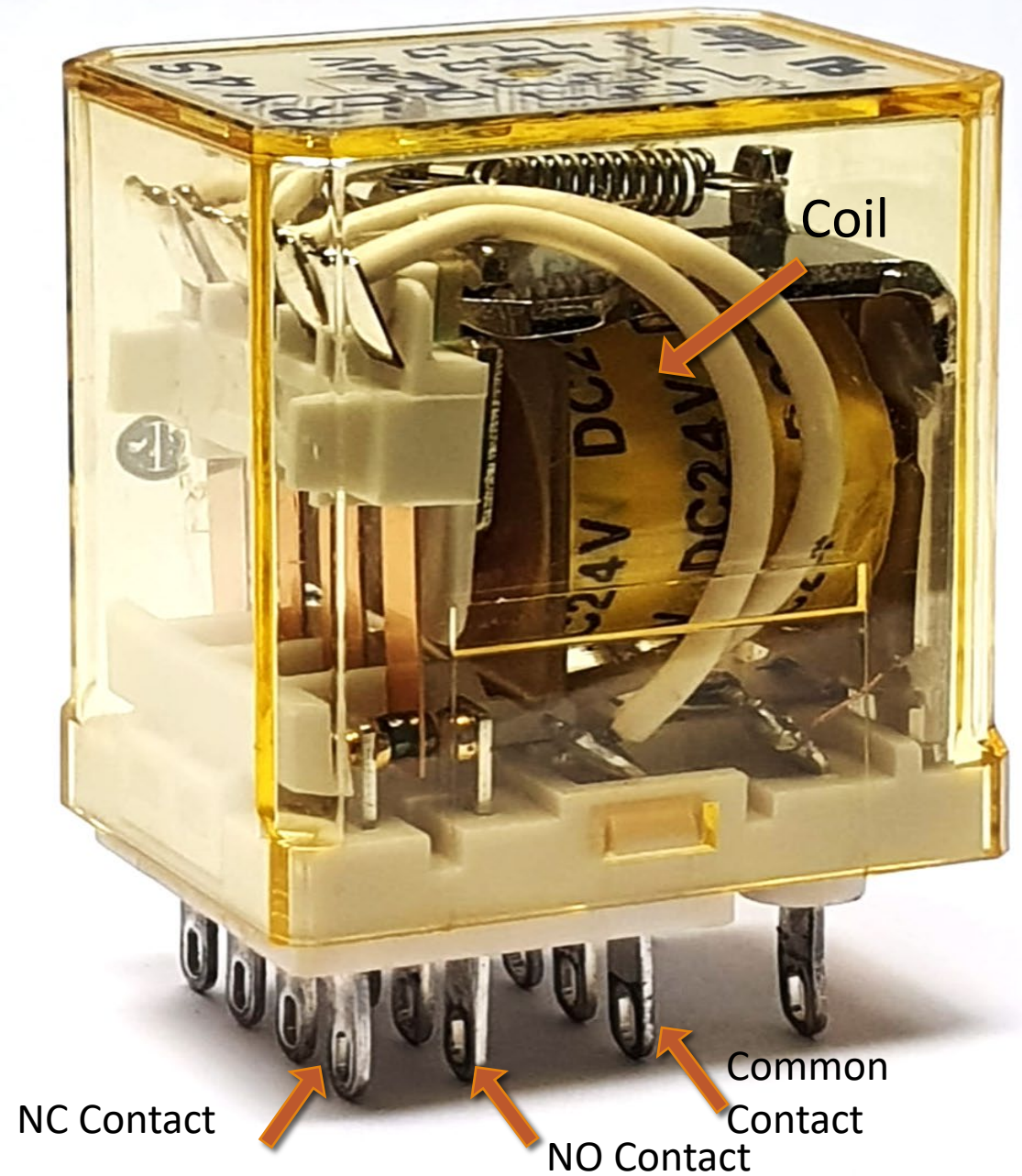
- a) 5 Vdc
- b) 24 Vdc
- c) 24 Vac
- d) 230 Vac



RELAY FUNDAMENTALS

- What is an electromechanical relay?
- How does a relay work?
- Why do we need a relay?
- How to select a relay?

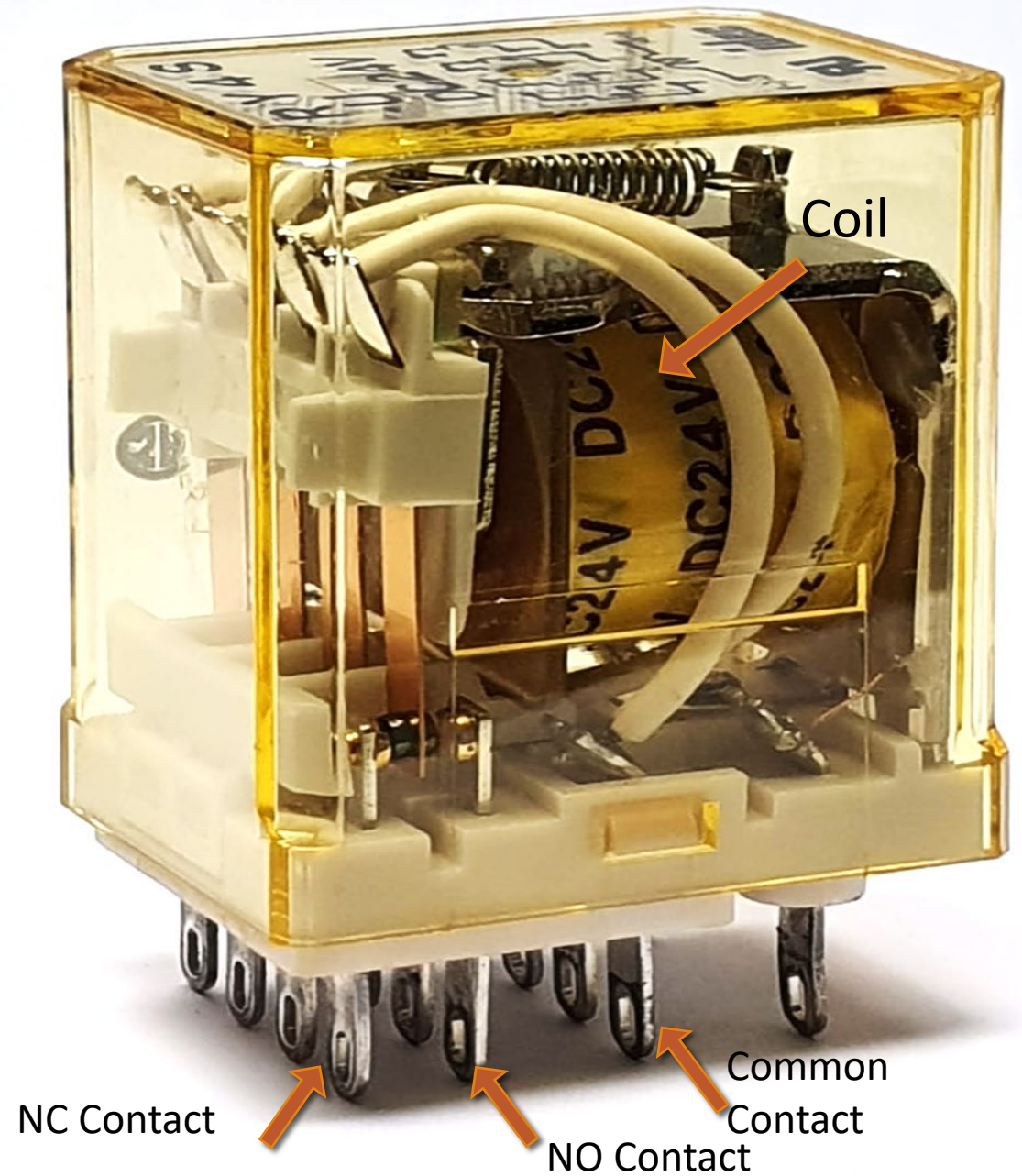In a few words, answer what you understand
(You could submit more than 1 answer)



Q1 - MCQ

The main purpose of inventing PLC is to _____ Hardwired Relay Logic.

- a) replace
- b) understand
- c) simulate
- d) test

Q2 - MCQ

Ladder programming make sense as they are almost _____ to Hardwired Relay logic. Therefore widely understood by technicians and control engineers.


- a) real
- b) replace
- c) identical
- d) virtually

Q3 - MCQ

If the PLC logic needs to be changed, it can be achieved through programming, without _____ at all.

- a) intervention
- b) software
- c) replacement
- d) rewiring

Q4 - MCQ

In PLC ladder diagram, all inputs, sensors, and internal relay contacts, are represented as “contacts” , and all outputs are represented as “_____”.

- a) relays
- b) coils
- c) software
- d) ladder

Q5 – MCQ

Which of the following is NOT considered as benefit of PLC:


- a) Ability to handle multiple inputs and outputs with small footprint
- b) Suitable for industrial environment with electrical noise and vibration
- c) Provide control using wired relay logic
- d) Ease of changing logic

Q6 – MCQ

Select the correct sequence of PLC Scan Cycle

- a) Read Outputs -> Update Inputs -> Execute Program
- b) Read Inputs -> Execute Program -> Update Outputs
- c) Execute Program -> Read Inputs -> Update Outputs
- d) Read Inputs -> Update Outputs -> Execute Program

Q7 – Word

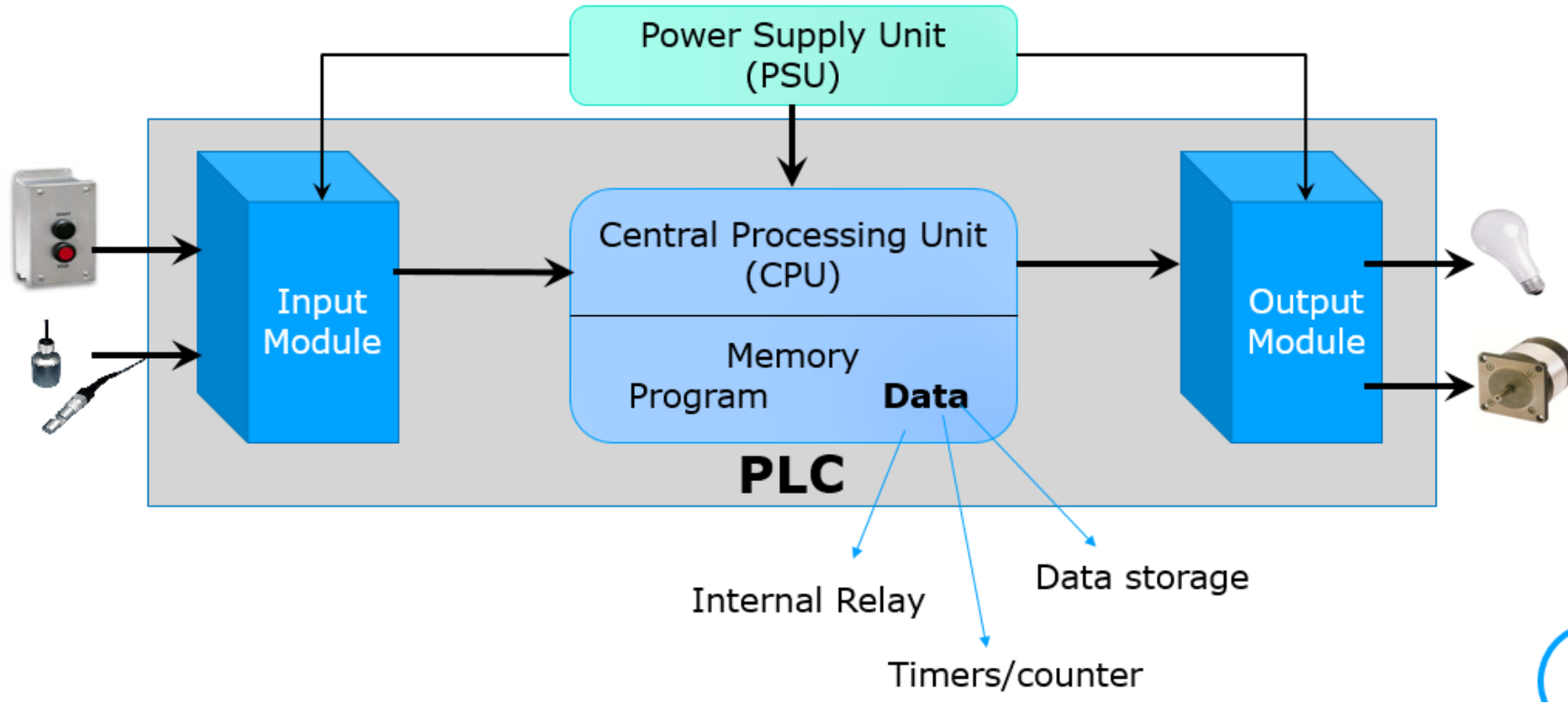

Why do we say that PLC has infinite number of relays, counters & timers?


In a few words, answer what you understand.

(You could submit more than 1 answer)

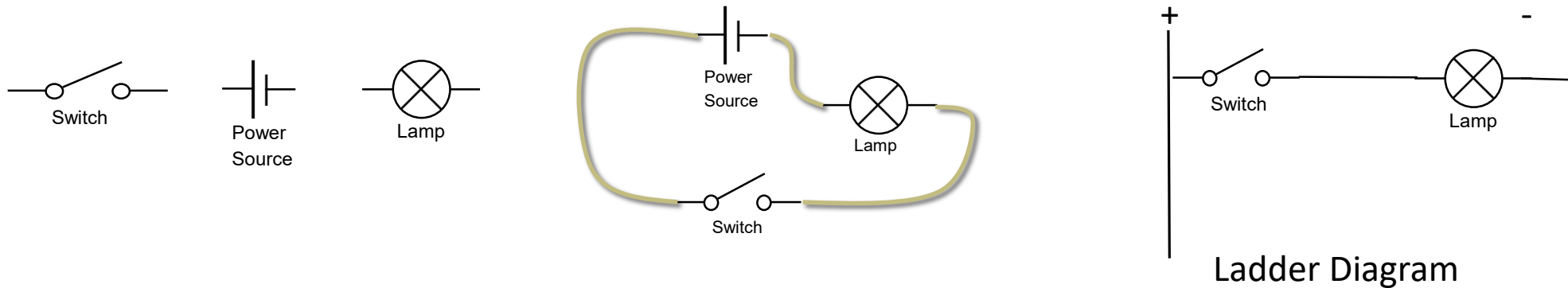Example

Given the components below, **WIRE UP** the switch to light up the lamp.




DRAW circuit representation in Ladder Diagram.



Q8 – Drawing “AND” Logic.

Given the components (2x switches, 1x lamp) **wire** up the required circuit such that Sw A and Sw B needs to be closed to turn on the lamp.





Next, represent in ladder diagram

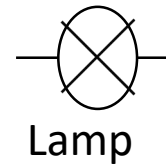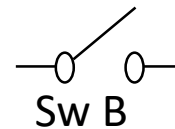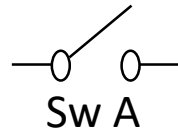

Q9 – Drawing “OR” Logic.

Given the components (2x switches, 1x lamp) **wire** up the required circuit such that Sw A or Sw B needs to be closed to turn on the lamp.

Next, represent in ladder diagram

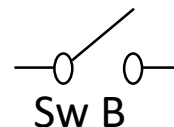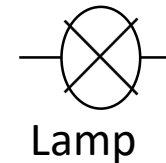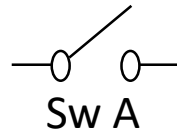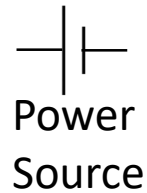

Q10 – Drawing “Latch Circuit”

Given the components (2x Push Buttons, 1x DPDT relay, 1x lamp) **design the ladder diagram** such that push button PB A is pressed momentarily (press and release) would turn on the lamp. The lamp would turn off when push button PB B is pressed.

