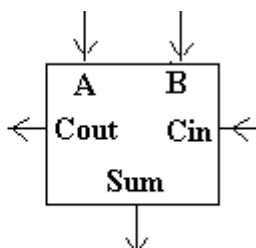
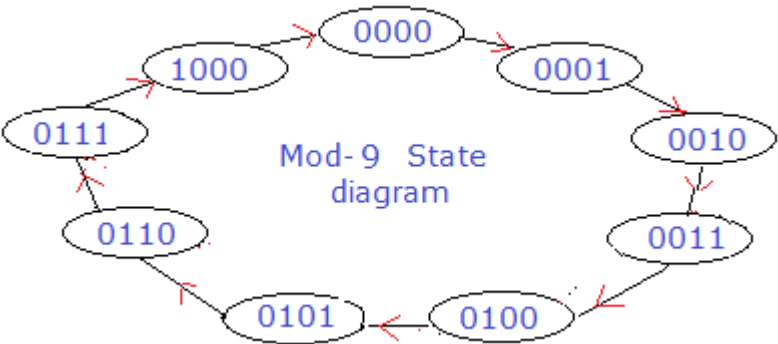
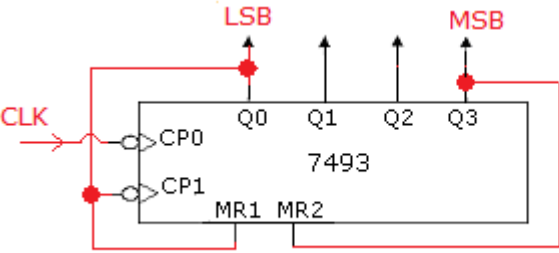
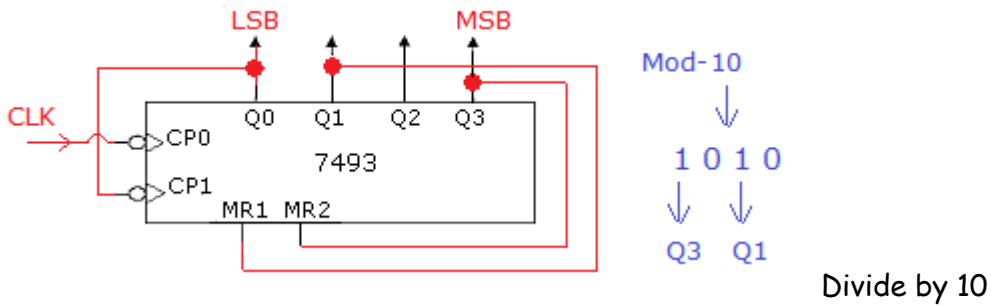


| No | SOLUTION | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
|------------|--|----------|----------|----------|----------|----------|----------|----------|----------|------------------------------|--|------------|---|----------|----------|----------|----------|----------|----------|----------|----------|-----------------------|------------|---|---|---|---|---|---|---|---|---|-----------------------|------------|---|----------|----------|----------|----------|----------|----------|----------|----------|--------|------------|---|----------|----------|----------|----------|----------|----------|----------|----------|--------|------------|---|---|---|---|---|---|---|---|---|------------------|------------|---|----------|----------|----------|----------|----------|----------|----------|----------|------------------|--|--|---|---|---|----|---|---|---|---|--------|--|--|--|--|--|--|-----|---|---|--|---------------------|-----------|---|---|---|---|---|---|---|---|---|------------------------------|
| | <p><u>SECTION – A</u></p> <p>A) 1. (b) 2. (c) 3. (a) 4. (c) 5. (d) 6. (b) 7. (a)</p> <p> 8. (c) 9. (d) 10. (c)</p> <p><u>SECTION – B</u></p> <p>B1) Add -53₁₀ to +88₁₀</p> <p>(a)</p> <table><tr><td></td><td>sign</td><td>64</td><td>32</td><td>16</td><td>8</td><td>4</td><td>2</td><td>1</td><td></td></tr><tr><td>+53</td><td>=</td><td><u>0</u></td><td><u>0</u></td><td><u>1</u></td><td><u>1</u></td><td><u>0</u></td><td><u>1</u></td><td><u>0</u></td><td><u>1</u></td><td>←----- +ve Equivalent</td></tr><tr><td>-53</td><td>=</td><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td><td>←----- 2's complement</td></tr><tr><td>+88</td><td>=</td><td><u>0</u></td><td><u>1</u></td><td><u>0</u></td><td><u>1</u></td><td><u>1</u></td><td><u>0</u></td><td><u>0</u></td><td><u>0</u></td><td>←-----</td></tr><tr><td>+35</td><td>=</td><td><u>1</u></td><td><u>0</u></td><td><u>0</u></td><td><u>1</u></td><td><u>0</u></td><td><u>0</u></td><td><u>0</u></td><td><u>1</u></td><td>←-----</td></tr></table> <p>(b)</p> <p> Add +57₁₀ to +35₁₀ in BCD</p> <table><tr><td>+57</td><td>=</td><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td><td>←----- BCD of 57</td></tr><tr><td>+35</td><td>=</td><td><u>0</u></td><td><u>0</u></td><td><u>1</u></td><td><u>1</u></td><td><u>0</u></td><td><u>1</u></td><td><u>0</u></td><td><u>1</u></td><td>←----- BCD of 35</td></tr><tr><td></td><td></td><td>1</td><td>0</td><td>0</td><td>10</td><td>1</td><td>1</td><td>0</td><td>0</td><td>←-----</td></tr><tr><td></td><td></td><td></td><td></td><td></td><td></td><td>+ 1</td><td>1</td><td>0</td><td></td><td>←----- Adjust_by +6</td></tr><tr><td>92</td><td>=</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>←----- correct Result</td></tr></table> | | sign | 64 | 32 | 16 | 8 | 4 | 2 | 1 | | +53 | = | <u>0</u> | <u>0</u> | <u>1</u> | <u>1</u> | <u>0</u> | <u>1</u> | <u>0</u> | <u>1</u> | ←----- +ve Equivalent | -53 | = | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | ←----- 2's complement | +88 | = | <u>0</u> | <u>1</u> | <u>0</u> | <u>1</u> | <u>1</u> | <u>0</u> | <u>0</u> | <u>0</u> | ←----- | +35 | = | <u>1</u> | <u>0</u> | <u>0</u> | <u>1</u> | <u>0</u> | <u>0</u> | <u>0</u> | <u>1</u> | ←----- | +57 | = | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | ←----- BCD of 57 | +35 | = | <u>0</u> | <u>0</u> | <u>1</u> | <u>1</u> | <u>0</u> | <u>1</u> | <u>0</u> | <u>1</u> | ←----- BCD of 35 | | | 1 | 0 | 0 | 10 | 1 | 1 | 0 | 0 | ←----- | | | | | | | + 1 | 1 | 0 | | ←----- Adjust_by +6 | 92 | = | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | ←----- correct Result |
| | sign | 64 | 32 | 16 | 8 | 4 | 2 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| +53 | = | <u>0</u> | <u>0</u> | <u>1</u> | <u>1</u> | <u>0</u> | <u>1</u> | <u>0</u> | <u>1</u> | ←----- +ve Equivalent | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| -53 | = | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | ←----- 2's complement | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| +88 | = | <u>0</u> | <u>1</u> | <u>0</u> | <u>1</u> | <u>1</u> | <u>0</u> | <u>0</u> | <u>0</u> | ←----- | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| +35 | = | <u>1</u> | <u>0</u> | <u>0</u> | <u>1</u> | <u>0</u> | <u>0</u> | <u>0</u> | <u>1</u> | ←----- | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| +57 | = | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | ←----- BCD of 57 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| +35 | = | <u>0</u> | <u>0</u> | <u>1</u> | <u>1</u> | <u>0</u> | <u>1</u> | <u>0</u> | <u>1</u> | ←----- BCD of 35 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| | | 1 | 0 | 0 | 10 | 1 | 1 | 0 | 0 | ←----- | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| | | | | | | + 1 | 1 | 0 | | ←----- Adjust_by +6 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 92 | = | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | ←----- correct Result | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |

| No | SOLUTION | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
|-----|---|-----|------|-----|------|-----|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| B2 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| (a) | <div>Symbol of Full Adder</div> <div></div> | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| (b) | <table><tr><th>A</th><th>B</th><th>Cin</th><th>Cout</th><th>Sum</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr></table> <p><u>NB</u> Output combinations obtained by adding A + B + Cin</p> $\text{Sum} = \overline{A} \overline{B} \text{Cin} + \overline{A} B \overline{\text{Cin}} + A \overline{B} \overline{\text{Cin}} + A B \text{Cin}$ $\text{Cout} = \overline{A} B \text{Cin} + A \overline{B} \text{Cin} + A B \overline{\text{Cin}} + A B \text{Cin}$ | A | B | Cin | Cout | Sum | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| A | B | Cin | Cout | Sum | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 1 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| (c) | $\begin{aligned} \text{Sum} &= \overline{A} \overline{B} \text{Cin} + \overline{A} B \overline{\text{Cin}} + A \overline{B} \overline{\text{Cin}} + A B \text{Cin} \\ &= \overline{A} (B \overline{\text{Cin}} + \overline{B} \text{Cin}) + A (\overline{B} \overline{\text{Cin}} + B \text{Cin}) \\ &= \overline{A} (B \oplus \text{Cin}) + A (\overline{B \oplus \text{Cin}}) \\ &= A \oplus (B \oplus \text{Cin}) \\ &= A \oplus B \oplus \text{Cin} \end{aligned}$ | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |

| No | SOLUTION |
|----|--|
| B3 | <p>(a)</p> <p>Important points to note Correct Connections between the three flip-flops. Logic H to the J and K inputs of each JK flip-flop for toggle mode.</p> <p>(b)</p> <p>(c)</p> <p>Given the clock frequency is 3000 Hz Frequency at Q2 (MSB) = $3000/6 = 500$ Hz Duty cycle at Q2 (MSB) = $2/6 * 100 \% = 33.3\%$</p> |

| | SOLUTION |
|---|--|
| <p>C1</p> <p>(a)</p> <p>(b)</p> <p>(c)</p> | <p><u>Section C (25 marks)</u></p> <p>Counter with table given is a Mod-9 counter</p>  <p>Mod-9 State diagram</p>  <p>Mod-9</p> <p>1 0 0 1</p> <p>↓ ↓</p> <p>Q3 Q0</p> <p>NB: Important points to note:</p> <ul style="list-style-type: none"> Use of 4 flip-flops & connection between flip-flops Indicate correct MSB & LSB outputs. Correct CLK input used . Correct feedback from outputs to MR1 and MR2. |

| No | SOLUTION |
|-----|---|
| (d) | <p>If the signal frequency at the Mod-9 MSB output is 10kHz, then the clock frequency applied is $9 \times 10 \text{ kHz}$ $= 90 \text{ kHz}$</p> |
| (e) | <p>To obtain a 1 kHz signal from 10 kHz, a mod-10 counter is required. Using one 7493, the connections is as follows:</p>  <p><u>Important points to note</u> Q0 to CP1 connection for 4 Flip-flops connection. CLK to CP0. MSB and LSB indication. Correct Feedback from outputs to MR1/MR2.</p> |