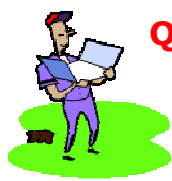


## Tutorial 4

### Thevenin's and Norton's Theorems

1. Obtain the Thevenin and Norton equivalent circuits between terminals AB for the active network shown in Figure 1.  
**Ans:**  $V_{TH} = 6.29 \text{ V}$  with B +Ve,  $R_{TH} = 9.43 \Omega$ ,  $I_N = -0.67 \text{ A}$ ,  $R_N = 9.43 \Omega$
2. For the circuit shown in Figure 2, find the current through the  $8 \Omega$  using the Thevenin and Norton equivalent circuits.  
**Ans:**  $V_{TH} = 4.27 \text{ V}$ ,  $R_{TH} = 2.69 \Omega$ ,  $I_N = 1.59 \text{ A}$ ,  $R_N = 2.69 \Omega$ ,  $I_{8\Omega} = 0.4 \text{ A}$
3. Obtain the Thevenin equivalent and Norton equivalent by applying the respective theorems as seen across terminals AB of the circuit in Figure 3.  
**Ans:**  $V_{TH} = 11.17 \angle -63.4^\circ \text{ V}$ ,  $Z_{TH} = 10.6 \angle 45^\circ \Omega$ ,  $I_N = 1.06 \angle -108.4^\circ \text{ A}$ ,  
 $Z_N = 10.6 \angle 45^\circ \Omega$
4. For the circuit shown in Figure 4, apply Thevenin's and Norton's theorems to
  - (a) Find the equivalent circuit parameters between the terminals A and B.
  - (b) Calculate the voltage across the load  $R_L$ .**Ans:**  $V_{AB} = V_{TH} = -5 \text{ V}$ ,  $R_{TH} = 15 \Omega$ ,  $I_{AB} = I_N = -0.33 \text{ A}$ ,  $R_N = 15 \Omega$ ,  $V_{RL} = 2.22 \text{ V}$
5. For the circuit shown in Figure 5,
  - (a) Applying Norton's theorem, find the Norton equivalent circuit parameters  $I_N$  and  $R_N$  at the terminals AB.
  - (b) Using the Norton equivalent circuit obtained above calculate the current flowing and voltage across the load  $R_L$ .
  - (c) Convert the Norton equivalent circuit to find its Thevenin equivalent circuit.**Ans:**  $I_N = 1.818 \text{ A}$ ,  $R_N = 5.5 \Omega$ ,  $I_{RL} = 1.33 \text{ A}$ ,  $V_{RL} = 2.66 \text{ V}$ ,  $V_{TH} = 10 \text{ V}$ ,  $R_{TH} = 5.5 \Omega$



**Quiz** – 3 questions  
(Thevenin's Theorem)  
– 3 questions  
(Norton's Theorem)

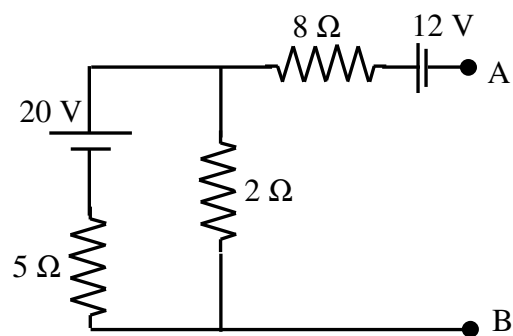


Figure 1

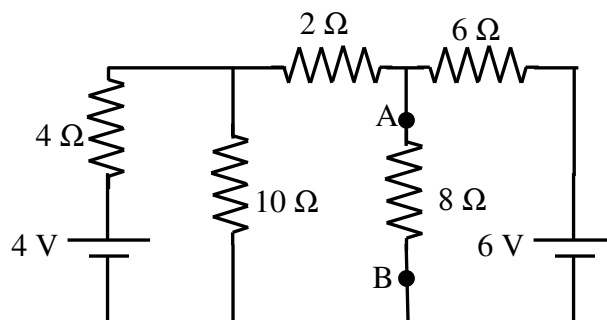


Figure 2

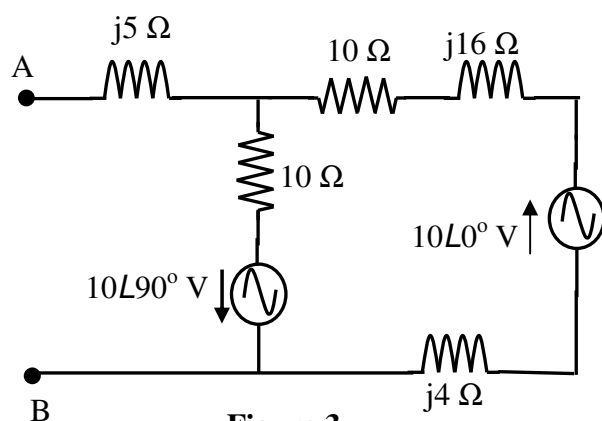


Figure 3

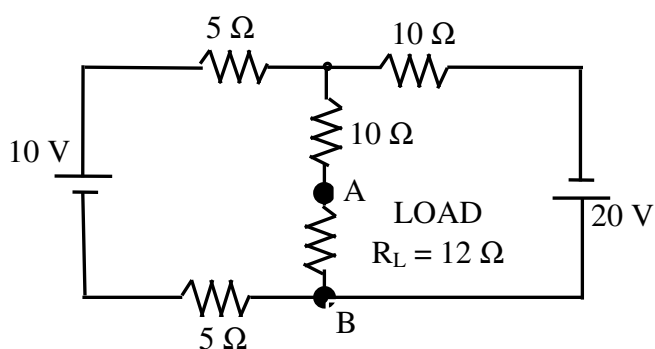


Figure 4

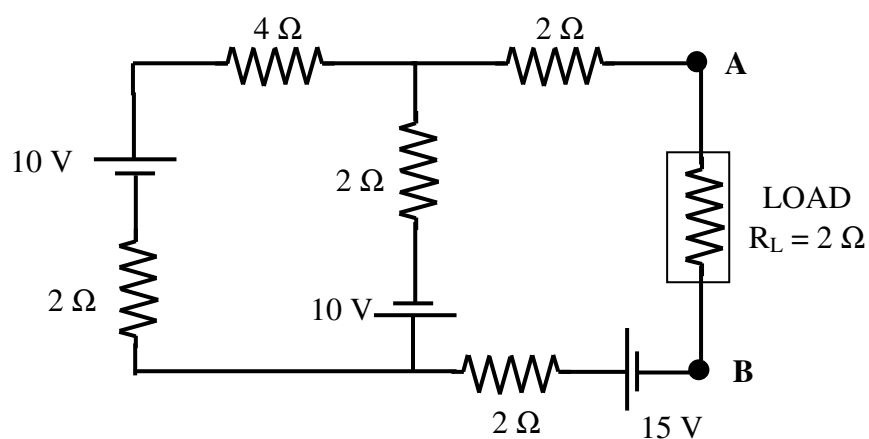


Figure 5