

2019/2020 SEMESTER ONE EXAMINATION

Diploma in Aerospace Electronics (DASE) 2<sup>nd</sup> Year FT  
Diploma in Engineering with Business (DEB) 3<sup>rd</sup> Year FT  
Diploma in Electrical & Electronic Engineering (DEEE) 2<sup>nd</sup> Year FT  
Diploma in Engineering Systems (DES) 2<sup>nd</sup> Year FT  
Diploma in Energy Systems and Management (DESM) 2<sup>nd</sup> Year FT

**CIRCUIT THEORY & ANALYSIS**

Time Allowed: 2 Hours

---

Instructions to Candidates

1. The examination rules set out on the last page of the answer booklet are to be complied with.
2. This paper consists of **TWO** sections:
  - Section A - 6 Short Questions, 10 marks each.
  - Section B - 2 Long Questions, 20 marks each.
3. **ALL** questions are **COMPULSORY**.
4. All questions are to be answered in the answer booklet. Start each question on a new page.
5. Fill in the Question Numbers in the boxes found on the front cover of the answer booklet under the column "Question Answered".
6. This paper consists of 6 pages, inclusive of the formulae sheet.

**SECTION A: 6 QUESTIONS** (10 marks each)

- A1. Using the source conversion method, simplify the circuit shown in Figure A1 to its equivalent current source across terminals X and Y. (10 marks)

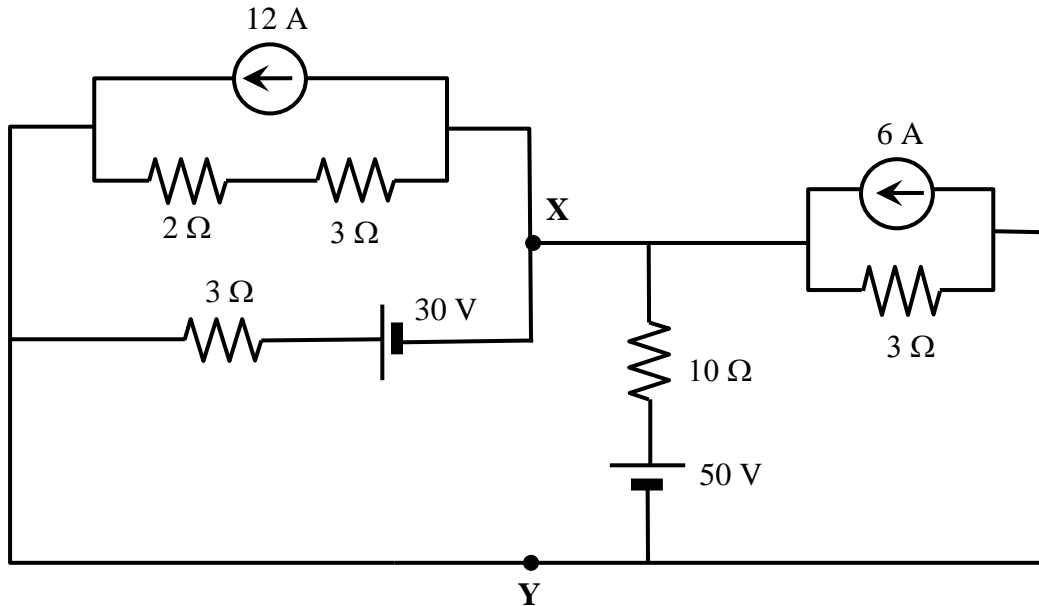


Figure A1

- A2. For the circuit shown in Figure A2,
- convert the delta-connected resistors as shown in the dotted box into an equivalent star-connection, and (6 marks)
  - hence calculate the total supply current. (4 marks)

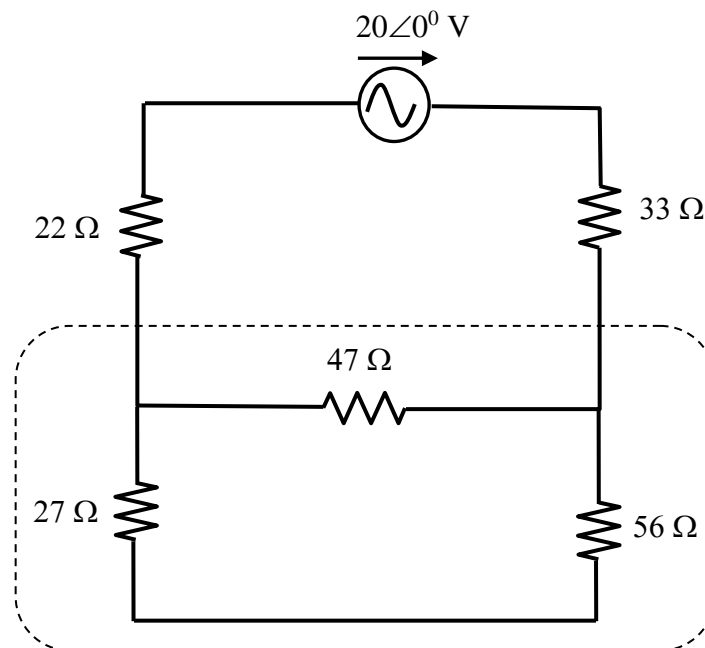


Figure A2

A3. A three-phase balanced star-connected load is connected to a 350 V, 50 Hz, ABC supply. Taking  $V_{BC}$  as the reference voltage, the line current  $I_B$  is  $15\angle-65^\circ$  A.

- (a) Calculate the line currents ( $I_A$ ,  $I_C$ ), (2 marks)
- (b) Calculate the value of the resistance for each phase of the load. (4 marks)
- (c) Draw a phasor diagram showing the reference voltage and line currents. (4 marks)

A4. A three-phase, 3-wire, ABC system supplies a delta-connected load of phase impedance  $(10 - j8) \Omega$ . The line current  $I_A$  drawn is found to be  $60\angle-60^\circ$  A.

- (a) Calculate the line voltage  $V_{AB}$ , (4 marks)
- (b) Calculate the total real power. (2 marks)
- (c) Draw a phasor diagram showing the line current  $I_A$  and all the phase currents. (4 marks)

A5. A three phase, four-wire, 415 V system has the following currents flowing towards the loads:

$$I_A = 12\angle-240^\circ \text{ A}, I_B = 30\angle40^\circ \text{ A and } I_C = 25\angle-30^\circ \text{ A}$$

Taking  $V_{BN}$  as the reference voltage, calculate

- (a) the neutral current flowing from the load to the supply, (2 marks)
- (b) the phase impedances  $Z_B$  and  $Z_C$ , (4 marks)
- (c) the apparent and reactive power in the 'C' phase. (4 marks)

A6. A balanced delta-connected inductive load is connected to a 300 V, 50 Hz, three-phase, 3-wire supply. When using the two-wattmeter method to measure the power supplied to the load, the readings on the two wattmeters are 1500 W and 500 W. Calculate

- (a) the total power, (2 marks)
- (b) the power factor, (3 marks)
- (c) the phase impedance of the delta-connected load in polar form. (5 marks)

**SECTION B: 2 QUESTIONS** (20 marks each)

B1(a). For the network shown in Figure B1,

- (i) write the mesh current equations for  $I_1$  and  $I_2$  in matrix form by inspection, and hence (9 marks)
  - (ii) determine the voltage across terminals X and Y. (8 marks)
- (b). If the  $4\angle 0^\circ$  V supply is short-circuit, determine the total supply current. (3 marks)

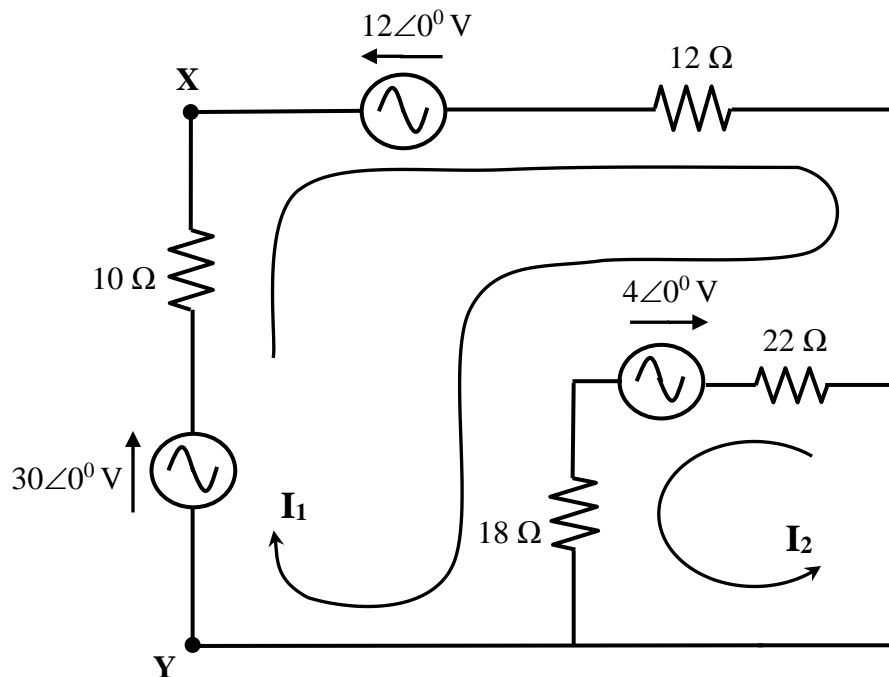


Figure B1

B2(a). A balanced star-connected load of phase impedance  $(6 + j8) \Omega$  is connected to a three-phase, 3-wire, 400 V, ABC system. Determine

- (i) the power factor, (3 marks)
  - (ii) the total apparent, real and reactive power of the star-connected load. (8 marks)
- (b). A 10 kVAR three-phase capacitor bank is connected across the load terminals, determine
- (i) the overall apparent, real and reactive power, (6 marks)
  - (ii) the new power factor. (3 marks)

- End of Paper -


Formulae

Resistors in series	$R_T = R_1 + R_2 + R_3 + \dots$
Resistors in parallel	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$
Resistors in parallel (for 2 resistors)	$R_T = \frac{R_1 R_2}{R_1 + R_2}$
Voltage Divider Rule	$V_x = \frac{R_x}{R_T} V_s$
Current Divider Rule (for 2 resistors)	$I_1 = \frac{R_2}{R_1 + R_2} I_T$
Source Conversion	$E = I_s R_s \qquad I_s = \frac{E}{R_s}$
Mesh Current Analysis	$[Z] [I] = [V]$
Nodal Voltage Analysis	$[Y] [V] = [I]$
Delta to Star Conversion	$Z_1 = \frac{Z_A Z_C}{Z_A + Z_B + Z_C}$ $Z_2 = \frac{Z_A Z_B}{Z_A + Z_B + Z_C}$ $Z_3 = \frac{Z_B Z_C}{Z_A + Z_B + Z_C}$
Star to Delta Conversion	$Z_A = Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3}$ $Z_B = Z_2 + Z_3 + \frac{Z_2 Z_3}{Z_1}$ $Z_C = Z_1 + Z_3 + \frac{Z_1 Z_3}{Z_2}$
Inductive Reactance	$X_L = 2\pi f L$
Capacitive Reactance	$X_C = \frac{1}{2\pi f C}$
Three Phase Star – Connected Load	$V_L = \sqrt{3} V_{PH}$ $I_L = I_{PH}$ $Z_{PH} = \frac{V_{PH}}{I_{PH}}$

Three Phase Delta - Connected Load	$V_L = V_{PH}$ $I_L = \sqrt{3} I_{PH}$ $Z_{PH} = \frac{V_{PH}}{I_{PH}}$
Three Phase Apparent Power	$S_T = 3 V_{PH} I_{PH} = \sqrt{3} V_L I_L$
Three Phase Active/Real/True Power	$P_T = 3 V_{PH} I_{PH} \cos \phi = \sqrt{3} V_L I_L \cos \phi$
Three Phase Reactive Power	$Q_T = 3 V_{PH} I_{PH} \sin \phi = \sqrt{3} V_L I_L \sin \phi$
Power factor	Power factor = $\cos \phi = \frac{P}{S}$
Two-Wattmeter Method	$W_1 = V_L \times I_L \times \cos (\theta - 30^\circ)$ $W_2 = V_L \times I_L \times \cos (\theta + 30^\circ)$ $P_T = W_1 + W_2$ Power factor = $\cos \left( \tan^{-1} \left[ \sqrt{3} \left( \frac{W_1 - W_2}{W_1 + W_2} \right) \right] \right)$

Answers:

A1

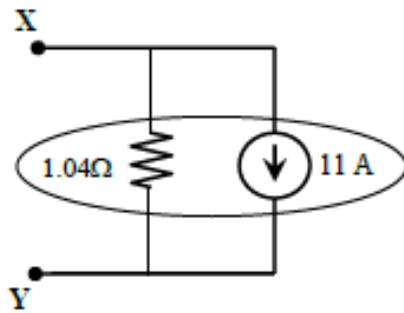

A2

(a)  $R_1 = 9.76\Omega$ ;  $R_2 = 11.63\Omega$ ;  $R_3 = 20.25\Omega$

(b)  $I_T = 0.24\text{ A}$


A3

(a)  $I_A = 15\angle -305^\circ$  or  $15\angle 55^\circ\text{ A}$

$I_C = 15\angle -185^\circ$  or  $15\angle 175^\circ\text{ A}$

(b)  $R_{PH} = 11.03\ \Omega$

(c)

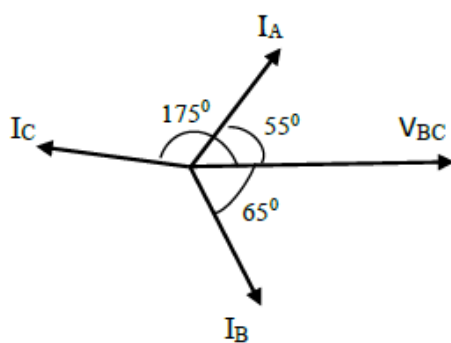

A5

(a)  $I_N = 42.28\angle 23.97^\circ\text{ A}$

(b)  $Z_B = 7.99\angle -40^\circ$

$$Z_C = 9.58 \angle -90^\circ$$

(c)  $S_C = 5.99 \text{ kVA}$

$$Q_C = 5.99 \text{ kVAR}$$

A6

(a)  $P_T = 2 \text{ kW}$

(b) power factor = 0.756 lagging

(c)  $Z_{PH} = 102.04 \angle 40.89^\circ$

B1

(a)

(i)  $\begin{bmatrix} 62 & 40 \\ 40 & 40 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 14 \\ -4 \end{bmatrix}$

(ii)  $V = 21.8 \text{ V}$  or  $-21.8 \text{ V}$

(b)  $I_T = 0.82 \text{ A}$

B2

(a)

(i) Power factor = 0.6 lagging

(ii)  $S_T = 16 \text{ kVA}$        $P_T = 9.6 \text{ kW}$        $Q_T = 12.8 \text{ kVAR}$

(b)  $S_T = 10 \text{ kVA}$        $P_T = 9.6 \text{ kW}$        $Q_T = 2.8 \text{ kVAR}$

(ii) new power factor = 0.96 lagging