

SAMPLE SUMMATIVE CLASS TEST

Diploma in Electrical & Electronic Engineering (DEEE)

2nd Year FT

CA8

DIGITAL SYSTEM DESIGN (ET0901)

Time Allowed: 50 Minutes

Instructions to Candidates:

- This paper consists of TWO sections:
 Section A - 10 Multiple Choice Questions, (40%)
 Section B - 2 Long Questions, (60%)
- All questions are COMPULSORY.
- Section A** : ONLINE using Blackboard . Require Lockdown Browser.
 Go to BB => Assessment < Tab > => SummativeClassTest_MCQ
 Note: Questions similar to Tutorials MCQs. No sample questions for MCQs in this SAMPLE paper.
- Section B** : Write your working in this question paper.
- This test paper consists of 5 pages.
- Submit this question paper to the invigilator after the test.
- Ask the lecturer to fill in the Section A (MCQ) marks

Name : _____ Admin _____ Class _____

QUESTION ANSWERED	MARKS	
A(MCQ)		
B1		
B2		
Total		
Percentage		

SECTION B

ANSWER ALL QUESTIONS

- B1 (a) Derive the simplified Boolean expressions for D & E in the lookup table shown in Figure B1(a). [10 marks]

 


Figure B1(a)

Answer for B1(a)

- (b) Write the Verilog code for the circuit in Figure B1(b) using gate instantiations. [20 marks]

 


Figure B1(b)

Answer for B1(b)

B2. Figure B2 shows a Verilog code for a sequence detector.

- (a) Draw the state diagram for this sequence detector showing the state name, input w and output z. Label the reset state. [20 marks]
- (b) Determine the number of flip-flops required for this sequence detector. [5 marks]
- (c) What is the input sequence that it is able to detect? [5 marks]

```
module detector (Clock, Reset, w, z);  
  input Clock, Reset, w;  
  output z;  
  reg [2: 1] y, Y;  
  parameter [2:1] A=2'b00, B=2'b01, C=2'b10, D=2'b11;  
  // Define the next state combinational circuit  
  always @(w,y)  
    case (y)  
      A: if (w) Y=B;  
        else Y=A;  
      B: if (w) Y=B;  
        else Y=C;  
      C: if (w) Y=D;  
        else Y=A;  
      D: if (w) Y=B;  
        else Y=C;  
      default: Y = 2'bxx;  
    endcase  
  // Define the sequential block  
  always @(posedge Reset, posedge Clock)  
    if (Reset==1) y<= A;  
    else y <= Y;  
  // Define output  
  assign z = (y == D);  
endmodule
```

Figure 2

Answer for B2

***** End of Paper *****