

Tutorial 3

ET0917 / ET0817 / ET0832

PROGRAMMING TIMER, COUNTER, EDGE DETECTION, SET, RESET



Q1 - MCQ


The hotel would cut off the power to the room 5 seconds after the access card is removed. Which type of timer is the most suitable?

- a) Pulse Timer
- b) On delay timer
- c) Off delay timer
- d) Retentive Timer

Q2 - MCQ

Which type of timer correspond to the timing diagram?

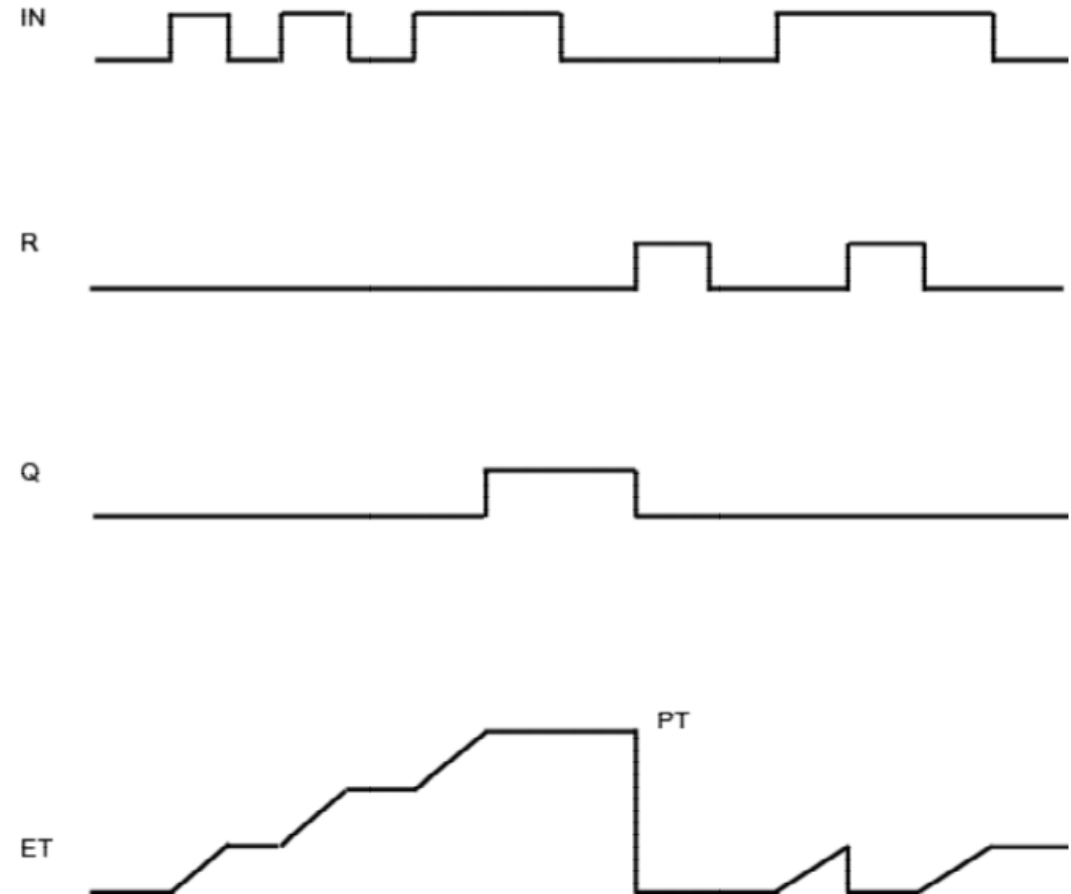
- a) Pulse Timer
- b) On delay timer
- c) Off delay timer
- d) Retentive Timer



Q3 - MCQ

What will happen when Tag_PV = 3, TagIn_1 = 0 and TagIn_2 = 1?

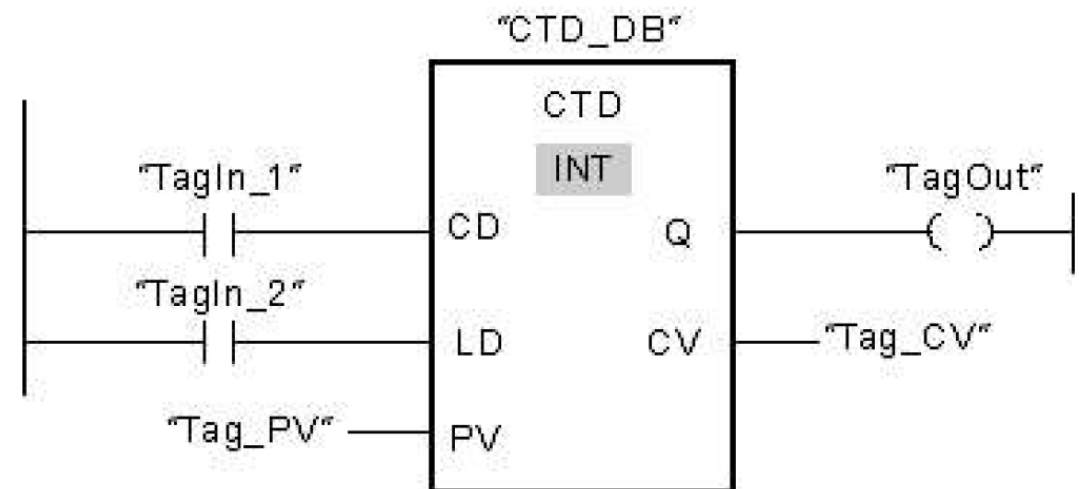
- a) Tag_CV = 0
- b) Tag_CV = 1
- c) Tag_CV = 2
- d) Tag_CV = 3



Q4 - MCQ

When will %M0.5 turn on for 1 scan cycle?

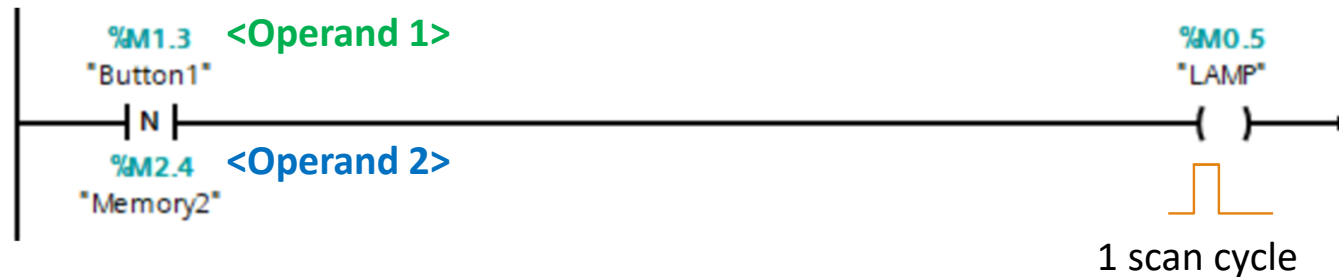- a) When Button1 %M1.3 is pressed (off to on state)
- b) When Button1 %M1.3 is released (on to off state)
- c) When Button1 %M1.3 is pressed and held ON
- d) This is an invalid operation, %M0.5 will not turn on



Q5 – Tank Level Control

1. Prepare I/O table for physical input/output
2. Draw a flow chart and implement ladder diagram

When system starts, and Level Switch High (LSH) (NC) is not activated, SOL A will open (ON) to fill the tank.

When the tank is full - LSH is activated,


SOL A will close (OFF)

Agitator M1 will run (ON) for 30s

After 30s,


Agitator M1 will stop

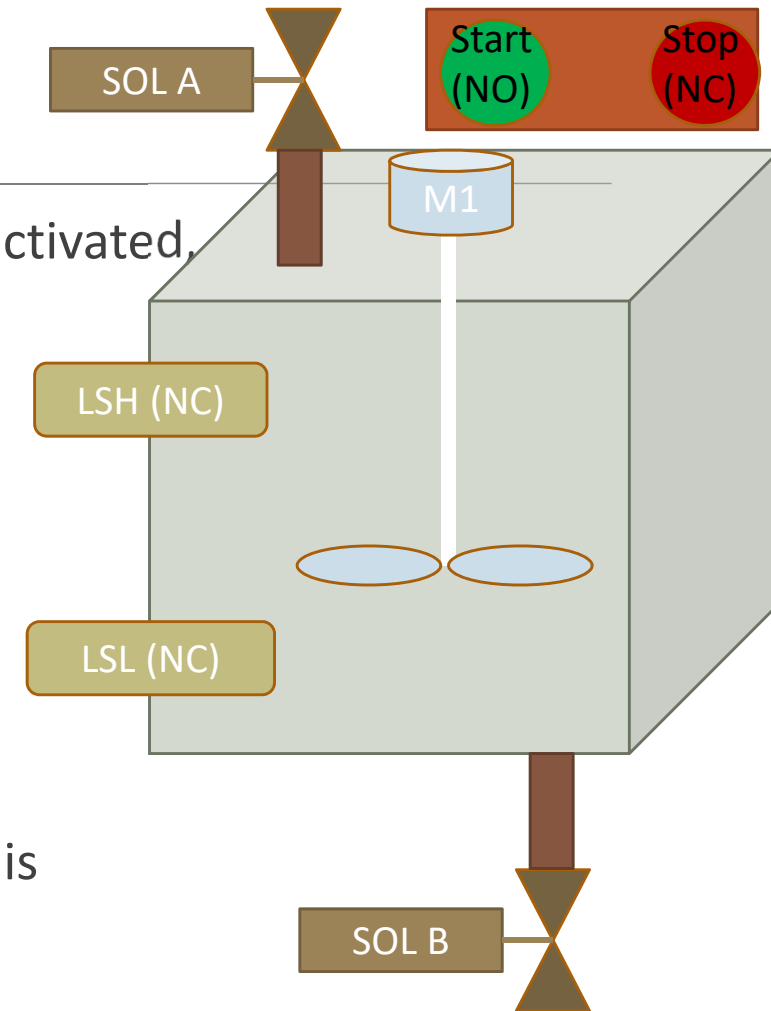SOL B will open (ON) to drain till Level Switch Low (LSL) (NC) is activated



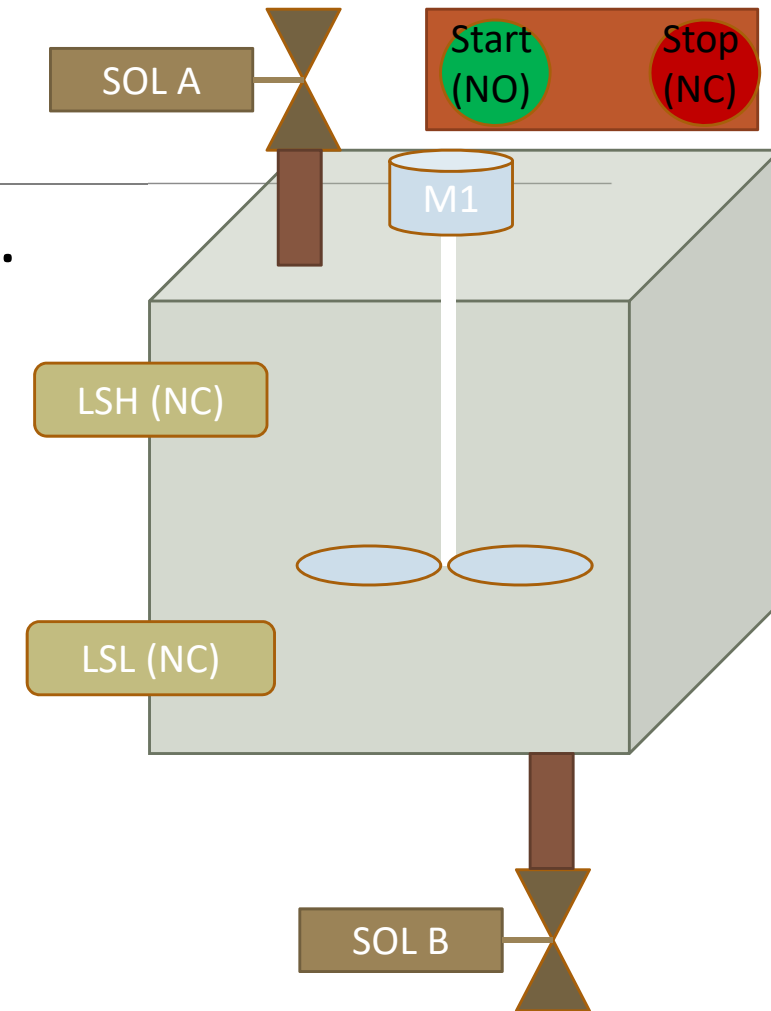Q6 – Tank Level Control

**Modify Q6 flow chart to allow repeat of the process 3 times.
Implement this modification in ladder diagram**



Q7 –Duty Standby Pump

Design a Ladder logic:

Duty Cycle Change Over Pump – 2 Pumps will alternate the operation.

When Start button (NO) is pressed, Pump 1 will run


Pump 1 will stop when Stop button (NC) is pressed.

When Start button is pressed, Pump 2 will run.

Similarly Stop button will stop the pump

Hint:

- *Set-Reset*
- *Edge Detection*

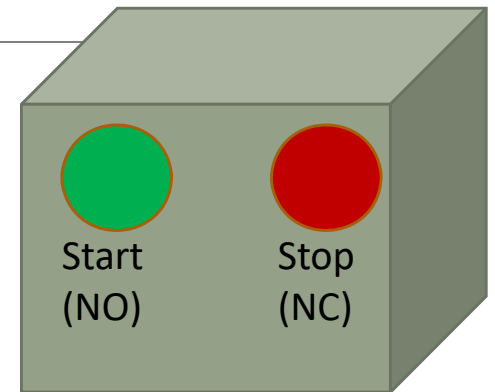

Pump 1



Pump 2