

Tutorial 6

Three-Phase Circuits: Balanced Delta Connected Load

1. A three-phase, three-wire, 110 V system supplies a delta connection of three equal impedances of $5\angle 45^\circ \Omega$. Determine the line currents I_A , I_B and I_C and draw the phasor diagram, taking V_{AB} as the reference.

Ans: $I_A = 38.1\angle -75^\circ$ A, $I_B = 38.1\angle -195^\circ$ A, $I_C = 38.1\angle 45^\circ$ or $38.1\angle -315^\circ$ A

2. A balanced delta connected load with impedances each of $5\angle -30^\circ \Omega$ is connected to a three phase, three wire, 208 V, 50 Hz supply system. Taking V_{BC} as reference, calculate the phase current I_{BC} and the line currents I_A , I_B and I_C in polar form.

Ans: $I_{BC} = 41.6\angle 30^\circ$ A, $I_B = 72.05\angle 0^\circ$ A, $I_C = 72.05\angle -120^\circ$ A, $I_A = 72.05\angle -240^\circ$ A

3. A three-phase, 3-wire, 220V system supplies a balanced delta connected load with a phase impedance of $10\angle 40^\circ \Omega$. Taking V_{CN} as the reference, determine:

- (a) the phase current I_{CA} in polar form.
(b) the total power consumed.

Ans: $I_{CA} = 22\angle -10^\circ$ A, $P_T = 11.12$ kW

4. A 220 V, three-phase voltage is applied to a balanced delta-connected three-phase load of phase impedance $(15 + j20) \Omega$. Taking V_{BC} as the reference, determine:

- (a) the line current I_C , and
(b) the power consumption per phase.

Ans: $I_C = 15.242\angle -203.13^\circ$ A or $15.242\angle 156.87^\circ$ A, $P_{PH} = 1162$ W


5. A star-connected, three-phase load consists of three similar impedances. When the load is connected to a three-phase, 500 V, 50 Hz supply, the line current is 28.85 A and the power factor is 0.8 lagging.

- (a) Calculate
(i) the total power taken by the load, and
(ii) the resistance of each phase of the load.
(b) If the phase loads were now re-connected in delta and supplied from the same three-phase system, determine the current flowing in each line.

Ans: $P_T = 20$ kW, $R_{PH} = 8 \Omega$, $I_{L(\Delta)} = 86.6$ A

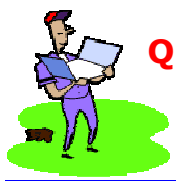6. A balanced delta-load with impedances each of $27\angle -25^\circ \Omega$ and a balanced Y-load with impedances each of $10\angle -30^\circ \Omega$ are both connected to a three-phase, three-wire, 208 V, ABC system. Find the total line currents in phasor form and the power in each load. Take V_{AB} as the reference.

Ans: $I_A = 25.3\angle -2.62^\circ$ A, $I_B = 25.3\angle -122.62^\circ$ A, $I_C = 25.3\angle 117.38^\circ$ A or $25.3\angle -242.62^\circ$ A, $P_\Delta = 4355.6$ W, $P_Y = 3744$ W



Quiz – 3 questions
(Balanced Delta Load)