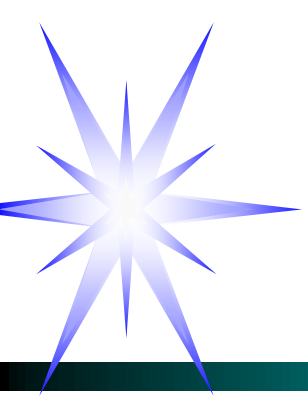




Resonant Circuits

Series RLC Resonant Circuit






Resonant Circuits

- ☺ RLC Series resonant circuit
 - ☞ RLC circuit in series
 - ☞ Phasor diagram
 - ☞ Resonance in RLC circuit
 - ☞ Graphical representation of resonance
 - ☞ Bandwidth of series RLC
 - ☞ Half power frequencies
 - ☞ Q-factor of series circuit





Series RLC Resonant Circuit

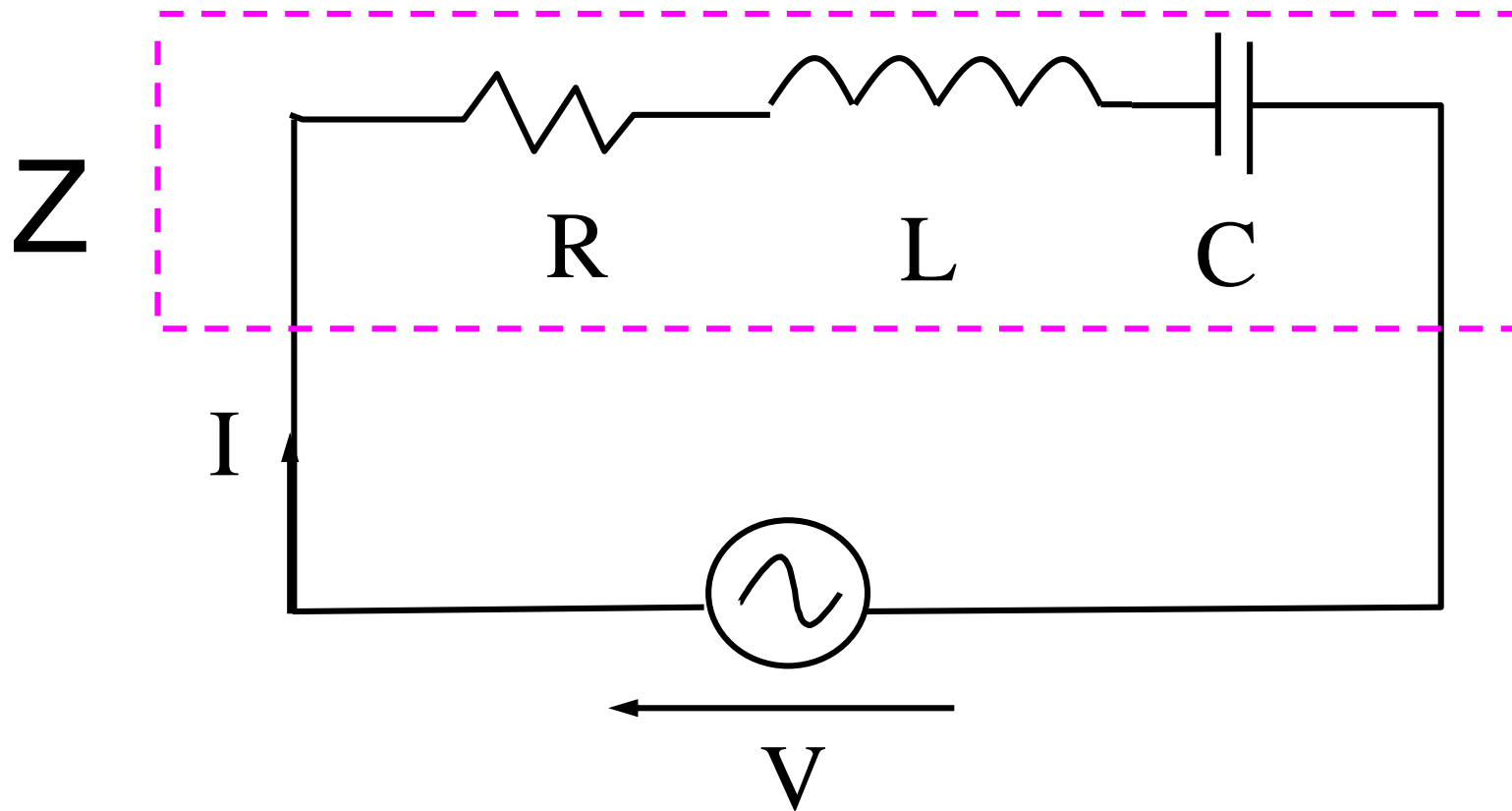

$$\text{Impedance } Z = R + jX_L - jX_C$$





Conditions for Series Resonance

$$\text{Impedance } Z = R + jX_L - jX_C$$

- When Z becomes real i.e. when Z consists of only the resistive part i.e. $Z = R$
- $X_L - X_C = 0$
- Magnitude of Z , i.e. $|Z|$, is a minimum


This resonance is known as

Low Impedance Resonance






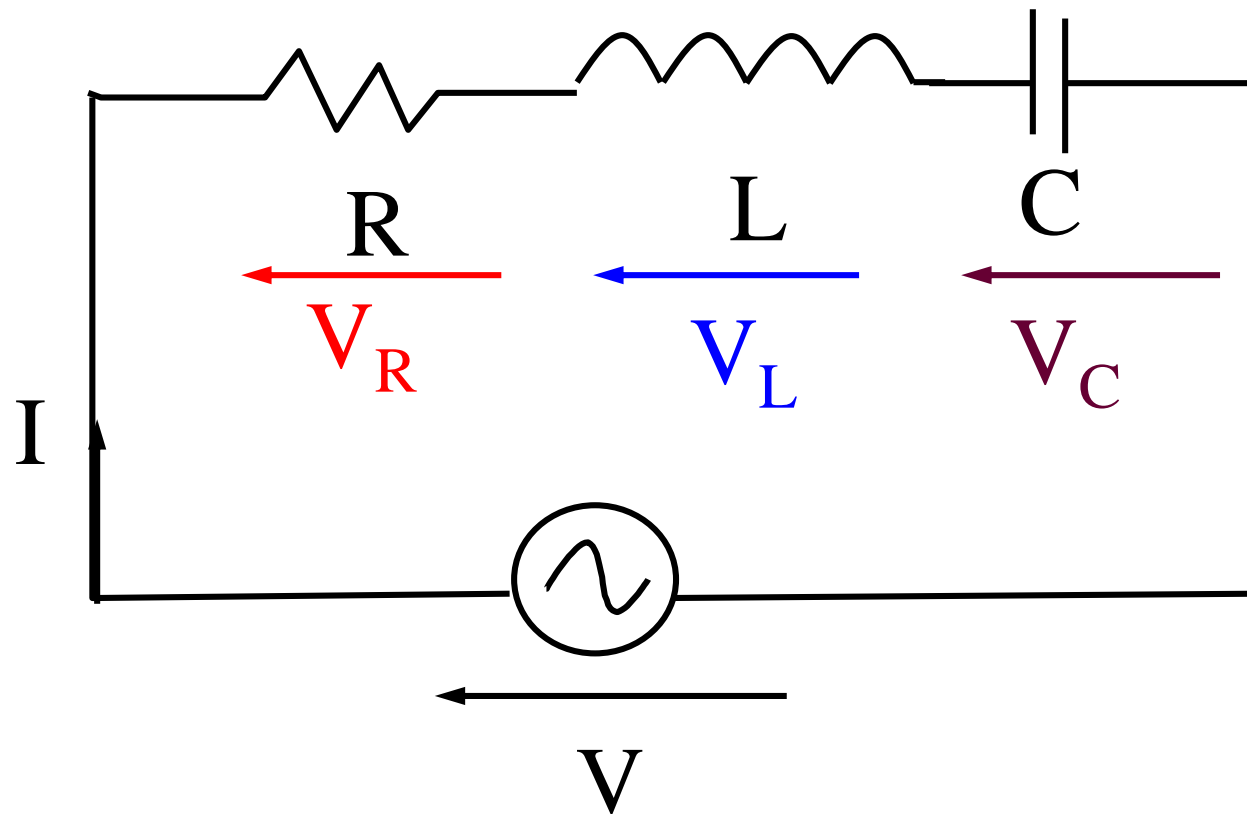Phasor Diagram of a RLC series circuit at resonance


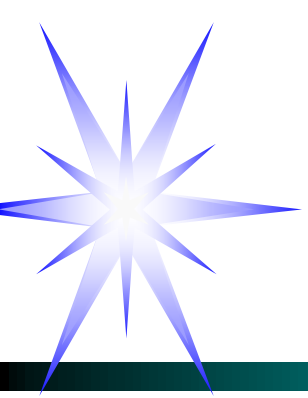
$$V = V_R + V_L + V_C \text{ (vector addition by KVL)}$$






Phasor Diagram of a RLC series circuit at resonance



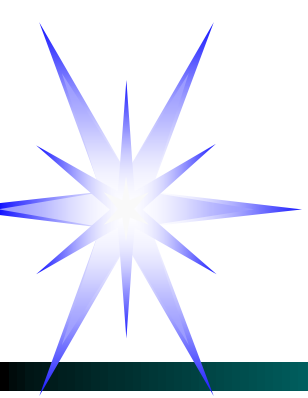There are 4 voltages but only 1 current in the circuit. The current is therefore usually chosen as the Reference.






Phasor Diagram of a RLC series circuit at resonance


V_R is the voltage across a pure resistor and is therefore in phase with I .

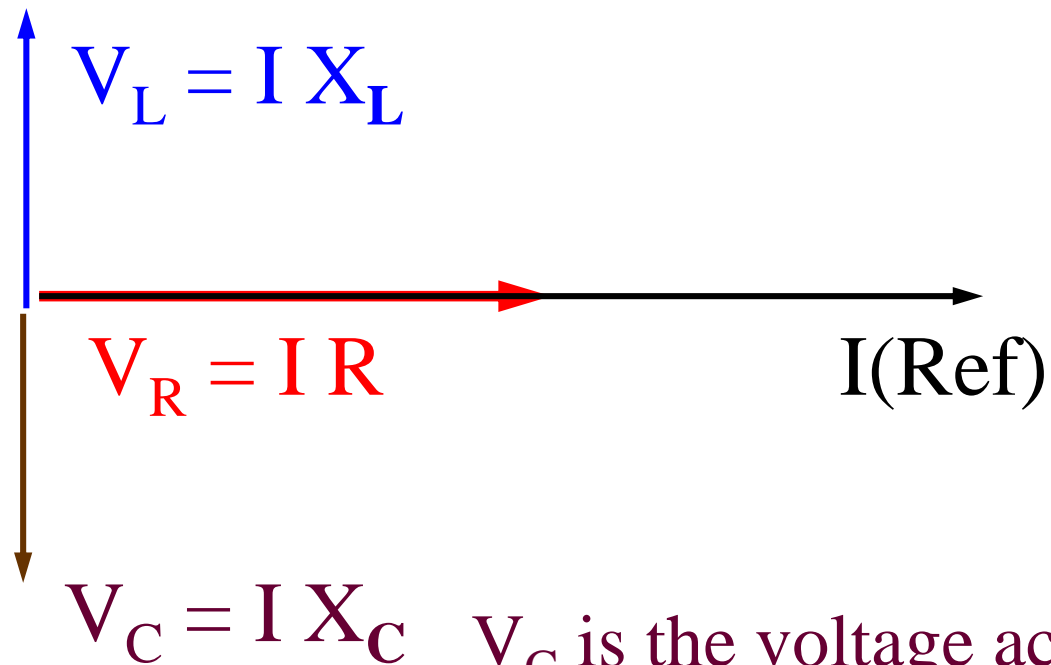V_L is the voltage across a pure inductor and is therefore leading the current I by 90° .




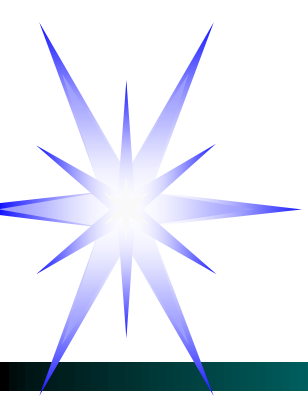V_C is the voltage across a pure capacitor and is therefore lagging behind the current I by 90° .





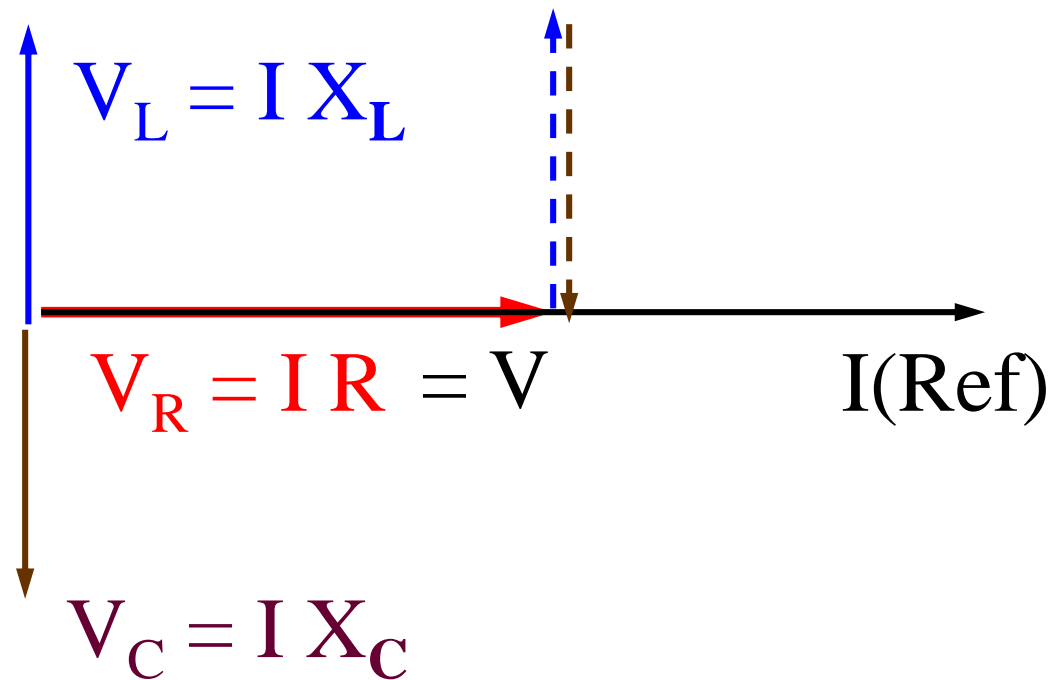Phasor Diagram of a RLC series circuit at resonance




$$V = V_R + V_L + V_C \text{ (By KVL)}$$

At resonance, $|V_L| = |V_C|$, making $V_L + V_C = 0$,
leaving only $V = V_R$





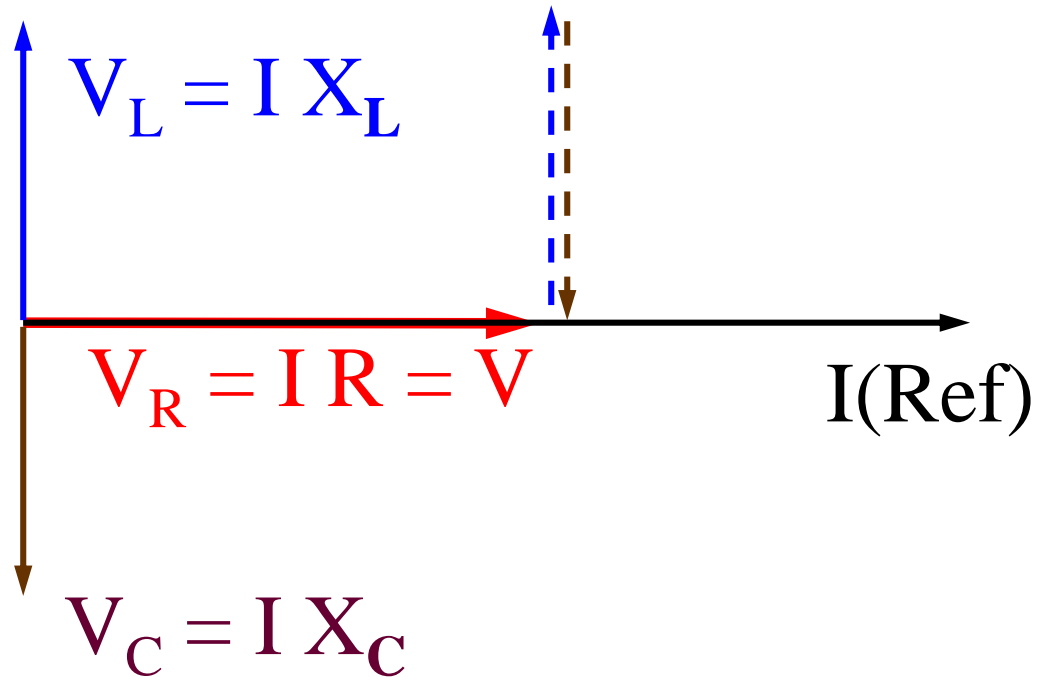Phasor Diagram of a RLC series circuit at resonance




At resonance, the applied voltage V and current I are in phase.


$Z = R$ and

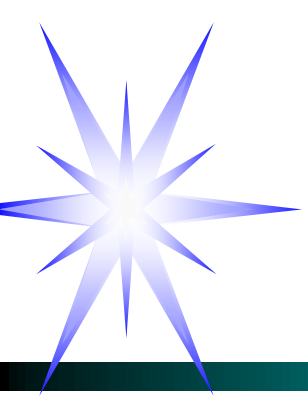the power factor of the circuit is unity (equals to 1).





Series RLC Circuit at Resonant

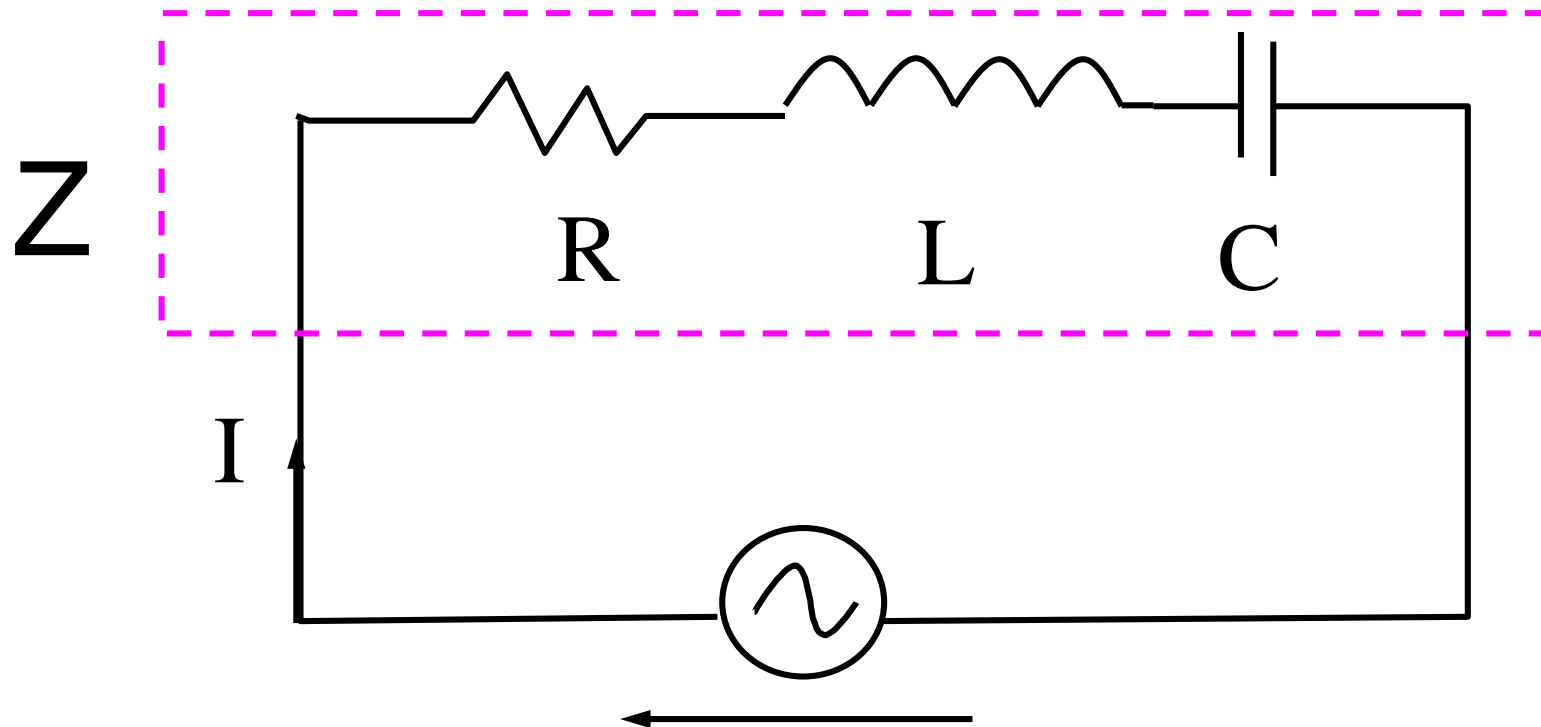

At resonance, V & I are in phase and $Z = R$.
The circuit is still an RLC circuit but is now
behaving like a pure resistor given by R





Equations for Series Resonant Frequency

Resonant Frequency (f_o) is the frequency at which the resonance occurs.

At resonance, Z is real ($= R$)

Giving $X_L - X_C = 0$

Therefore $\omega L = 1 / \omega C$,


giving $\omega = 1 / \sqrt{LC}$ rad/s $= \omega_o (= 2\pi f_o)$

or $f_o = 1 / 2\pi \sqrt{LC}$ Hz






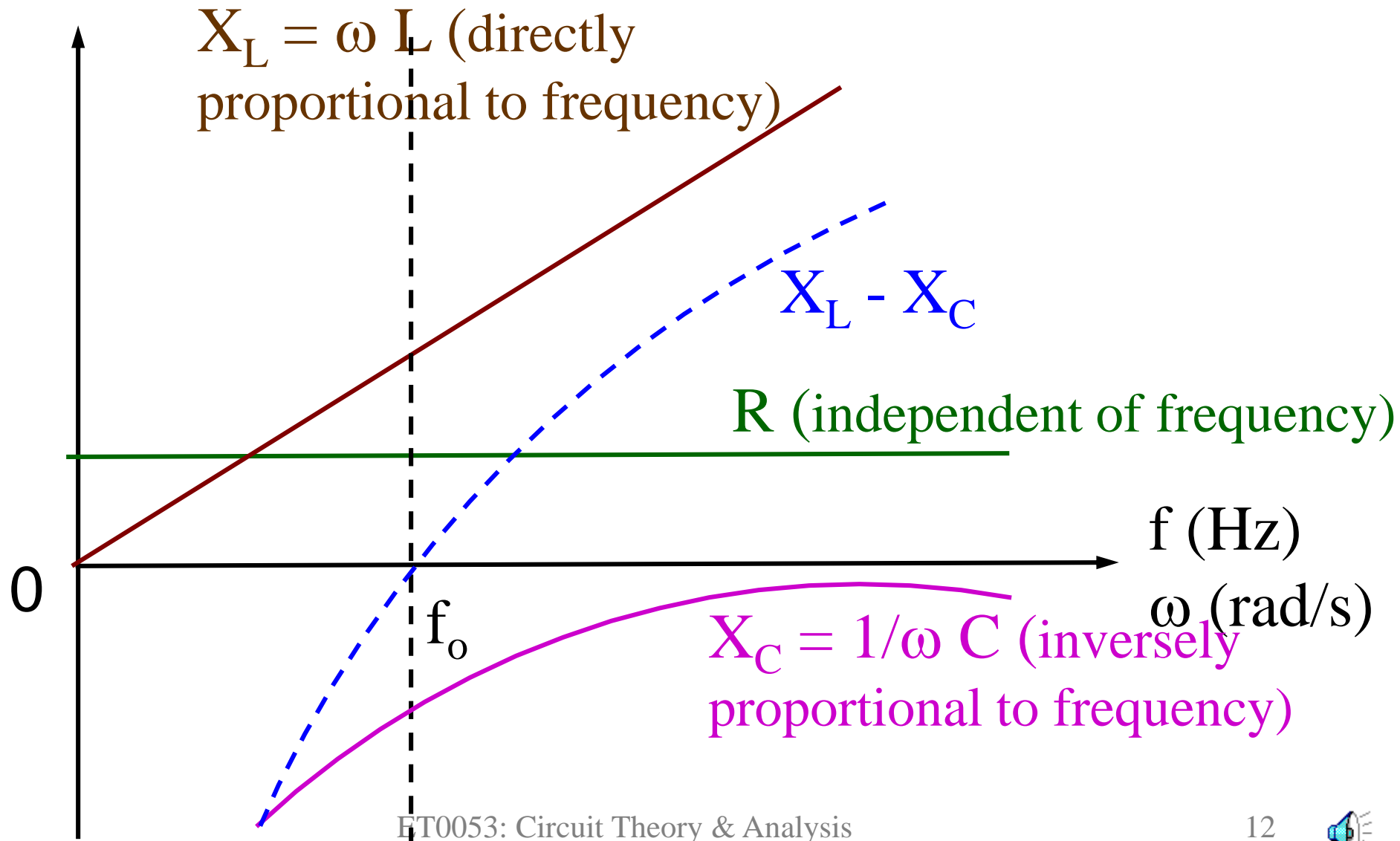
Variations of Resistance, Impedance and Current with Frequency - Series Circuit





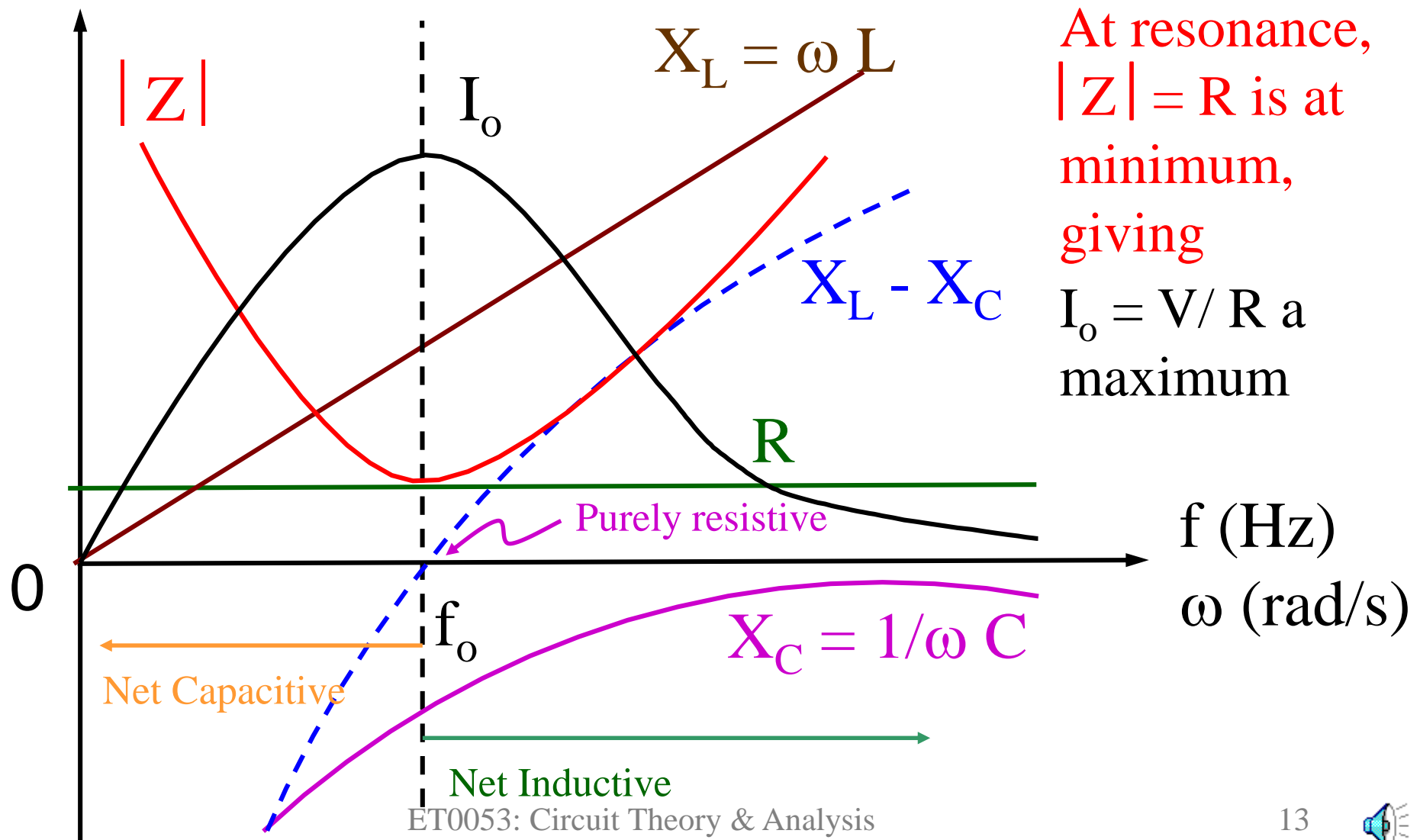Variations of Resistance, Impedance and Current with Frequency - Series Circuit



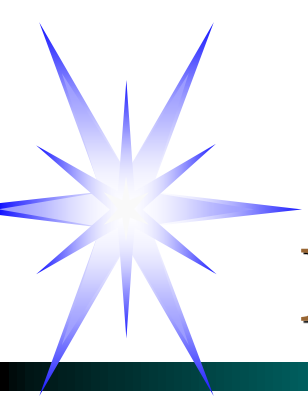


Half Power Frequencies and Bandwidth of a series resonant circuit


f_2 and f_1 are frequencies at which the power dissipation of the circuit is half the power dissipated at resonance. f_2 and f_1 are known as upper and lower half power frequencies (or cut-off frequencies) respectively.

BW is the range of frequency within which the current I is equal to or greater than 70.7 % of its value at resonance (I_0)



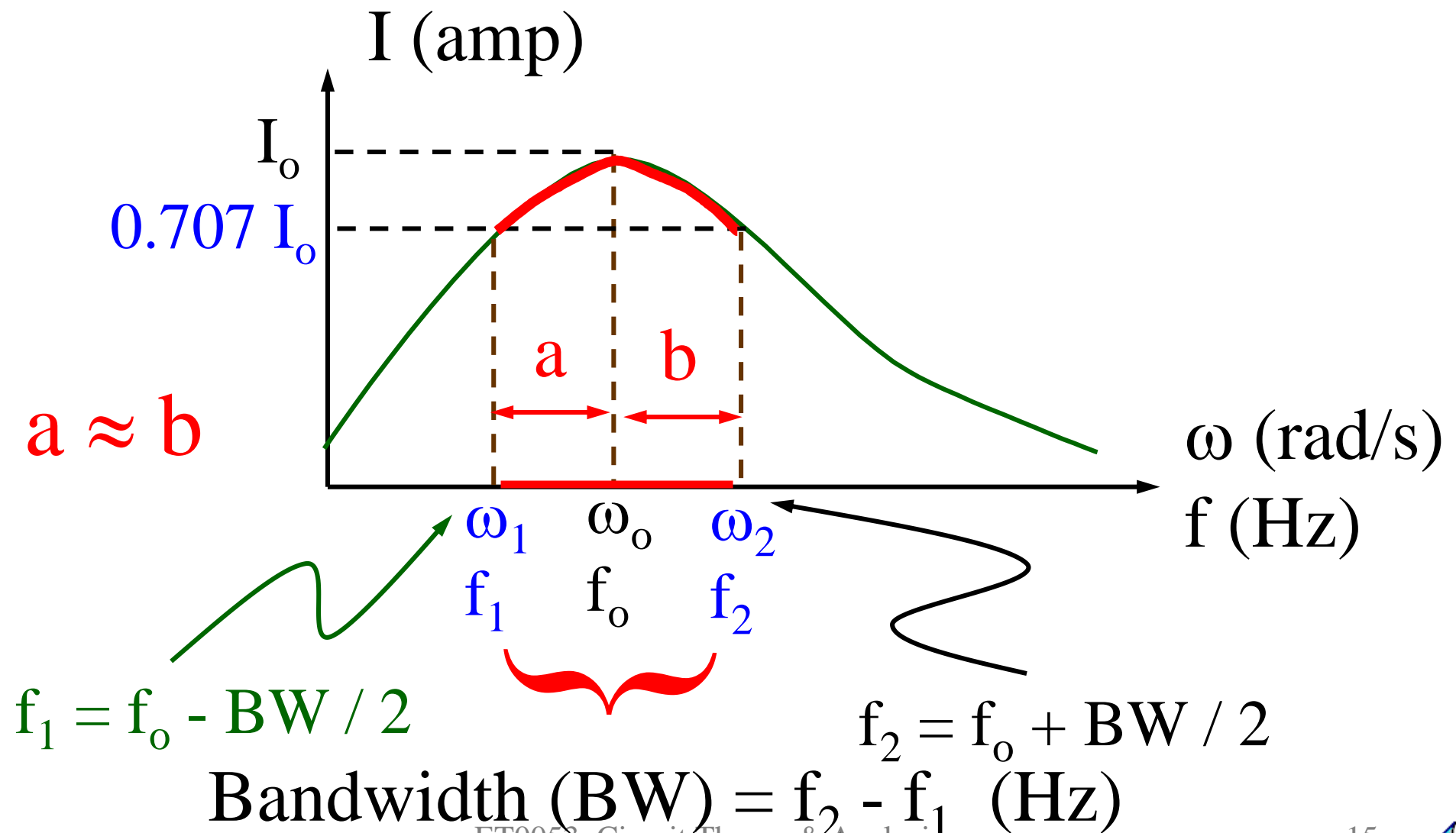Bandwidth and Half Power Frequencies of a series resonant circuit



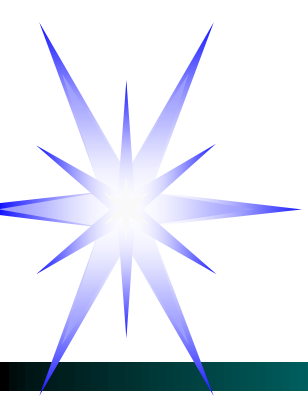

Bandwidth of a series resonant circuit

$$BW = f_2 - f_1 \text{ (in Hz) or } = \omega_2 - \omega_1 \text{ (in rad/s)}$$

BW serves as a measure of the sharpness of the peak.






Quality Factor or Q Factor of Series Resonance Circuit

The ratio of the capacitor or inductor voltage at resonance to the supply voltage is a measure of the quality of a resonance circuit.

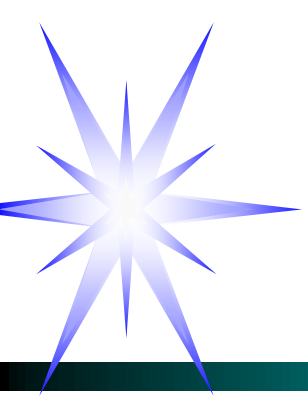This ratio is termed the Q factor of the circuit, and is also known as the **voltage magnification factor**.





Effects of varying R, L and C on the Q factor of series RLC circuit


$$\begin{aligned} \text{Q factor} &= V_L / V = \omega_o L / R \\ \text{or} \quad &= V_c / V = 1 / \omega_o RC \end{aligned}$$

Q factor of a circuit at resonance can be improved (increased) by reducing the effective resistance R of the circuit.





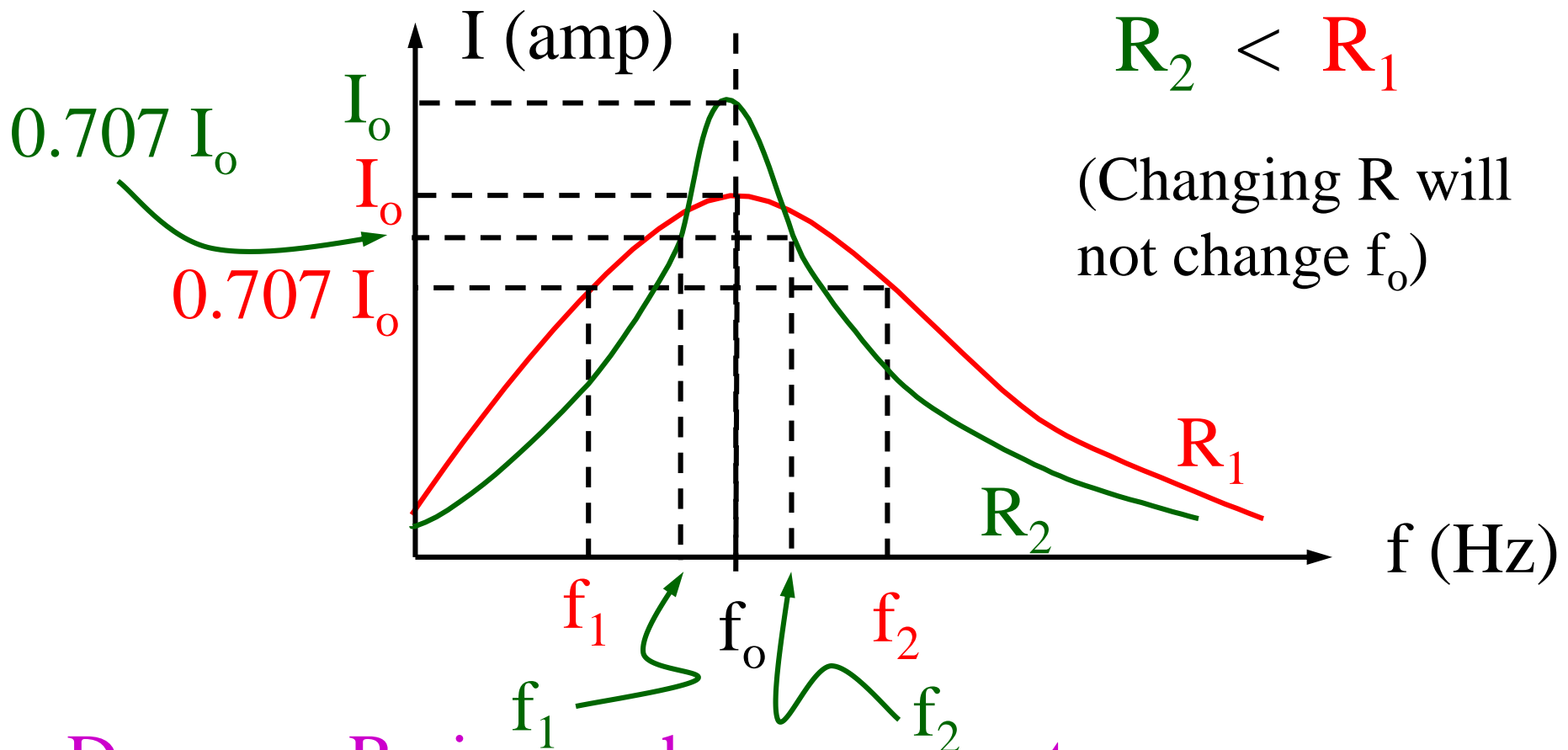Effect of changing R on bandwidth and Q factor



Decrease R gives a sharper current response, narrower bandwidth and higher Q factor





Relationship between Bandwidth, resonant frequency and Q factor

$$BW = f_o / Q \text{ (Hz)}$$

or

$$BW = 2 \pi f_o / Q \text{ (rad/s)}$$






Example 3.1

A series resonant circuit has the following parameters:
frequency at resonance = $5000/2\pi$ Hz; impedance at resonance = 56Ω ; Q factor = 25.

- (a) Assuming that the capacitor is pure, calculate
 - (i) the capacitance value
 - (ii) the inductance value
- (b) Determine the upper and lower half power frequencies.



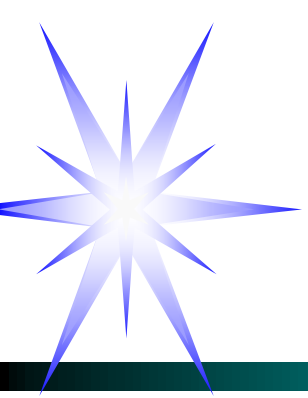

Example 3.1

Frequency at resonance = $5000/2\pi$ Hz = f_o

giving $\omega_o = 2\pi f_o = 5000$ rad/s


impedance at resonance = $56 \Omega = R$

Q factor = 25

$$(i) \quad Q = 25 = \omega_o L / R = 5000 \times L / 56$$
$$\text{giving } L = 25 \times 56 / 5000 = 0.28 \text{ H}$$

$$(ii) \quad Q = 25 = 1/\omega_o RC = 1/5000(56)C$$
$$\text{giving } C = 1/(25 \times 56 \times 5000) = 0.143 \mu\text{F}$$



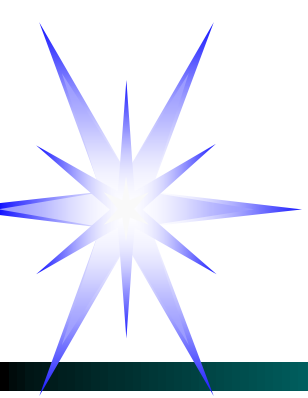

Example 3.1

Frequency at resonance = $5000/2\pi$ Hz = $f_o = 795.8$ Hz

Q factor = 25

$$\begin{aligned} \text{(b) Bandwidth BW} &= f_2 - f_1 \\ &= f_o / Q = (5000/2\pi) / 25 \\ &= 31.83 \text{ Hz} \end{aligned}$$

$$f_1 = f_o - \text{BW} / 2 = 795.8 - 31.83/2 = 779.9 \text{ Hz}$$

$$f_2 = f_o + \text{BW} / 2 = 795.8 + 31.83/2 = 811.7 \text{ Hz}$$

