

Tutorial 3

Star-Delta and Delta-Star Transformation

1. A network is arranged as shown in Figure 1. Using star-delta transformation, calculate the equivalent resistance between A and C.
Ans: 2.86 Ω
2. Referring to the circuit shown in Figure 2, perform the delta-star conversion on the 500 Ω , 2500 Ω , 100 Ω branches and hence, find the current I in the 50 ohm resistor.
Ans: 1.32 mA
3. Convert the three impedances forming a Δ in Figure 3 into an equivalent Y. Hence find an overall Y-equivalent.
Ans: (11 + j2) Ω ; (4 - j1) Ω ; (1 + j2) Ω
4. The three-terminal network shown in Figure 4 contains a balanced delta in parallel with a balanced Y. Obtain the Y-connected equivalent.
Ans: 2.28 $\angle -3.54^\circ$ Ω (balanced)
5. By converting the star-connected resistors of 2 Ω , 4 Ω and 6 Ω (shown in the dotted box) into an equivalent delta connection, calculate the effective resistance between the terminals A and B of the circuit shown in Figure 5.
Ans: 22 Ω ; 11 Ω ; 7.33 Ω ; $R_{AB} = 4.09 \Omega$.
6. Simplify the circuit shown in Figure 6 to prove that the equivalent resistance at the terminals AB is $R_{AB} = 4.87 \Omega$ using star to delta transformation for the 6 Ω star connected resistances connected to the terminals ABC.
Ans: $R_A = 18 \Omega$; $R_{AB} = 4.87 \Omega$.

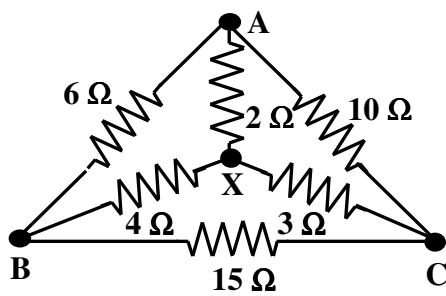


Figure 1

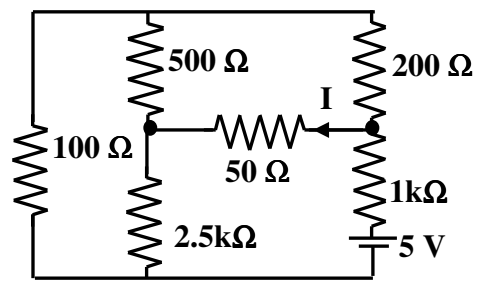


Figure 2

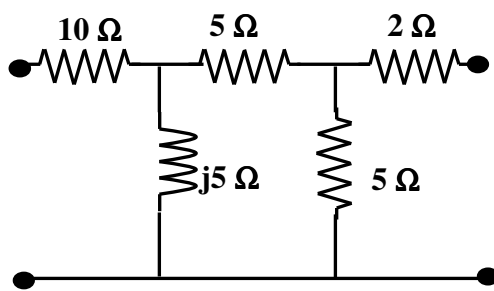


Figure 3

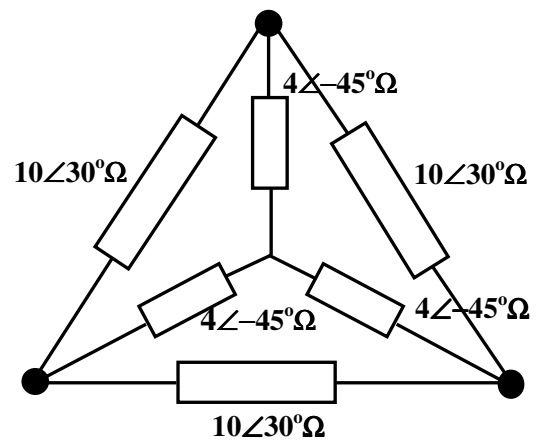


Figure 4

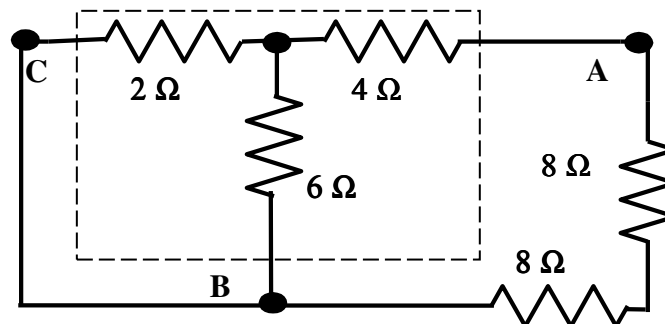


Figure: 5

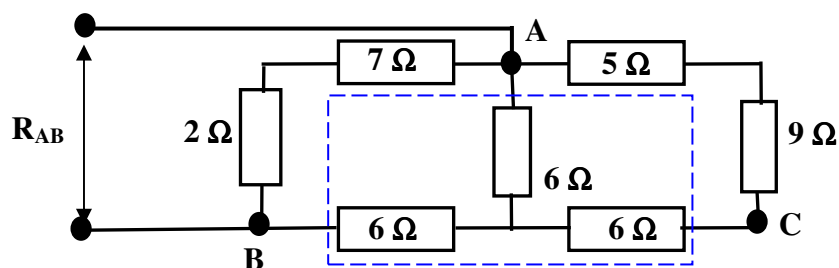


Figure: 6