

## Tutorial 2

### Mesh Current and Nodal Voltage Analysis

- Write the mesh current equations for  $I_1$ ,  $I_2$  and  $I_3$  in matrix form by inspection for the network shown in Figure 1.

$$\text{Ans: } \begin{bmatrix} 5-j5 & j5 & 4 \\ j5 & 5 & j5 \\ 4 & j5 & 5+j5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10\angle 0^\circ \\ 0 \\ 20\angle 90^\circ \end{bmatrix}$$

- Loop currents are shown in the network of Figure 2. Write the matrix equation by inspection and solve for  $I_1$ ,  $I_2$  and  $I_3$ .

$$\text{Ans: } I_1 = 3.55 \text{ A, } I_2 = -1.98 \text{ A, } I_3 = -2.98 \text{ A}$$

- Find the node voltages  $V_1$  and  $V_2$  in the network of Figure 2 and with them verify the three currents obtained in Problem 2.

$$\text{Ans: } V_1 = 7.11 \text{ V, } V_2 = -3.96 \text{ V}$$

- Obtain the node voltage  $V_1$  in the network shown in Figure 3.

$$\text{Ans: } 74.9 \angle 62.84^\circ \text{ V}$$

- Write the nodal voltage equations for  $V_1$ ,  $V_2$  and  $V_3$  in matrix form by inspection for the network shown in Figure 4.

**Ans:**

$$\begin{bmatrix} 0.55+j0.25 & -0.25-j0.25 & -0.1 \\ -0.25-j0.25 & 0.375+j0.05 & -0.125 \\ -0.1 & -0.125 & 0.325+j0.2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -2.5-j2.5 \\ 3.037+j2.813 \\ -0.541-j0.313 \end{bmatrix}$$


- For the circuit shown in Figure 5
  - Write down in matrix form, by inspection, the node voltage equations required to calculate the voltages at nodes A and B, with respect to the ground node C.
  - By solving the matrix equation in (a), calculate the current flowing in the  $1000 \Omega$  resistor.
  - Write down in matrix form, by inspection, the mesh current equations required to calculate the currents  $I_1$ ,  $I_2$ , and  $I_3$ .
  - By solving the matrix equation in (c), show that current  $I_2$  is the same as obtained in (b).

**Ans:**

$$\begin{bmatrix} 0.103 & -0.001 \\ -0.001 & 0.008 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix}, \quad \begin{bmatrix} 510 & 10 & 0 \\ 10 & 1510 & -500 \\ 0 & -500 & 700 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 10 \\ 0 \end{bmatrix}$$

$$V_A = 9.72 \text{ V, } V_B = 1.215 \text{ V}$$
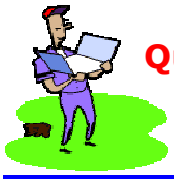
$$I_{1000\Omega} = I_2 = 8.5 \text{ mA}$$



**Quiz** – 2 questions  
(Mesh Analysis)

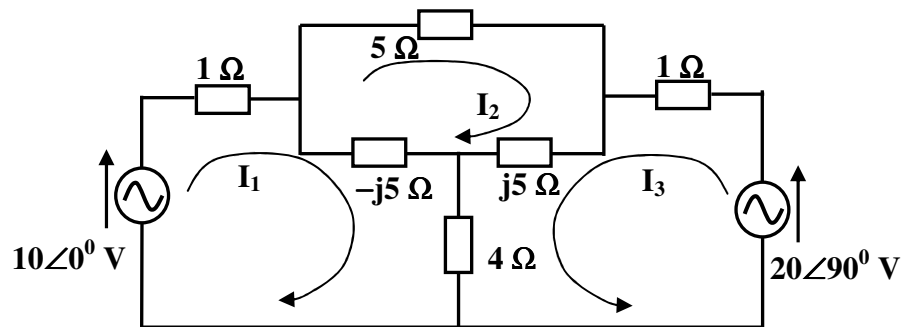


Figure 1

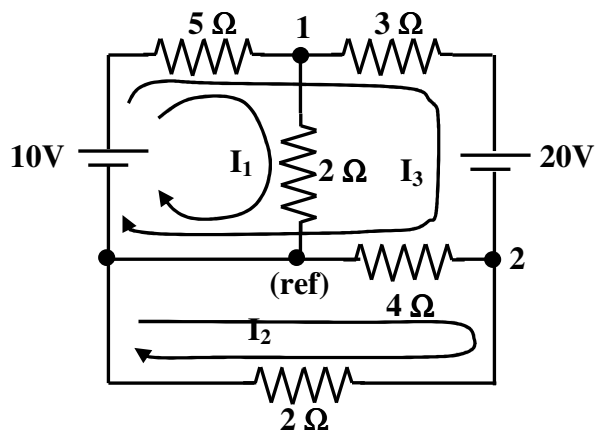


Figure 2

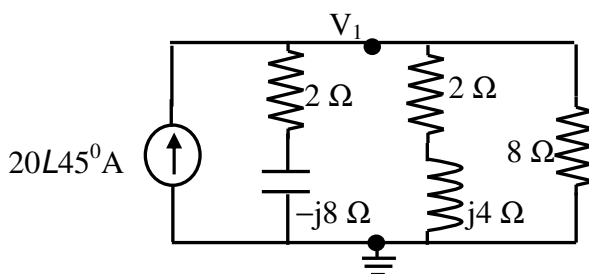


Figure 3

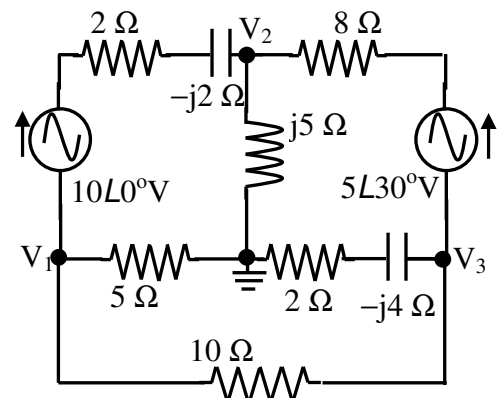


Figure 4

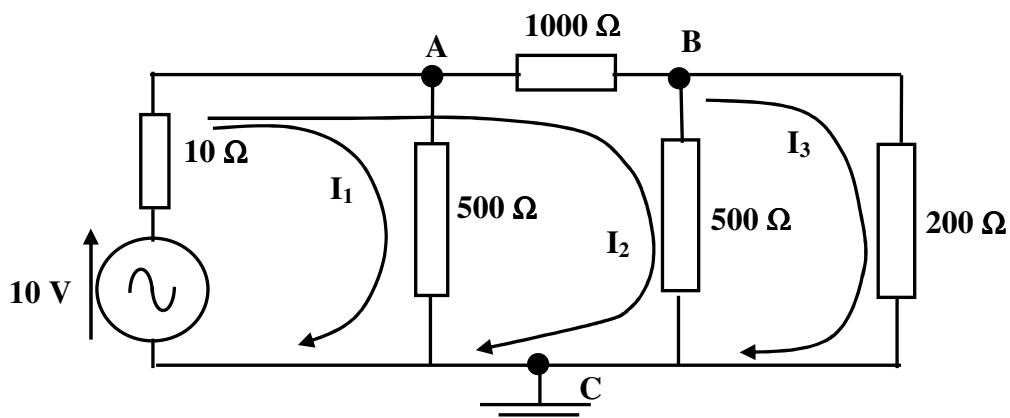


Figure 5