
## Lecture 2 – Part 4 Programming PLC

Set - Reset for PLC

Edge Detection for PLC

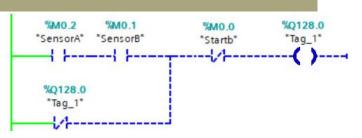

# Set Output or Reset Output Instruction




- "Set Output" instruction set the signal state of a specified operand to "1"
- "Reset Output" instruction reset the signal state of a specified operand to "o"

When "SensorA" AND "SensorB" = 1, Set Output of "Tag\_1 would be activated, "Tag\_1" bit would be set (=1) and remains ON

When "Startb" = 1, Reset Output of "Tag\_1" would be activated, "Tag\_1" bit would reset (= 0)




### Set-Reset Reset-Set Flip Flops

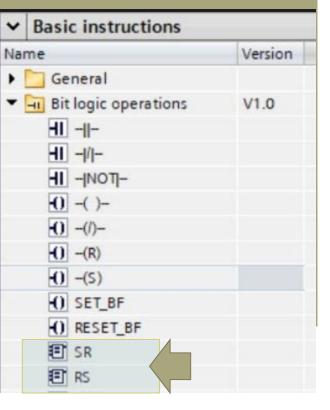


Parameters	Declaration	Data Type	Description
S or S1	Input	BOOL	Enable Setting
R or R1	Input	BOOL	Enable Resetting
<operand></operand>	InOut	BOOL	Operand that is set or reset.
Q	Output	BOOL	Signal state of the operand

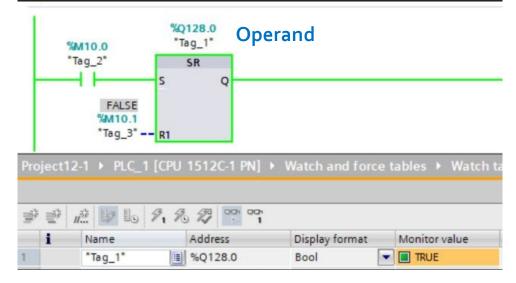- Set-Reset Flip Flop or Reset-Set Flip Flops are Functions that set or reset the specified operand
- Functions (FC) codes that do not store memory (Do Not Declare instance)
- · Note: Function Blocks (FB) stores memory in DB as an instance






Set-Reset Reset-Set Flip Flops

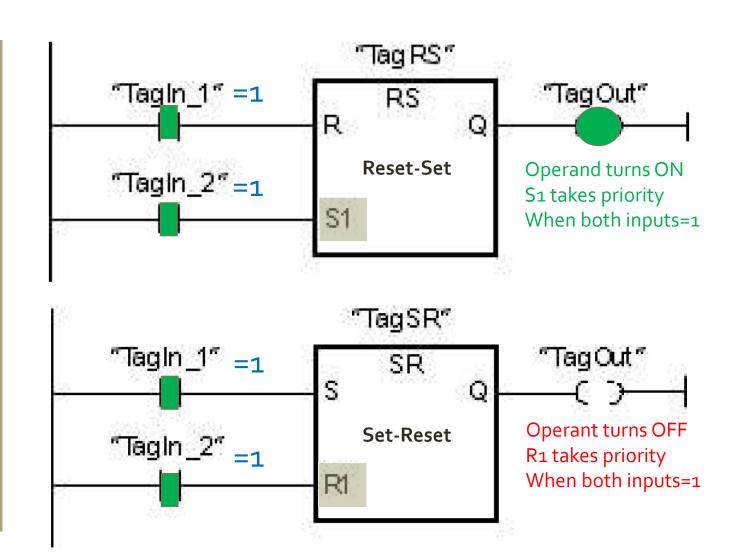



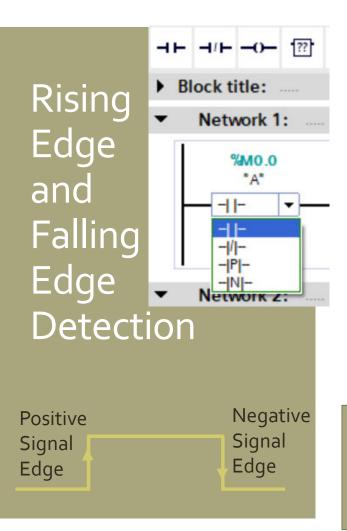


- "Scan operand for positive signal edge" instruction determine if there is a "o" to "1" state of specified operand (<Operand1>)
- Compares the current signal state of <Operand1> with the signal state of the previous scan, which is saved in an edge memory bit (<Operand2>)
- Instruction detects change "o" to "1", positive rising edge detected
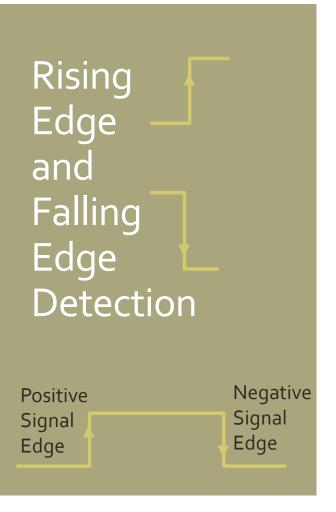
#### Note:

Operand 2 (edge memory bit) shall be defined bit memory as Global Memory %M Edge memory bit address cannot be used more than once in the program Edge memory bit influence the edge evaluation





- "Scan operand for negative signal edge" instruction determine if there is a "1" to "o" state of specified operand (<Operand1>)
- Compares the current signal state of <Operand1> with the signal state of the previous scan, which is saved in an edge memory bit (<Operand2>)
- Instruction detects change "1" to "o", negative signal edge detected

```
%M1.3 <Operand 1>

"Button1"

N |

%M2.4 <Operand 2>


"Memory2"

1 scan cycle
```
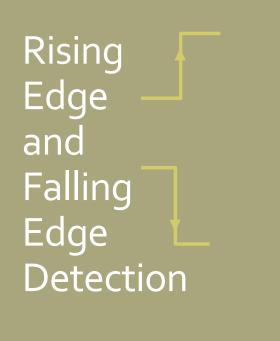
#### Note:

Operand 2 (edge memory bit) shall be defined bit memory as Global Memory %M Edge memory bit address cannot be used more than once in the program Edge memory bit influence the edge evaluation






Positive

Signal

Edge

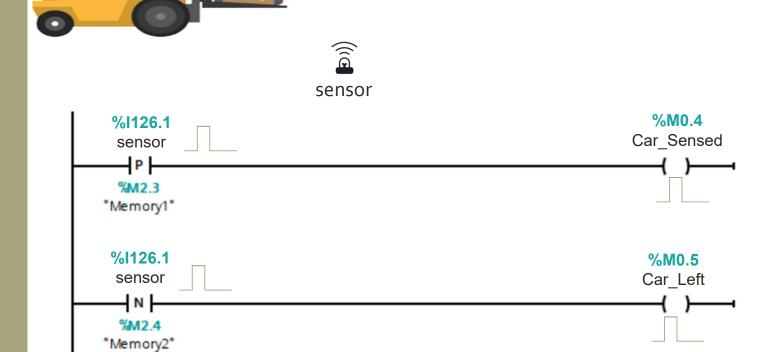





#### Click the Quiz button to edit this object

#### Select the correct statement about the image:

- When "SensorA" AND "SensorB" = 1, "Tag\_1" will set (=1) and remain ON regardless of the state of "SensorA" AND "SensorB" till "Startb" reset (=0) "Tag\_1"
- When "SensorA" AND "SensorB" = 1, "Tag\_1" will set (=1) and remain ON.

  Whenever "SensorA" AND "SensorB" = 0, "Tag\_1" will reset (=0) as there is no latching
- When "SensorA" AND "SensorB" AND "Startb" = 1, "Tag\_1" will set (=1) and remain ON. When "Startb" = 0, it will reset (=0) "Tag\_1"

%M0.2	TM0.1	70128.0
781501		
mer v		
- MAO D		90128.0
		189_1