

## TUTORIAL 3 (Chapter 2)

## SECTION A

## MULTIPLE CHOICE QUESTIONS

A1. What is the time period of clock for the command: **always** #10 clock = ~clock;?

- (a) 5
- (b) 10
- (c) 20
- (d) 40

Ans( )

A2. What could be the expression for Figure 1 where in1 and in2 are input reg variables and out is output variable of wire type?

 


Figure 1

- (a) **assign** out = in1 & in2;
- (b) **assign** out = in1 | in2;
- (c) **assign** #10 out = in1 & in2;
- (d) **assign** #10 out = in1 | in2;

Ans( )

A3. Which of the following loops are supported by Verilog?

- (I) forever
  - (II) if-else
  - (III) repeat
  - (IV) while
- (a) (I) & (II)
  - (b) (III) & (IV)
  - (c) (I), (II) & (III)
  - (d) (I), (III) & (IV)

Ans( )

**SECTION B**

B1. Write a Verilog program for the circuit in Figure 1 using gate instantiation.

 


Figure 1

B2. Figure 2 shows the testbench for Figure 1. Draw the waveform of A, B, C and Y after simulation for 80 ns.

```
`timescale 1ns / 1ps  
module Figure1_tb();  
  wire Y;  
  reg A=0;  
  reg B=0;  
  reg C=0;  
  always #40 A=~A;  
  always #20 B=~B;  
  always #10 C=~C;  
  Figure1 dut(A,B,C,Y);  
endmodule
```

Figure 2