

2017/2018 SEMESTER TWO EXAMINATION

Diploma in Aerospace Electronics (DASE) 2<sup>nd</sup> Year FT  
Diploma in Engineering with Business (DEB) 3<sup>rd</sup> Year FT  
Diploma in Electrical & Electronic Engineering (DEEE) 2<sup>nd</sup> Year FT  
Diploma in Engineering Systems (DES) 2<sup>nd</sup> Year FT  
Diploma in Energy Systems and Management (DESM) 2<sup>nd</sup> Year FT

**CIRCUIT THEORY & ANALYSIS**

Time Allowed: 2 Hours

---

Instructions to Candidates

1. The examination rules set out on the last page of the answer booklet are to be complied with.
2. This paper consists of **TWO** sections:
  - Section A - 6 Short Questions, 10 marks each.
  - Section B - 2 Long Questions, 20 marks each.
3. **ALL** questions are **COMPULSORY**.
4. All questions are to be answered in the answer booklet. Start each question on a new page.
5. Fill in the Question Numbers in the boxes found on the front cover of the answer booklet under the column "Question Answered".
6. This paper consists of 6 pages, inclusive of the formulae sheet.

**SECTION A: 6 QUESTIONS** (10 marks each)

- A1. Using the source conversion method, simplify the circuit shown in Figure A1 to its equivalent current source across terminals A and B. (10 marks)

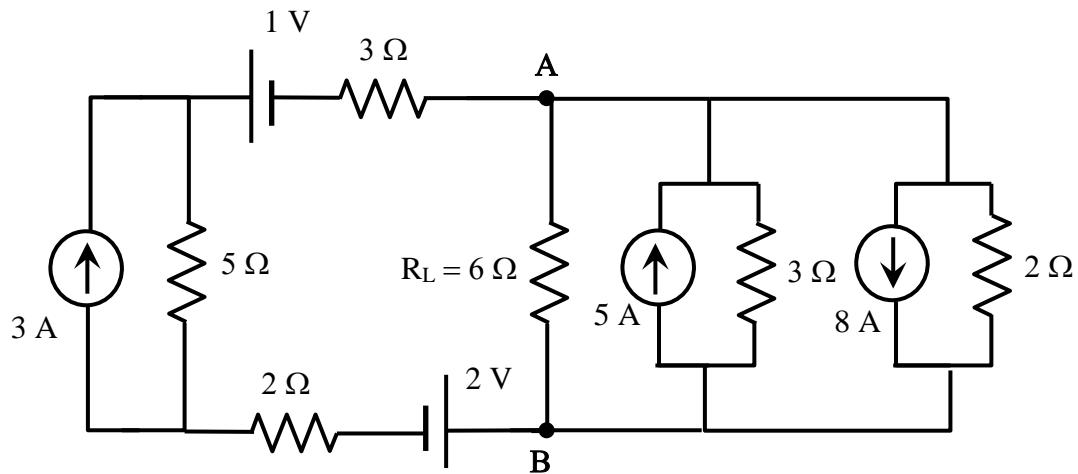


Figure A1

- A2. For the circuit shown in Figure A2, convert the star-connected resistors as shown in the dotted box into an equivalent delta-connection, and hence determine the total resistance across terminals A and B. (10 marks)

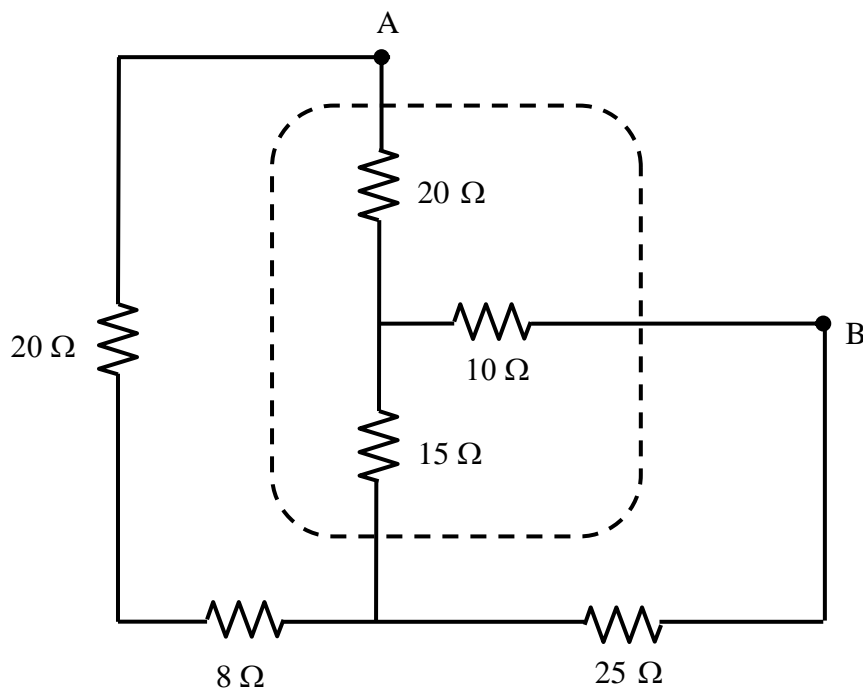


Figure A2

- A3. A balanced star-connected load draws 5 kVA at a power factor of 0.8 lagging from a 200 V, 50 Hz, three-phase distribution system. Taking  $V_{AN}$  as the reference voltage, calculate the:
- (a) phase impedance of the star-connected load in polar form, and (7 marks)
  - (b) line current ( $I_A$ ) in polar form. (3 marks)
- A4. A three-phase load having a power factor of 0.8 lagging absorbs 60 kW from a 350 V, 50 Hz, three-phase supply. It is required to correct the power factor to 0.92 leading. Determine the:
- (a) magnitude of the original and final line currents, and (4 marks)
  - (b) kVAR rating of a three-phase capacitor bank to be added to achieve the required power factor correction. (6 marks)
- A5. An unbalanced star-connected load with impedances  $Z_A = 10 \Omega$ ,  $Z_B = -j5 \Omega$  and  $Z_C = j4 \Omega$  is connected to a three phase, 4-wire, 100 V, ABC system. Taking  $V_{CN}$  as the reference voltage, calculate the:
- (a) line currents of the star-connected load, and (7 marks)
  - (b) total real power of the system. (3 marks)
- A6. A three-phase, delta-connected motor is connected to a 250 V, 50 Hz, three-phase, 3-wire supply. When using the two-wattmeter method to measure the power supplied to the motor, the readings on the two wattmeters are 1000 W and -300 W respectively. Calculate the:
- (a) power factor, and (4 marks)
  - (b) magnitude of the motor phase impedance. (6 marks)

**SECTION B: 2 QUESTIONS** (20 marks each)

- B1. (a) Apply Thevenin's Theorem to find the Thevenin equivalent circuit parameters  $V_{TH}$  and  $Z_{TH}$  between terminals A and B for the circuit shown in Figure B1. (Include circuit diagrams for finding  $V_{TH}$  and  $Z_{TH}$ ) (17 marks)
- (b) Draw the Thevenin's equivalent circuit obtained. (3 marks)

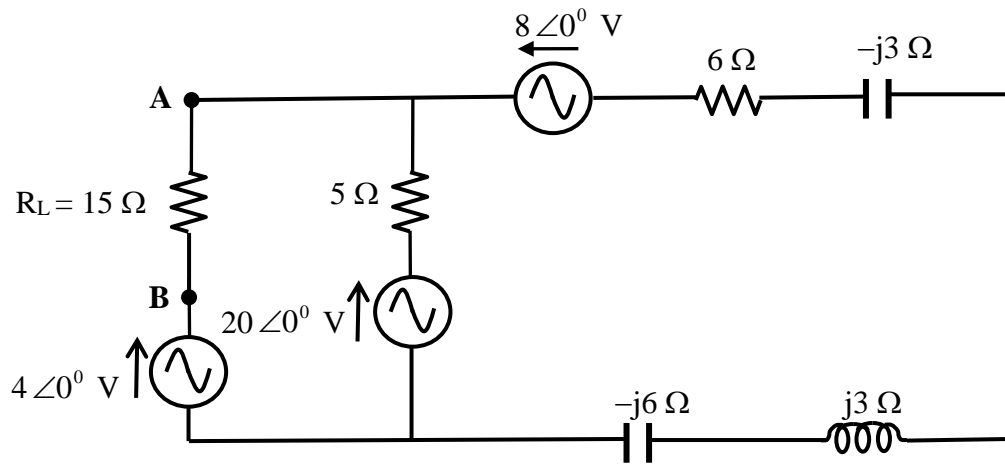


Figure B1

- B2. A 3-phase, 3 wire, 415 V, ABC system feeds a delta-connected load as shown in Figure B2. Taking  $V_{CA}$  as the reference voltage, determine the:
- phase impedance of delta-connected load in polar form, (2 marks)
  - line current ( $I_C$ ), (5 marks)
  - total apparent and reactive power consumed, and (4 marks)
  - power factor of the load. (3 marks)

Draw a phasor diagram showing the line voltages and line currents. (6 marks)

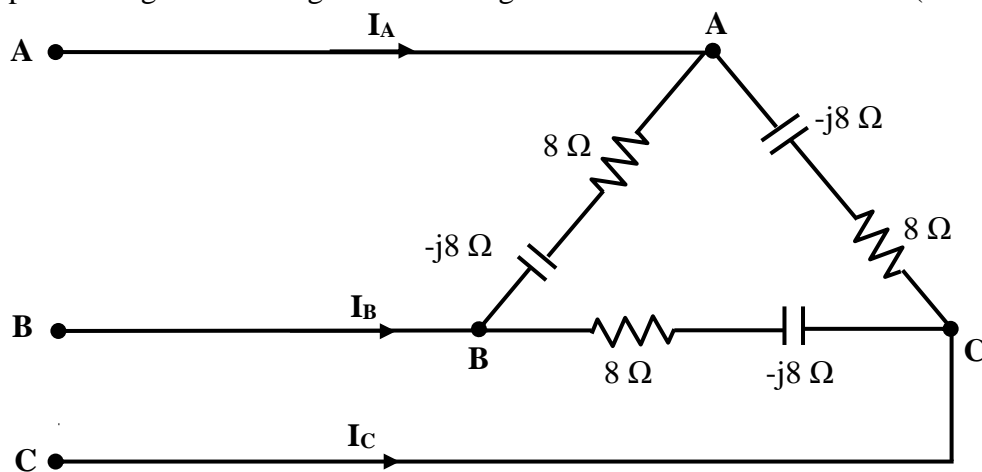


Figure B2

- End of Paper -

Formulae

Resistors in series	$R_T = R_1 + R_2 + R_3 + \dots$
Resistors in parallel	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$
Resistors in parallel (for 2 resistors)	$R_T = \frac{R_1 R_2}{R_1 + R_2}$
Voltage Divider Rule	$V_X = \frac{R_X}{R_T} V_S$
Current Divider Rule	$I_1 = \frac{R_2}{R_1 + R_2} I_T$
Source Conversion	$E = I_S R_S \qquad I_S = \frac{E}{R_S}$
Mesh Current Analysis	$[Z] [I] = [V]$
Nodal Voltage Analysis	$[Y] [V] = [I]$
Delta to Star Conversion	$Z_1 = \frac{Z_A Z_C}{Z_A + Z_B + Z_C}$ $Z_2 = \frac{Z_A Z_B}{Z_A + Z_B + Z_C}$ $Z_3 = \frac{Z_B Z_C}{Z_A + Z_B + Z_C}$
Star to Delta Conversion	$Z_A = Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3}$ $Z_B = Z_2 + Z_3 + \frac{Z_2 Z_3}{Z_1}$ $Z_C = Z_1 + Z_3 + \frac{Z_1 Z_3}{Z_2}$
Inductive Reactance	$X_L = 2\pi fL$
Capacitive Reactance	$X_C = \frac{1}{2\pi fC}$
Three Phase Star – Connected Load	$V_L = \sqrt{3} V_{PH}$ $I_L = I_{PH}$ $Z_{PH} = \frac{V_{PH}}{I_{PH}}$

Three Phase Delta - Connected Load	$V_L = V_{PH}$ $I_L = \sqrt{3} I_{PH}$ $Z_{PH} = \frac{V_{PH}}{I_{PH}}$
Three Phase Apparent Power	$S_T = 3 V_{PH} I_{PH} = \sqrt{3} V_L I_L$
Three Phase Active/Real/True Power	$P_T = 3 V_{PH} I_{PH} \cos \phi = \sqrt{3} V_L I_L \cos \phi$
Three Phase Reactive Power	$Q_T = 3 V_{PH} I_{PH} \sin \phi = \sqrt{3} V_L I_L \sin \phi$
Power factor	Power factor = $\cos \phi = \frac{P}{S}$
Two-Wattmeter Method	$W_1 = V_L \times I_L \times \cos (\theta - 30^\circ)$ $W_2 = V_L \times I_L \times \cos (\theta + 30^\circ)$ $P_T = W_1 + W_2$ Power factor = $\cos \left( \tan^{-1} \left[ \sqrt{3} \left( \frac{W_1 - W_2}{W_1 + W_2} \right) \right] \right)$

**ANSWERS:**

A1.  $I_N = 1.8 \text{ A}$ ,  $R = 1.07 \Omega$

A2.  $R_{AB} = 18.96 \Omega$

A3(a).  $Z_{PH} = 8 \angle 36.87^\circ \Omega$

(b).  $I_A = 14.43 \angle -36.87^\circ \text{ A}$

A4(a). Original Line Current = 123.72 A, Final Line Current = 107.58 A

(b).  $Q_C = 70.56 \text{ kVAR}$

A5(a).  $I_A = 5.77 \angle -120^\circ \text{ A}$ ,  $I_B = 11.55 \angle -150^\circ \text{ A}$ ,  $I_C = 14.43 \angle -90^\circ \text{ A}$


(b).  $P_T = 333.16 \text{ W}$

A6(a). Power factor = 0.297

(b).  $Z_{PH} = 79.62 \Omega$

B1(a).  $V_{TH} = 12.01 \angle -11.04^\circ \text{ V}$ ,  $Z_{TH} = 3.39 \angle -16.46^\circ \Omega$

(b). Thevenin's Equivalent Circuit

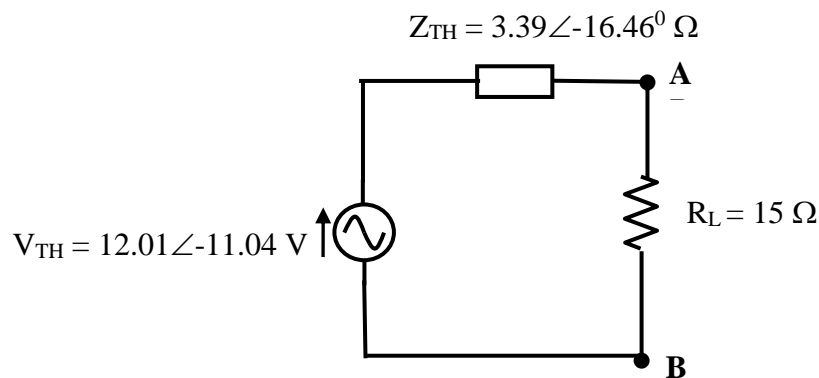

B2(a).  $Z_{PH} = 11.31 \angle -45^\circ \Omega$

(b).  $I_C = 63.55 \angle 15^\circ \text{ A}$

(c).  $S_T = 45.68 \text{ kVA}$ ,  $Q_T = 32.3 \text{ kVAR}$

(d). Power factor = 0.707 leading

