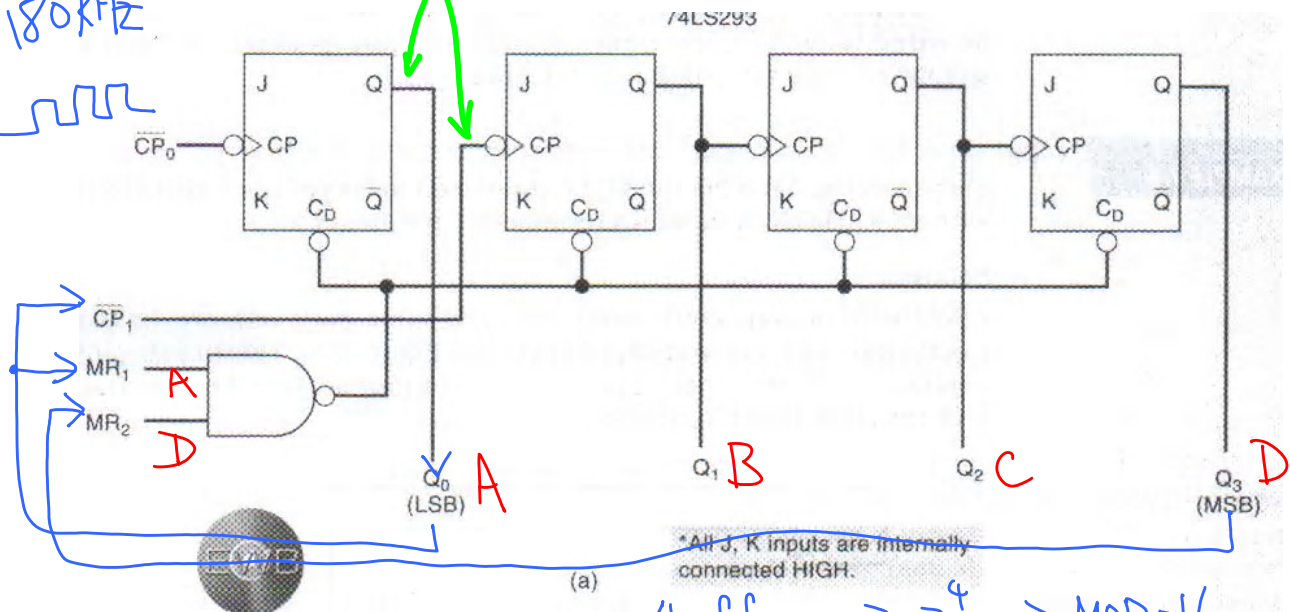


7-9. In Figure 7-8, connect Q_0 to \overline{CP}_1 and MR_1 , and connect Q_3 to MR_2 . If 180-kHz pulses are applied to \overline{CP}_0 , determine the following: (a) the count sequence; (b) MOD number; (c) frequency at Q_3 .

i.e.
Connect them

180kHz

4 f.f.s $\rightarrow 2^4 \rightarrow \text{MOD-16}$

Reset all f.f.s when D and A = 1

ie DCBA
1 0 0 1 = 9

ie Reset to 0 as soon as the count = 9.

Hence, we have counting seq:

0 to 8

ie MOD-9 counter.

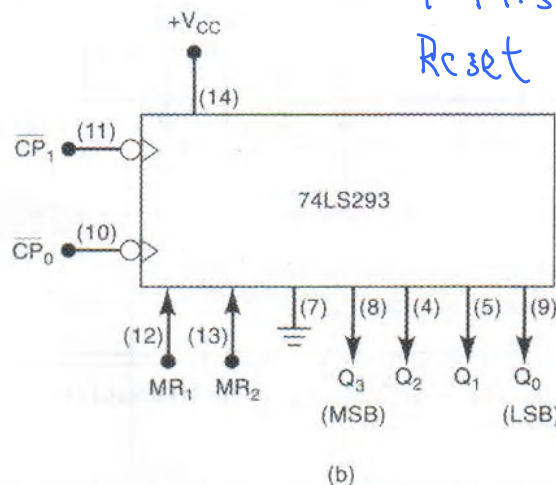


FIGURE 7-8 (a) Logic diagram for 74LS293 asynchronous counter IC; (b) block symbol, with pin numbers in parentheses.