

Tutorial 2 – B2

timescale 1ns / 1ps

module **Four_bit_adder**(A,B,Cin,SUM,Cout);

input [3:0] A,B;


input Cin;

output [3:0] SUM;

output Cout;

assign {Cout,SUM} = A + B + Cin;

endmodule Concatentate to become 5-bit

 

timescale 1ns / 1ps

Test Bench (not required
in this question).

module Four_bit_adder_tb();

reg [3:0] A=0,B=0; **reg** Cin=0; **wire** [3:0] SUM; **wire** Cout;

integer i, j;

Four_bit_adder dut(A, B, Cin, SUM, Cout);

initial

begin

for (i=0; i<=15; i=i+3)

for (j=0; j<=15; j=j+3)

begin


#10 A=i; B=j; Cin=~Cin;

end


end

endmodule

This is not the
only way to test.

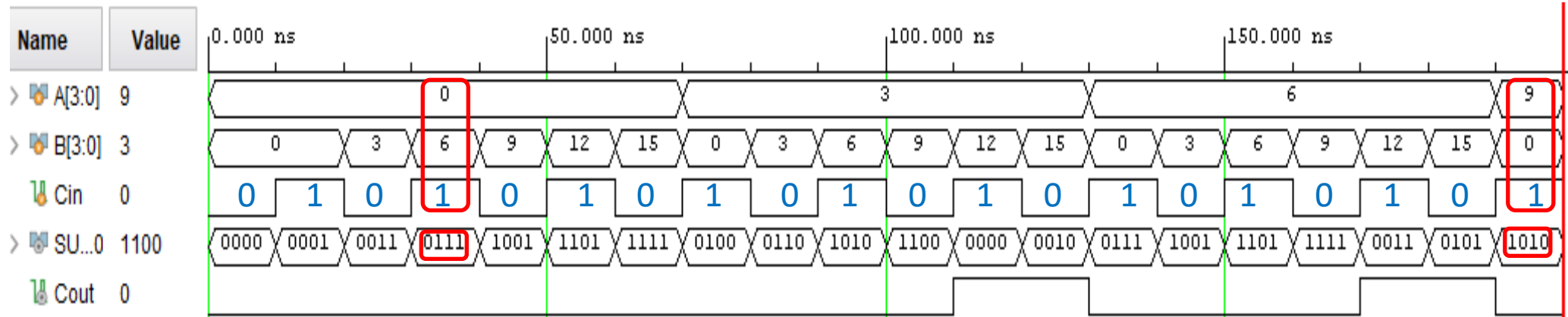

Vivado RTL Schematic

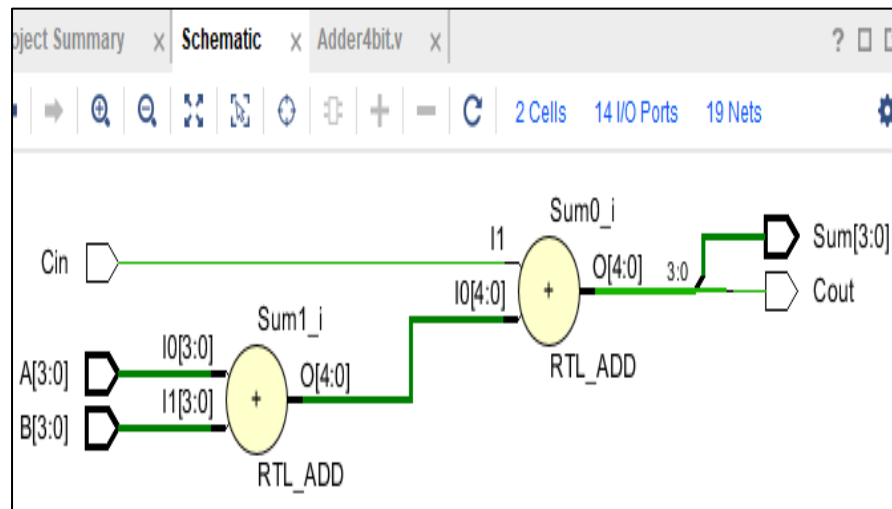

Observation

Vivado produces identical circuits for the 4-bit adder even with different ways of programming.

Compare with the circuits produced after synthesis & implementation steps in:

- N-bit Adder (Fig. 2-10)
- 4-bit Adder with FA sub-circuits (Fig. 2-12)

