

Tutorial 7

Real, reactive, apparent power, power factor and power factor correction

1. A 440 V, 50 Hz, star-connected induction motor takes a line current of 50 A at a power factor of 0.8 lagging. A three-phase capacitor bank, connected in star, is to be used to improve the power factor to 0.95 lagging. Determine the capacitance of each capacitor.
Ans: $C = 211 \mu\text{F}$
2. A 415 V, 50 Hz, three-phase distribution system supplies a 20 kVA, three-phase induction motor load at a power factor of 0.8 lagging, and a star-connected set of impedances, each having a resistance of 10Ω in series with an inductive reactance of 8Ω . Calculate the phase capacitance of delta-connected capacitors required to improve the overall power factor to 0.95 lagging.
Ans: $C = 72.1 \mu\text{F}$
3. A three-phase, 50 hp (1 hp = 746 W), 440 V, 50 Hz induction motor operates on full load with an efficiency of 89% and at a p.f. of 0.85 lagging. Calculate the total kVA rating of capacitors required, to raise the full load p.f. to 0.95 lagging. What will be the capacitance per phase if the capacitors are
 - (a) delta-connected, and
 - (b) star-connected.**Ans: $S_C = 12.193 \text{ kVA}$, $C_\Delta = 66.77 \mu\text{F}$, $C_Y = 200.27 \mu\text{F}$**
4. A 3-phase, 50 Hz induction motor is connected to a 3-phase 450V, 50 Hz, power supply. The motor has 4000 W output power on full-load operation. If the efficiency of the motor running on full load is 89%, calculate the input power of the motor.
 - (a) If the power factor of the motor running on full load is 0.8 lagging, calculate its apparent input power at full load.
 - (b) Calculate the reactive input power supplied to the motor on full load.
 - (c) Calculate the total kVA rating of the capacitor bank required, to raise the full load power factor to 0.95 leading.
 - (d) Calculate the capacitance per phase if the 3 balanced capacitors are connected in delta.**Ans: $S = 5.618 \text{ kVA}$, $Q = 3.373 \text{ kVAR}$, $S_C = Q_C = 4.85 \text{ kVA}$, $C = 25.39 \mu\text{F}$**
5. A 400 V, 60 Hz distribution system supplies a 15 kVA three-phase motor at a power factor of 0.7 lagging. A three-phase capacitor bank of 6 kVAR is connected across the motor terminals to improve the power factor. Determine the new power factor.
Ans: 0.912 (lagging)



Quiz – 2 questions