

2018/2019 SEMESTER TWO EXAMINATION

Diploma in Aerospace Electronics (DASE) 2<sup>nd</sup> Year FT  
Diploma in Engineering with Business (DEB) 3<sup>rd</sup> Year FT  
Diploma in Electrical & Electronic Engineering (DEEE) 2<sup>nd</sup> Year FT  
Diploma in Engineering Systems (DES) 2<sup>nd</sup> Year FT  
Diploma in Energy Systems and Management (DESM) 2<sup>nd</sup> Year FT

**CIRCUIT THEORY & ANALYSIS**

Time Allowed: 2 Hours

---

Instructions to Candidates

1. The examination rules set out on the last page of the answer booklet are to be complied with.
2. This paper consists of **TWO** sections:
  - Section A - 6 Short Questions, 10 marks each.
  - Section B - 2 Long Questions, 20 marks each.
3. **ALL** questions are **COMPULSORY**.
4. All questions are to be answered in the answer booklet. Start each question on a new page.
5. Fill in the Question Numbers in the boxes found on the front cover of the answer booklet under the column "Question Answered".
6. This paper consists of 6 pages, inclusive of the formulae sheet.

**SECTION A: 6 QUESTIONS** (10 marks each)

- A1. Using the source conversion method, simplify the circuit shown in Figure A1 to its equivalent current source across terminals A and B. (10 marks)

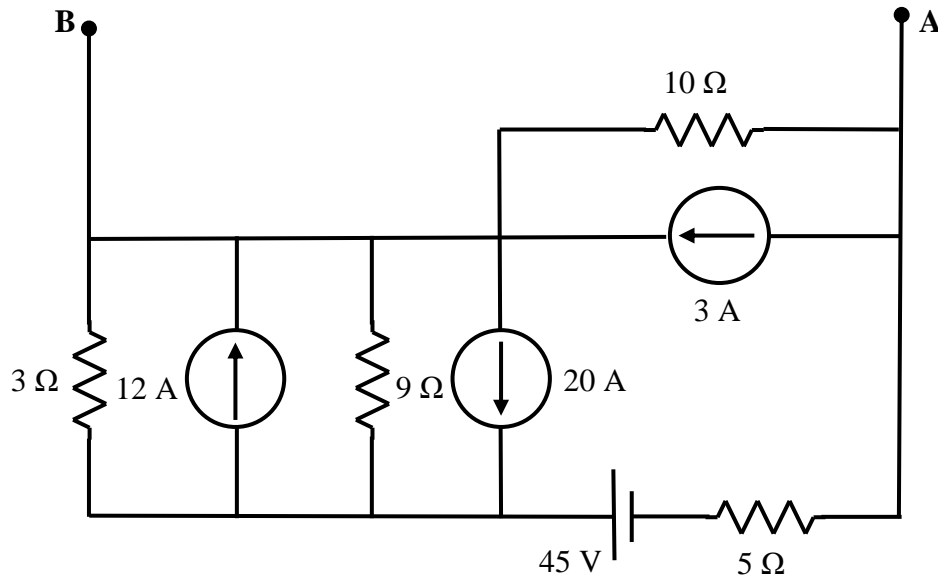


Figure A1

- A2. For the circuit shown in Figure A2,
- convert the star-connected resistors as shown in the dotted box into an equivalent delta-connection, and (6 marks)
  - hence calculate the total circuit resistance across terminals X and Y. (4 marks)

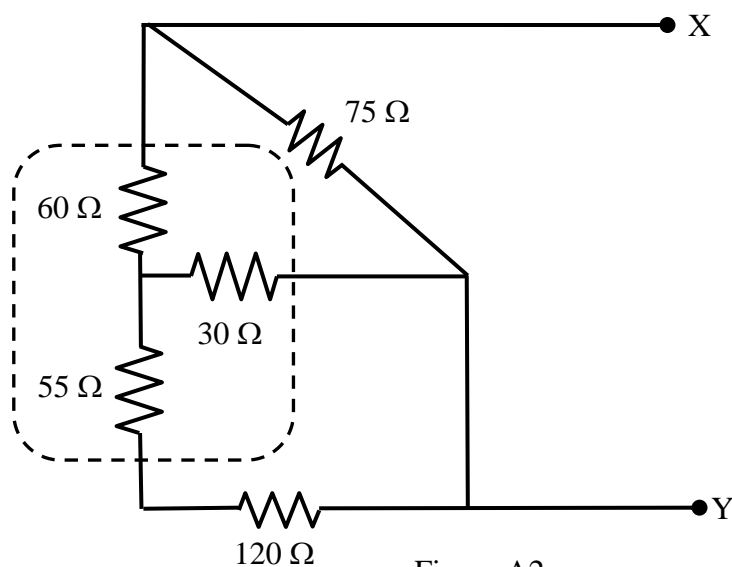


Figure A2

- A3. A 3-phase, 3-wire, 150 V, 50 Hz, ABC system is applied to a balanced star-connected load. Taking  $V_{CA}$  as the reference voltage, the line current  $I_C$  is  $15\angle 20^\circ$  A. Determine the:
- (a) phase impedance in polar form, (4 marks)
  - (b) total active and apparent power, and (4 marks)
  - (c) power factor of the star-connected load. (2 marks)
- A4. A balanced delta load having a power factor of 0.68 leading is connected to a 250 V, 3-phase, 3-wire balanced supply. If the total reactive power of the load is 8 kVAR, calculate the:
- (a) magnitude of the phase current, and (5 marks)
  - (b) resistance and reactance for each phase of the load. (5 marks)
- A5. A 300 V, 50 Hz, three-phase distribution system supplies a 15 kW three-phase load at a power factor of 0.7 lagging. A three-phase delta-connected capacitor bank is connected across the load to improve the overall power factor to unity. Calculate the:
- (a) kVA rating of the capacitor bank, and (2 marks)
  - (b) capacitance per phase of the capacitor bank. (8 marks)
- A6. A 300 V, 3-phase motor has an output of 30 kW and operates at a power factor of 0.85 lagging with an efficiency of 80 %. Calculate the:
- (a) input power of the motor, (2 marks)
  - (b) magnitude of the line current, and (3 marks)
  - (c) reading on each of two wattmeters connected to measure the input power. (5 marks)

**SECTION B: 2 QUESTIONS** (20 marks each)

- B1(a). Apply Norton's Theorem to find the Norton equivalent circuit parameters  $I_N$  and  $Z_N$  between terminals A and B for the circuit shown in Figure B1. (Include circuit diagrams for finding  $I_N$  and  $Z_N$ ) (16 marks)
- (b). Draw the Norton's equivalent circuit obtained above and hence calculate the current in the load  $R_L$ . (4 marks)

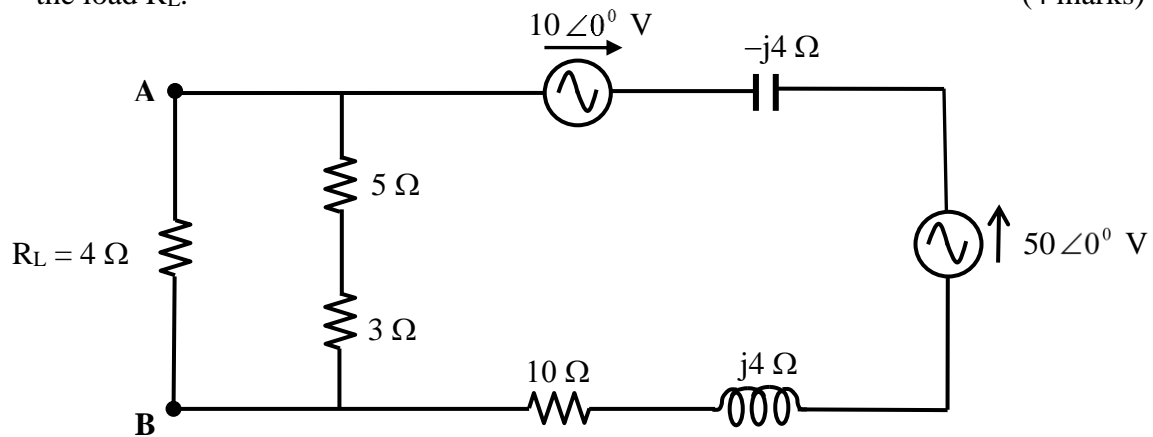


Figure B1

- B2. An unbalanced star-connected load is connected to a three-phase, 400 V, 50 Hz, ABC supply as shown in Figure B2. Taking  $V_{AN}$  as the reference voltage, determine the:
- neutral current, (2 marks)
  - phase impedances of the unbalanced star-connected load in polar form, (7 marks)
  - total real and reactive power. (7 marks)
- Draw a phasor diagram showing the reference voltage and line currents. (4 marks)

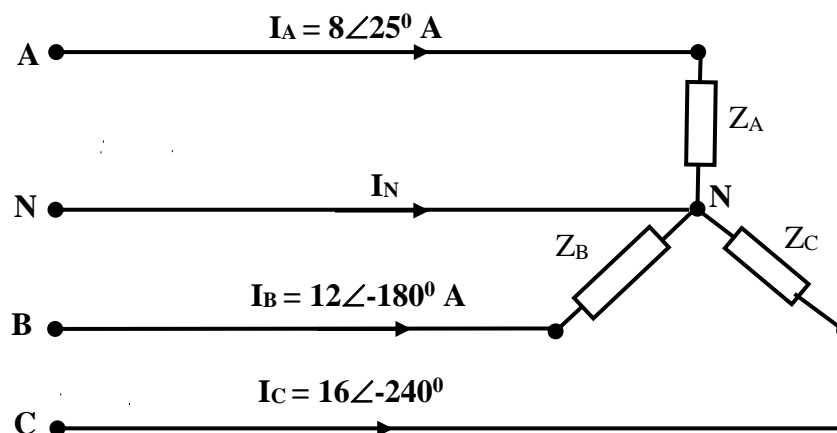
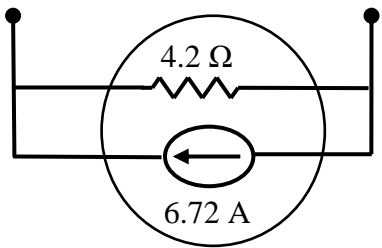


Figure B2

Formulae

Resistors in series	$R_T = R_1 + R_2 + R_3 + \dots$
Resistors in parallel	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$
Resistors in parallel (for 2 resistors)	$R_T = \frac{R_1 R_2}{R_1 + R_2}$
Voltage Divider Rule	$V_x = \frac{R_x}{R_T} V_s$
Current Divider Rule (for 2 resistors)	$I_1 = \frac{R_2}{R_1 + R_2} I_T$
Source Conversion	$E = I_s R_s \qquad I_s = \frac{E}{R_s}$
Mesh Current Analysis	$[Z] [I] = [V]$
Nodal Voltage Analysis	$[Y] [V] = [I]$
Delta to Star Conversion	$Z_1 = \frac{Z_A Z_C}{Z_A + Z_B + Z_C}$ $Z_2 = \frac{Z_A Z_B}{Z_A + Z_B + Z_C}$ $Z_3 = \frac{Z_B Z_C}{Z_A + Z_B + Z_C}$
Star to Delta Conversion	$Z_A = Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3}$ $Z_B = Z_2 + Z_3 + \frac{Z_2 Z_3}{Z_1}$ $Z_C = Z_1 + Z_3 + \frac{Z_1 Z_3}{Z_2}$
Inductive Reactance	$X_L = 2\pi f L$
Capacitive Reactance	$X_C = \frac{1}{2\pi f C}$
Three Phase Star – Connected Load	$V_L = \sqrt{3} V_{PH}$ $I_L = I_{PH}$ $Z_{PH} = \frac{V_{PH}}{I_{PH}}$

Three Phase Delta - Connected Load	$V_L = V_{PH}$ $I_L = \sqrt{3} I_{PH}$ $Z_{PH} = \frac{V_{PH}}{I_{PH}}$
Three Phase Apparent Power	$S_T = 3 V_{PH} I_{PH} = \sqrt{3} V_L I_L$
Three Phase Active/Real/True Power	$P_T = 3 V_{PH} I_{PH} \cos \phi = \sqrt{3} V_L I_L \cos \phi$
Three Phase Reactive Power	$Q_T = 3 V_{PH} I_{PH} \sin \phi = \sqrt{3} V_L I_L \sin \phi$
Power factor	Power factor = $\cos \phi = \frac{P}{S}$
Two-Wattmeter Method	$W_1 = V_L \times I_L \times \cos (\theta - 30^\circ)$ $W_2 = V_L \times I_L \times \cos (\theta + 30^\circ)$ $P_T = W_1 + W_2$ Power factor = $\cos \left( \tan^{-1} \left[ \sqrt{3} \left( \frac{W_1 - W_2}{W_1 + W_2} \right) \right] \right)$

NO	Answers
A1.	

A2.	
(a)	$R_1 = 225 \, \Omega$ $R_2 = 122.73 \, \Omega$ $R_3 = 112.5 \, \Omega$
(b)	$R_{XY} = 39.98 \, \Omega$

A3.	
(a)	$Z = 5.77 \angle -50^\circ \, \Omega$
(b)	Total Active Power, $P_T = 2.51 \, \text{kW}$ Total Apparent Power, $S_T = 3.897 \, \text{kVA}$
(c)	Power factor = 0.643    leading


A4.	
(a)	$I_{PH} = \frac{25.2}{\sqrt{3}} = 14.55 \, \text{A}$
(b)	$R = 11.68 \, \Omega$ $X_C = 12.6 \, \Omega$

A6.	
(a)	Input Power = $\frac{30 \text{ k}}{0.8} = 37.5 \text{ kW}$
(b)	$I_L = \frac{37.5 \text{ k}}{\sqrt{3} (300)(0.85)} = 84.9 \text{ A}$
(c)	$W_1 = 25.46 \text{ kW}$
	$W_2 = 12.04 \text{ kW}$

Page 8 of 6



B2(a).	$I_N = - (21.44 \angle 126.49^\circ) \text{ A}$ or $21.44 \angle -53.51^\circ \text{ A}$
(b)	$Z_A = 28.87 \angle -25^\circ \Omega$
	$Z_B = 19.25 \angle 60^\circ \Omega$
	$Z_C = 14.43 \angle 0^\circ \Omega$

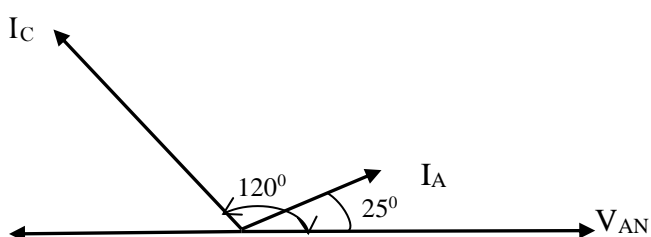(c)	$P_T = 6.76 \text{ kW}$
	$Q_T = 1.62 \text{ kVAR}$
	 <p>Phasor diagram showing three current vectors <math>I_A</math>, <math>I_B</math>, and <math>I_C</math> originating from a common point. <math>I_A</math> is at <math>25^\circ</math>, <math>I_B</math> is at <math>120^\circ</math>, and <math>I_C</math> is at <math>235^\circ</math> (or <math>120^\circ + 115^\circ</math>). A voltage vector <math>V_{AN}</math> is shown along the positive x-axis.</p>