

2017/2018 SEMESTER ONE EXAMINATION

Diploma in Aerospace Electronics (DASE) 2<sup>nd</sup> Year FT  
Diploma in Engineering with Business (DEB) 3<sup>rd</sup> Year FT  
Diploma in Electrical & Electronic Engineering (DEEE) 2<sup>nd</sup> Year FT  
Diploma in Engineering Systems (DES) 2<sup>nd</sup> Year FT  
Diploma in Energy Systems and Management (DESM) 2<sup>nd</sup> Year FT

**CIRCUIT THEORY & ANALYSIS**

Time Allowed: 2 Hours


---

Instructions to Candidates

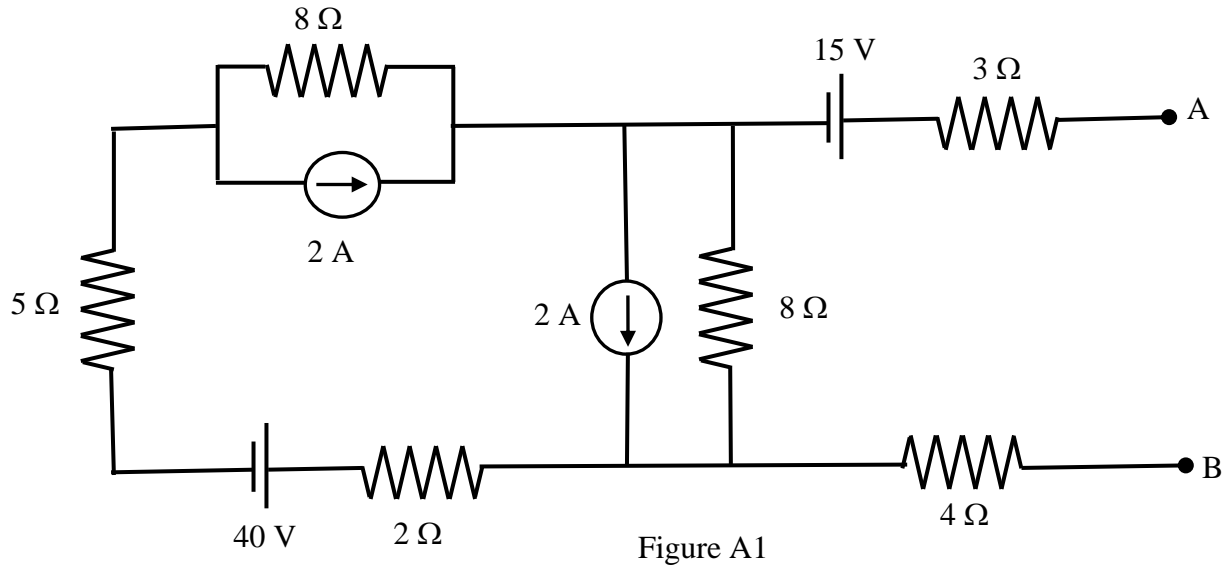
1. The examination rules set out on the last page of the answer booklet are to be complied with.
2. This paper consists of **TWO** sections:
  - Section A - 6 Short Questions, 10 marks each.
  - Section B - 2 Long Questions, 20 marks each.
3. **ALL** questions are **COMPULSORY**.
4. All questions are to be answered in the answer booklet. Start each question on a new page.
5. Fill in the Question Numbers in the boxes found on the front cover of the answer booklet under the column "Question Answered".
6. This paper consists of 6 pages, inclusive of the formulae sheet.

**SECTION A: 6 QUESTIONS** (10 marks each)

- A1. Using the source conversion method, simplify the circuit shown in Figure A1 to its equivalent voltage source across terminals A and B. (10 marks)



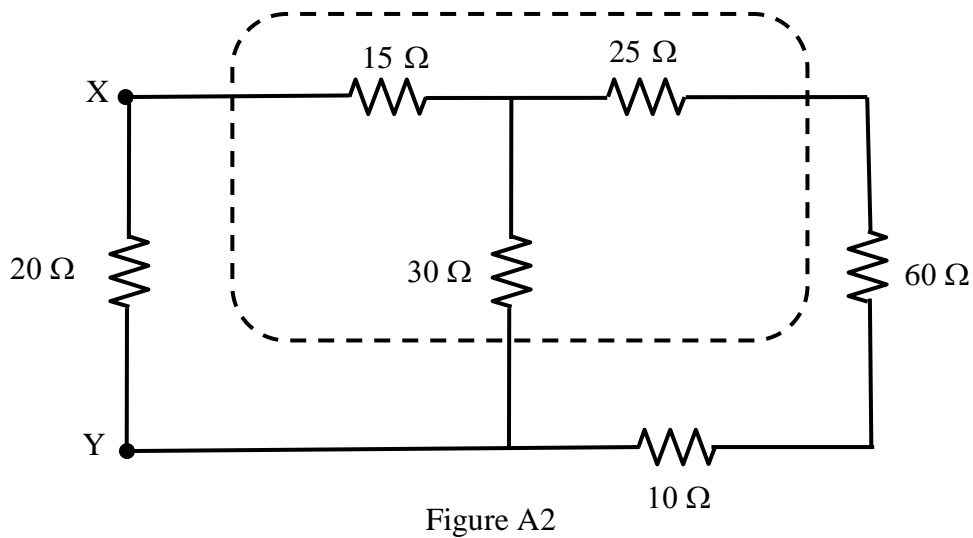- A2. For the circuit shown in Figure A2, convert the star-connected resistors as shown in the dotted box into an equivalent delta-connection, and hence determine the total resistance across terminals X and Y. (10 marks)



- A3. A balanced delta-connected load with a phase impedance of  $(4 + j8) \Omega$  is connected to a 300 V, 50 Hz, ABC supply. Taking  $V_{BC}$  as the reference voltage, calculate the:
- (a) phase current ( $I_{BC}$ ), (4 marks)
  - (b) line current ( $I_B$ ), (2 marks)
  - (c) total apparent and reactive power supplied to the load. (4 marks)
- A4. A 400 V, 50 Hz, 3-phase distribution system supplies a 5 kVA load at a power factor of 0.6 lagging. A three-phase capacitor bank of 4 kVA is connected across the load terminals to improve the power factor. Calculate the:
- (a) real and reactive power of the load, (5 marks)
  - (b) power factor after adding the capacitor bank, and (3 marks)
  - (c) reactive power of the system after power factor improvement. (2 marks)
- A5. A 3-phase, 4-wire, 400 V, ABC system supplies an unbalanced star-connected load. Taking  $V_{BN}$  as the reference, the line currents flowing into the load are as follows:  
 $I_A = 5 \angle 90^\circ$  A,  $I_B = 10 \angle 45^\circ$  A and  $I_C = 6 \angle -30^\circ$  A  
Determine the:
- (a) phase impedances of the unbalanced star load, and (7 marks)
  - (b) total real power of the system. (3 marks)
- A6. A delta-connected load consists of three similar impedances. When the load is connected to a 3-phase, 4-wire, 250 V, 50 Hz supply, the phase current is 10 A and the power factor is 0.75 lagging.
- (a) Draw a circuit diagram showing the connection of a single wattmeter required for measuring the phase power of the delta-connected load. (4 marks)
  - (b) If the total power consumption of the delta-connected load is measured using the two-wattmeter method, determine the reading of each wattmeter. (6 marks)

**SECTION B: 2 QUESTIONS** (20 marks each)

B1(a). Design an equivalent circuit using Norton's Theorem across terminals A and B for the network shown in Figure B1. (Include circuit diagrams for finding  $I_N$  and  $R_N$ )

(17 marks)

(b). Draw the Norton's equivalent circuit.

(3 marks)

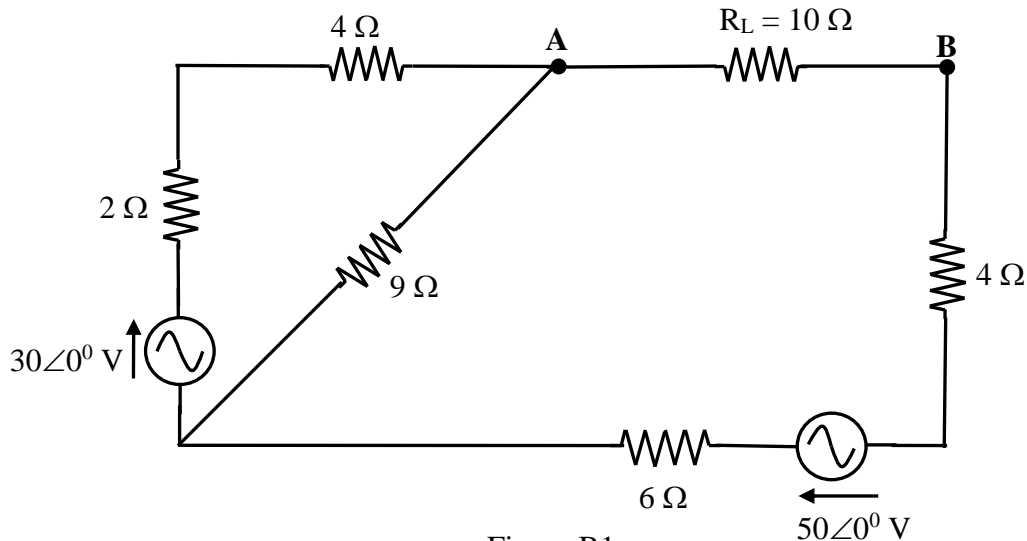


Figure B1

B2. Figure B2 shows a 3-phase star configuration network with equal loads, having a power factor of 0.8 leading. Calculate the:

(a) line voltages ( $V_{AB}$ ,  $V_{BC}$ ,  $V_{CA}$ ), (6 marks)

(b) phase impedance of the star-connected load in polar form, (4 marks)

(c) passive elements that make up each phase of the load. (4 marks)

Draw a phasor diagram showing the line voltages and line currents.

(6 marks)

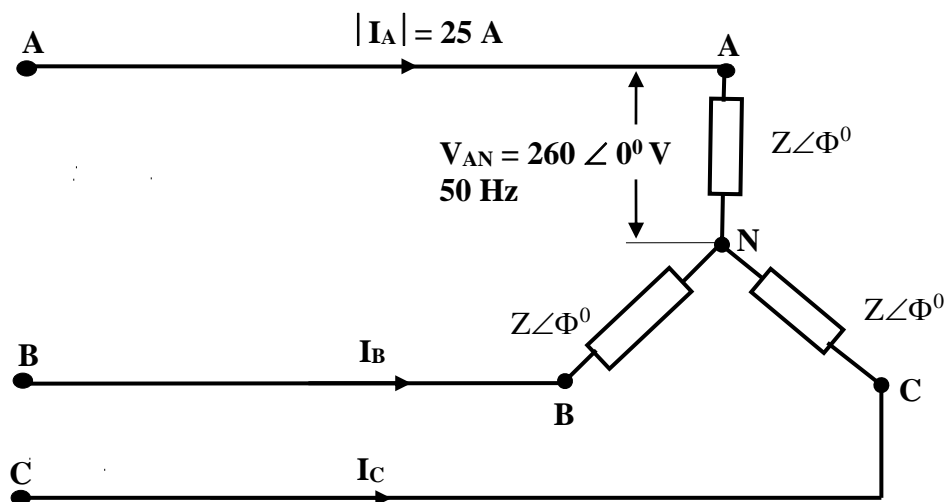


Figure B2

- End of Paper -

Formulae

Resistors in series	$R_T = R_1 + R_2 + R_3 + \dots$
Resistors in parallel	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$
Resistors in parallel (for 2 resistors)	$R_T = \frac{R_1 R_2}{R_1 + R_2}$
Voltage Divider Rule	$V_X = \frac{R_X}{R_T} V_S$
Current Divider Rule	$I_1 = \frac{R_2}{R_1 + R_2} I_T$
Source Conversion	$E = I_S R_S \qquad I_S = \frac{E}{R_S}$
Mesh Current Analysis	$[Z] [I] = [V]$
Nodal Voltage Analysis	$[Y] [V] = [I]$
Delta to Star Conversion	$Z_1 = \frac{Z_A Z_C}{Z_A + Z_B + Z_C}$ $Z_2 = \frac{Z_A Z_B}{Z_A + Z_B + Z_C}$ $Z_3 = \frac{Z_B Z_C}{Z_A + Z_B + Z_C}$
Star to Delta Conversion	$Z_A = Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3}$ $Z_B = Z_2 + Z_3 + \frac{Z_2 Z_3}{Z_1}$ $Z_C = Z_1 + Z_3 + \frac{Z_1 Z_3}{Z_2}$
Inductive Reactance	$X_L = 2\pi f L$
Capacitive Reactance	$X_C = \frac{1}{2\pi f C}$
Three Phase Star – Connected Load	$V_L = \sqrt{3} V_{PH}$ $I_L = I_{PH}$ $Z_{PH} = \frac{V_{PH}}{I_{PH}}$

Three Phase Delta - Connected Load	$V_L = V_{PH}$ $I_L = \sqrt{3} I_{PH}$ $Z_{PH} = \frac{V_{PH}}{I_{PH}}$
Three Phase Apparent Power	$S_T = 3 V_{PH} I_{PH} = \sqrt{3} V_L I_L$
Three Phase Active/Real/True Power	$P_T = 3 V_{PH} I_{PH} \cos \phi = \sqrt{3} V_L I_L \cos \phi$
Three Phase Reactive Power	$Q_T = 3 V_{PH} I_{PH} \sin \phi = \sqrt{3} V_L I_L \sin \phi$
Power factor	Power factor = $\cos \phi = \frac{P}{S}$
Two-Wattmeter Method	$W_1 = V_L \times I_L \times \cos (\theta - 30^\circ)$ $W_2 = V_L \times I_L \times \cos (\theta + 30^\circ)$ $P_T = W_1 + W_2$ Power factor = $\cos \left( \tan^{-1} \left[ \sqrt{3} \left( \frac{W_1 - W_2}{W_1 + W_2} \right) \right] \right)$

**ANSWERS:**

A1.  $V_S = 3.79 \text{ V}$ ,  $R = 12.22 \Omega$

A2.  $R_1 = 52.5 \Omega$ ,  $R_2 = 63 \Omega$ ,  $R_3 = 105 \Omega$

$R_{XY} = 12.99 \Omega$

A3.  $I_{BC} = 33.56 \angle -63.43^\circ \text{ A}$ ,  $I_B = 58.13 \angle -93.43^\circ \text{ A}$

$S_T = 30.21 \text{ kVA}$ ,  $Q_T = 27.02 \text{ kVAr}$

A4. Real Power,  $P = 3 \text{ kW}$ , Reactive Power,  $Q = 4 \text{ kVAr}$


New power factor = 1

Reactive Power,  $Q_T = 0 \text{ kVAr}$

A5.  $Z_A = 46.19 \angle -330^\circ \Omega$  or  $46.19 \angle 30^\circ \Omega$ ,  $Z_B = 23.09 \angle -45^\circ \Omega$ ,


$Z_C = 38.49 \angle -90^\circ \Omega$

$P_T = 2.63 \text{ kW}$

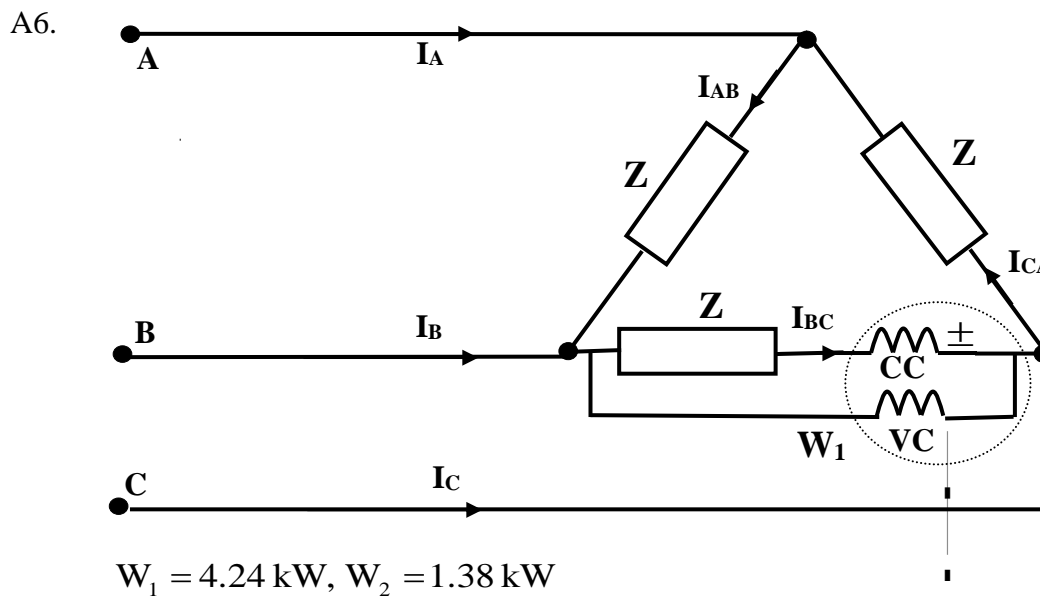

B1.  $I_N = 5 \text{ A}$ ,  $R_N = 13.6 \Omega$

Norton's Equivalent Circuit

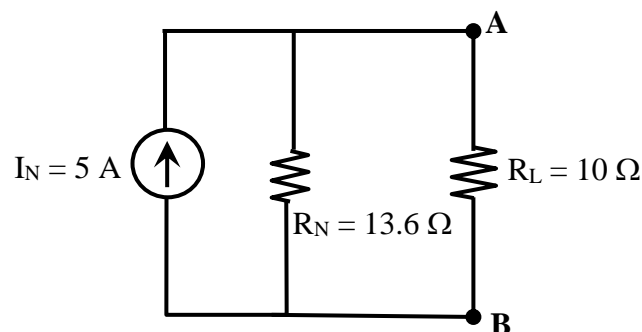

B2.  $V_{AB} = 450.33 \angle 30^\circ \text{ V}$ ,  $V_{BC} = 450.33 \angle -90^\circ \text{ V}$ ,  $V_{CA} = 450.33 \angle -210^\circ \text{ V}$  or  $450.33 \angle 150^\circ \text{ V}$

$$Z = 10.4 \angle -36.87^\circ \Omega,$$

$$R = 8.32 \Omega$$

$$C = 510.11 \mu\text{F}$$

