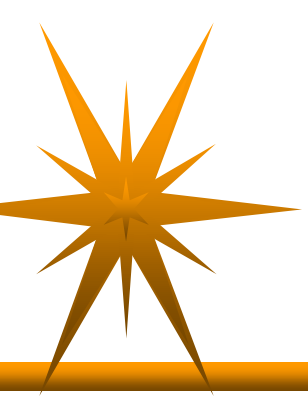



# Norton's Theorem

---


It states that any linear circuit between two points A and B can be replaced by an equivalent circuit consisting of a current source *in parallel* with a single impedance.




# Norton's Theorem

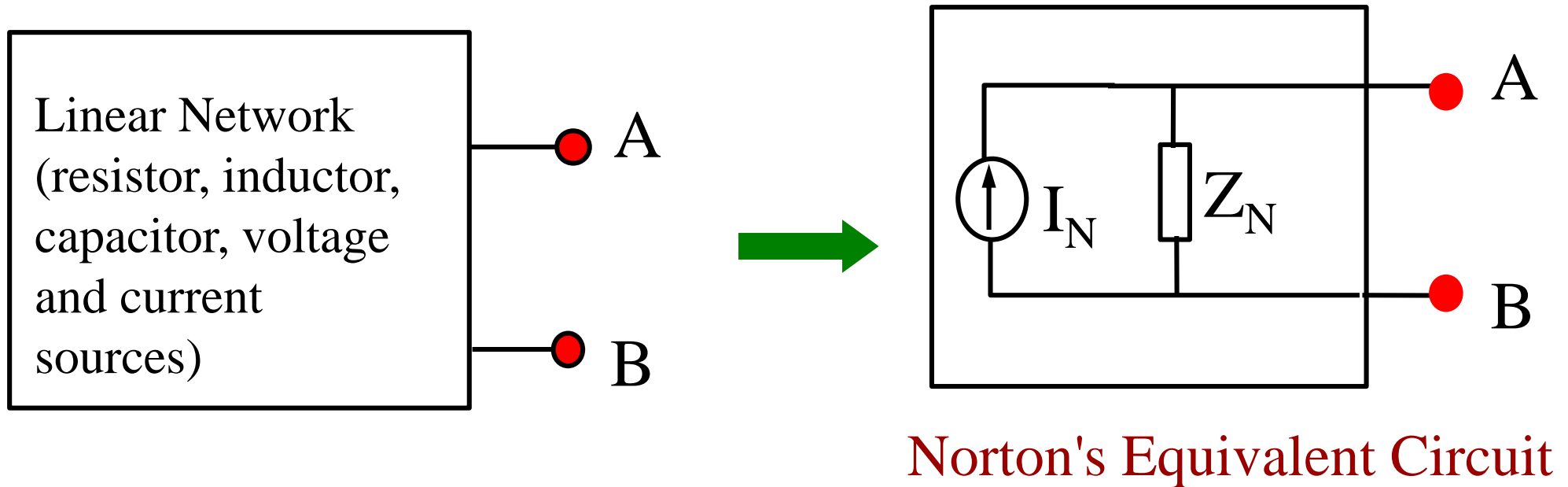

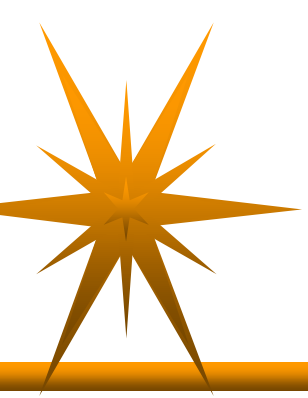$I_N$  - Norton's current, equals to the short-circuit current across terminals A & B when they are shorted in the original linear network.




# Norton's Theorem

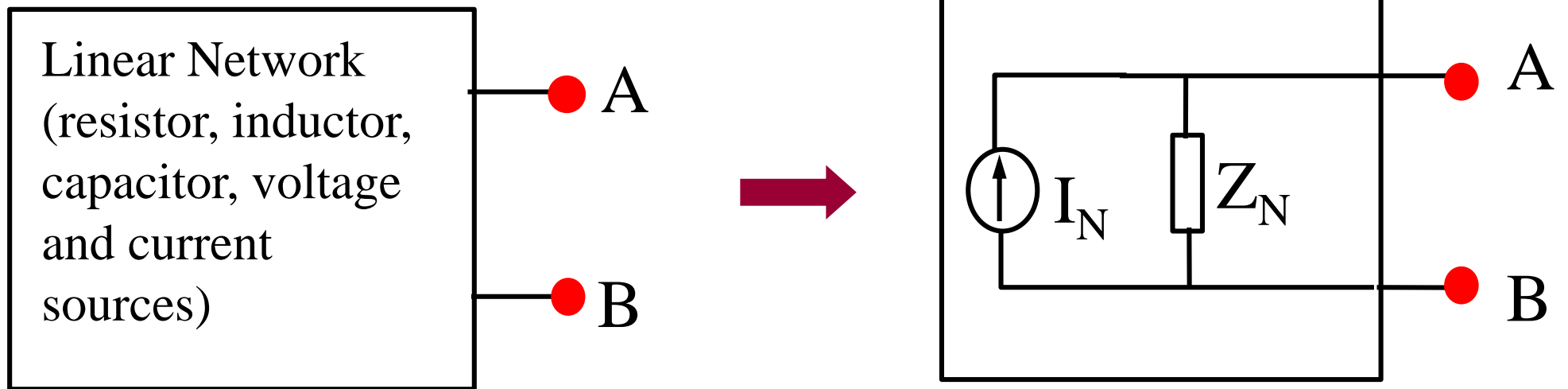


Norton's Equivalent Circuit

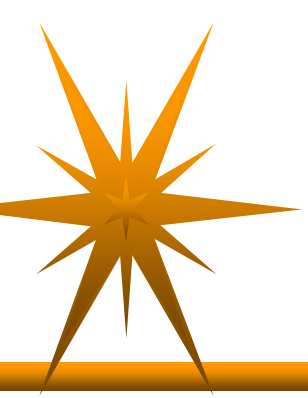$Z_N$  - Norton's impedance, equals to the impedance across terminals A & B in the original linear network, with all the voltage and current sources reduced to zero.




# Norton's Theorem

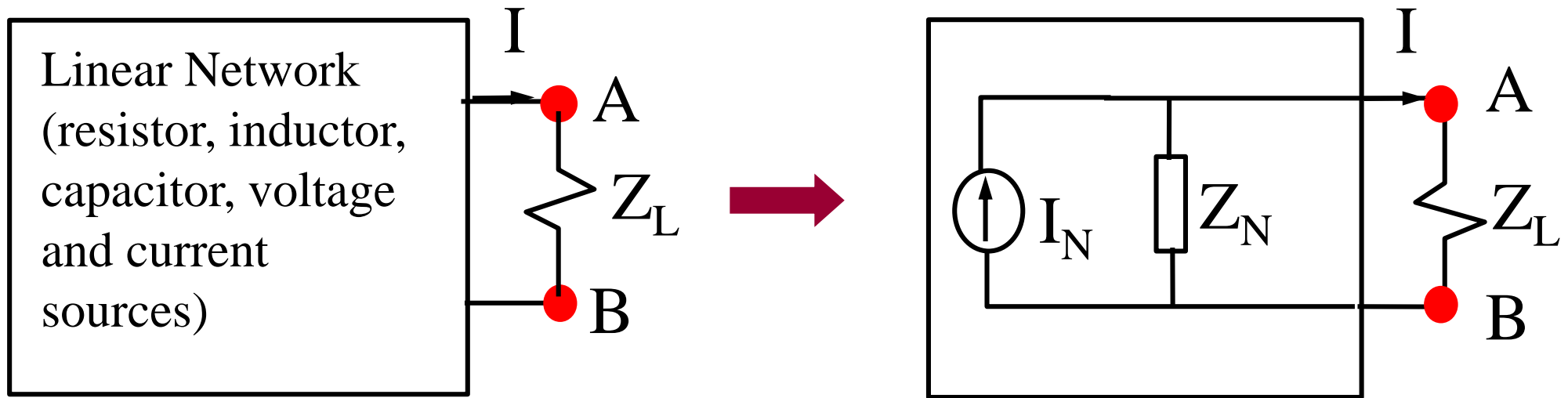


Norton's Equivalent Circuit

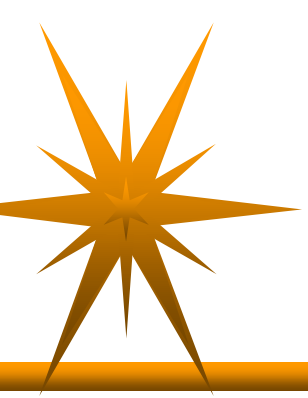A load impedance  $Z_L$  will experience the same current by connecting across AB in the original circuit and in the Norton's equivalent circuit.




# Norton's Theorem

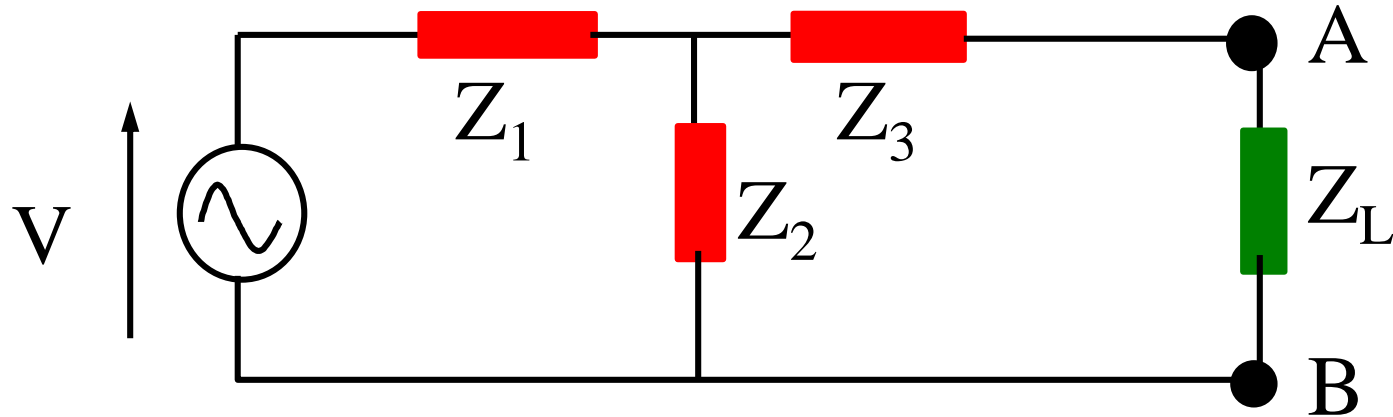


Given this original circuit, find the Norton's equivalent circuit across terminals A & B.

# Procedure in applying Norton's Theorem

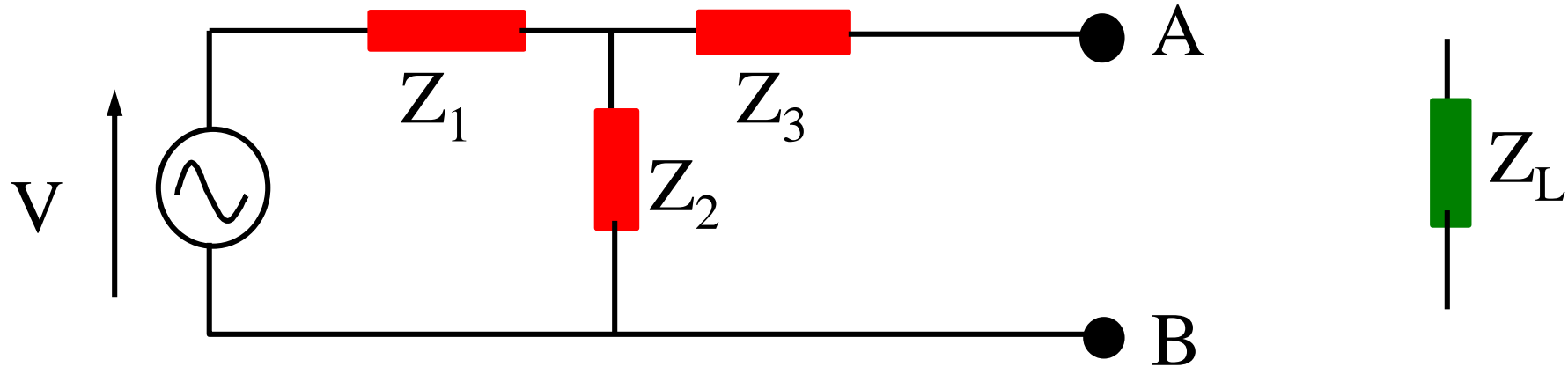

**Step 1** - Disconnect the load  $Z_L$  from the circuit such that terminals A & B are now open-circuit.


# Procedure in applying Norton's Theorem

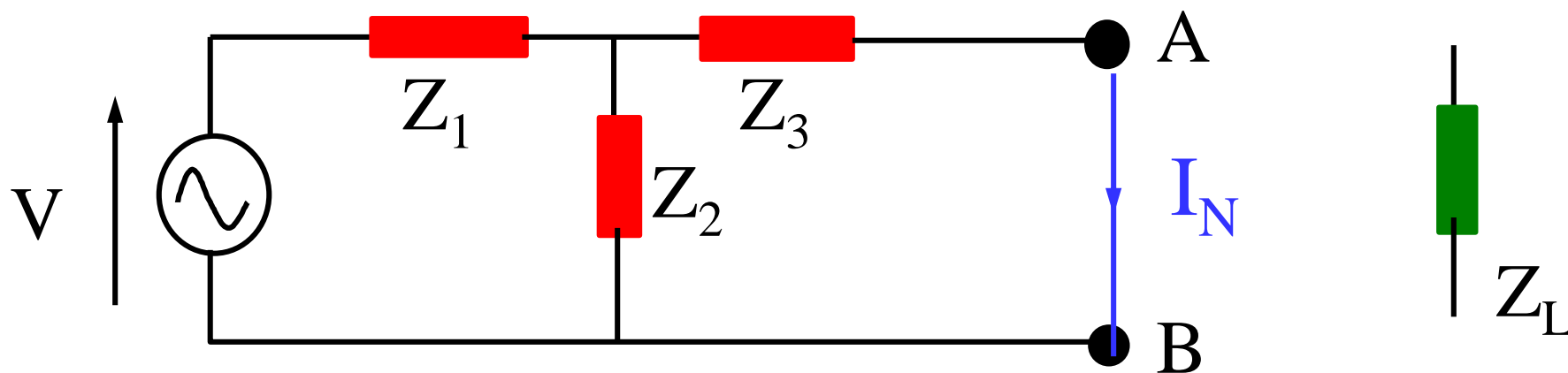

**Step 2** - put a short-circuit across terminals A & B and then calculate the short-circuit current. This is the Norton's current  $I_N$ .

*For computing you can only use either the application of Ohm's Law or Mesh/Loop Analysis method.*

# Procedure in applying Norton's Theorem

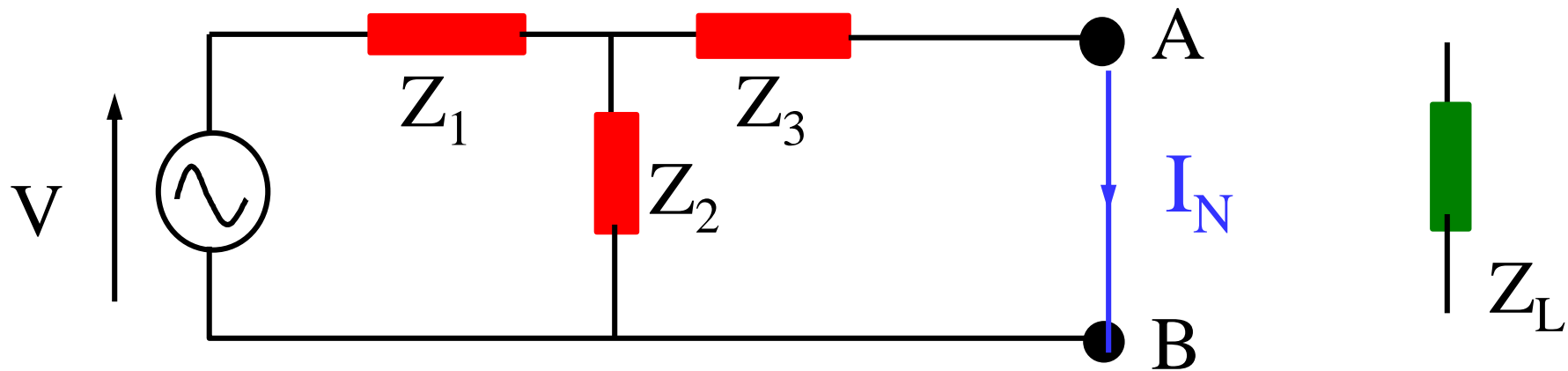


In this example,  $Z_T = Z_1 + (Z_2 // Z_3)$

$$I_T = V/Z_T$$

$$I_N = I_T \times Z_2 / (Z_2 + Z_3)$$




# Procedure in applying Norton's Theorem

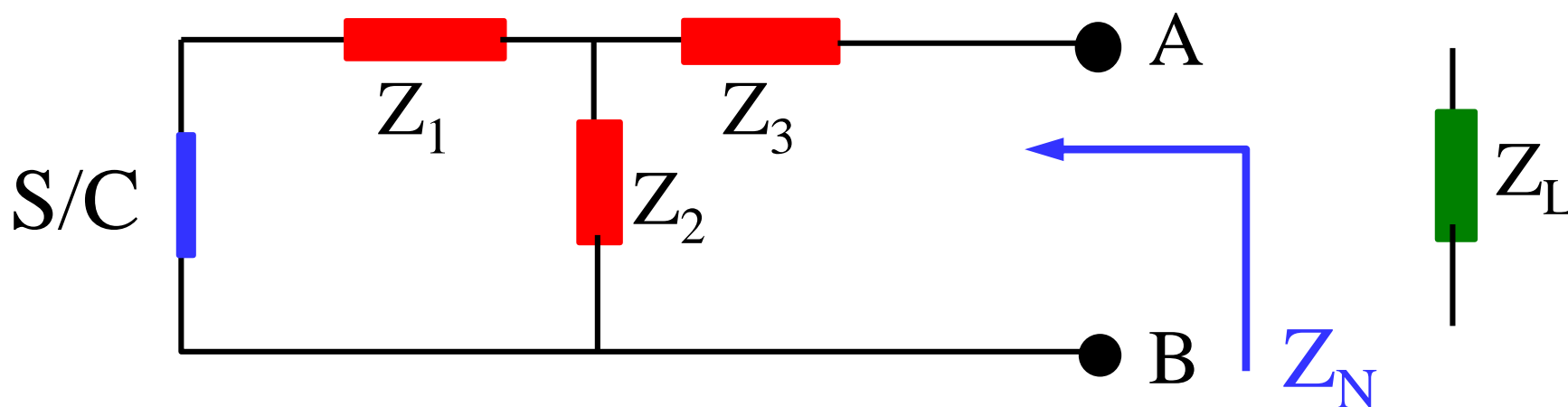

**Step 3** - Replace the voltage source by a short circuit (current source by open circuit) and calculate the impedance across  $A$  &  $B$  by looking into the source free circuit. **This is the  $Z_N$ .**

For this example,  $Z_N = (Z_1 // Z_2) + Z_3$


# Procedure in applying Norton's Theorem

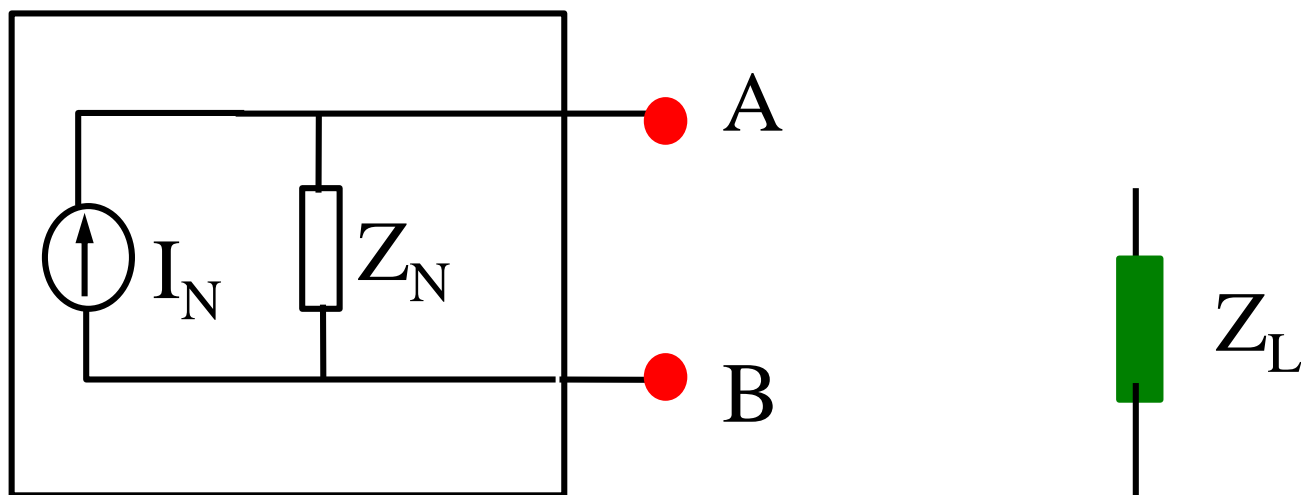

Norton's Equivalent Circuit

**Step 4** - Knowing  $I_N$  and  $Z_N$ , the Norton's equivalent circuit can now be formed.


# Procedure in applying Norton's Theorem

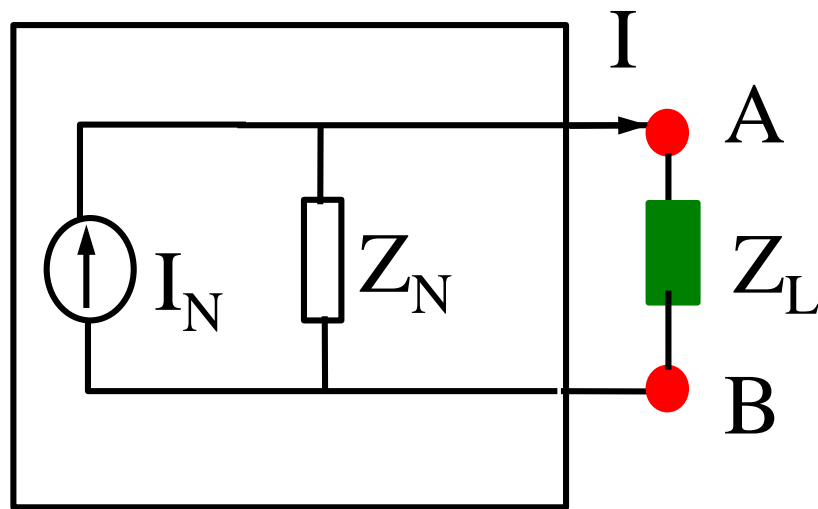

$$I = I_N \times Z_N / (Z_N + Z_L)$$

This value of  $I$  will have the same value when  $Z_L$  is connected in the original linear circuit.

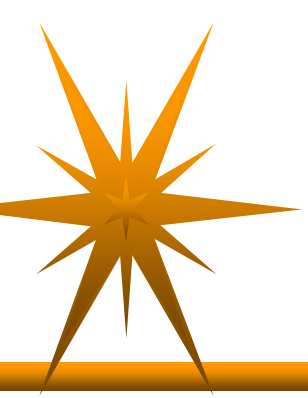If it is the current through  $Z_L$  you want to find, then  $Z_L$  should be reconnected across A & B.




# Procedure in applying Norton's Theorem

---


**NOTE:**


**Source Conversion is not allowed.**

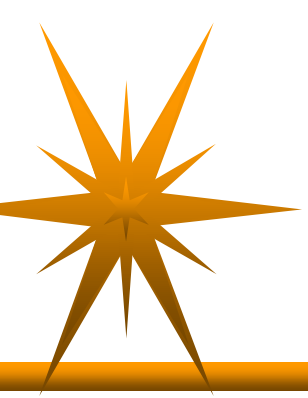


## Example 1.11

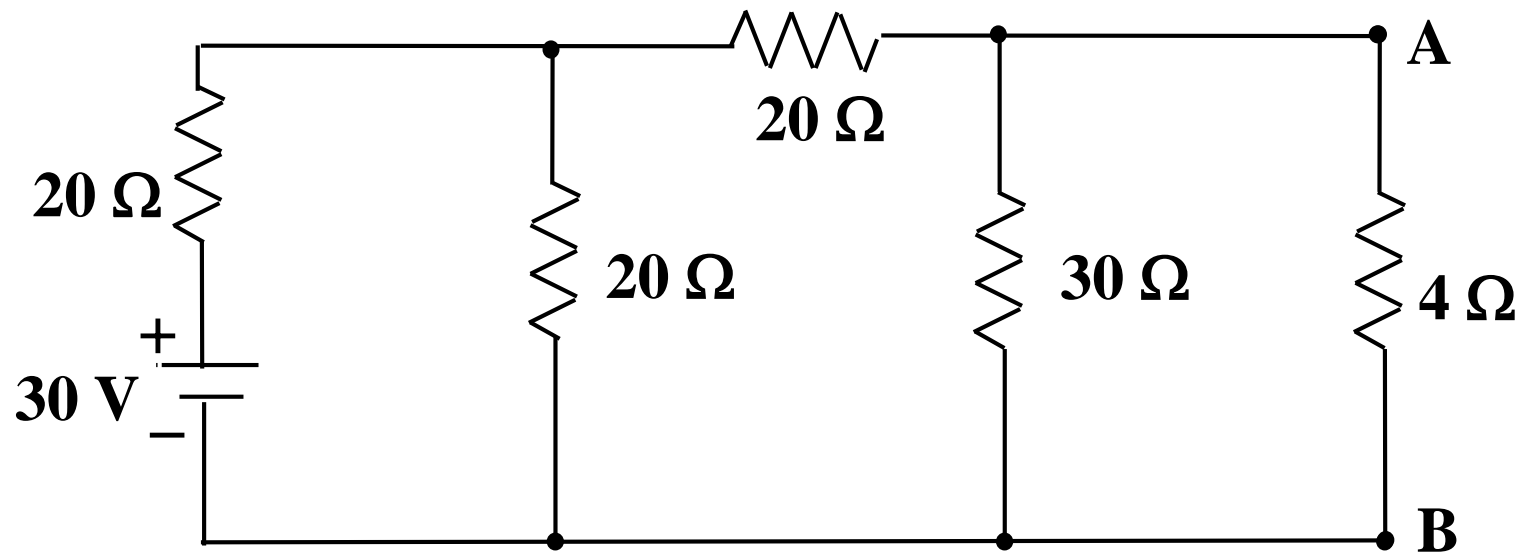**Apply Norton's theorem to find the current in the  $4\ \Omega$  resistor.**




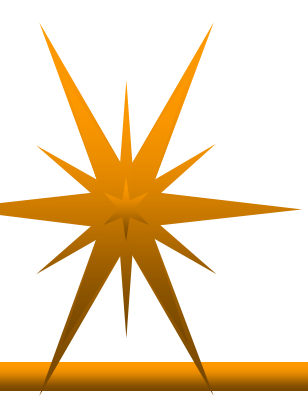


## Example 1.11

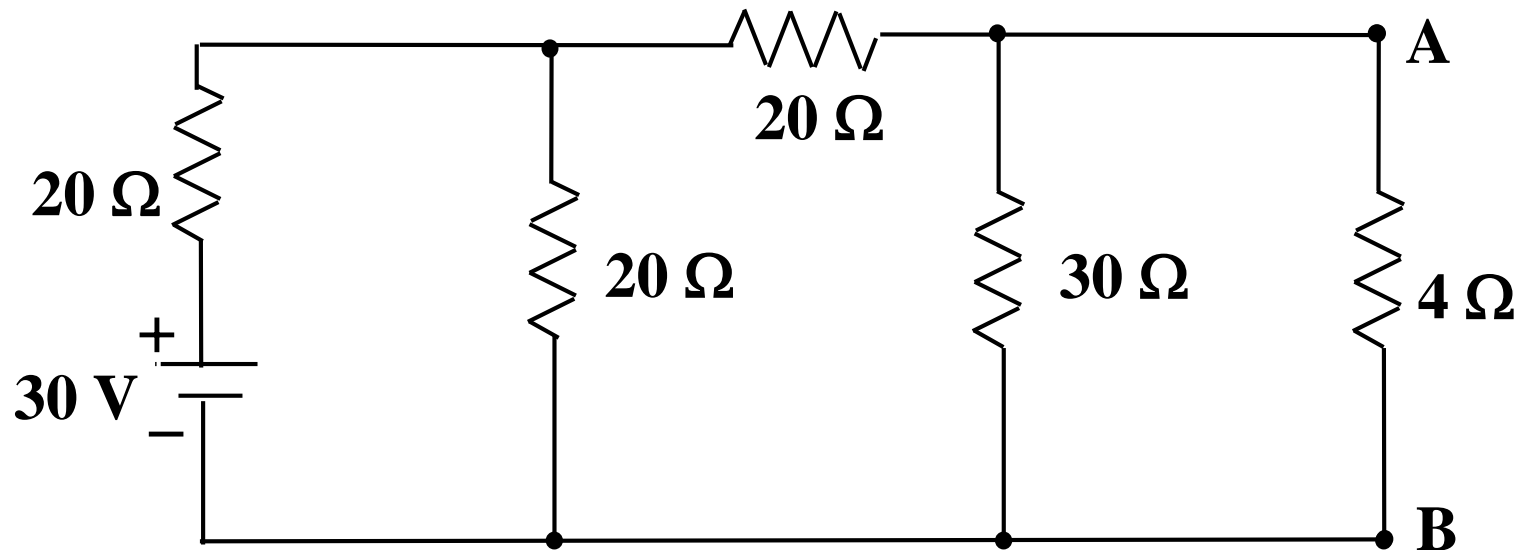

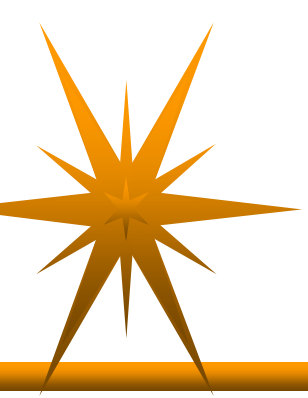
**To find the Norton's equivalent circuit across AB, the first thing to do is to remove  $R_L$  such that terminals A & B are now open-circuit.**




## Example 1.11

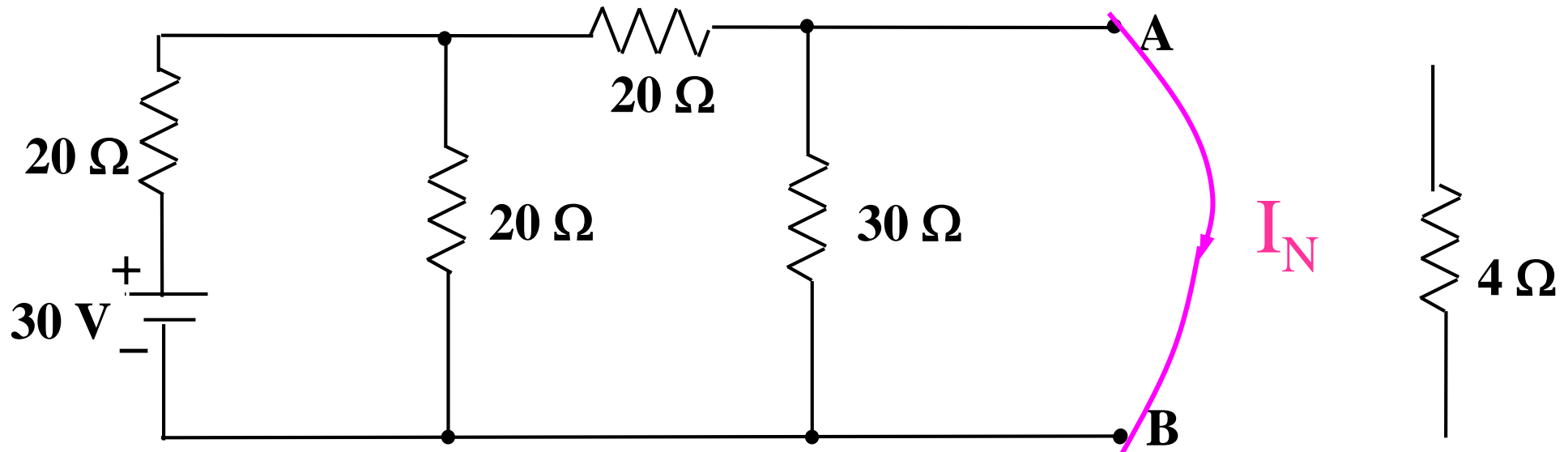

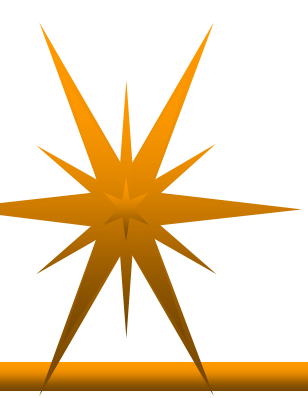To find the Norton's current sources  $I_N$ , put a short circuit across terminals AB. The current  $I_N$  flows through the short circuit is the Norton's current source.



## Example 1.11

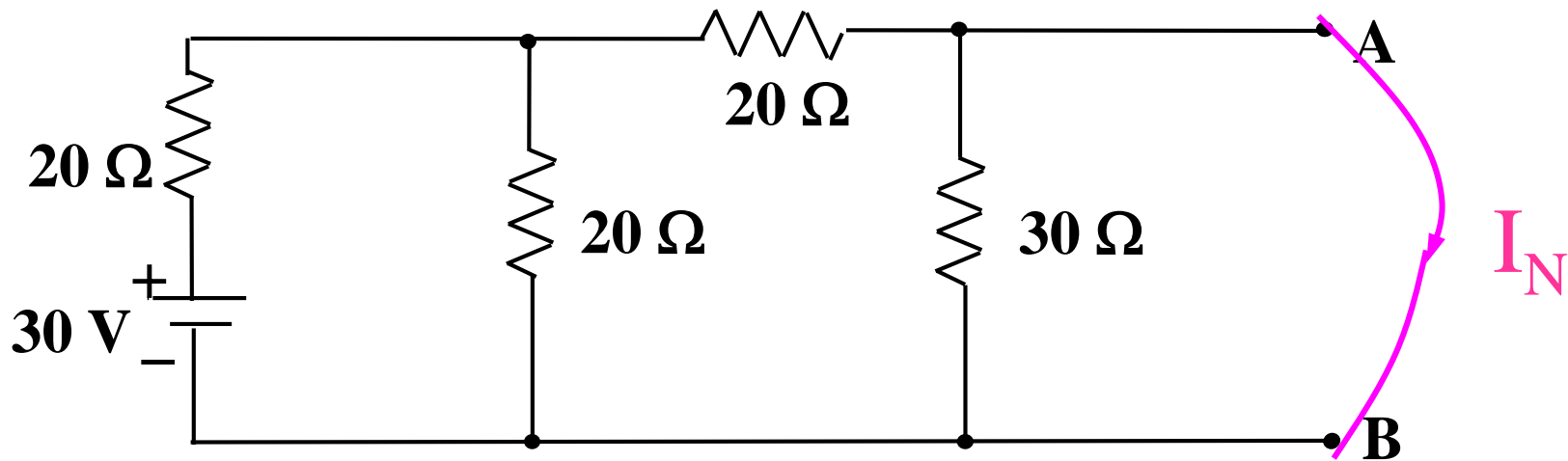


$$R_{//} = 10\Omega$$

$$R_T = 10 + 20 = 30\Omega$$


$$I_T = \frac{30}{30} = 1\text{ A}$$

$$I_N = \frac{1}{2} = 0.5\text{ A}$$




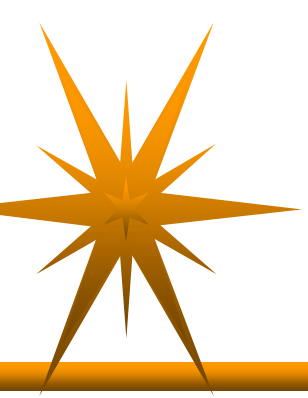


## Example 1.11

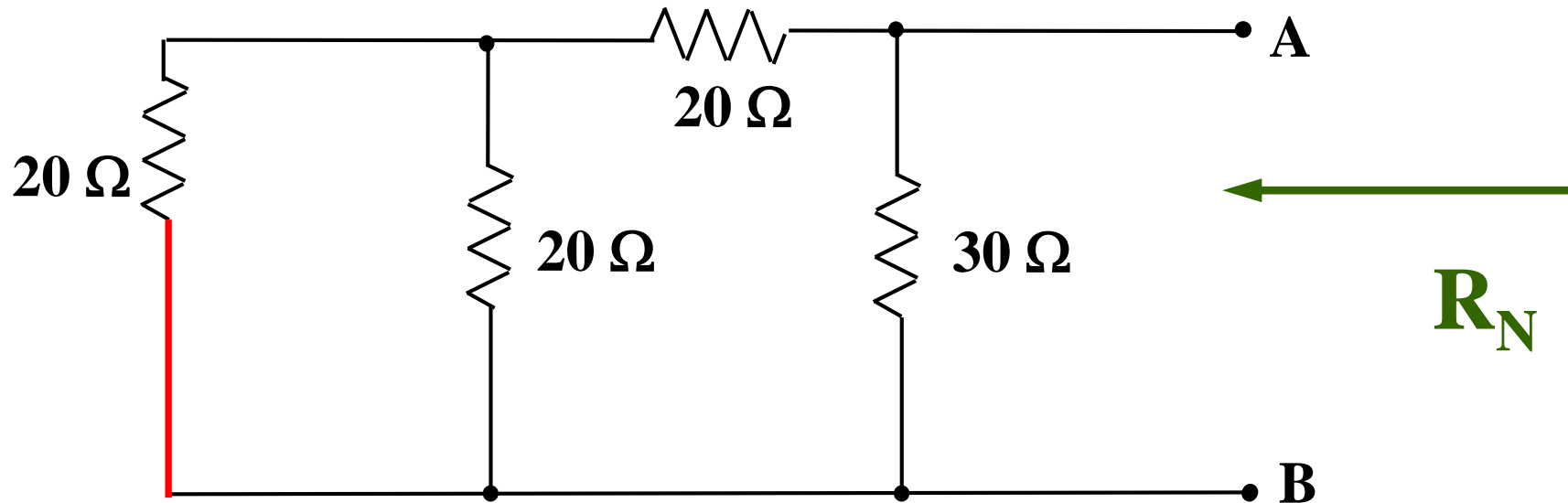

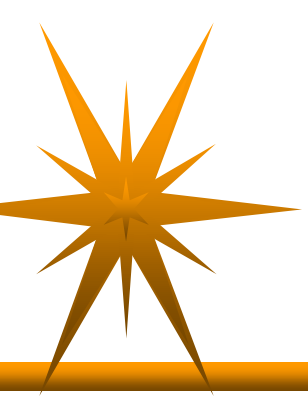Norton's equivalent resistance  $R_N$  is the resistance measured between A & B with all voltage sources replaced by short circuits, and current sources by open circuits.




## Example 1.11

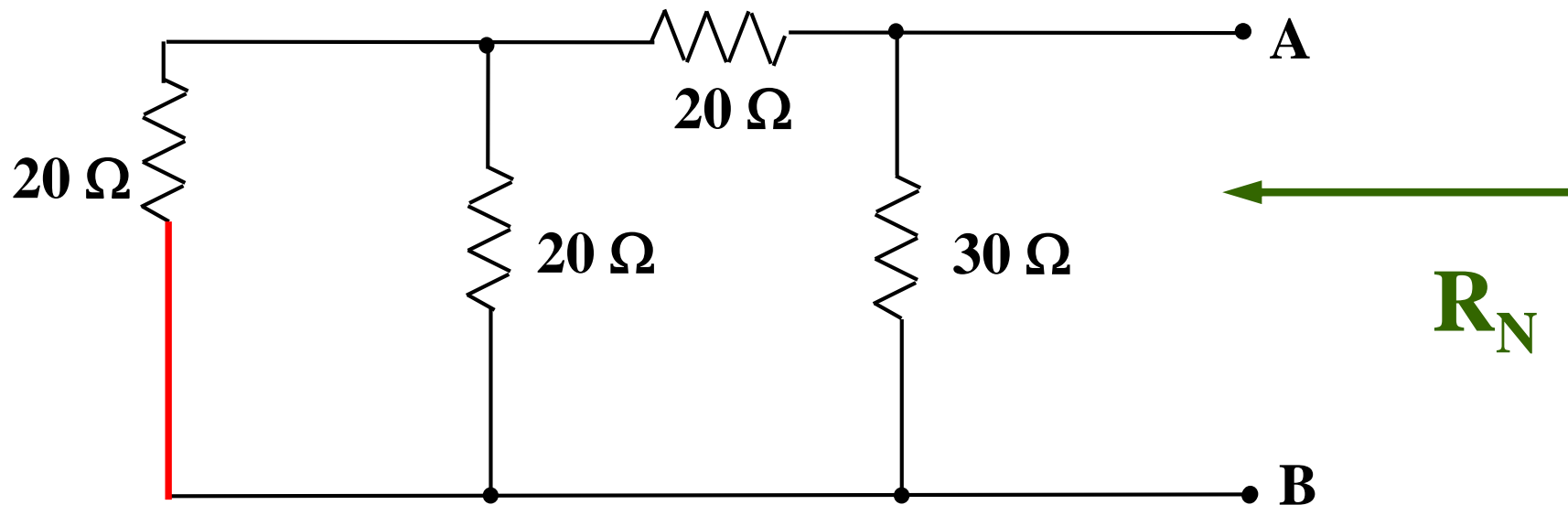

$$R_{//} = 10 \Omega$$


$$R_N = R_{AB} = (10 + 20) // 30 = 15 \Omega$$

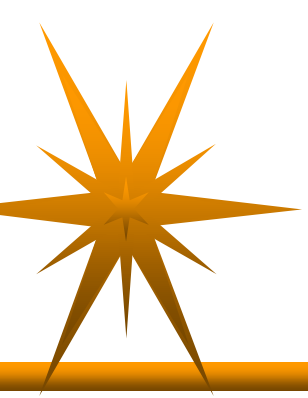So  $I_N = 0.5 \text{ A}$  and  $R_N = 15 \Omega$ , the Norton's equivalent circuit can now be drawn.



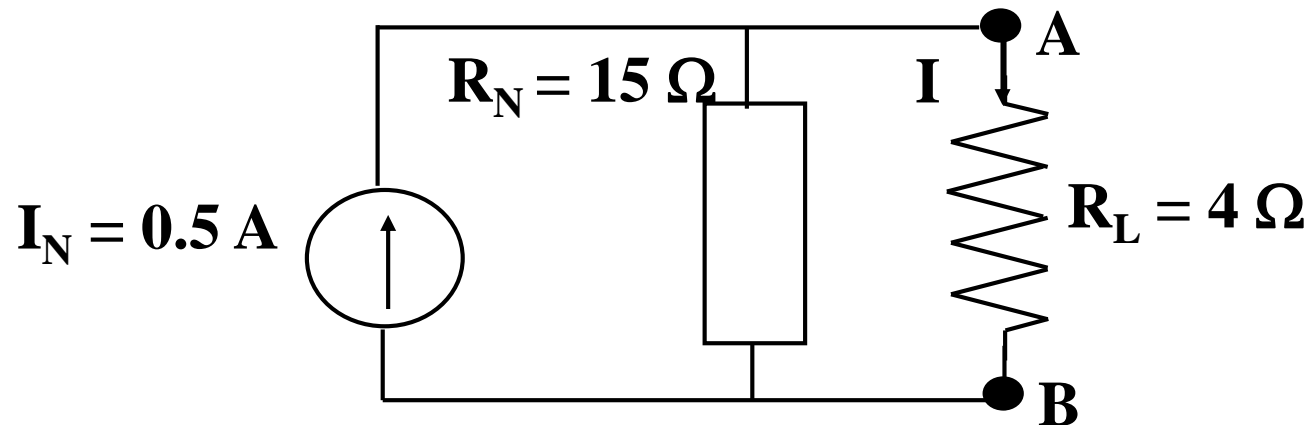
# Example 1.11

Norton's equivalent circuit with load ( $R_L$ )




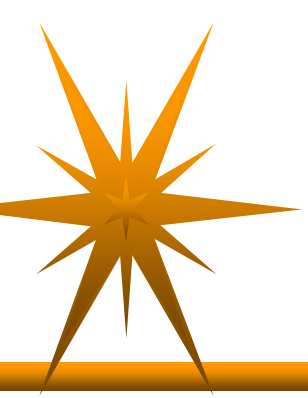
$$\text{Load current } I = \frac{I_N R_N}{R_N + R_L} = \frac{0.5 \times 15}{19} = 0.395 \text{ A}$$



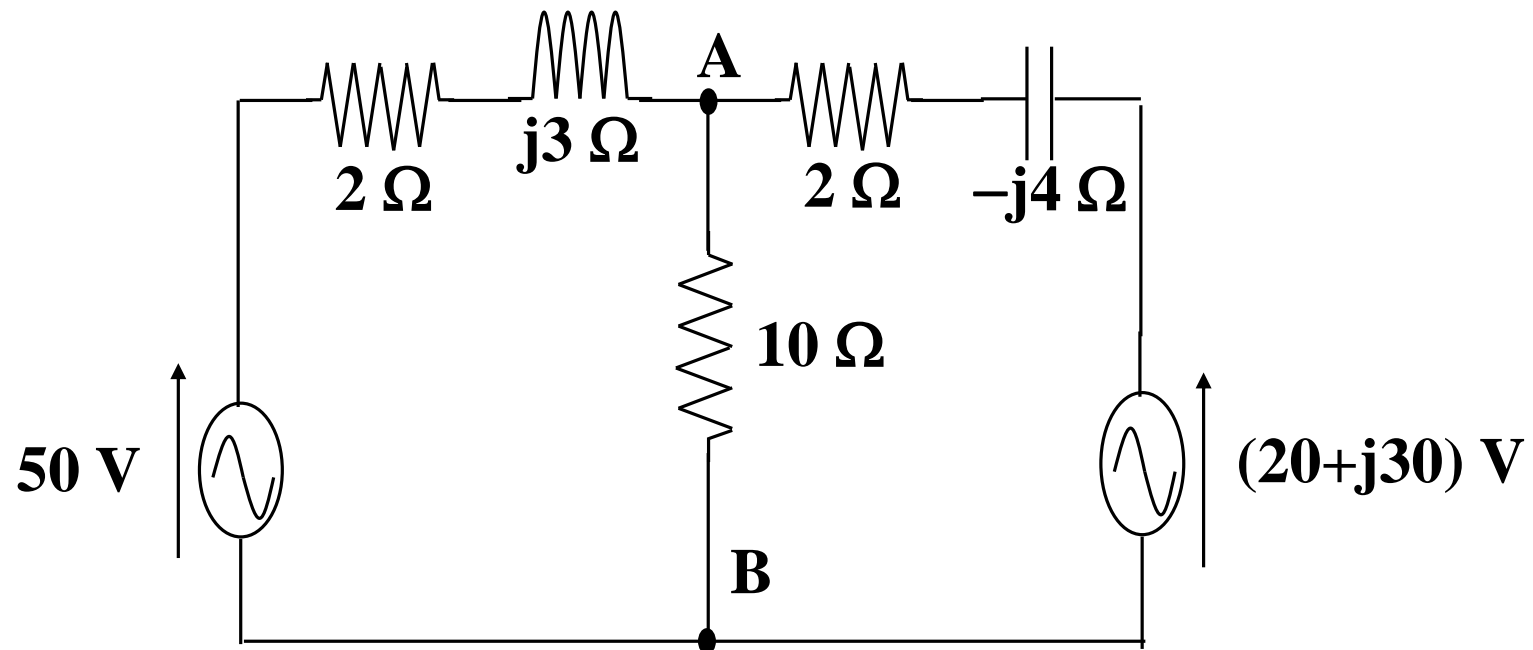
# Example 1.12

Apply Norton's theorem and calculate the current in the 10 ohm resistor.



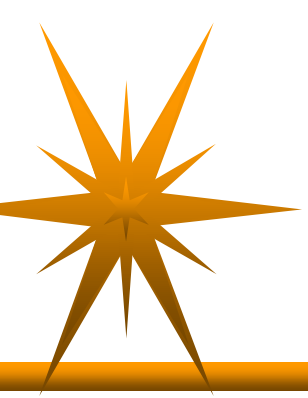


## Example 1.12

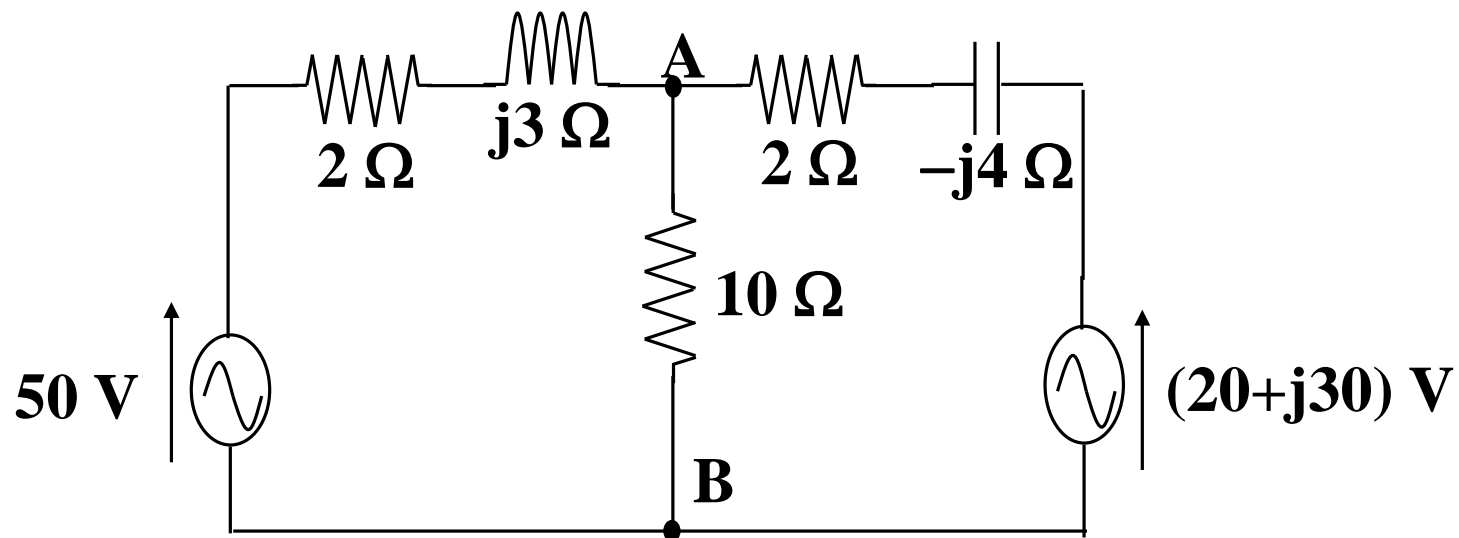


**To find the Norton's equivalent circuit across AB, remove  $R_L$  such that terminals A & B are now open-circuit.**


# Example 1.12

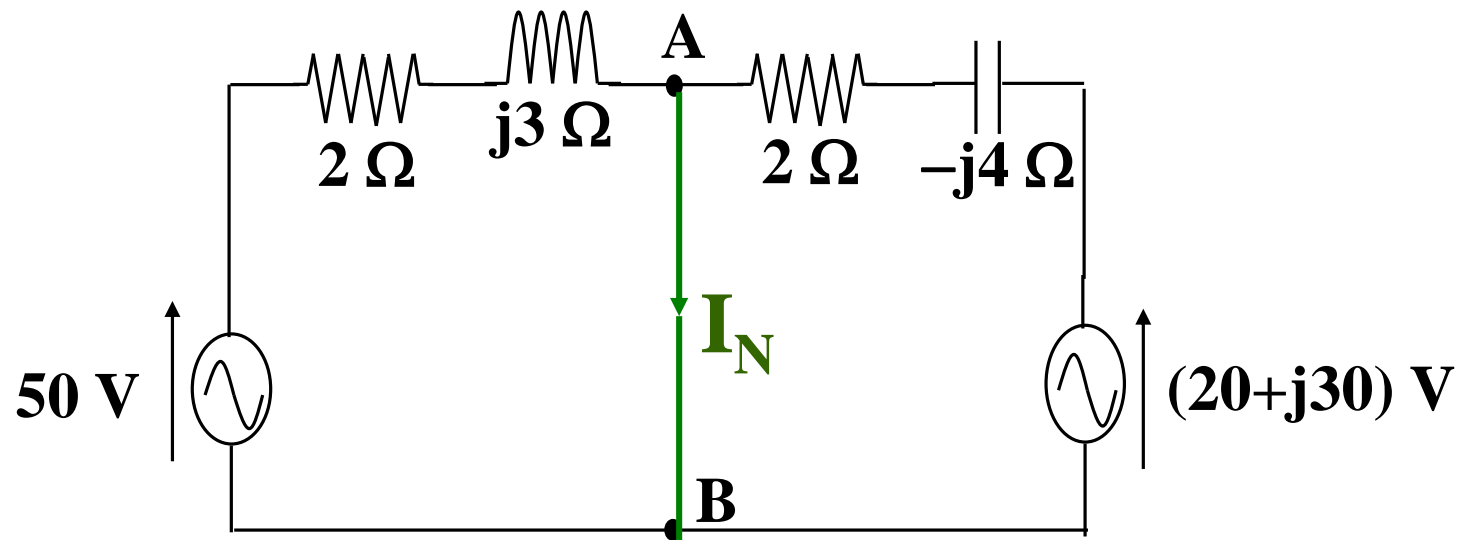

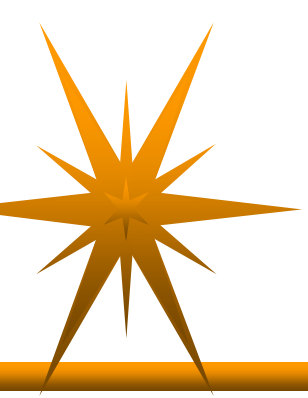Put a short circuit across terminals AB. The current  $I_N$  flows through the short circuit is the Norton's current source.




# Example 1.12

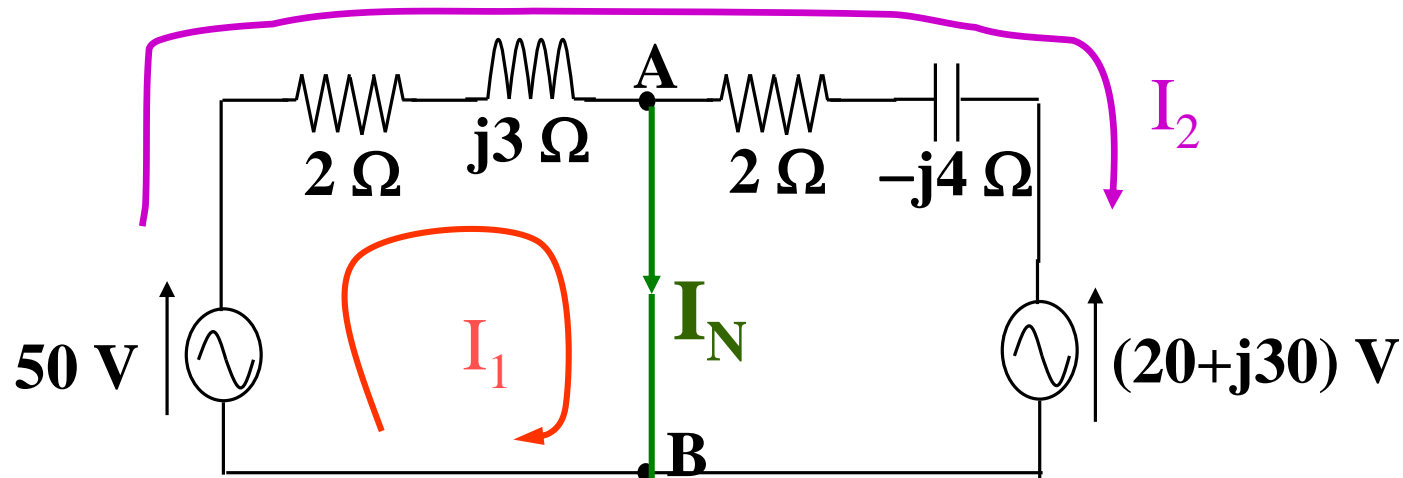


$$\begin{bmatrix} 2+j3 & 2+j3 \\ 2+j3 & 4-j1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 50+j0 \\ 50+j0 - (20+j30) \end{bmatrix}$$
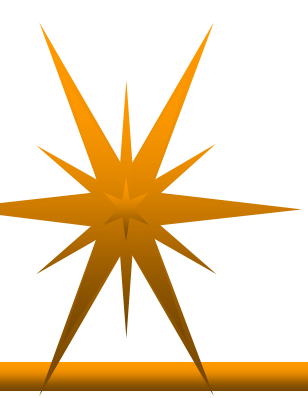
$$I_1 = \frac{\begin{vmatrix} 50 & 2+j3 \\ 30-j30 & 4-j1 \end{vmatrix}}{\begin{vmatrix} 2+j3 & 2+j3 \\ 2+j3 & 4-j1 \end{vmatrix}} = 5.84 \angle -50.81^\circ \text{ A}$$




## Example 1.12

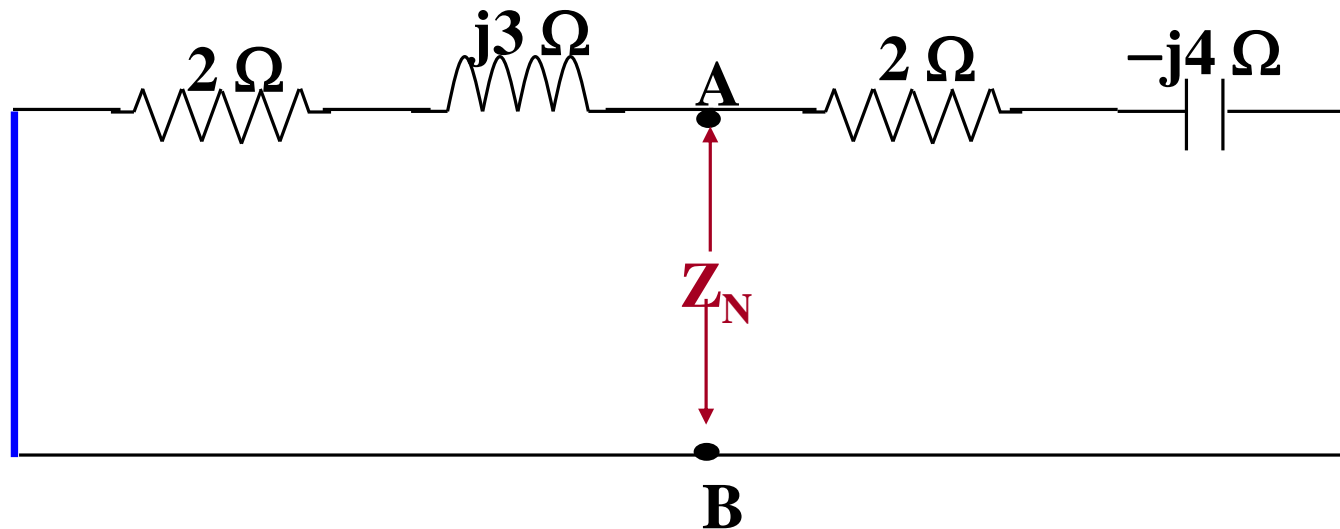

Norton's equivalent impedance  $Z_N$  is the impedance measured between A & B with all voltage sources replaced by short circuits, and current sources by open circuits.

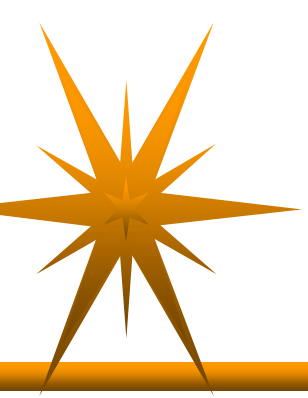
$$Z_{AB} = Z_N = \frac{(2 + j3)(2 - j4)}{(2 + j3) + (2 - j4)} = (3.88 + j0.47)\Omega$$





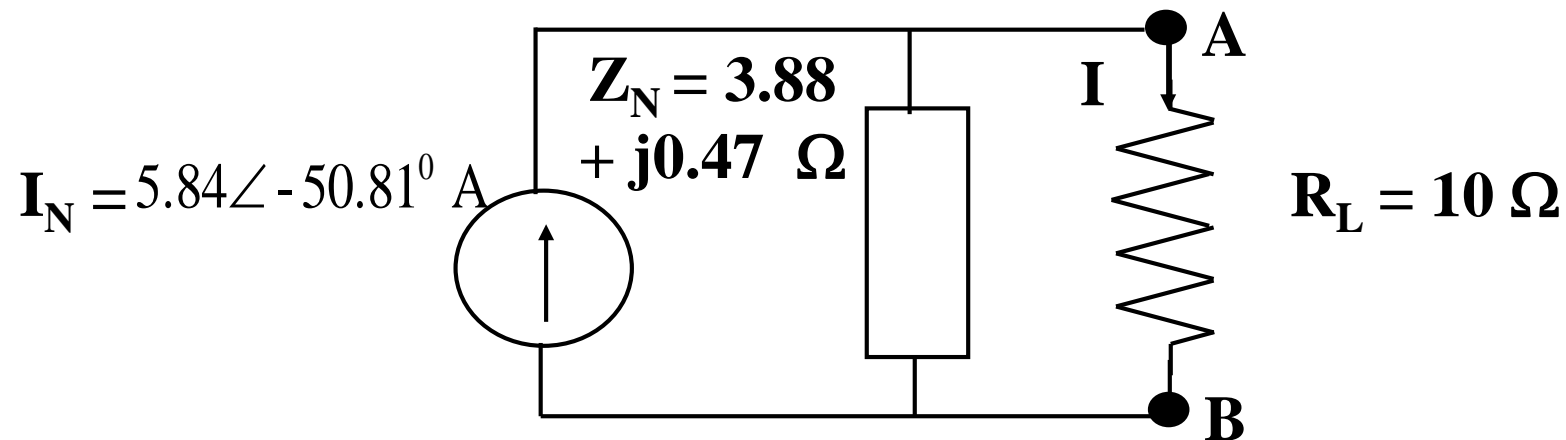
# Example 1.12


Norton's equivalent circuit with load ( $R_L$ )


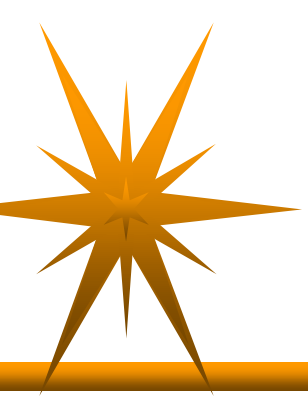
$$\begin{aligned}\text{Load current } I &= \frac{I_N Z_N}{Z_N + R_L} \\ &= \frac{5.84 \angle -50.81^\circ \times (3.88 + j0.47)}{13.88 + j0.47} \\ &= 1.64 \angle -45.84^\circ \text{ A}\end{aligned}$$



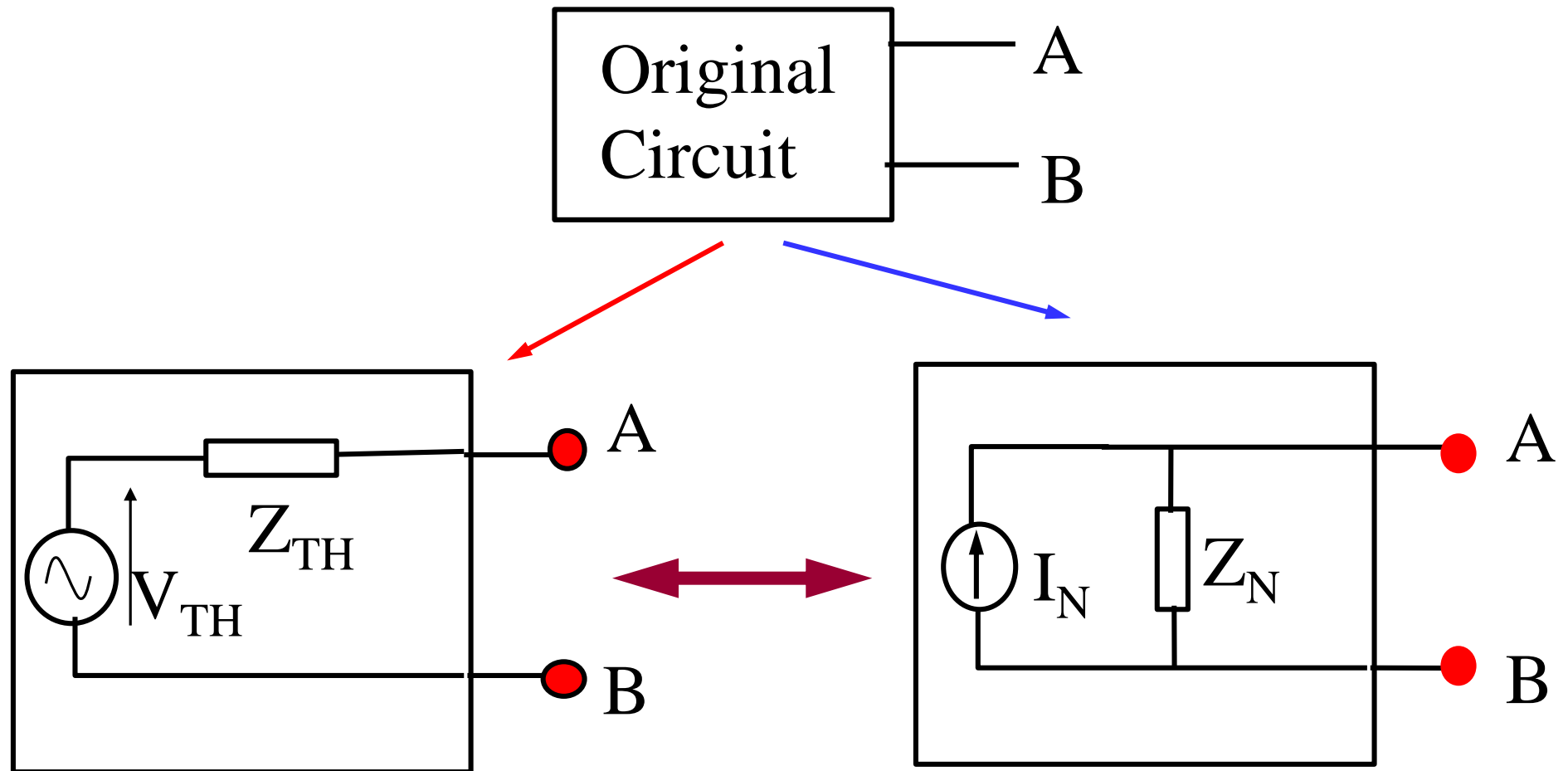
# Relationship between Thevenin and Norton Equivalent Circuits



Thevenin's Equivalent Circuit

Norton's Equivalent Circuit

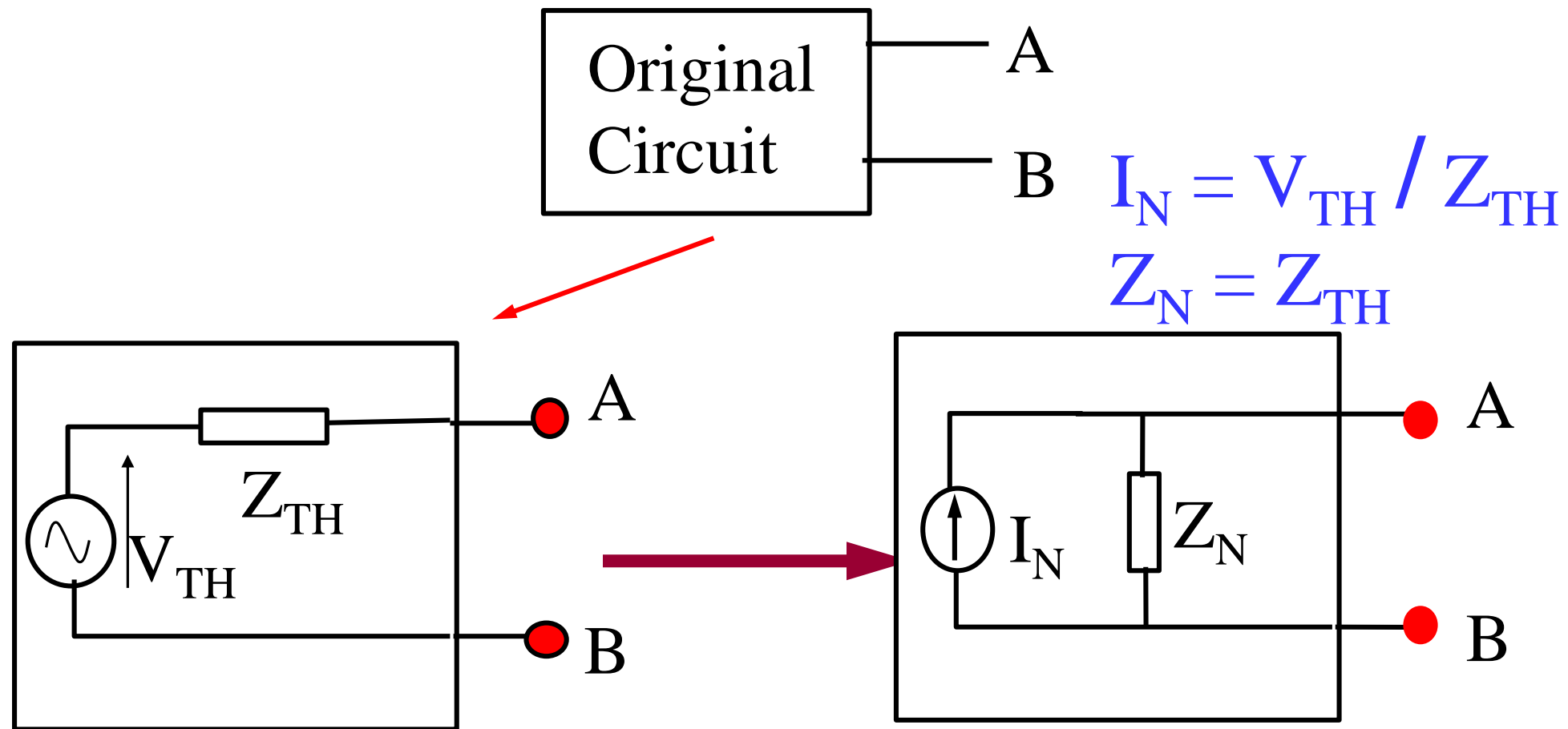
# Relationship between Thevenin and Norton Equivalent Circuits



Thevenin's Equivalent Circuit

Norton's Equivalent Circuit
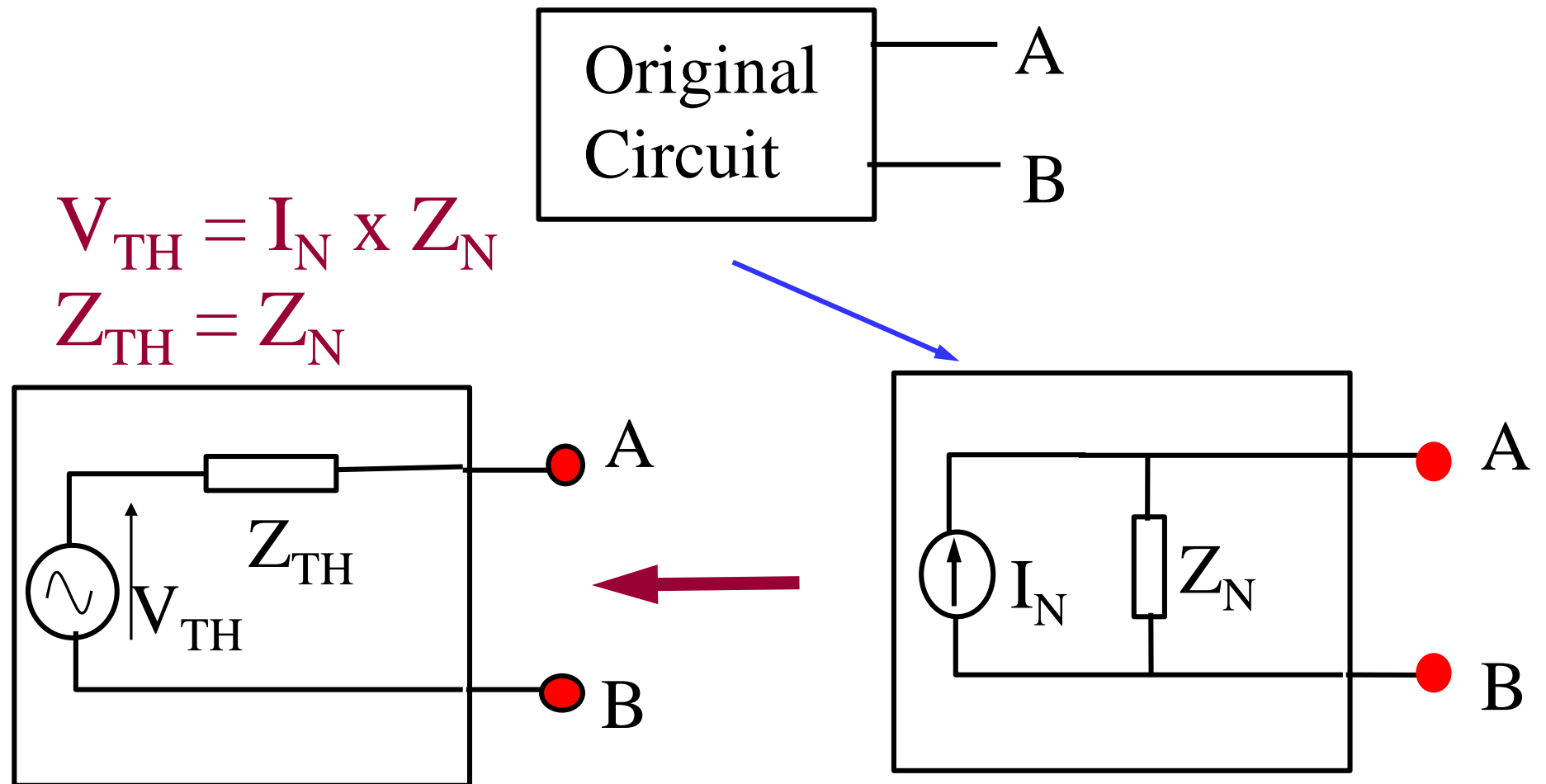
# Relationship between Thevenin and Norton Equivalent Circuits




Thevenin's Equivalent Circuit

Norton's Equivalent Circuit

# Relationship between Thevenin and Norton Equivalent Circuits


Example 1.10 & 1.12 (same circuit)

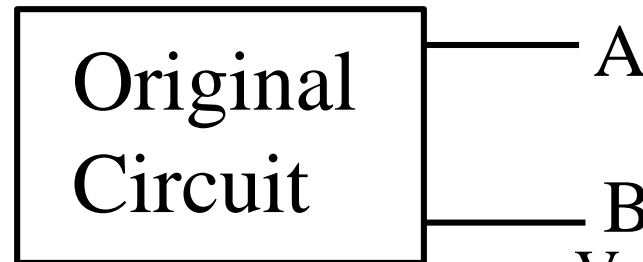

From Example 1.10,

$$V_{TH} = 22.88 \angle -43.96^\circ \text{ V}$$


$$Z_{TH} = (3.88 + j0.47) \Omega$$

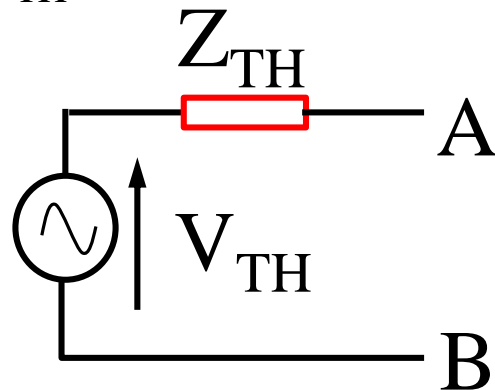

$$I_N = \frac{V_{TH}}{Z_{TH}} = \frac{22.88 \angle -43.96^\circ}{3.88 + j0.47}$$

$$= \frac{22.88 \angle -43.96^\circ}{3.91 \angle 6.91^\circ} = 5.85 \angle -50.87^\circ \text{ A}$$

$$Z_N = Z_{TH} = (3.88 + j0.47) \Omega$$

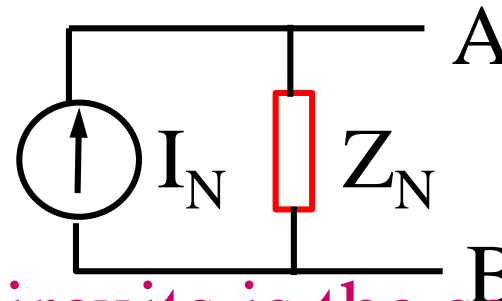

Same answer as  
Example 1.12

The load current for both circuits is the same.

*...next topic*

# *Three Phase Supply Generation*

Nurturing Curious Minds, Producing Passionate Engineers

**Lee M L**

Office: T12A522

School of EEE

Tel: 6879-0657