
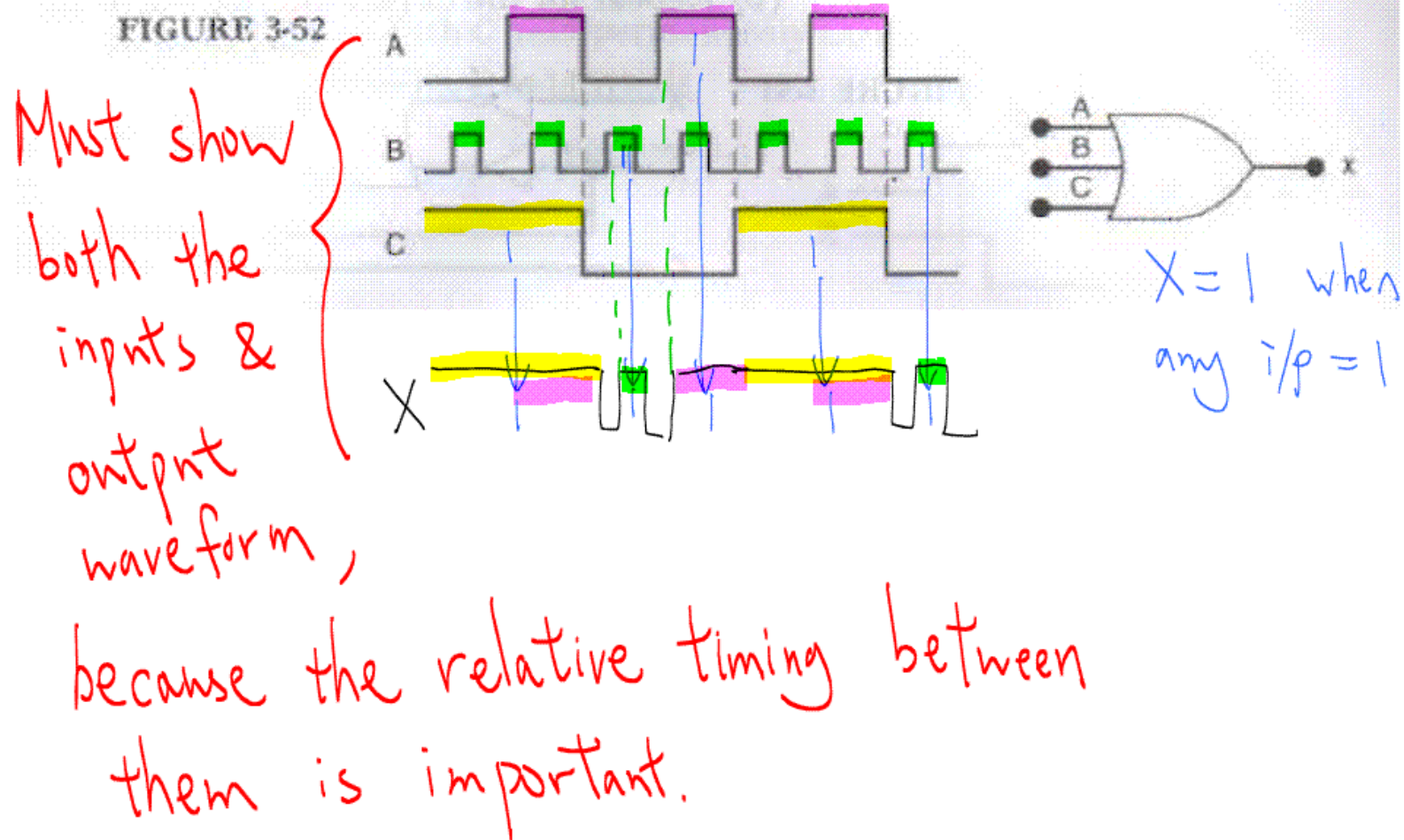


→ 3-1. Draw the output waveform for the OR gate of Figure 3-52.


FIGURE 3-52

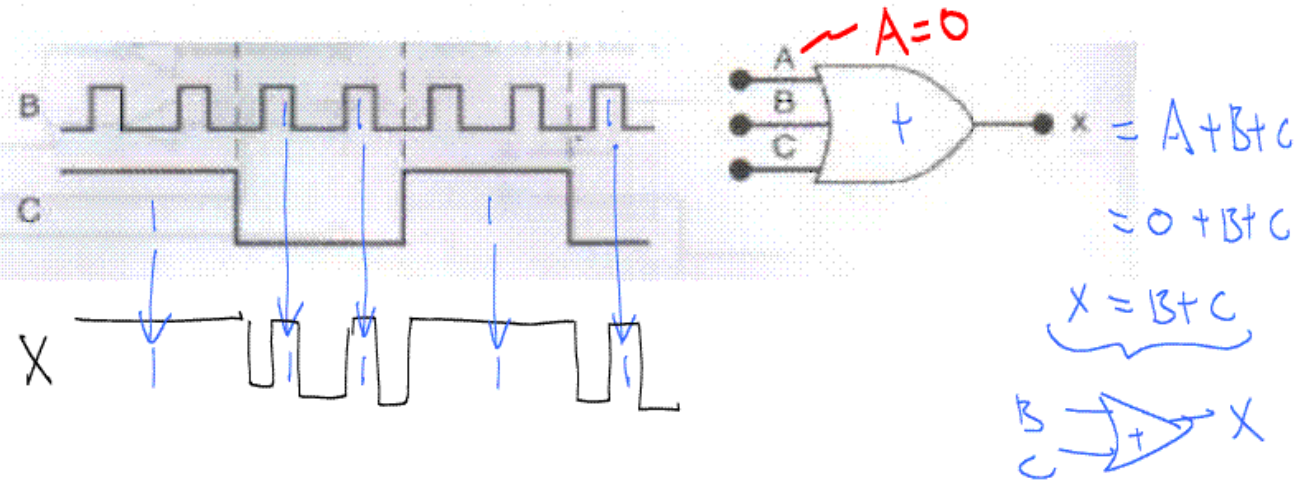


→ 3.2. Suppose that the A input in Figure 3-52 is unintentionally shorted to ground (i.e.,  $A = 0$ ). Draw the resulting output waveform.



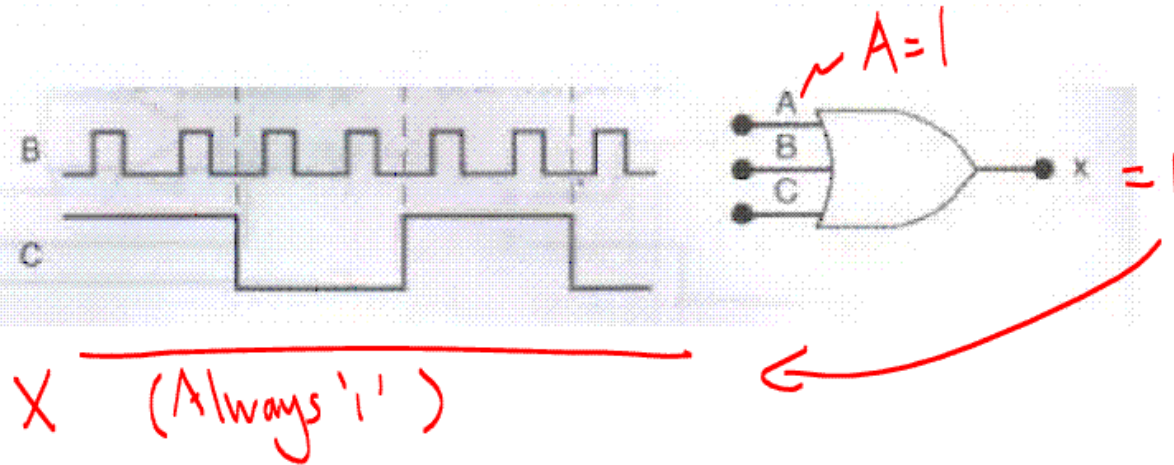→ 3-3. Suppose that the  $A$  input in Figure 3-52 is unintentionally shorted to the +5 V supply line (i.e.,  $A = 1$ ). Draw the resulting output waveform.



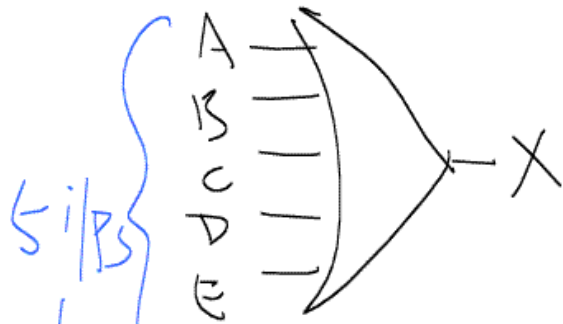→ 3-5. How many different sets of input conditions will produce a HIGH output from a five-input OR gate?



$2^5 = 32$  combinations

Ans


31 (out of 32)

input combinations will  
result in '1' output.

A	B	C	D	E	X
0	0	0	0	0	0
0	0	0	0	1	1
		1			1
		1			1
		1			1
		1			1
		1			1
		1			1
		1			1
1	1	1	1	1	1

$$O/P = 1$$

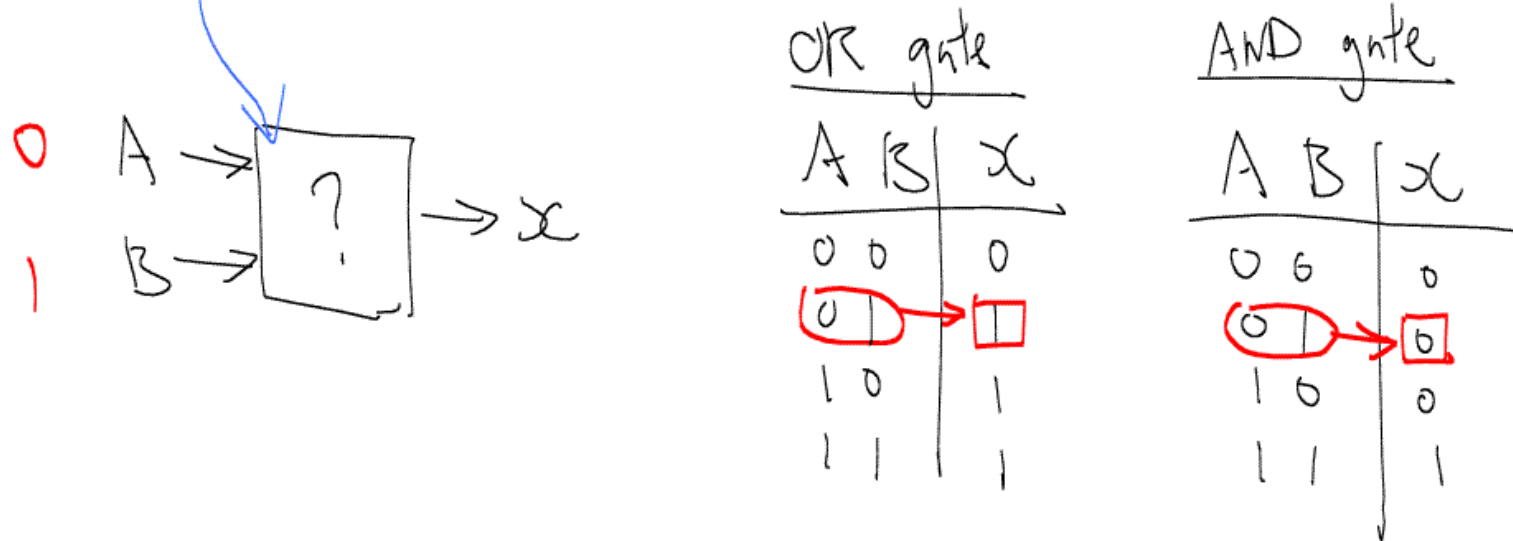3-9. Suppose that you have an unknown two-input gate that is **either an OR gate or an AND gate**. What combination of input levels should you apply to the gate's inputs to determine which type of gate it is?



Ans.

Apply '0' and '1' to A and B,

if  $x = 1 \Rightarrow$  OR gate,


if  $x = 0 \Rightarrow$  AND "

B → 3-12. (a) Write the **Boolean expression** for output x in Figure 3-53(a). Determine the value of x for all possible input conditions, and list the values in a **truth table**.

(b) Repeat for the circuit in Figure 3-53(b).

FIGURE 3-53

A	B	C	x
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

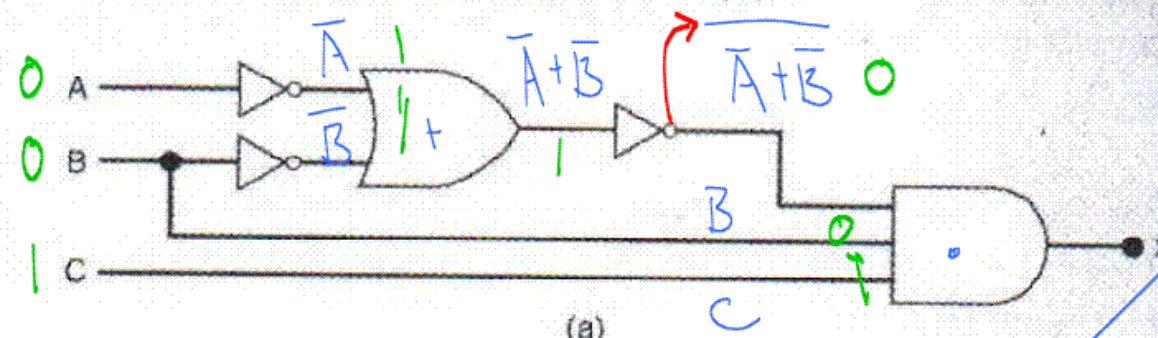


$$\text{Ans: } x = \overline{\overline{A+B}} \cdot B \cdot C$$

$$\begin{aligned} \overline{\overline{A+B}} &\neq A+B \\ &\downarrow \text{DMT} \\ &= \overline{\overline{A}} \cdot \overline{\overline{B}} \\ &= A \cdot B \end{aligned}$$

$$\begin{aligned} &\text{Not required in this question} \\ &\left\{ \begin{aligned} &= A \cdot B \cdot B \cdot C \\ &\simeq A \cdot B \cdot C \end{aligned} \right. \end{aligned}$$



3-12 (b)

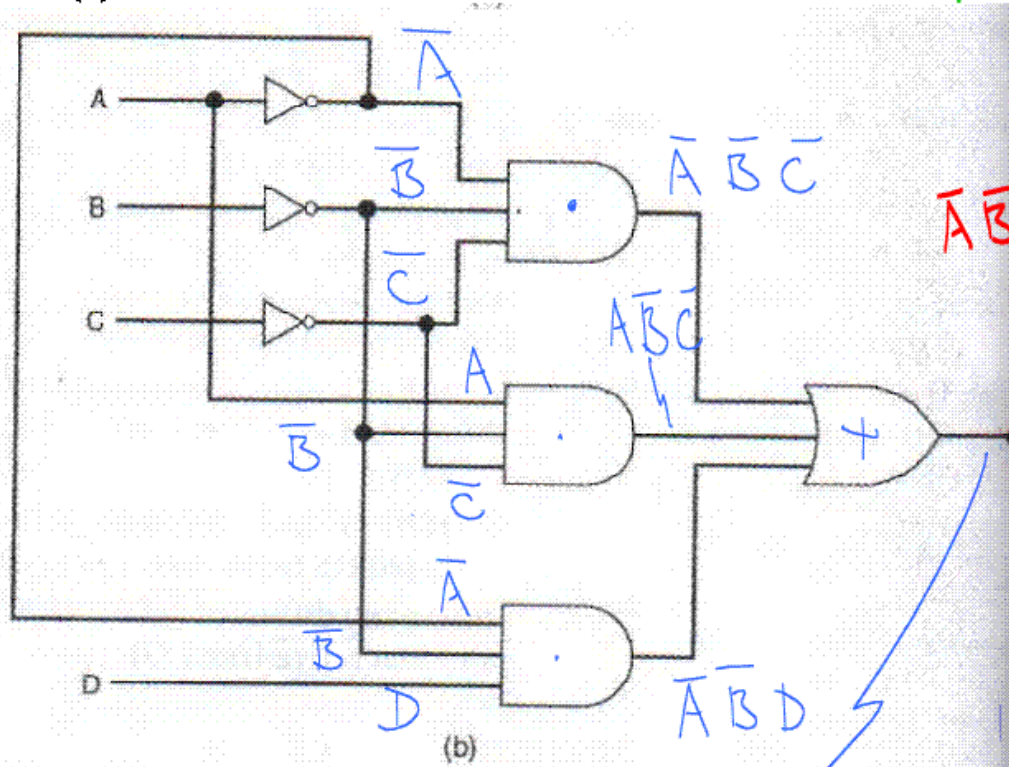

$\bar{A} \bar{B} \bar{C}$	A	B	C	D	X
	0	0	0	0	1
	0	0	0	1	1
	0	0	1	0	0
	0	0	1	1	0
	0	1	0	0	0
	0	1	0	1	0
	0	1	1	0	0
	0	1	1	1	0
	1	0	0	0	1
	1	0	0	1	0
	1	0	1	0	0
	1	0	1	1	0
	1	1	0	0	0
	1	1	0	1	0
	1	1	1	0	0
	1	1	1	1	0

Ans.  $X = \bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} D$

Simplification Not required  $\left\{ \begin{aligned} &= (\bar{A} + \bar{A}) \bar{B} \bar{C} + \bar{A} \bar{B} D \\ &= \bar{B} \bar{C} + \bar{A} \bar{B} D = \bar{B} (\bar{C} + \bar{A} D) \end{aligned} \right.$