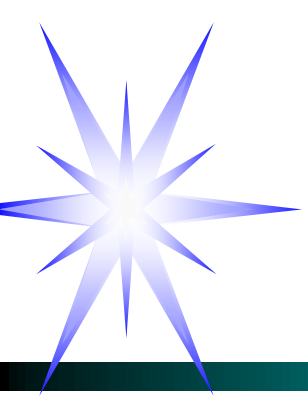




Resonant Circuits

Parallel RLC Resonant Circuit




Resonant Circuits

- ☺ RLC Parallel resonant circuit
 - ☞ RLC circuit in parallel
 - ☞ Phasor diagram
 - ☞ Resonance in RLC circuit
 - ☞ Graphical representation of resonance
 - ☞ Bandwidth of parallel RLC
 - ☞ Q-factor of parallel circuit




Pure RLC parallel circuit

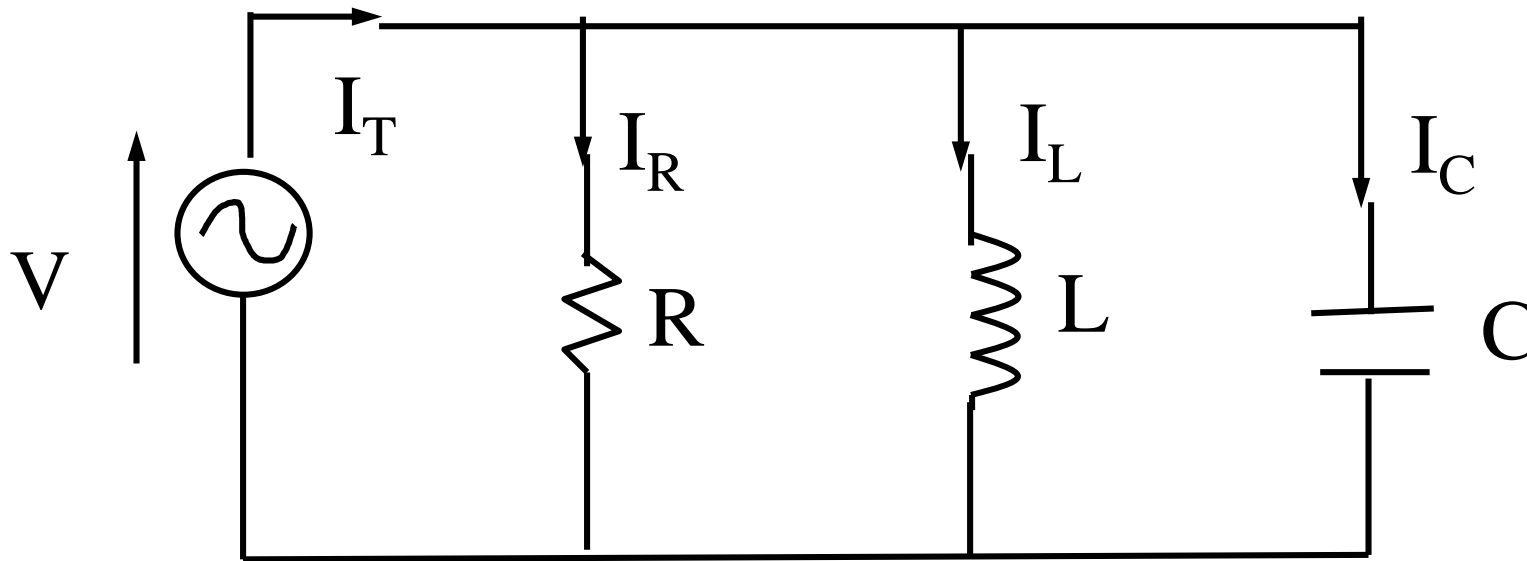

The R , L and C are all assumed to be pure. In practice, R and C can be very close to be pure but not L .



Pure RLC parallel circuit

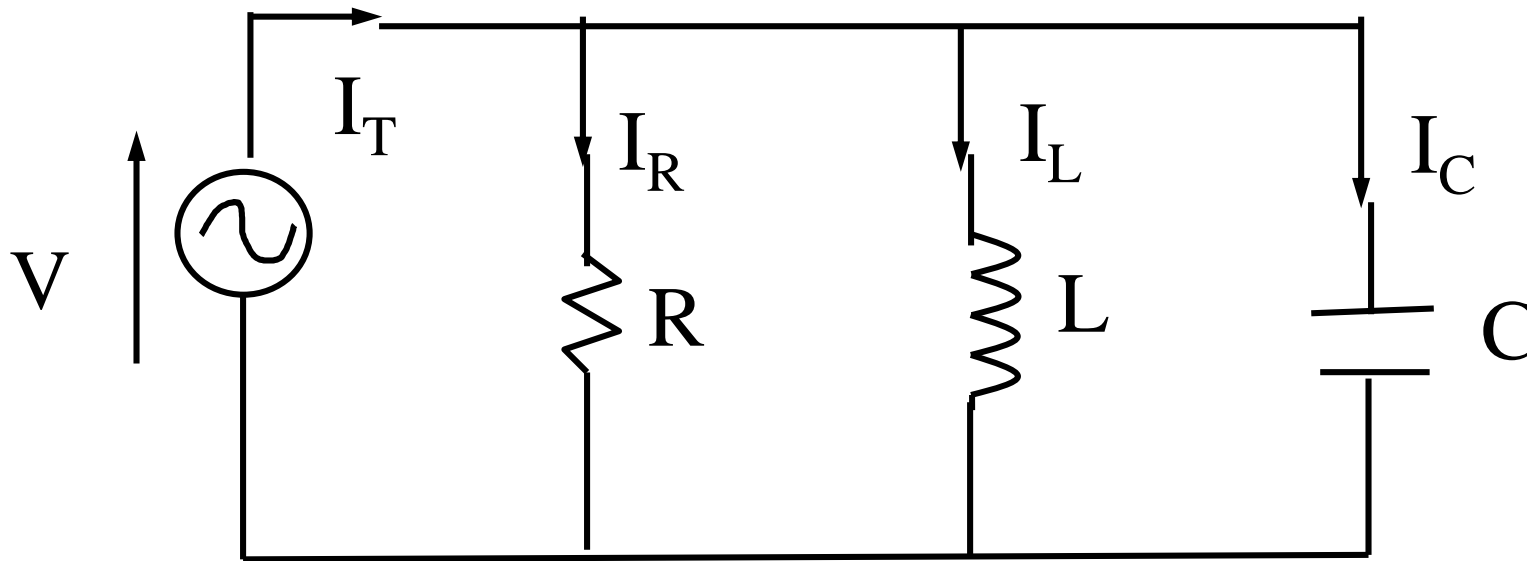

$$\begin{aligned}\text{Admittance } Y &= 1/R + 1/jX_L + 1/(-jX_C) \\ &= 1/R + 1/j\omega L + 1/(1/j\omega C) \\ &= 1/R + j(\omega C - 1/\omega L)\end{aligned}$$




Pure RLC parallel circuit - at resonance

$$\begin{aligned}\text{Admittance } Y &= 1 / R + 1 / j\omega L + 1 / (1 / j\omega C) \\ &= 1 / R + j (\omega C - 1 / \omega L) \\ &= G + jB \quad (\text{unit - siemen, S})\end{aligned}$$


where G is the conductance and B the susceptance.

Resonance occurs when $B = 0$, i.e. when $Y = G$ only and is a minimum ($Z = 1 / Y$ is at maximum)


Known as **High Impedance Resonance**

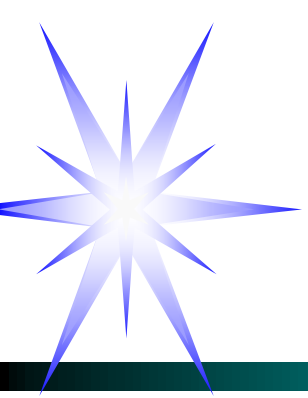

Pure RLC parallel circuit - at resonance

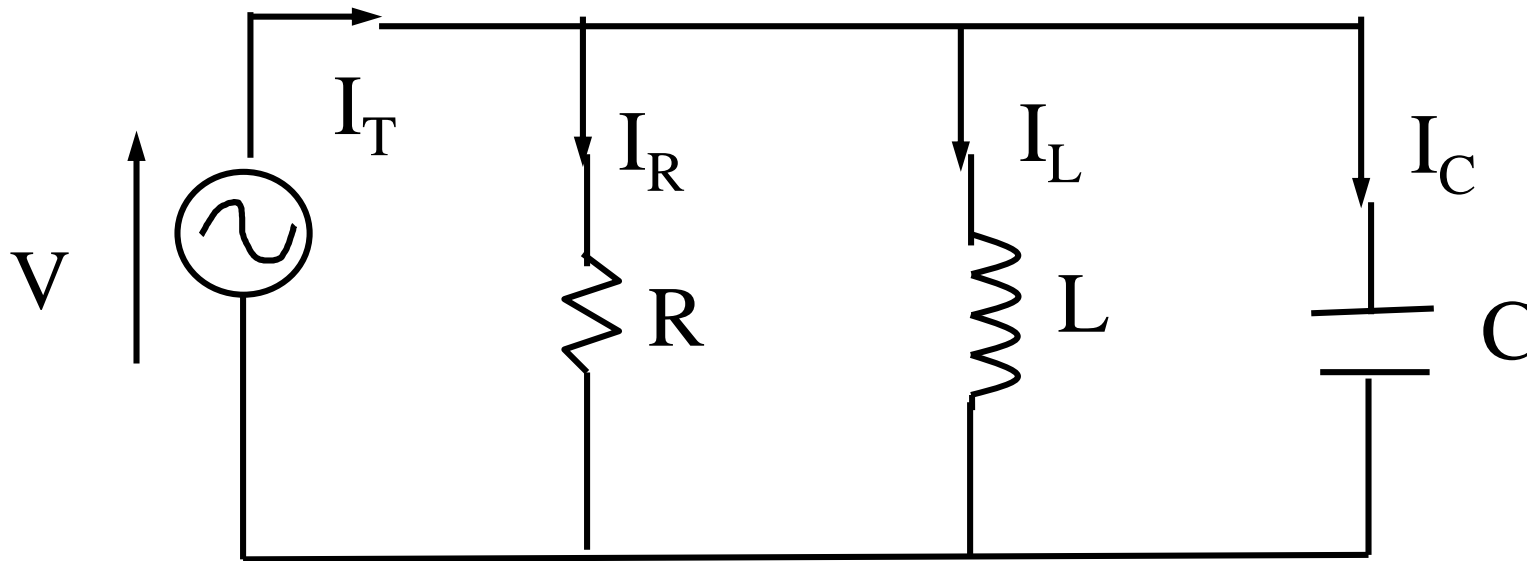

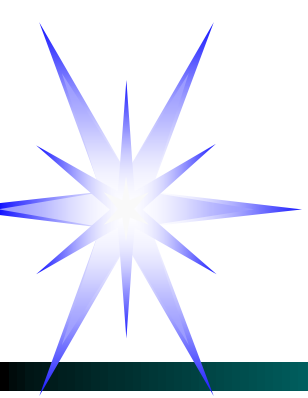
At resonance, V and I_T are in phase and the RLC circuit *behaves* like a pure resistor. With Y now equals to $1 / R$, therefore $I_T = V Y = V / R$




Phasor Diagram of a pure RLC parallel circuit at resonance

I_R is the current in the pure resistor and is therefore in phase with the voltage V .

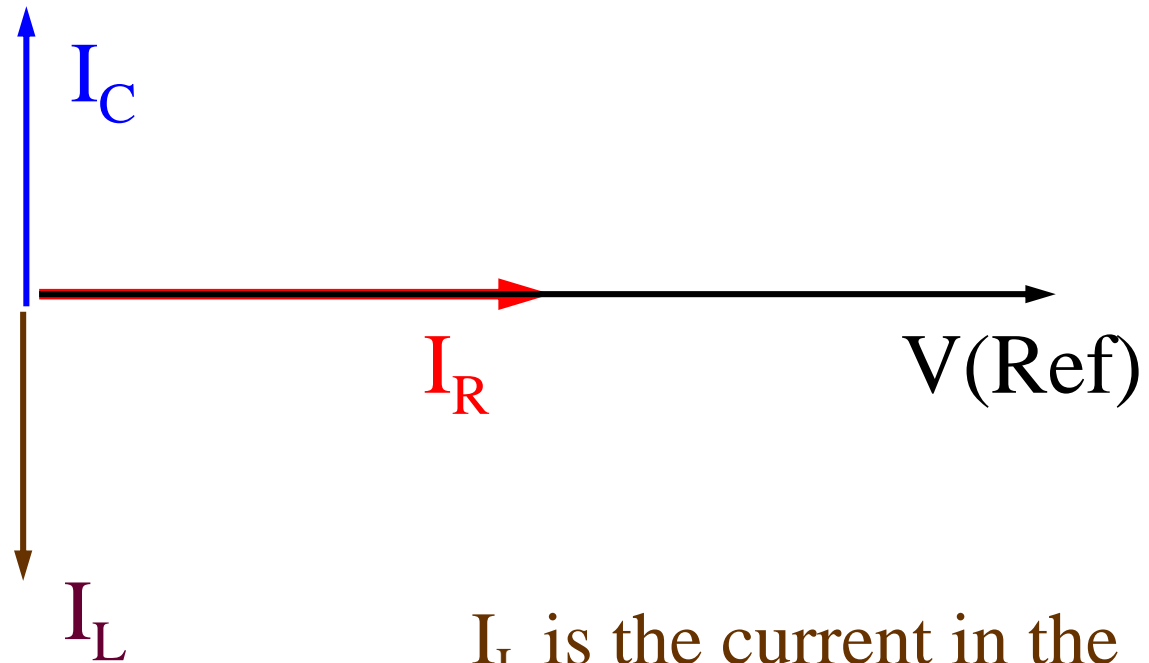
I_C is the current in the pure capacitor and is therefore leading the voltage by 90°



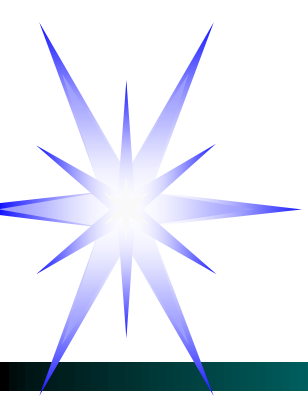I_L is the current in the pure inductor and is therefore lagging behind the voltage by 90°



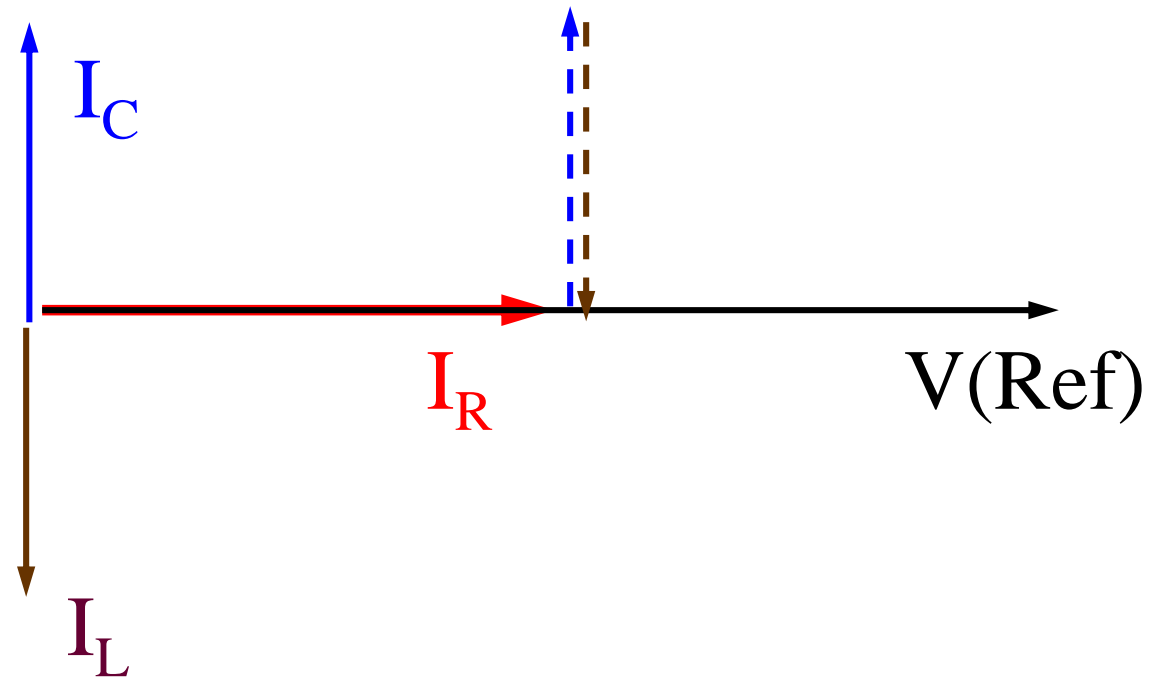Phasor Diagram of a pure RLC parallel circuit at resonance



$$I_T = I_R + I_L + I_C \text{ (By KCL)}$$

At resonance, $|I_L| = |I_C|$, making $I_L + I_C = 0$,
leaving only $I_T = I_R$



Phasor Diagram of a pure RLC parallel circuit at resonance

At resonance, $|I_C| = |I_L|$


Therefore $V / X_C = V / X_L$, giving

$$X_C = X_L$$


$$2 \pi f_o L = 1 / 2 \pi f_o C$$

$$4 \pi f_o^2 = 1 / LC$$
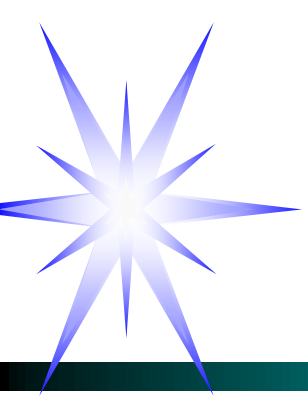
$$f_o = 1 / 2\pi \sqrt{LC} \quad \text{Hz}$$



Bandwidth of a parallel resonant circuit

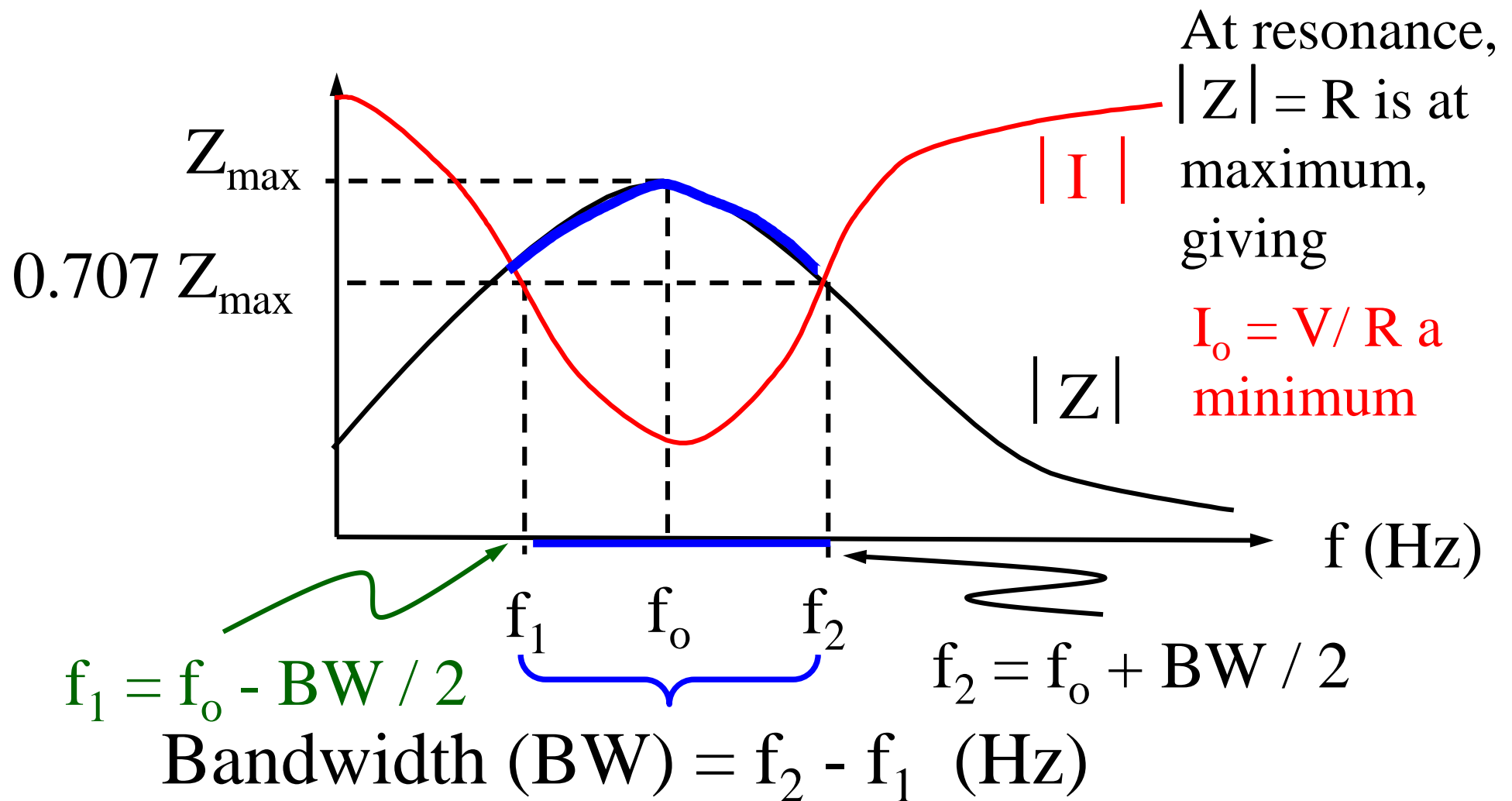



Q factor for a pure RLC 3-branch resonant circuit

$$Q \text{ factor} = I_L / I_T = (V / X_L) / (V / R) = R / X_L$$

or

$$Q \text{ factor} = I_C / I_T = (V / X_C) / (V / R) = R / X_C$$

With $X_L = X_C$ at resonance, these two Q factors actually have the same numerical value.

Q here is also called the *current magnification factor*.



Relationship between Bandwidth, resonant frequency and Q factor

$$BW = f_o / Q \quad (\text{Hz})$$

or


$$BW = 2 \pi f_o / Q \quad (\text{rad/s})$$



Example

A three branch parallel resonant circuit consists of an inductor of 4 mH, a resistor of 10 k Ω and a capacitor of 0.001 μ F. The supply for the tuned circuit is 20 V AC. Determine:

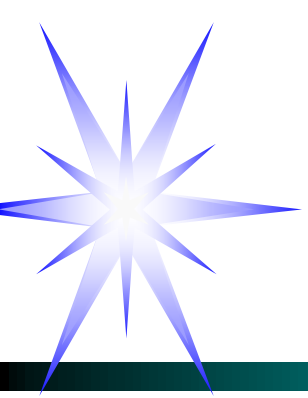- (a) the resonant frequency, maximum impedance Q factor and bandwidth and
- (b) supply current, capacitor current and inductor current at resonance.



Example


Using $f_o = \frac{1}{2\pi\sqrt{LC}}$

$$f_o = \frac{1}{2\pi\sqrt{4 \times 10^{-3} \times 0.001 \times 10^{-6}}} = 79.577 \text{ kHz}$$

$$Z_{\max} = R = 10 \text{ k}\Omega$$

$$Q = \frac{R}{X_L} = \frac{10000}{2\pi f_o L} = \frac{10000}{2 \times \pi \times 79.577 \times 10^3 \times 4 \times 10^{-3}} = 5$$
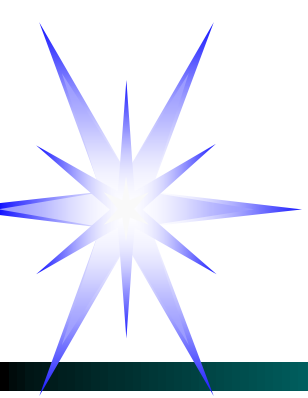
$$\text{Bandwidth BW} = \frac{f_o}{Q} = \frac{79.577 \times 1000}{5} = 15.91 \text{ kHz}$$




Example

$$\textit{Supply current } I_T = \frac{V}{R} = \frac{20}{10 \times 1000} = 2 \text{ mA}$$

$$\textit{Capacitor current } I_C = Q \times I_T = 5 \times 2 \text{ m} = 10 \text{ mA}$$
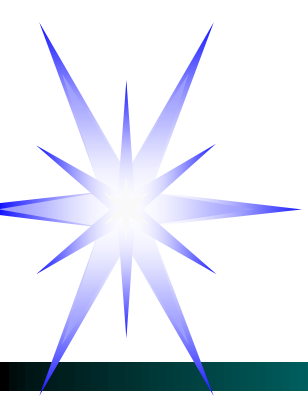
$$\textit{Inductor current } I_L = Q \times I_T = 5 \times 2 \text{ m} = 10 \text{ mA}$$



SUMMARY

Comparison of Series and Parallel Resonant Circuits

Parameter	Series RLC Circuit	Parallel RLC Circuit
1. Impedance	$Z = R$ (minimum)	$Z = R$ (maximum)
2. Current	$I = V/R$ (maximum)	$I = V/R$ (minimum)
3. Power Factor	Unity	
4. Resonant Frequency	$f_o = \frac{1}{2\pi\sqrt{LC}}$	
5. Type of Magnification, Q Factor	Voltage	Current
6. Q Factor	$Q = X_L / R = X_C / R$ $= V_L / V = V_C / V$	$Q = R / X_L = R / X_C$ $= I_L / I = I_C / I$
7. Bandwidth	$BW = \frac{f_o}{Q_o} = f_2 - f_1$	
8. Half power frequencies	$f_1 = f_o - \frac{BW}{2}$ $f_2 = f_o + \frac{BW}{2}$	