 


ie one connected to another one

7-35. How many cascaded BCD counters are needed to be able to count up to 8000? How many FFs does this operation require? Compare this with the number of FFs required for a normal binary counter to count up to 8000. Even though it uses more FFs, why is the cascaded BCD method used?

Recall:

BCD (Binary Coded Decimal) always uses 4-bit to represent each decimal digit. The possible BCD values are: 0000 to 1001 (for 0 to 9 in decimal).



Compare with binary counter :

$$8000_{10} = \underbrace{111101000000}_2$$

13-bit (ie needs 13 ff.s)

BCD method is used in some cases although it uses more flip-flops than binary counter as it can show the decimal digits directly on the 7-segment displays without any conversion.


7-55. Suppose a 74ALS174 is connected as follows:

$$\overline{MR} = \text{HIGH}; Q_5 \rightarrow D_2; Q_4 \rightarrow D_1; Q_3 \rightarrow D_0$$

$$D_5 = D_3 = \text{HIGH}; D_4 = \text{LOW}$$

Assume all FFs have a zero hold-time and are initially LOW.

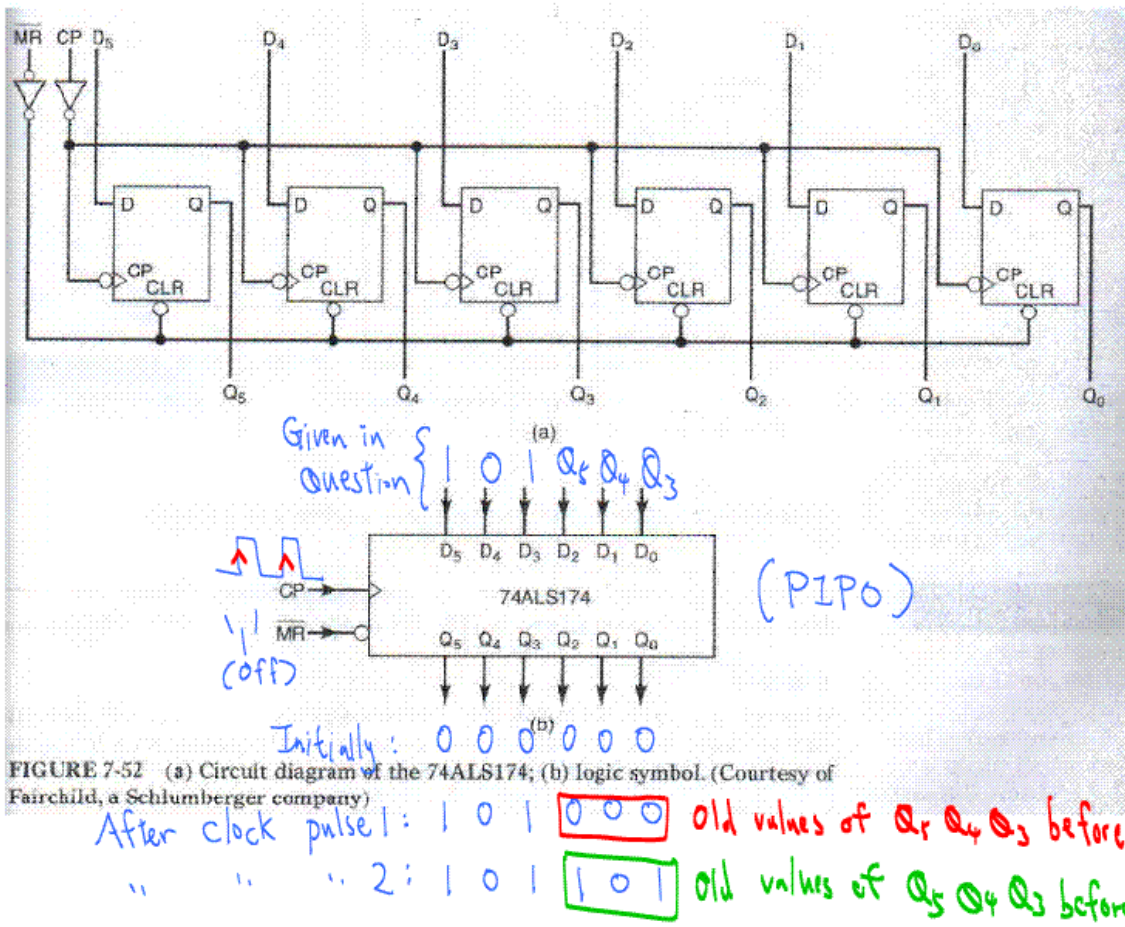- Determine the states of each FF after a single pulse is applied to CP.
- Repeat for a second clock pulse.



7-57. Show how the 4731B chip can be connected as a 256-bit shift register

