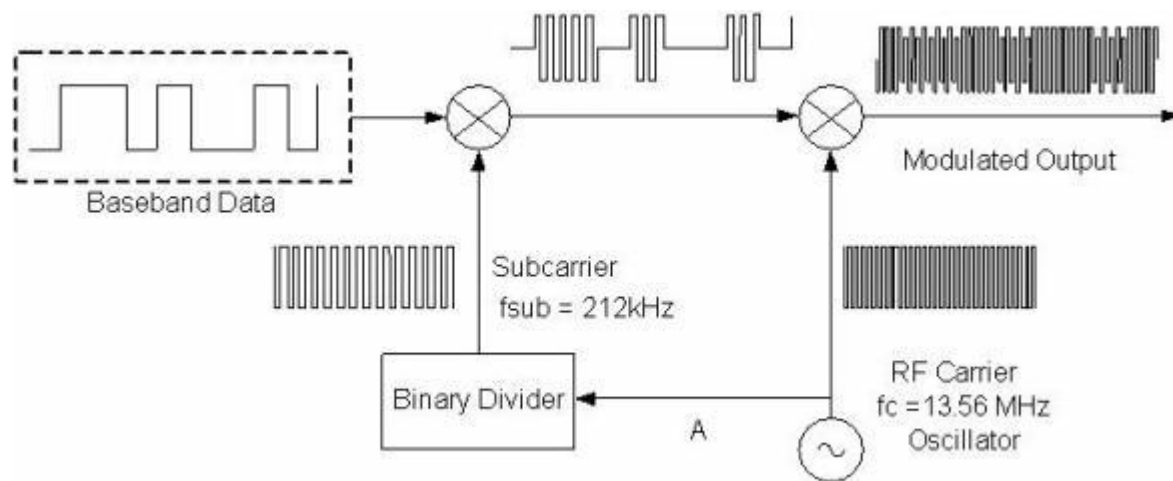



Tutorial 02

MCQ No. 2



You can refer to the above picture as an example for subcarrier modulation. Since we are using the binary divider of $2^6 = 64$ from 13.56 MHz carrier to produce the subcarrier. Hence, the frequency of should be 212 kHz in the above example.

MCQ No. 9

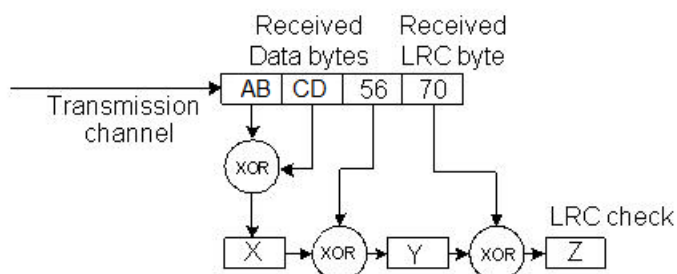

The following is an example of XOR for $(AB)_{hex}$ and $(CD)_{hex}$ for the above diagram.

$$(AB)_{hex} \rightarrow (10101011)_2$$

XOR

$$(CD)_{hex} \rightarrow (11001101)_2$$

↓

$$(66)_{hex} \leftarrow (01100110)_2$$